

Welcome to EECS 16A!

Designing Information Devices and Systems I

Ana Claudia Arias and Miki Lustig
Fall 2021

Module 2
Lecture 7

Capacitors and Capacitive Touchscreens
(Note 17)




Greetings from Miki & Ana




Last lecture: Capacitors

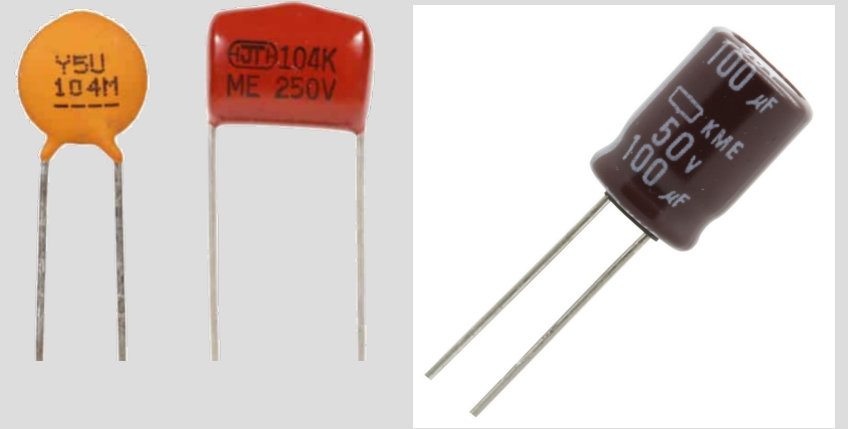- Charge storage device (like a 'bucket' for charge)
- holds electric charge when we apply a voltage across it, and gives up the stored charge to the circuit when voltage removed



Symbol:

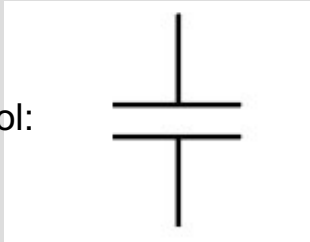


Capacitance:

C

Units: Farads [F]

IV equation:



$$I = C \cdot \frac{dV}{dt}$$

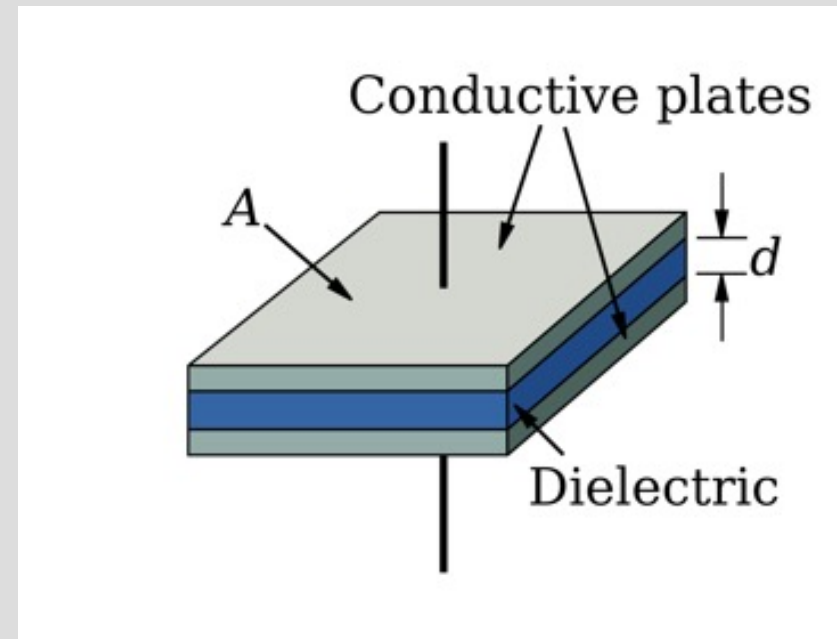

$$C = \epsilon \cdot \frac{A}{d}$$

Circuit Model: IV relationship

Capacitor Symbol

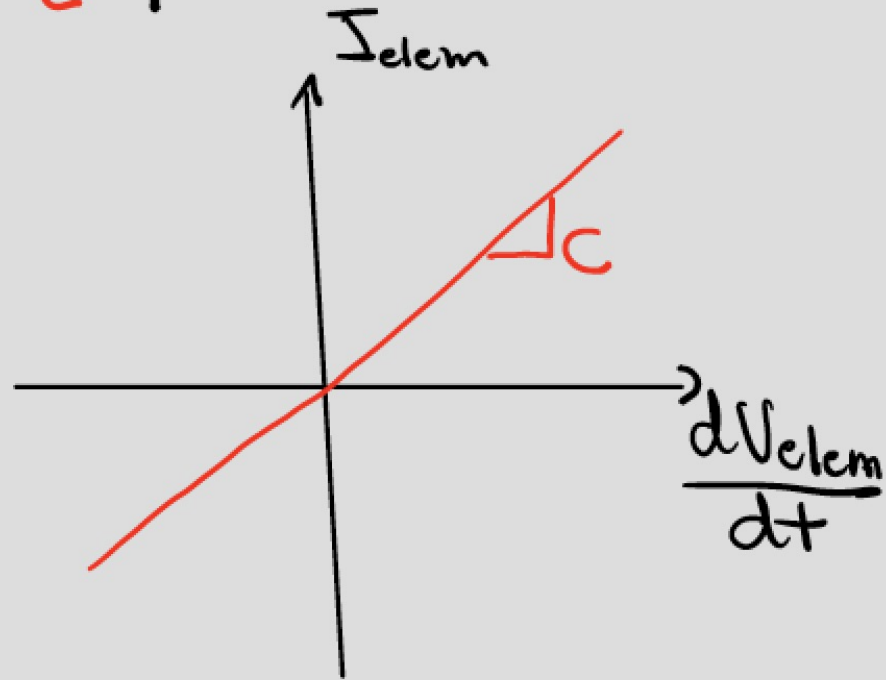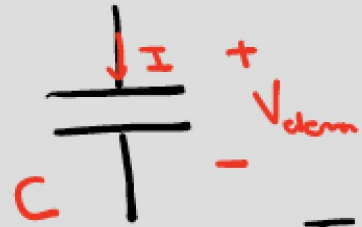

$$Q_{elem} = C \cdot V_{elem}$$

\uparrow \uparrow \uparrow
[C] [F] [V]
(Farad)

We know: $I_{elem} = \frac{dQ_{elem}}{dt}$

$$I_{elem} = \frac{d}{dt} C \cdot V_{elem}$$

C = constant over time

$$I_{elem} = C \cdot \frac{dV_{elem}}{dt}$$




↳ Can use the same 7-step analysis.

Equivalent Circuits with Capacitors

* Capacitor - only circuit


Step 1: ~~find V_{th} / I_{no}~~ no source

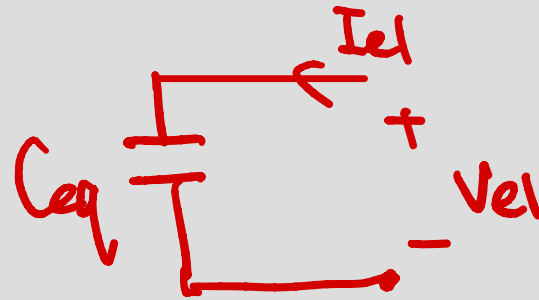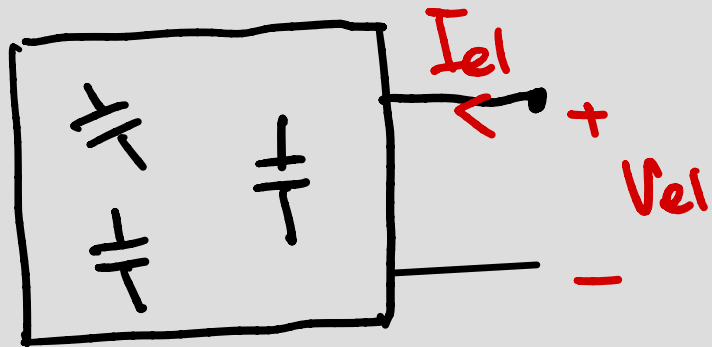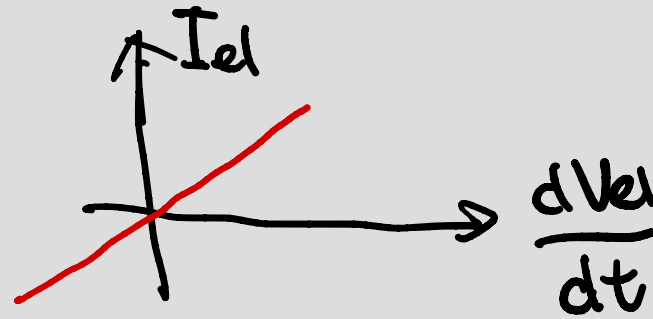Step 2:
$$C_{eq} = \frac{I_{eq}}{\frac{dV_{el}}{dt}}$$




- a) Apply I_{test} and measure $\frac{dV_{\text{test}}}{dt}$
- b) Apply $\frac{dV_{\text{test}}}{dt}$ and measure I_{test}
- $C_{\text{eq}} = \frac{I_{\text{test}}}{\frac{dV_{\text{test}}}{dt}}$


(a)

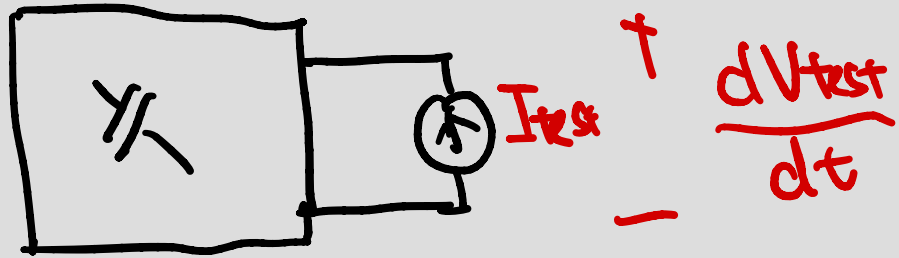

(b)

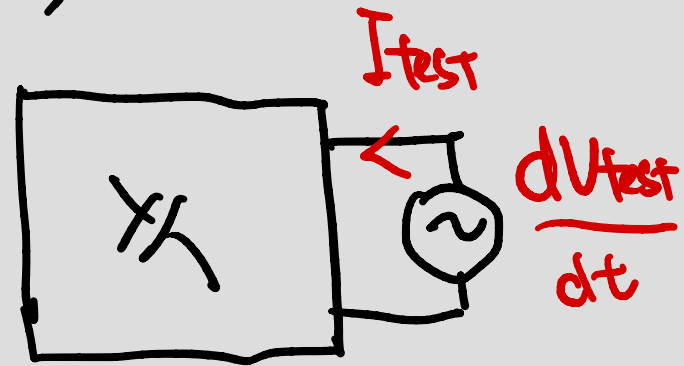

* These are methods for experiments

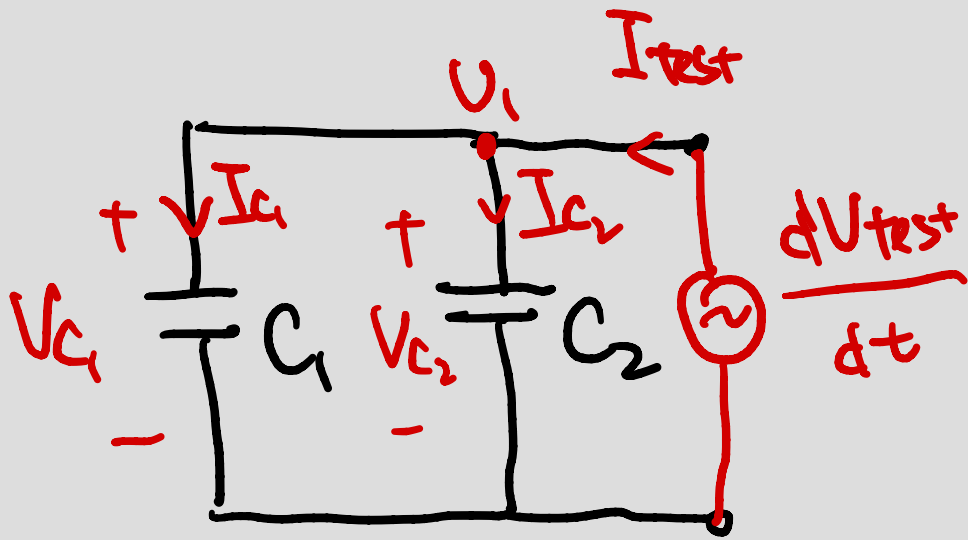

$$V_{C_1} = U_1, \quad V_{C_2} = U_1$$

$$U_1 = V_{\text{test}}$$

$$\frac{dU_1}{dt} = \frac{dV_{\text{test}}}{dt}$$

Elem Definition: $I_{C_1} = C_1 \frac{dV_{C_1}}{dt}$


$$I_{C_2} = C_2 \frac{dV_{C_2}}{dt}$$

$$\text{KCL: } I_{\text{test}} = I_{C_1} + I_{C_2} = C_1 \frac{dV_{\text{test}}}{dt} + C_2 \frac{dV_{\text{test}}}{dt} = (C_1 + C_2) \frac{dV_{\text{test}}}{dt}$$

$$I_{\text{test}} = (C_1 + C_2) \frac{dV_{\text{test}}}{dt}$$

$$C_{\text{eq}} = \frac{I_{\text{test}}}{\frac{dV_{\text{test}}}{dt}} = C_1 + C_2$$

parallel

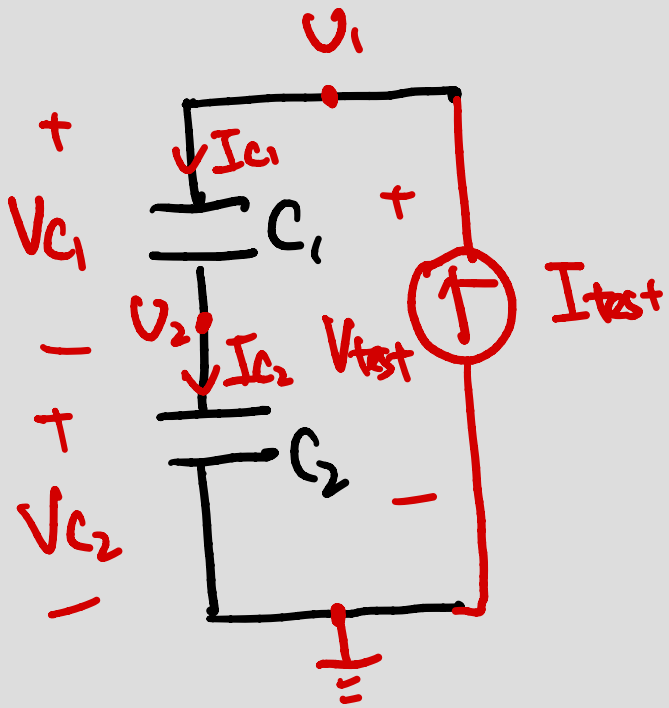

$$\text{KCL: } I_{C1} = I_{C2} = I_{test}$$

Elem Definition:

$$I_{C2} = C_2 \frac{dV_{C2}}{dt}$$

$$I_{C1} = C_1 \frac{dV_{C1}}{dt}$$

$$V_{C2} = U_2 - 0 = U_2$$

$$V_{C1} = U_1 - U_2$$

$$V_{test} = U_1$$

$$\text{For } V_{C_2}: \quad I_{\text{test}} = I_{C_2} = C_2 \frac{dV_2}{dt} \Rightarrow \frac{dV_2}{dt} = \frac{I_{\text{test}}}{C_2}$$

$$\text{For } V_{C_1}: \quad I_{C_1} = C_1 \frac{dV_1 - dV_2}{dt} \Rightarrow \frac{I_{C_1}}{C_1} = \frac{I_{\text{test}}}{C_1} = \frac{dV_1 - dV_2}{dt}$$


$$\frac{dV_1}{dt} = \frac{I_{\text{test}}}{C_1} + \frac{dV_2}{dt} \xrightarrow{\text{substitute}} \frac{dV_1}{dt} = \frac{I_{\text{test}}}{C_1} + \frac{I_{\text{test}}}{C_2}$$

$$\frac{dV_{\text{test}}}{dt} = I_{\text{test}} \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$


$$C_{\text{eq}} = \frac{I_{\text{test}}}{\frac{dV_{\text{test}}}{dt}} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2} = C_1 // C_2 \quad \text{Series!}$$


Equivalent capacitors

Capacitors in Series

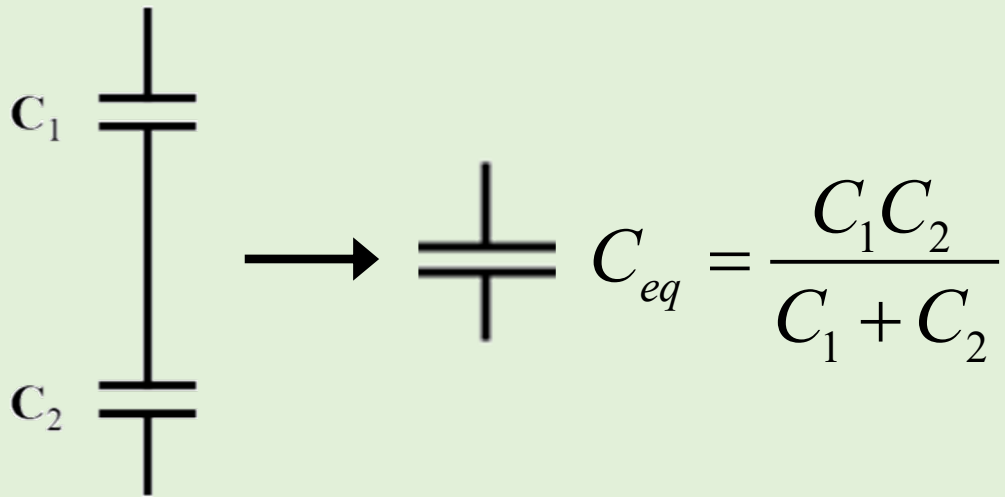


Capacitors in Parallel

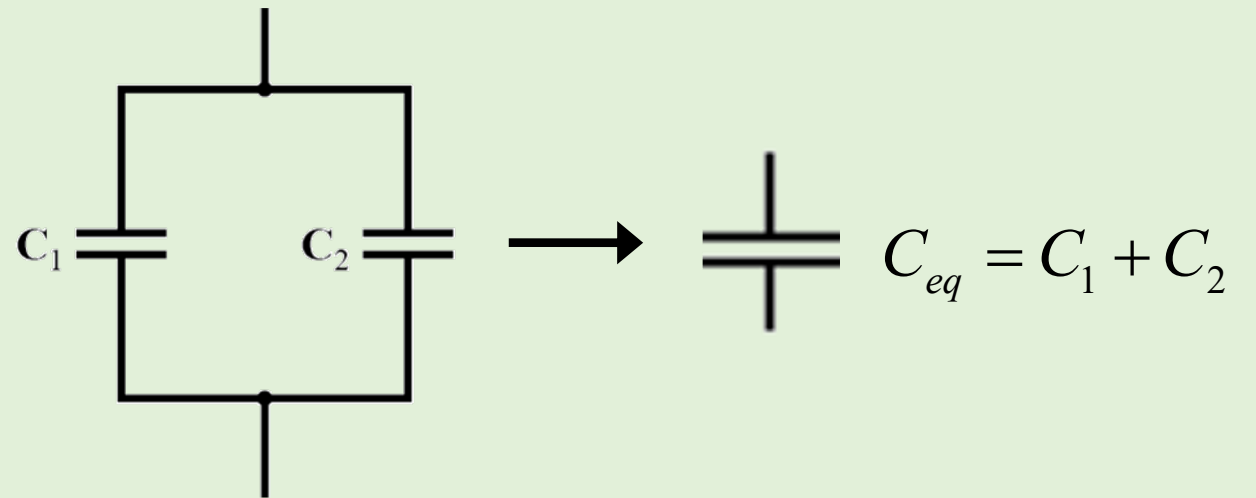


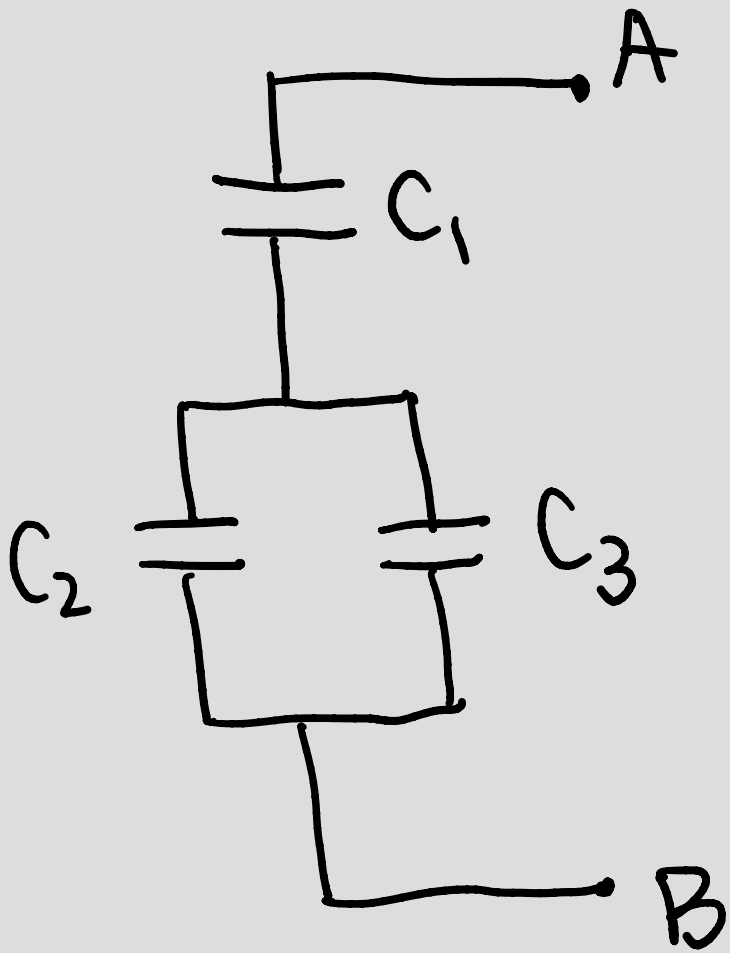

\Rightarrow

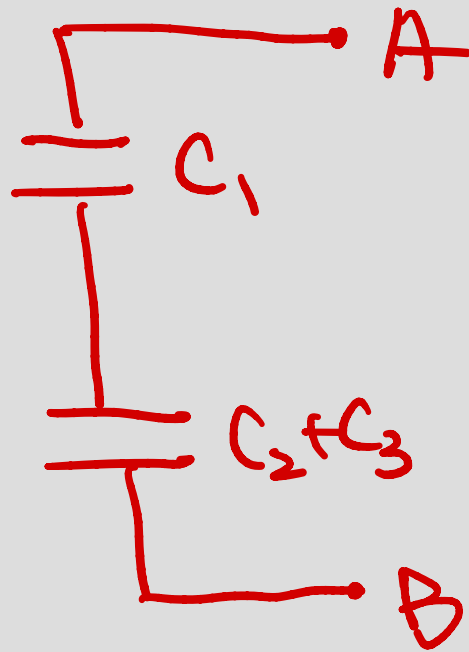


\Rightarrow


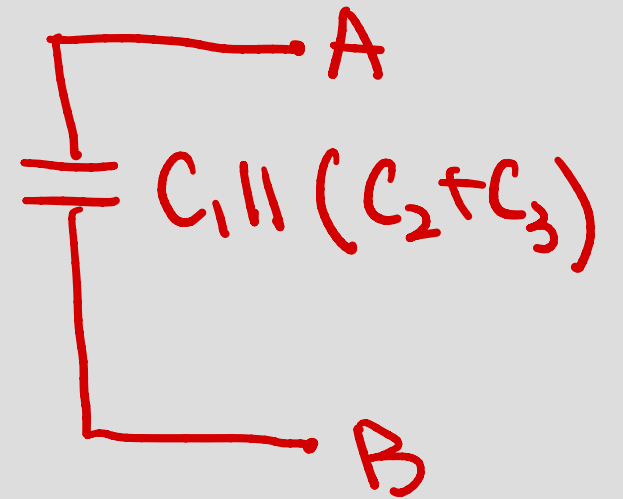


$$C_{eq} = C_1 \parallel (C_2 + C_3)$$

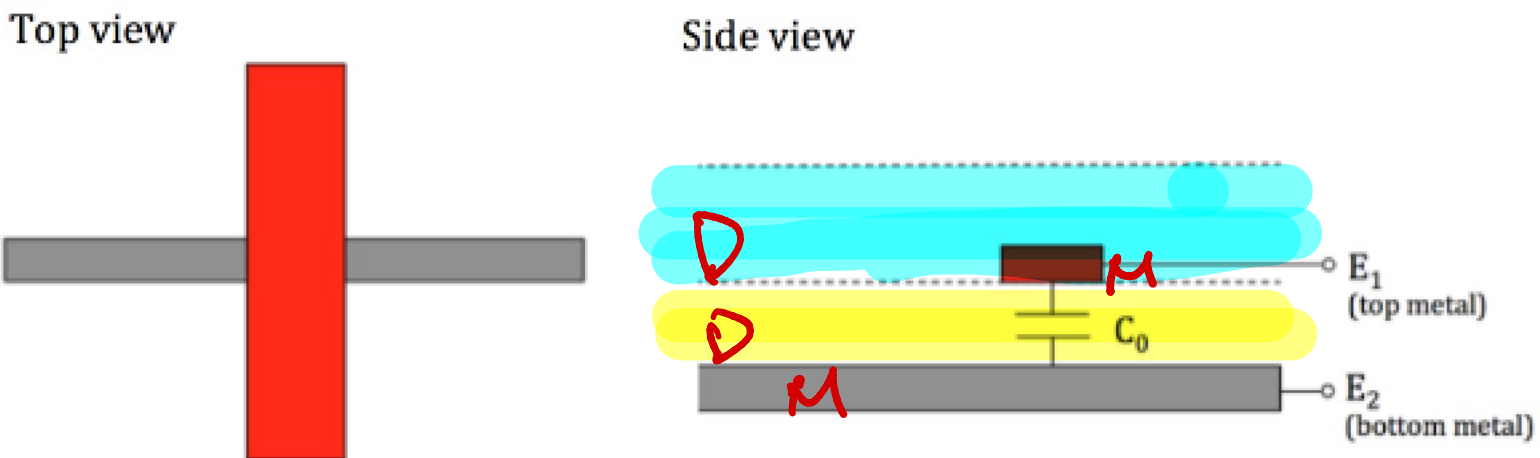Capacitive Touchscreen – Model without touch





M - metal
 D - dielectric

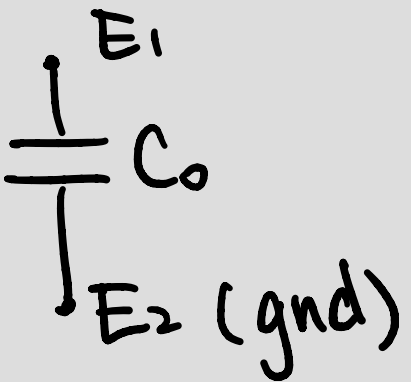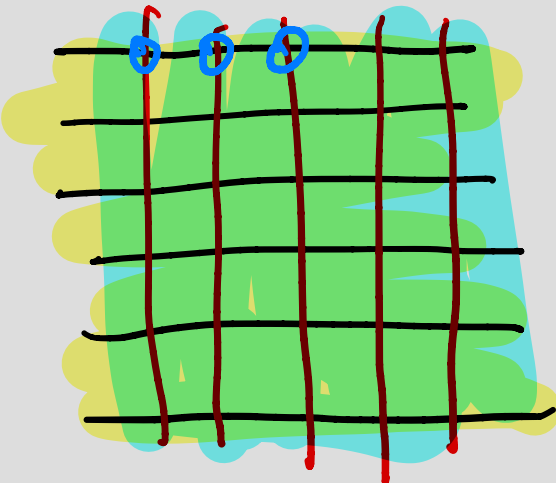


$$C_0 = \epsilon \frac{A}{d}$$

Capacitive Touchscreen – Model with touch


When there is touch, we form a capacitor

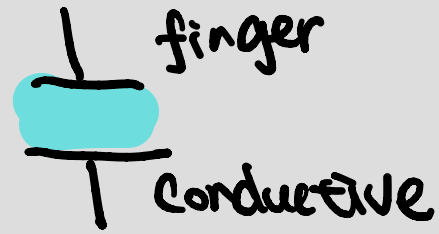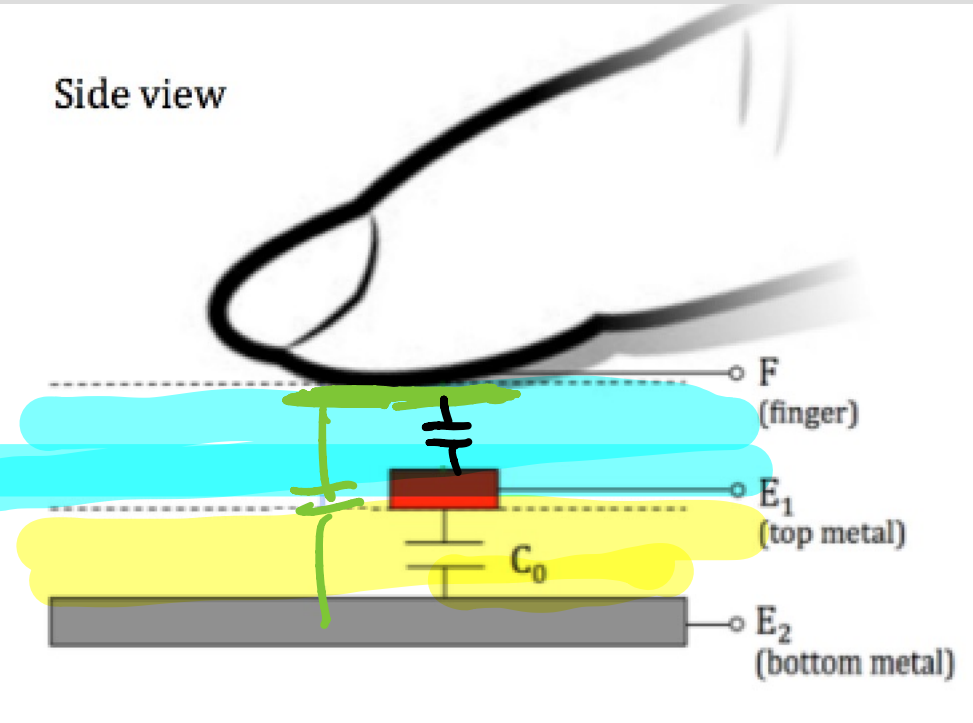

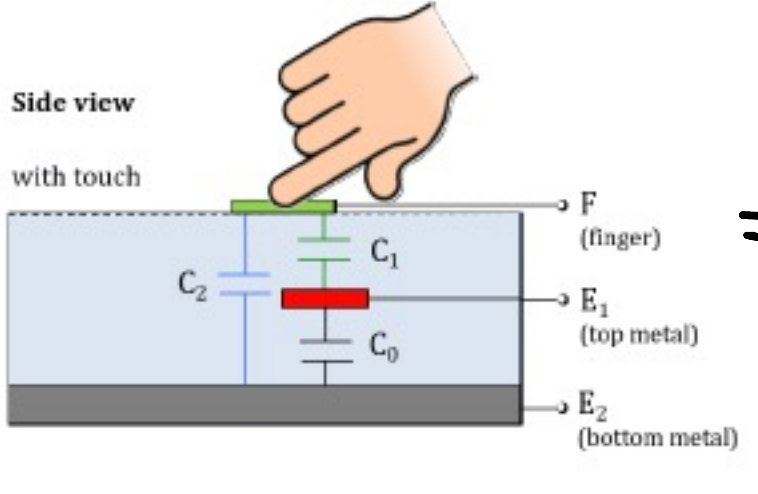Problem: How can we measure V or I if our electrode is a finger?




GrCUT model

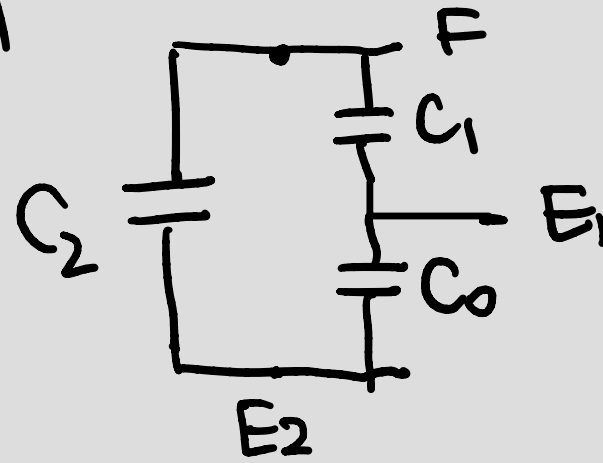



E₁ & E₂

When no touch

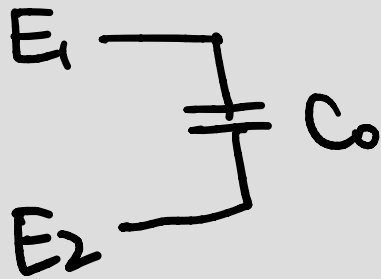

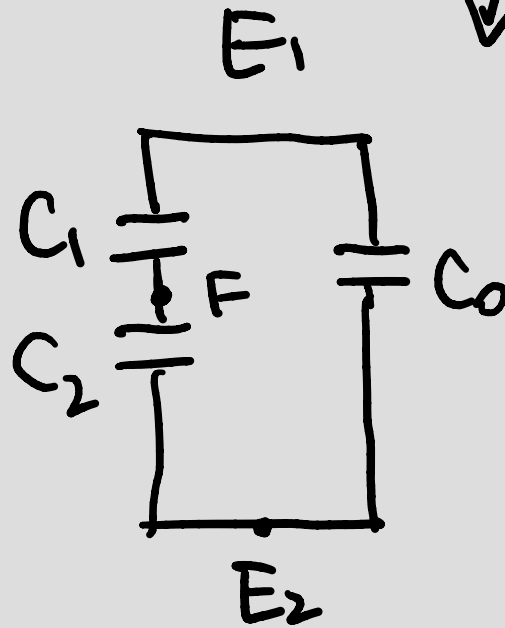
Redraw to focus on terminals we can measure



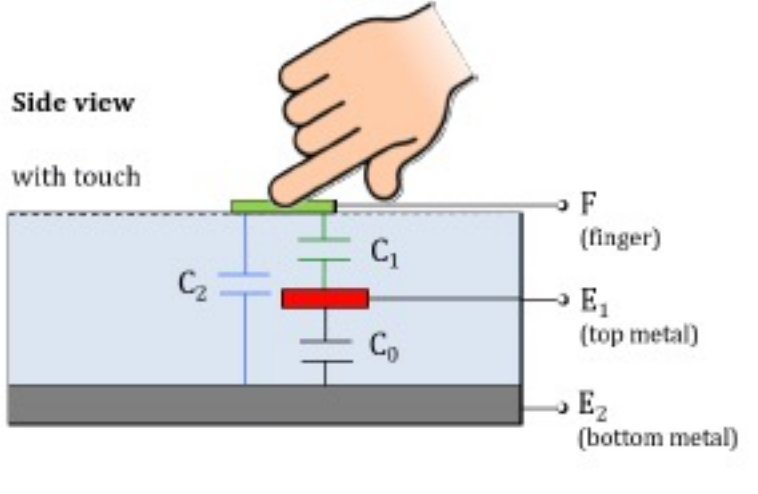


$$C_0 \parallel (C_1 \parallel C_2) = \frac{C_1 C_2}{C_1 + C_2}$$

No touch

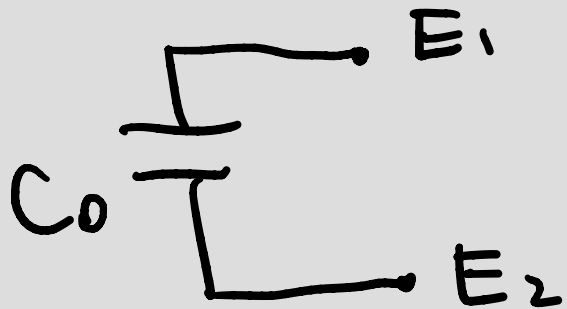

C_0


With Touch

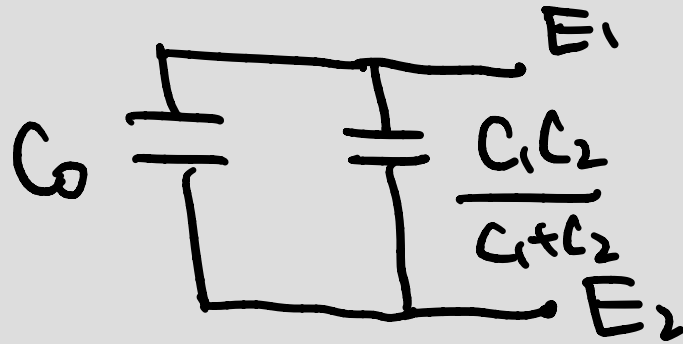


$$C_0 + \frac{C_1 C_2}{C_1 + C_2}$$

$$\frac{C_1 C_2}{C_1 + C_2} = C_{\Delta} \text{ (change)}$$

How do we measure change in capacitance?

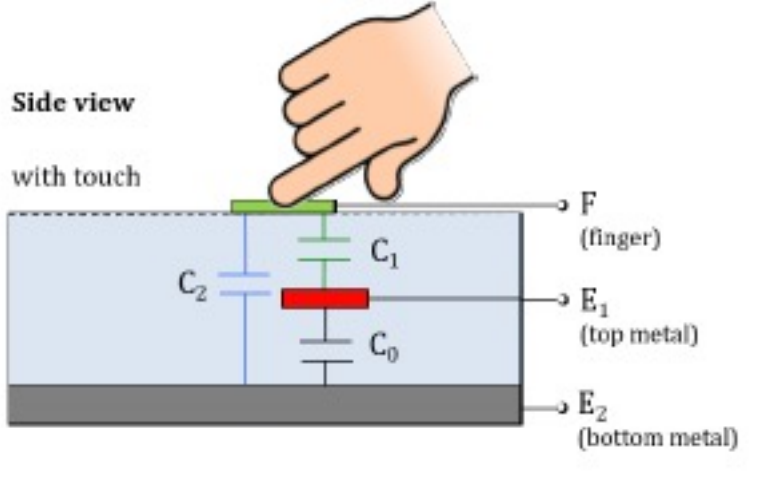

Option 1:

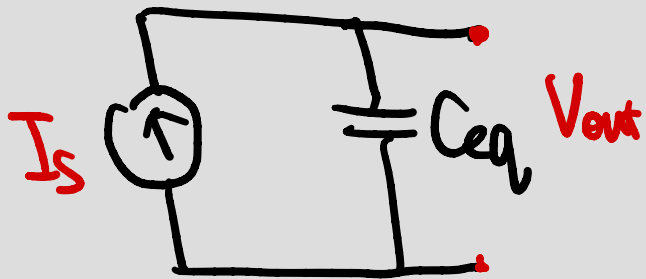


Assume $V_{out}(0) = 0$

$$I_s = C_{eq} \frac{dV_{out}(t)}{dt} \rightarrow V_{out}(t) = \int_0^t \frac{I_s}{C_{eq}} dt$$

$$V_{out} = \frac{I_s \cdot t}{C_{eq}} \Rightarrow C_{eq} = \frac{I_s \cdot t}{V_{out}}$$

Can't build current source easily

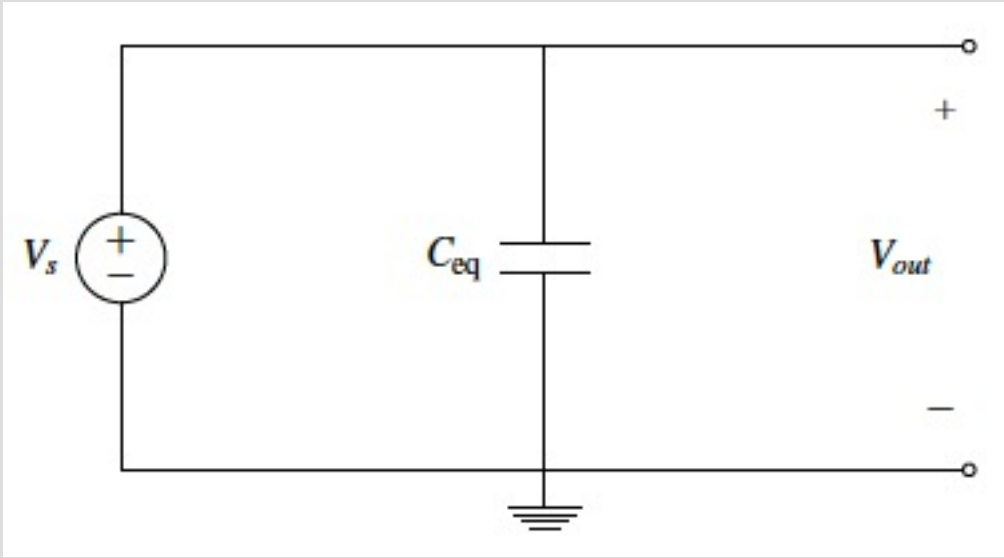Measuring Capacitance Models – Attempt #1




If there is touch : $V_{out} = V_s$

If there is no touch: $V_{out} = V_s$

Bad Idea!

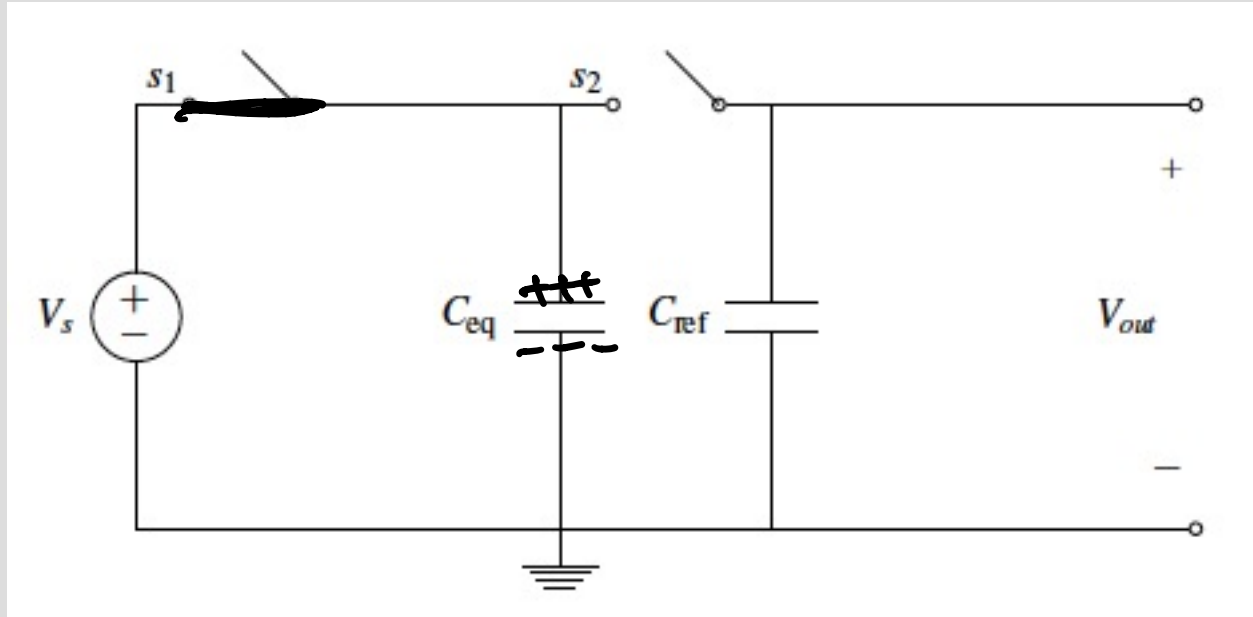Measuring Capacitance Models – Attempt #2 – add switches and a reference capacitor



① Close both switches


Same as before

② Phase 1: Close S_1 , open S_2

$$Q = V_s \cdot C_{eq}$$

Measuring Capacitance Models – Attempt #2 – add switches and a reference capacitor


Phase 2:
Close S_2 , open S_1

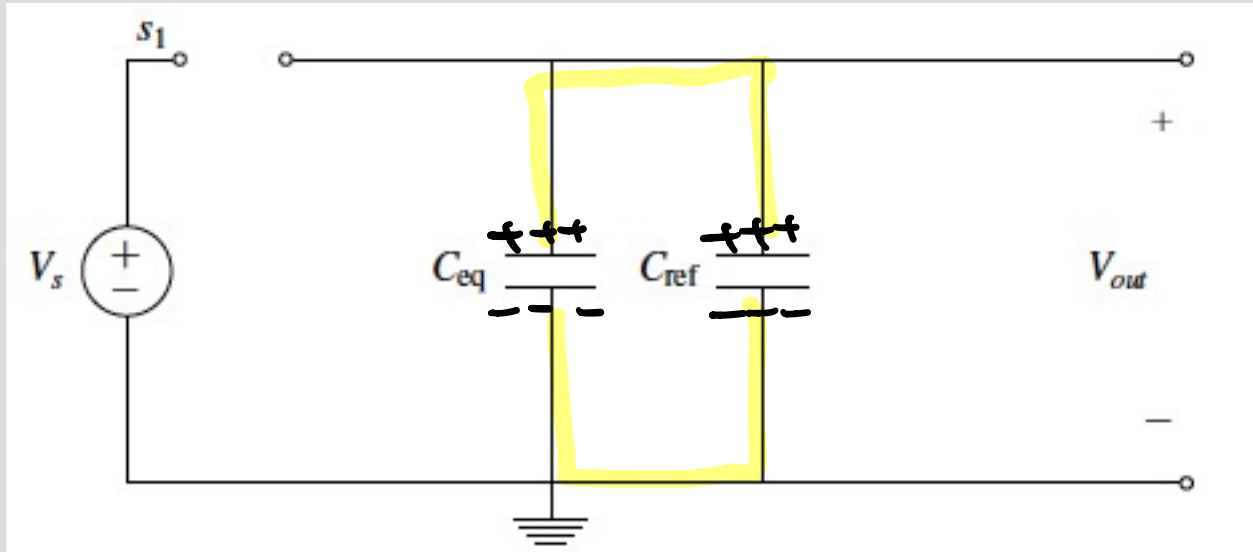

Initial condition?

Charge sharing

Measuring Capacitance Models – Attempt #3 – known initial condition

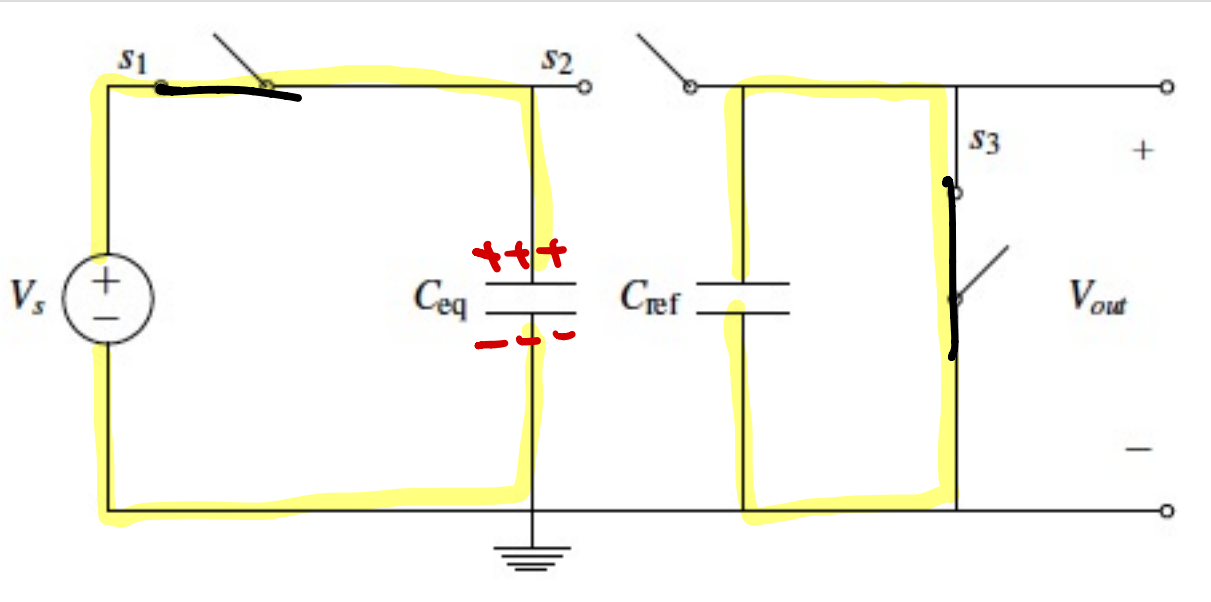

Phase 1: S_1, S_3 closed, S_2 open

– Charge C_{eq}


– Discharge C_{ref}

$$Q_{ref} = C_{ref} \cdot V_{out} = 0 \quad (V_{out} = 0)$$

$$Q_{eq} = C_{eq} \cdot V_s$$

Measuring Capacitance Models – Attempt #3 – known initial condition

redistribute, until same voltage

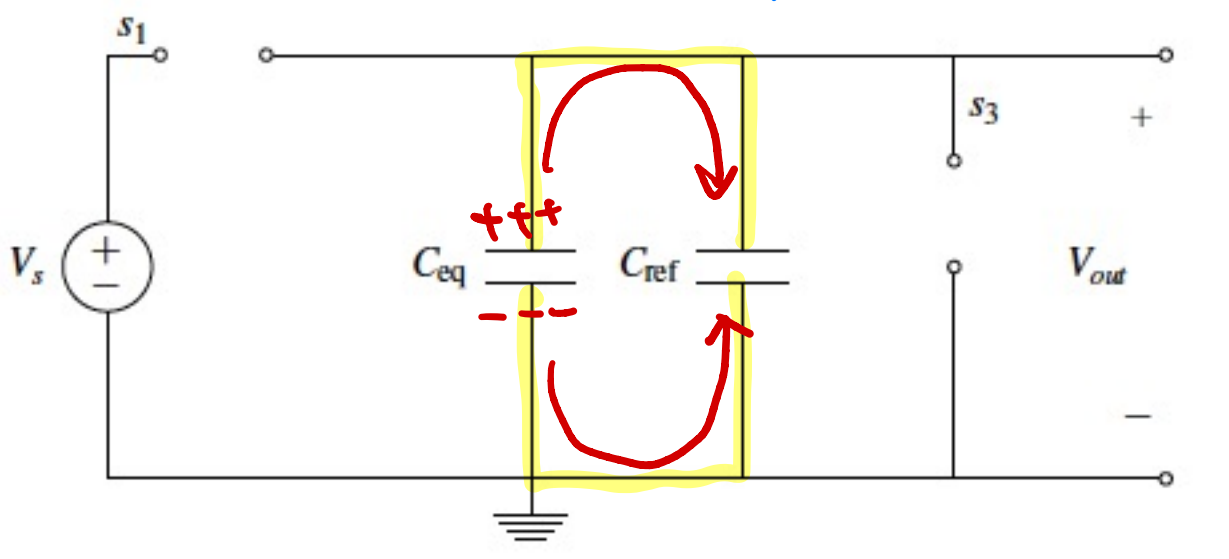

Phase 2: S_1, S_3 open, S_2 closed

Voltage across C_{eq} : V_{out}

Voltage across C_{ref} : V_{out}

$$Q_{total_2} = C_{eq} \cdot V_{out} + C_{ref} \cdot V_{out}$$

Effect of touch on total capacitance

Total charge is conserved!!



$$Q_{\text{total}1} = Q_{\text{total}2}$$

$$C_{\text{eq}} \cdot V_s = C_{\text{eq}} \cdot V_{\text{out}} + C_{\text{ref}} \cdot V_{\text{out}}$$


$$V_{\text{out}} = \frac{C_{\text{eq}}}{C_{\text{eq}} + C_{\text{ref}}} \cdot V_s$$

By touching, we change voltage

Effect of touch on total capacitance

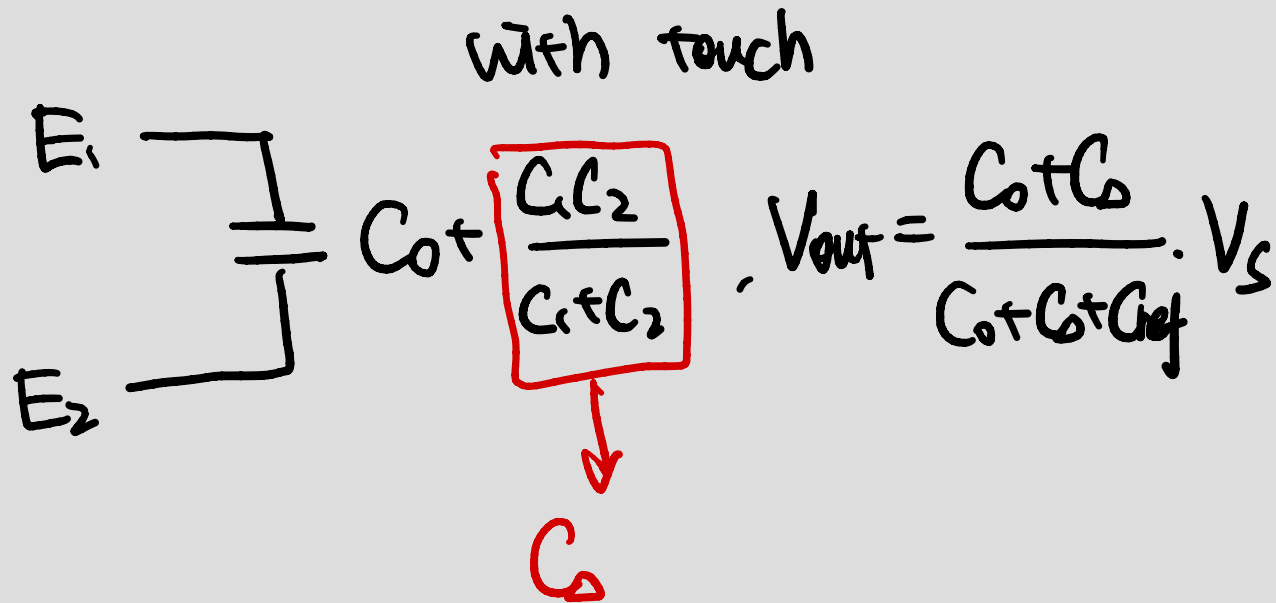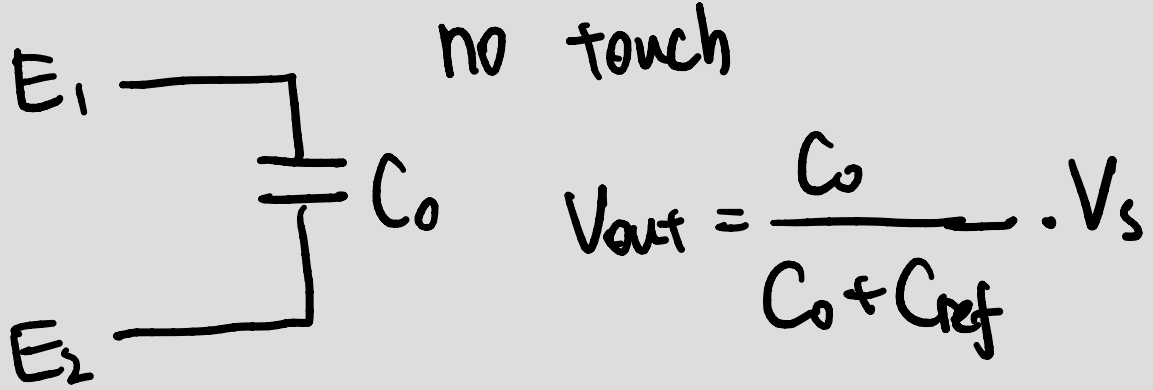

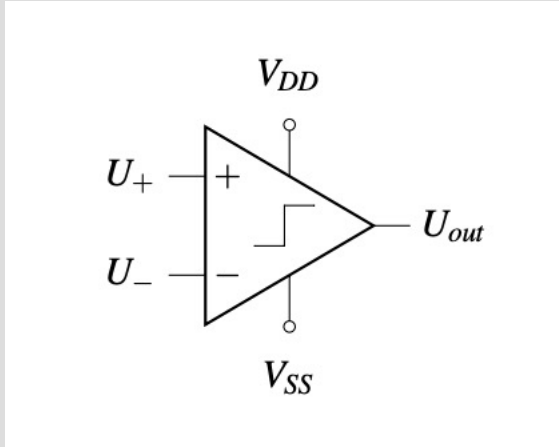How can we go from voltage measurement to binary answer: touch or no touch?




- Threshold Voltage (V_{th}):

between V_{out_touch} & $V_{out_notouch}$

- Above V_{th} : 1 (touch)


- Below V_{th} : 0 (no touch)

We need to compare V_{out} to V_{th}

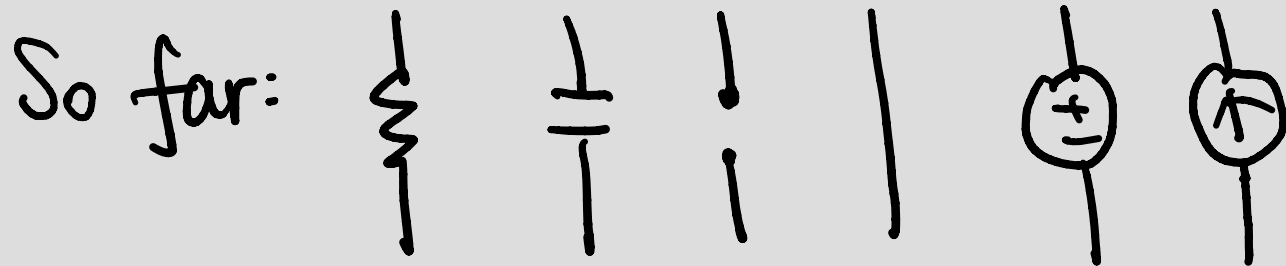

How can we go from voltage measurement to binary answer: touch or no touch?

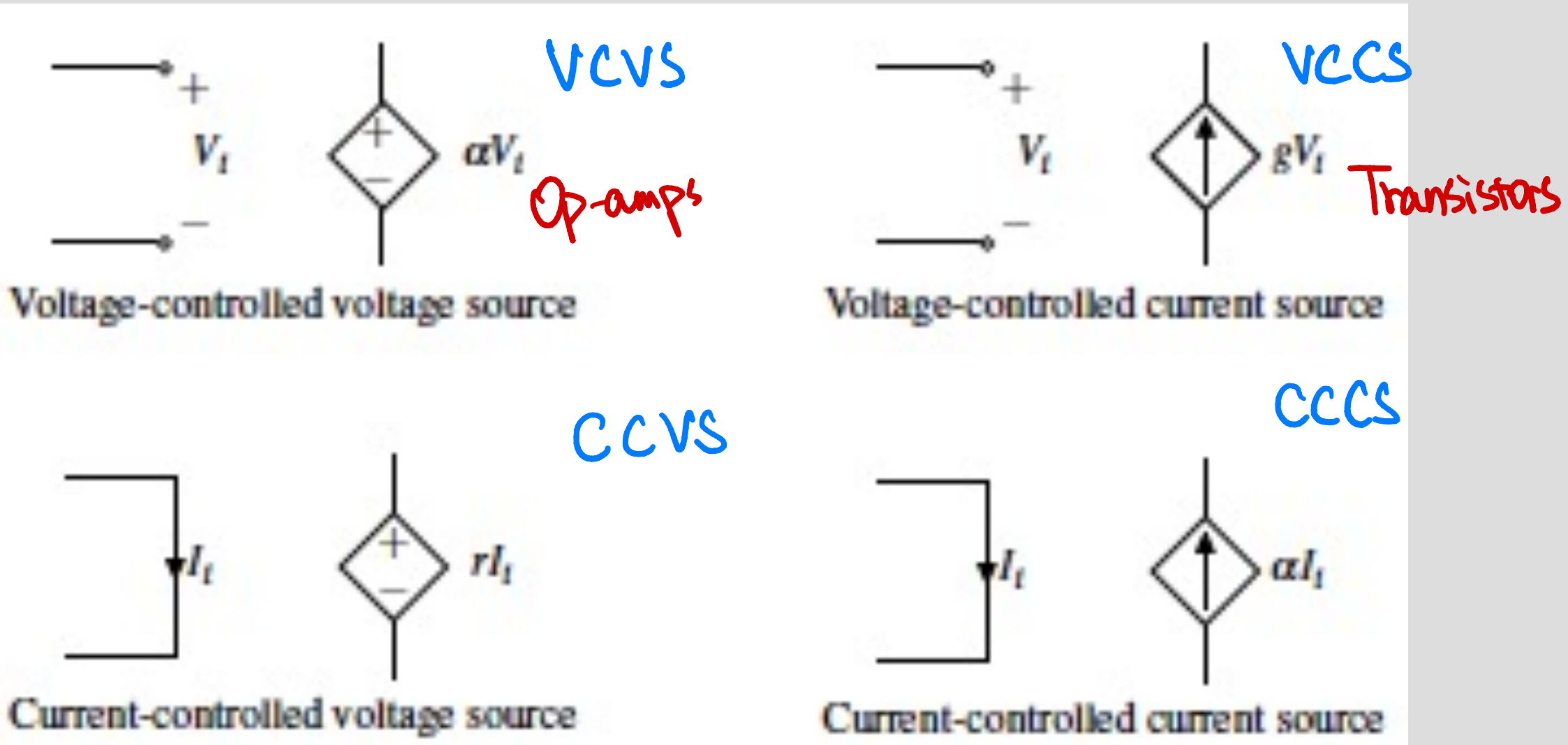
- New tools are needed – new circuit elements



An example of an Op-amp circuit diagram


EE105

EE140

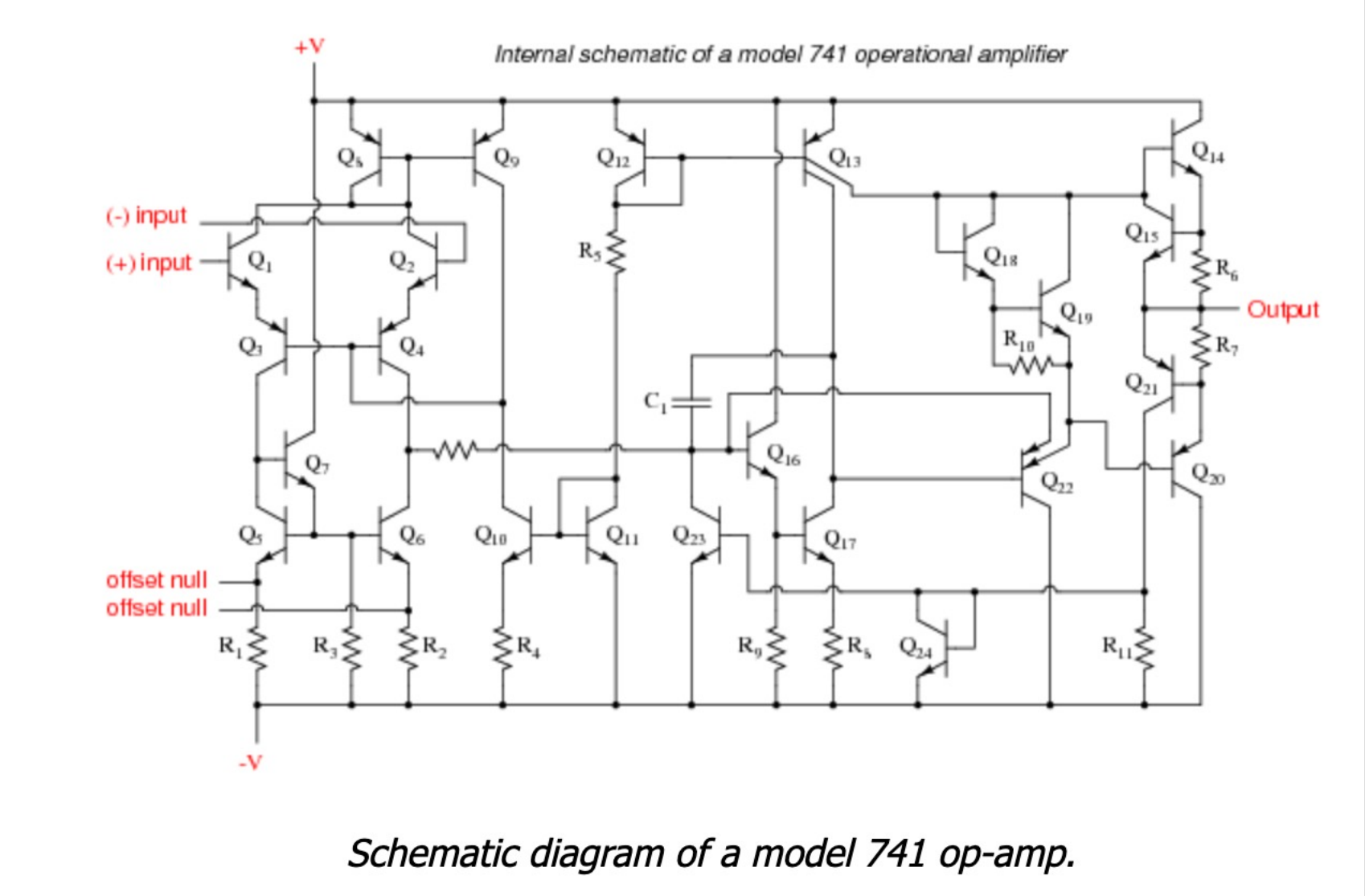


Operational Amplifier

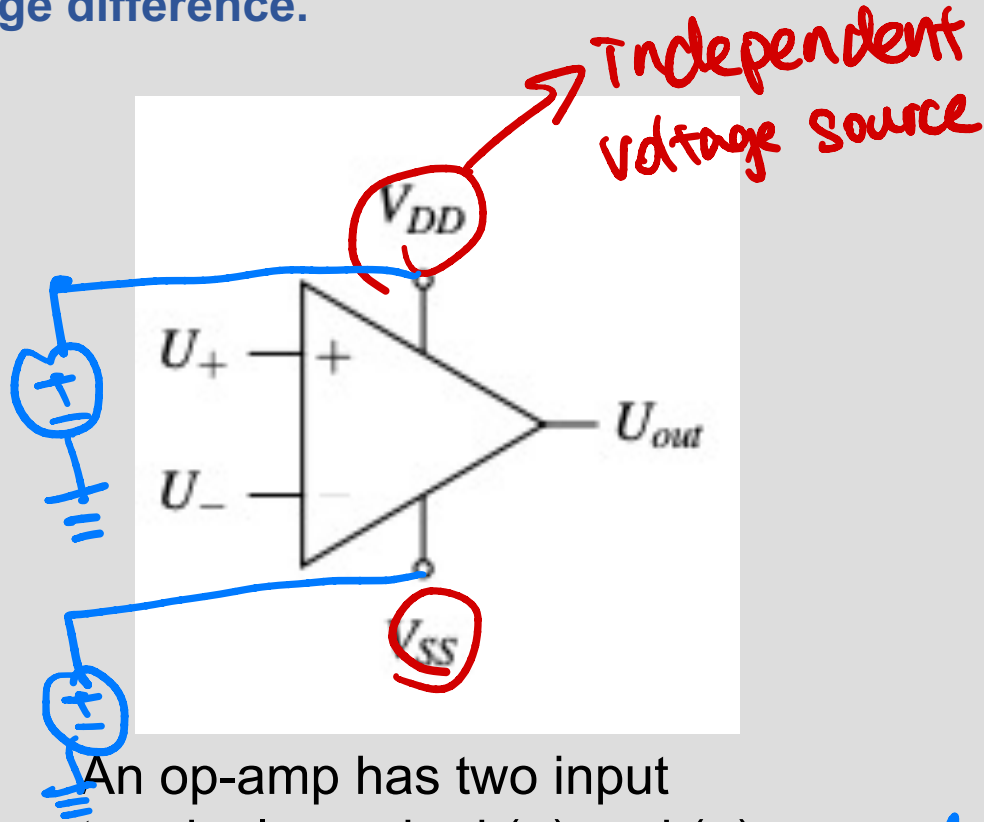An op-amp (operational amplifier) is a device that transforms a small voltage difference into a very large voltage difference.



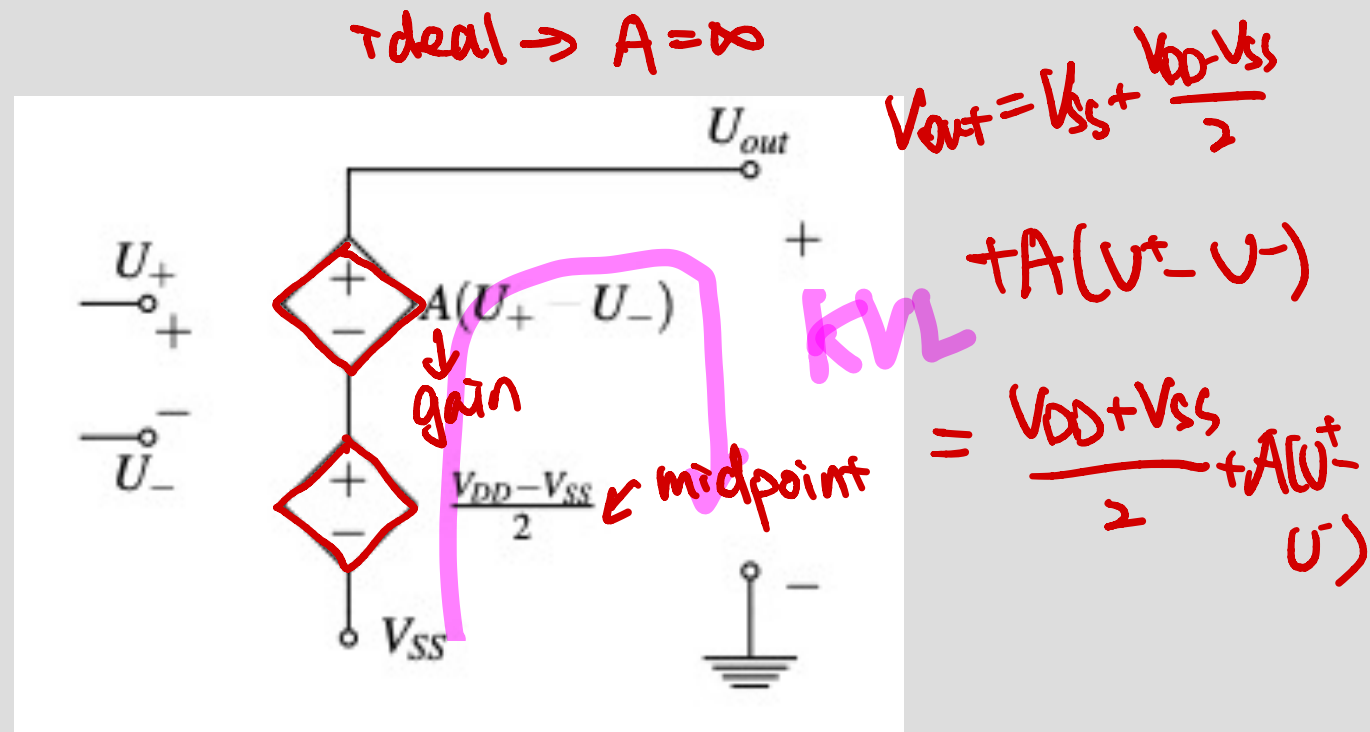An op-amp has two input terminals marked (+) and (-) with potentials U_+ and U_- , two power supply terminals called V_{DD} and V_{SS} , and one output terminal with potential U_{out} .



U_+ connect to V_{out}

U_- connect to V_{in}


V_{DD}, V_{SS} limits upper & lower bounds

Comparator – optimized for binary output & speed



$$V_{out} = V_{DD} \text{ if } V^* > V_{DD}$$

$$V_{out} = V_{SS} \text{ if } V^* < V_{SS}$$

Assume $A = \infty$

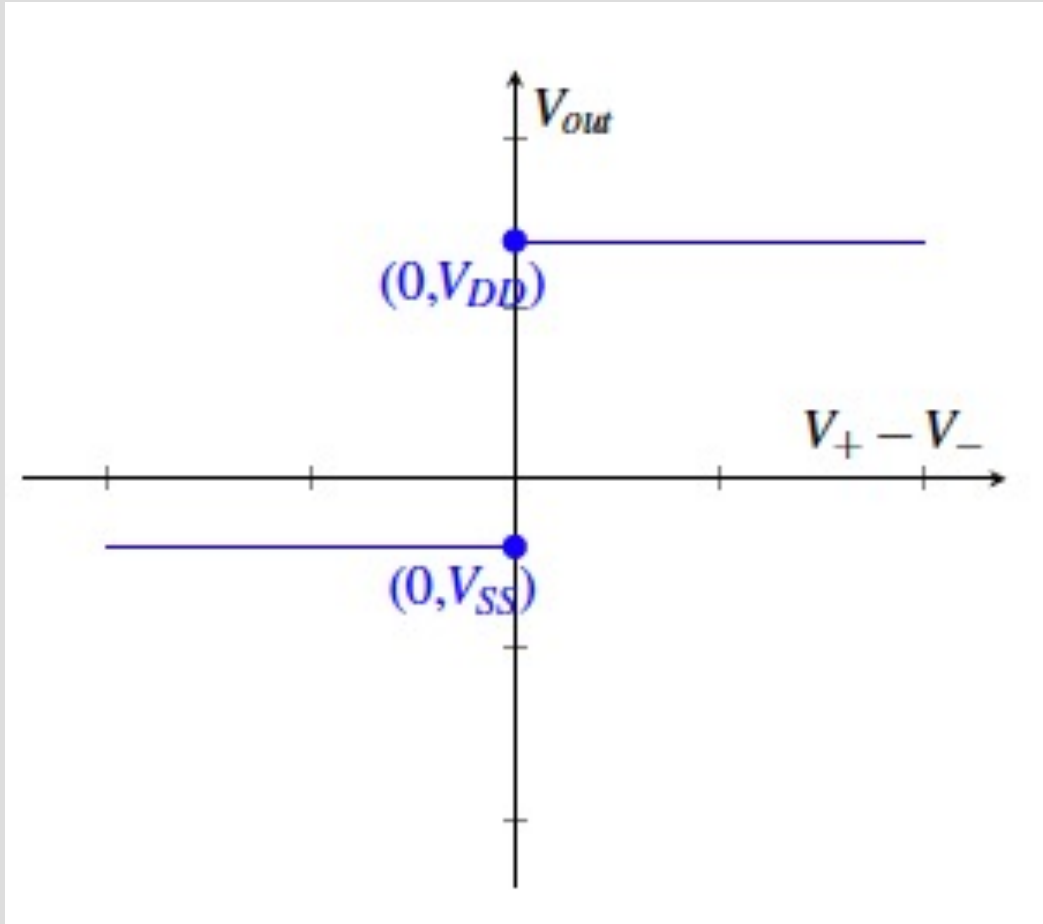


Comparator – optimized for binary output

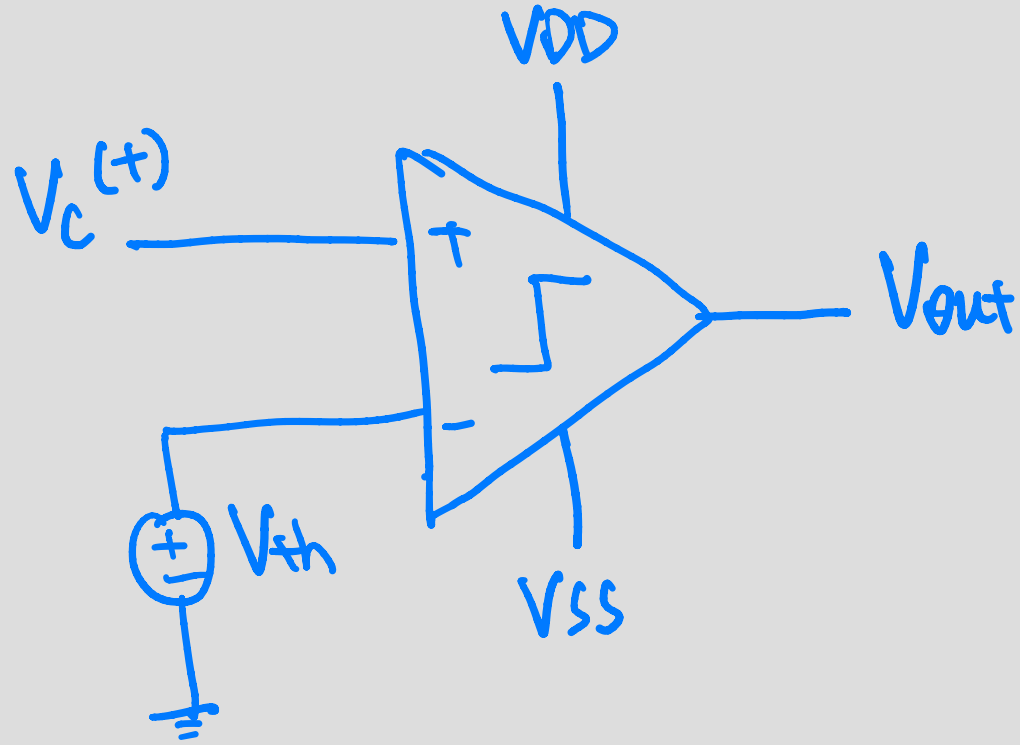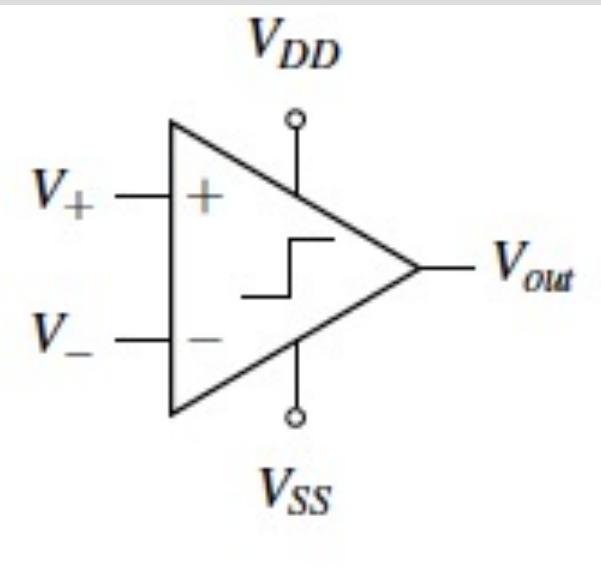

If $V_c(t) > V_{th}$, $V_{out} = V_{DD}$

If $V_c(t) \leq V_{th}$, $V_{out} = V_{SS}$

Back to our Capacitive Touchscreen

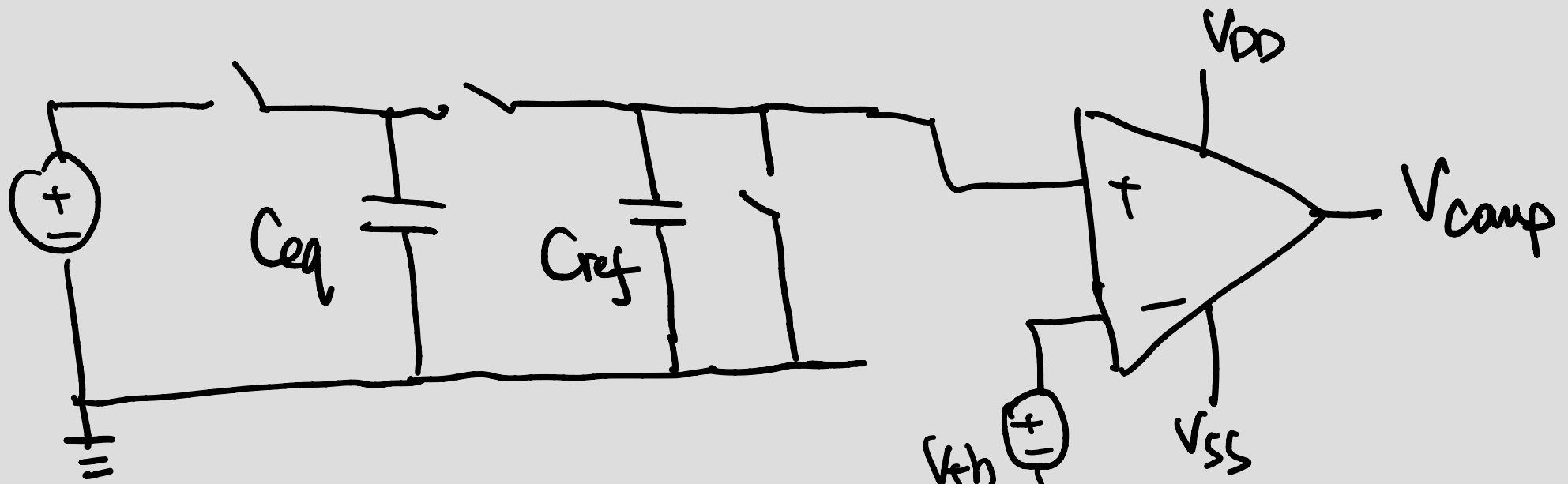

no touch
 V_{SS}

V_{DD} touch

V_{th}

between V_{touch} & $V_{notouch}$

Enjoy Spring Break!

