

EECS 16A Designing Information Devices and Systems I

Spring 2023 Discussion 7B

1. Resist the Touch

Investigate the $N \times N$ resistive touchscreen with vertical length L and horizontal width W shown in Figure 1. The touchscreen is constructed in two layers: a flexible conductive top layer comprised of N vertically oriented strips with even spacing $\frac{W}{N+1}$; and a rigid conductive bottom layer comprised of horizontally oriented strips with even spacing $\frac{L}{N+1}$.

The vertical and horizontal strips form a grid of detectable touch points. The upper left touch point in Figure 1(b) is position $(1, 1)$, and the upper right touch point is $(N, 1)$. All strips in top and bottom layers have equal resistivity, ρ , and cross-sectional area, A .

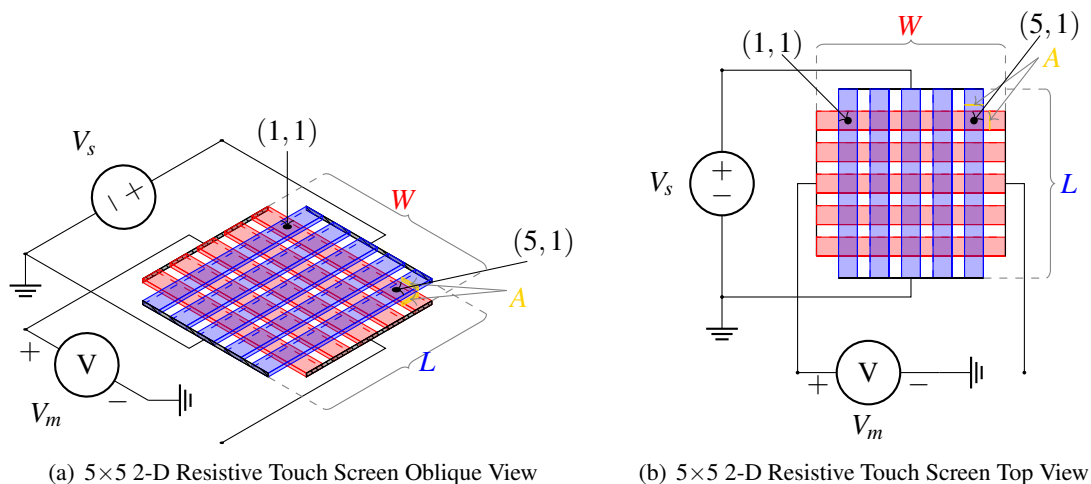


Figure 1: $N \times N$ Resistive Touch Screen, $N = 5$

- (a) Find the resistance R_y for a single vertical blue strip and R_x for a single horizontal red strip as a function of the screen dimensions W and L , the strip resistivity ρ , and the cross-sectional area A .

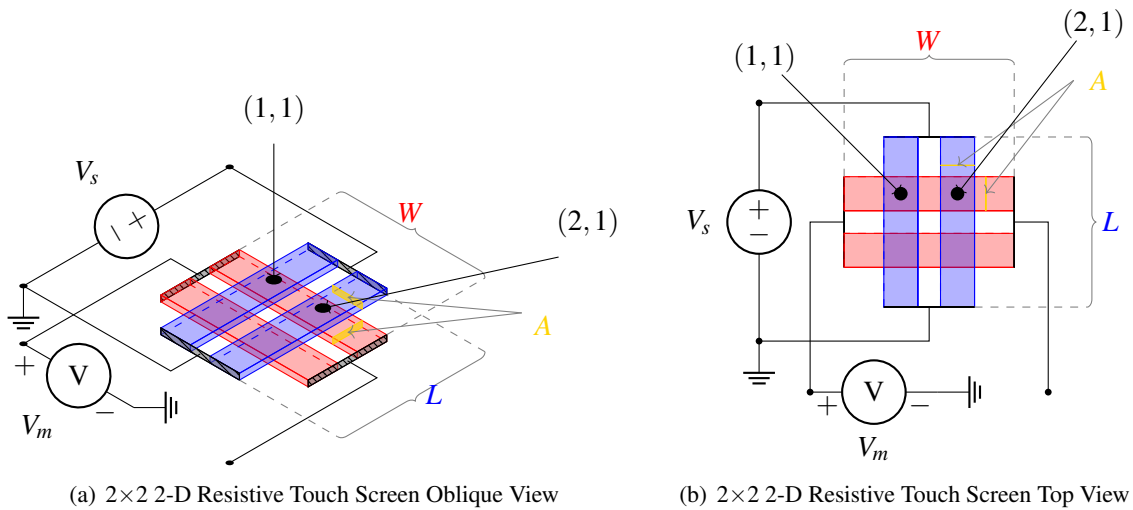


Figure 2: 2×2 Resistive Touch Screen

(b) Consider a 2×2 example for the touchscreen circuit, as shown in Figure 2.

Assume a voltage source V_s is connected from the top to bottom terminals of all the vertical (blue) strips, and a voltmeter V_m is connected from the left terminal of all horizontal (red) strips to the negative terminal of the voltage source.

If $V_s = 3\text{ V}$, $R_x = 2000\ \Omega$, and $R_y = 2000\ \Omega$, draw the equivalent circuit for when the point $(2, 2)$ is pressed and solve for the measured voltage, V_m , with respect to ground.

- (c) Suppose a touch occurs at coordinates (i, j) for an arbitrary $N \times N$ touchscreen, and the voltage source and meter are connected as in the diagrams. Find an expression for V_m as a function of V_s , N , i , and j .