

# EECS 16A    Designing Information Devices and Systems I

## Spring 2023    Discussion 9B

*Note to students:*


In this worksheet, we will begin exploring comparators (denoted by the little square wave within the triangle).

Here is the inherent logic of a comparator:

- If  $V_+ > V_-$ , then  $V_{out} = V_{DD}$  (positive supply rail)
- If  $V_+ < V_-$ , then  $V_{out} = V_{SS}$  (negative supply rail)

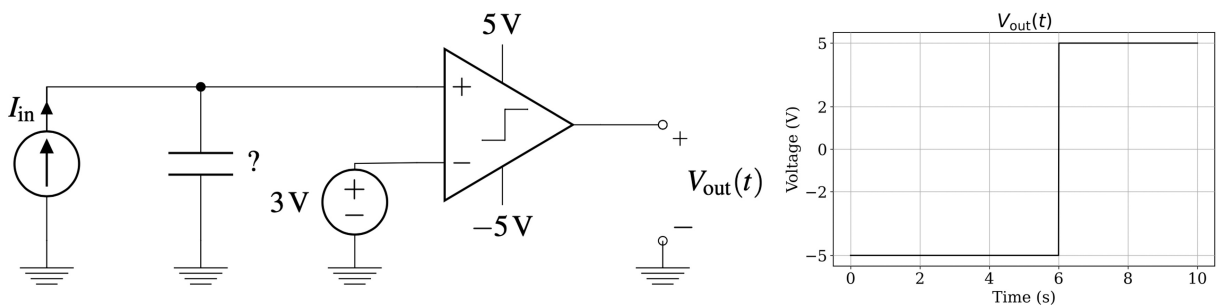
### 1. Comparators

We want to find the value of an unknown capacitor using the comparator outputs. For the circuit shown below (left),  $I_{in1} = 1\mu\text{A}$ ,  $I_{in2} = 3\mu\text{A}$ , and  $I_{in3} = 0.5\mu\text{A}$  and the initial voltage across the capacitor is 0 when  $t = 0$ . The plot of  $V_{out}(t)$  for time  $t$  from 0-10s is shown on the right. Note that  $\mu = 10^{-6}$ . What is the value of the capacitor for each value of  $I_{in}$ ? *Note: the initial voltage across the capacitor at time  $t = 0$  is 0V in all three cases.*



## 2. Data Conversion Circuits

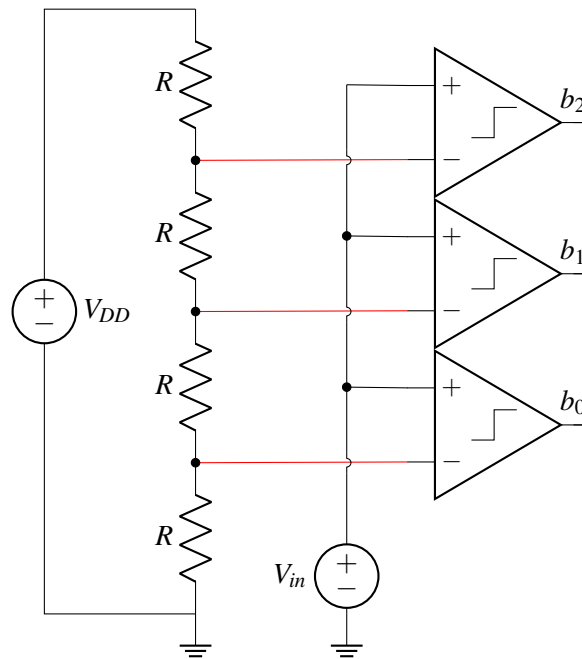- (a) The dual to DAC circuits are analog-to-digital converters, or ADC circuits. Here is an example of one, called a "Flash ADC," using resistors and comparators:



*Note: The red wires in the diagram are regular wires, but have been colored to show that they do not touch the crossing black wires.*

The resistor ladder gives us a set of reference voltages to compare against. We use a set of comparators to compare the input voltage  $V_{in}$  against these reference levels, and we get out a corresponding digital code  $b_0$ ,  $b_1$ , and  $b_2$ .

Assume that  $V_{DD} = 1\text{ V}$ , and that the comparators are connected to rails  $V_{DD} = 1\text{ V}$  and  $V_{SS} = 0\text{ V}$ . If  $V_{in}$  is  $0.3\text{ V}$ , **what are the outputs  $b_0$ ,  $b_1$ , and  $b_2$ ?**