

---


# EECS 16A    Designing Information Devices and Systems I

## Spring 2023    Discussion 13A

---

### 1. Superposition

Consider the following circuit:

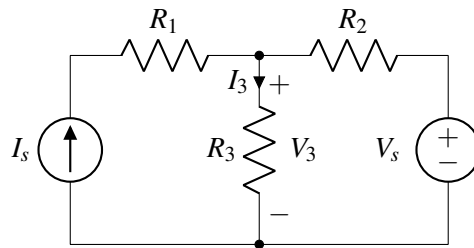


(a) With the current source turned on and the voltage source turned off, find the current  $I_3$ .

(b) With the voltage source turned on and the current source turned off, find the voltage drop  $V_3$  across  $R_3$ .


(c) Find the power dissipated by  $R_3$ .

### 2. Thévenin/Norton Equivalence

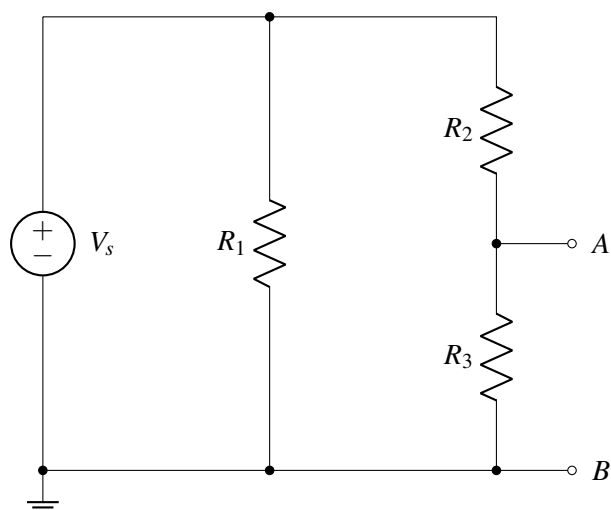
(a) Find the Thévenin resistance  $R_{th}$  of the circuit shown below, with respect to its terminals  $A$  and  $B$ .



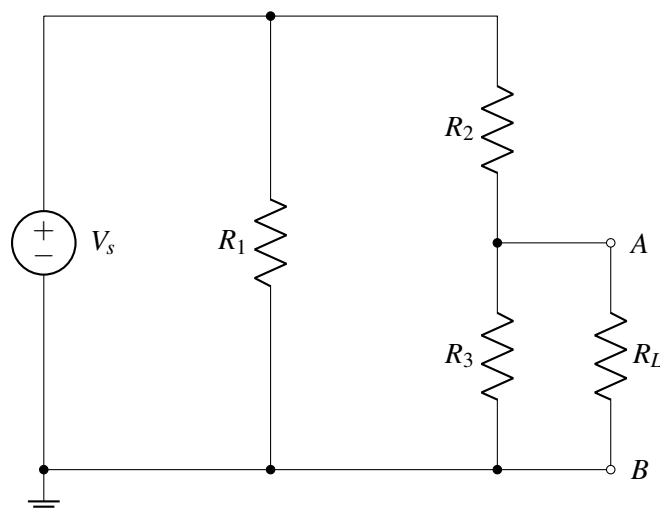- (b) Now a load resistor,  $R_L$ , is connected across terminals  $A$  and  $B$ , as shown in the circuit below. Using Thévenin equivalence, find the power dissipated in the load resistor in terms of the given variables.



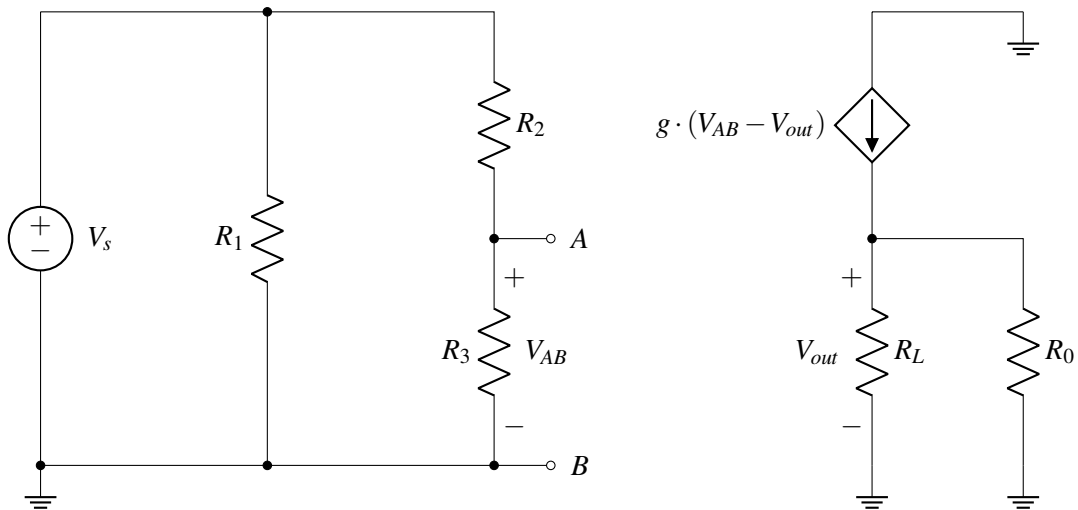- (c) We modify the circuit as shown below, where  $g$  is a known constant:




Find a symbolic expression for  $V_{out}$  as a function of  $V_s$ .

*Hint: Redraw the left part of the circuit using its Thévenin equivalent.*


### 3. A Versatile Opamp Circuit

For each circuit configuration, determine the voltage at  $O$ , given that  $v_1$  and  $v_2$  are voltage sources. All circuit configurations are in negative feedback.

(a) Configuration 1:

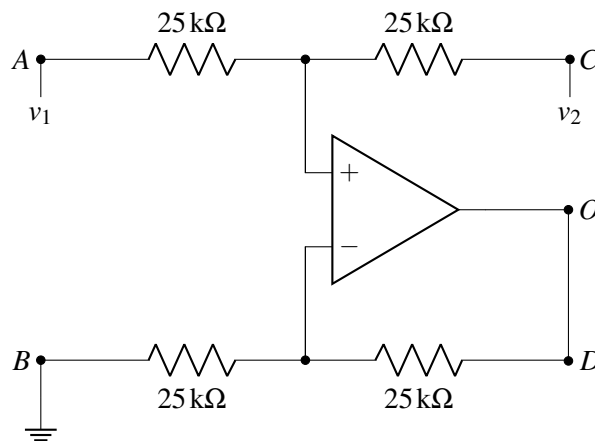

(b) Configuration 2:

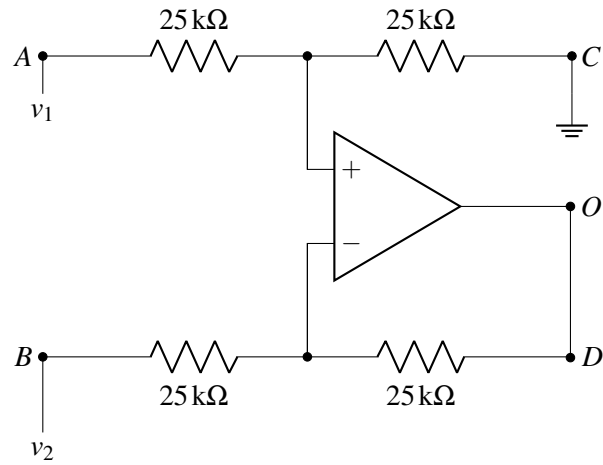

(c) Configuration 3:

