



EECS 16A

Spring 2023 - Profs. Muller & Waller
Lecture 11A – Op Amp Circuit Analysis

Toolbox

KVL: Voltage drops around a loop sum to 0


KCL: All currents coming out of a node sum to 0

$$V = IR$$

$$P = IV$$


$$R = \frac{\rho L}{A}$$
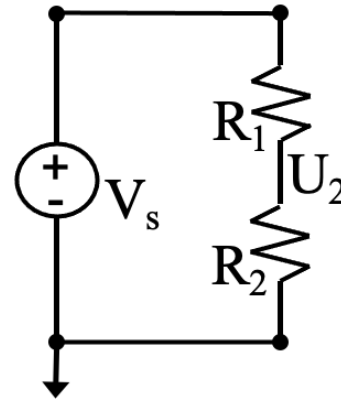
$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$



$$I = \frac{V_s}{R_1 + R_2}$$

$$U_2 = \frac{V_s R_2}{R_1 + R_2}$$

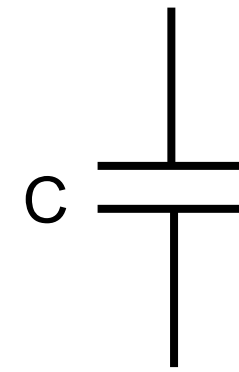


$$Q = CV$$

$$I = C \frac{dV}{dt}$$

$$C = \frac{\epsilon A}{d}$$


* $V_{\text{source}}(\text{off}) \rightarrow \text{short}$
 $I_{\text{source}}(\text{off}) \rightarrow \text{open}$

Thevenin Equivalent Circuit

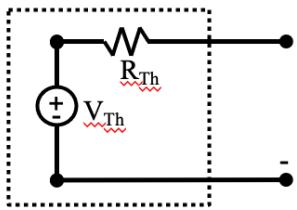


Measure V with open

Norton Equivalent Circuit

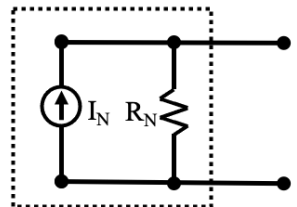


$$R_{Th} = V_{Th} / I_N$$


Measure I with short

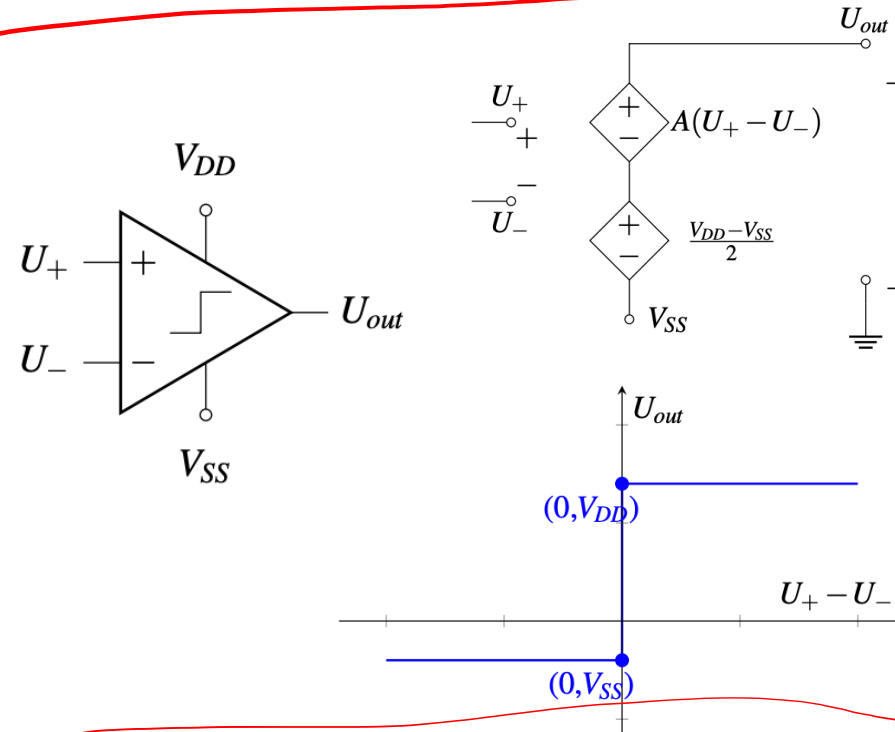



Capacitors in Series

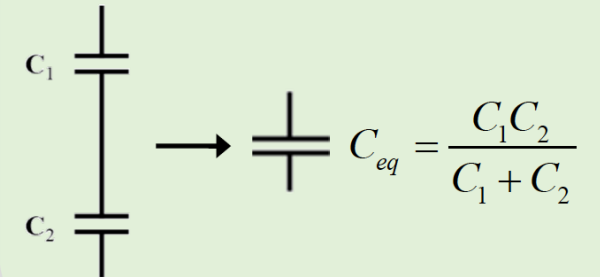




Capacitors in Parallel

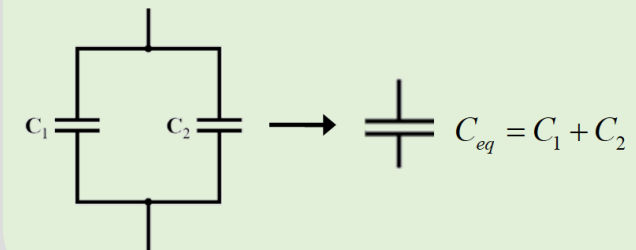



Recap: Op Amps

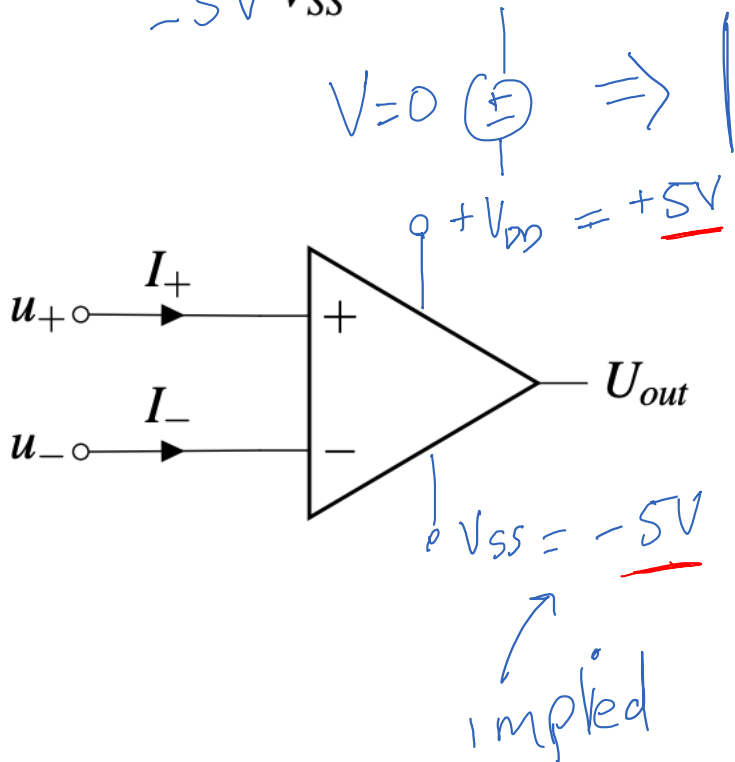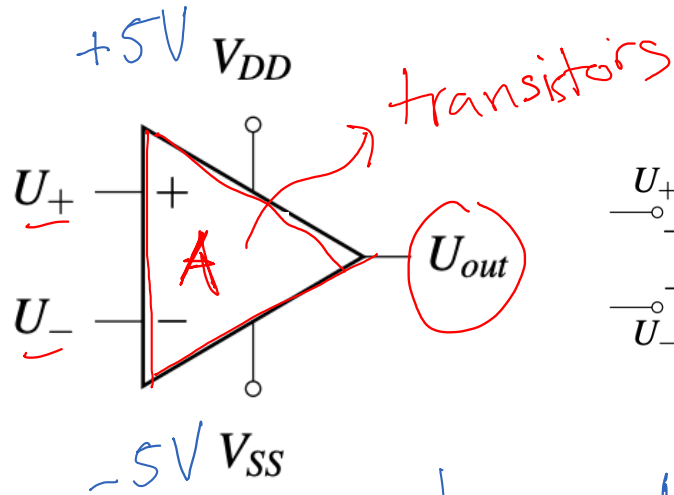

$V_{DD} > V_{SS}$

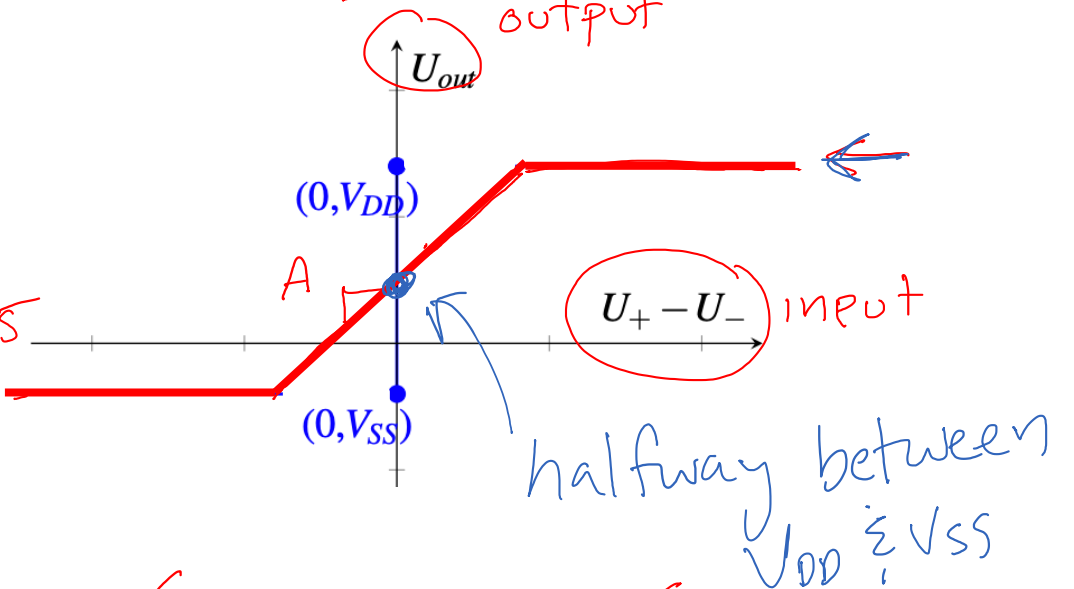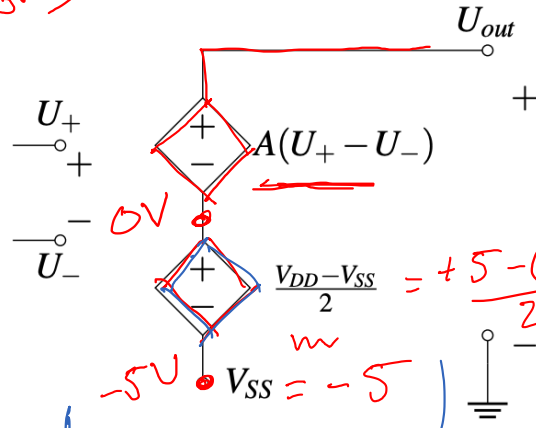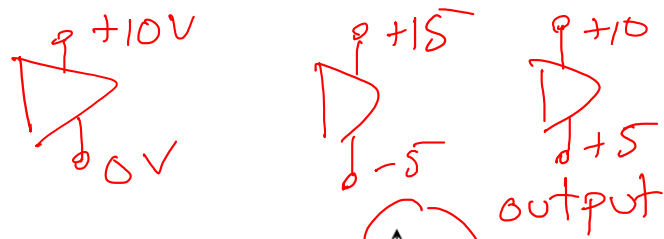

Simplified model:

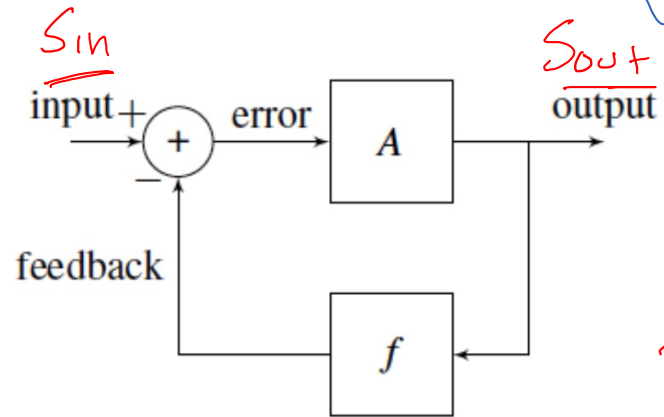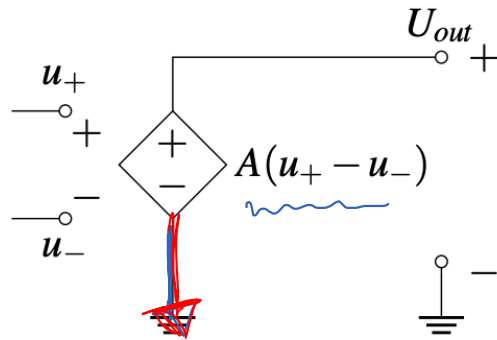


negative feedback


$$\frac{S_{out}}{S_{in}} = \frac{A}{1 + Af}$$

Black's formula

Recap: Need to Isolate DAC and Speaker!

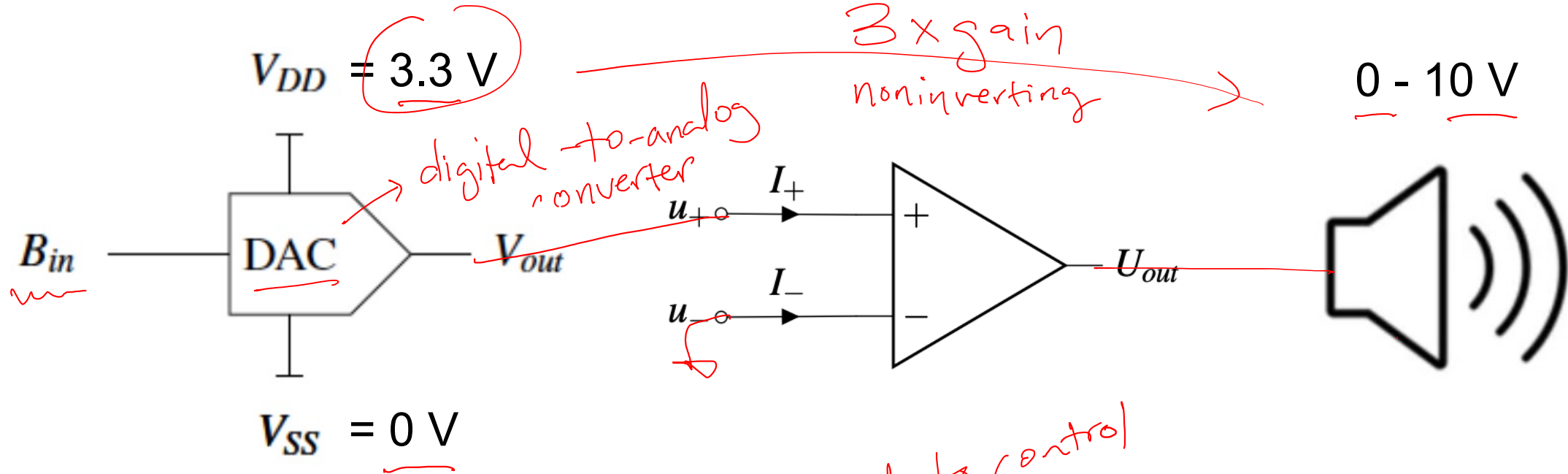


Thevenin Equivalent Circuit

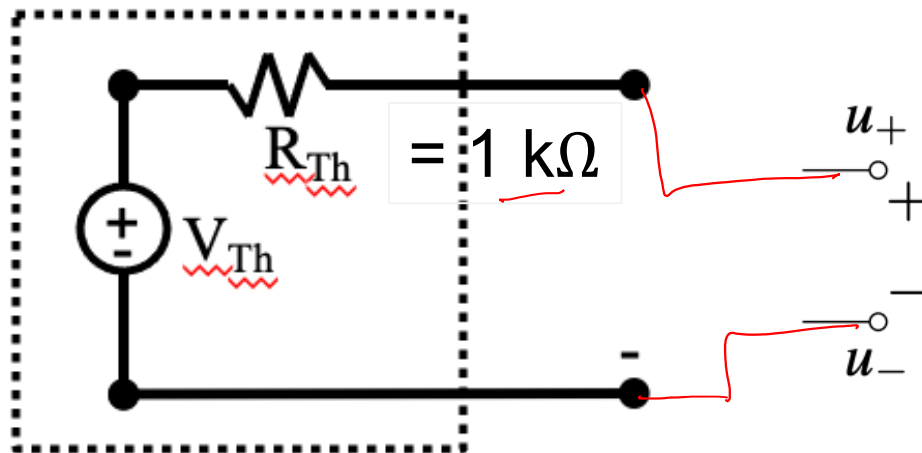

hard to control the gain



Thevenin Equivalent Circuit

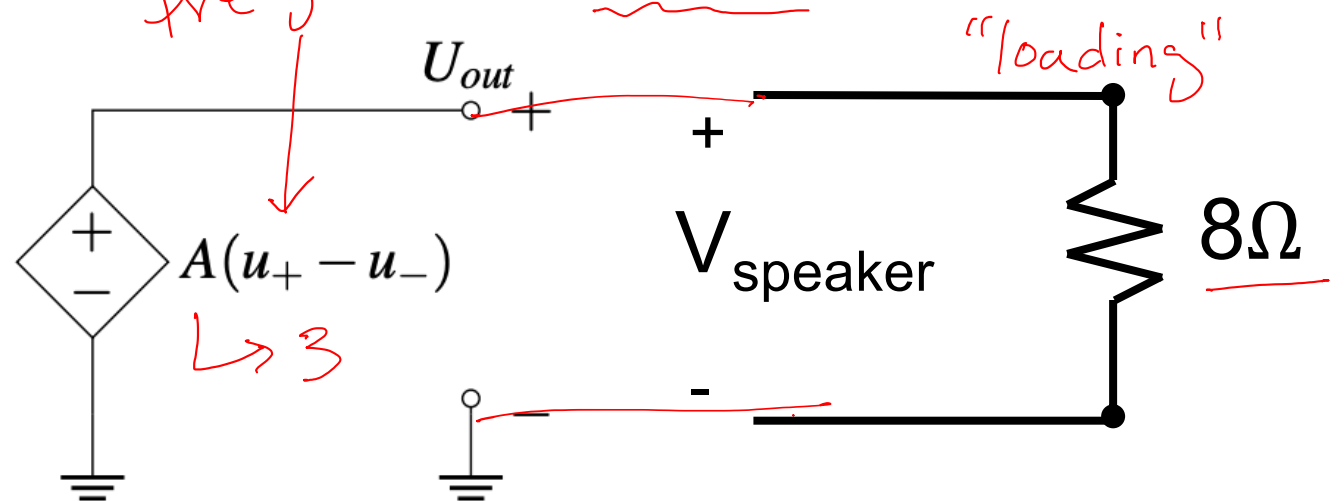

Recap: An Op Amp with Negative Feedback!

$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + Af}$$

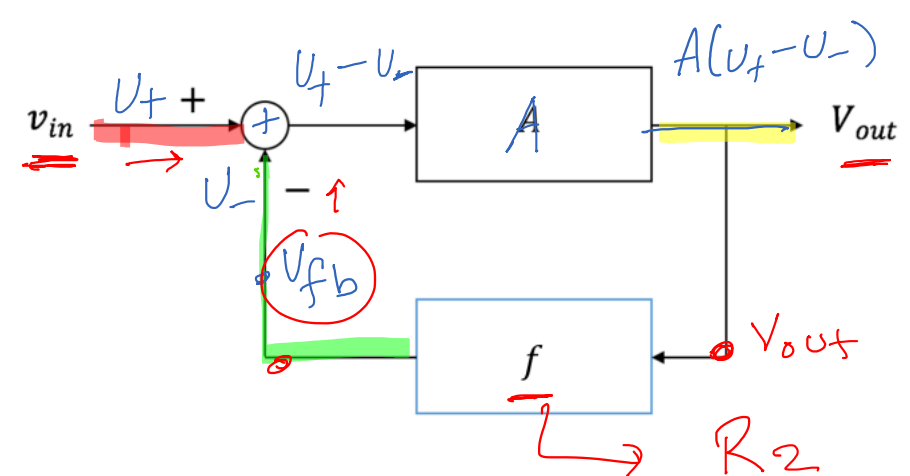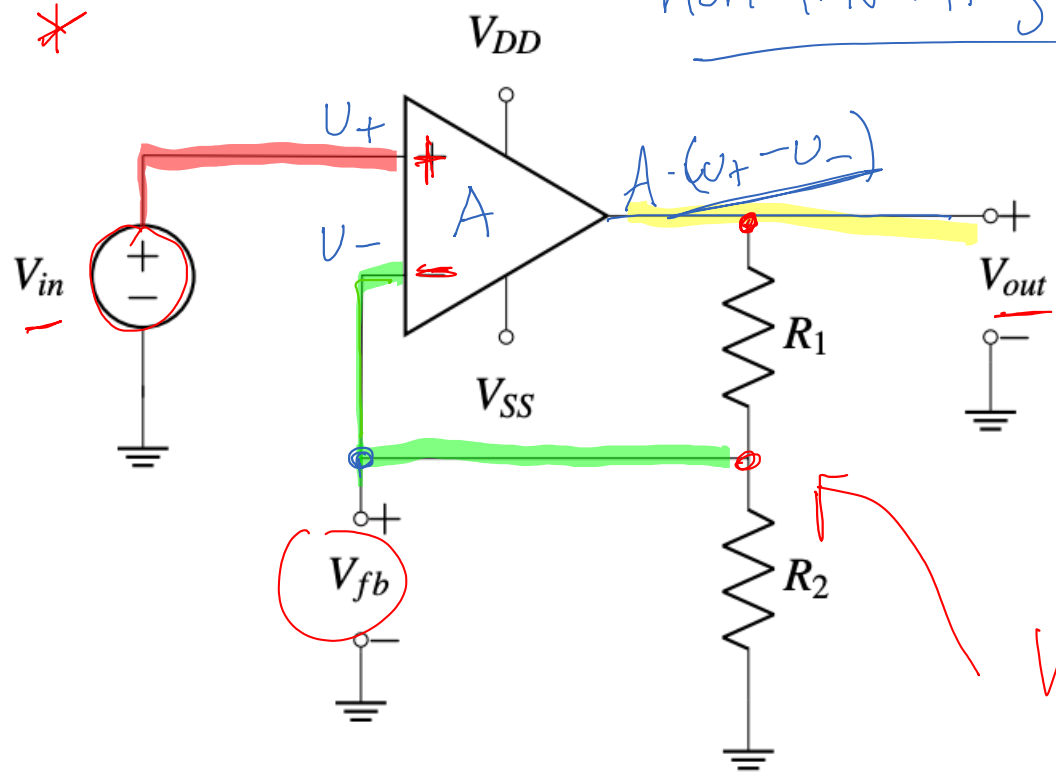
non-inverting amplifier *controls the gain*



$$V_{fb} = \frac{V_{out} \cdot R_2}{R_1 + R_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + A \left(\frac{R_2}{R_1 + R_2} \right)} = \frac{A}{A \left(\frac{R_2}{R_1 + R_2} \right)} = \frac{R_1 + R_2}{R_2} = \frac{R_1}{R_2} + 1$$

Need to Gain and Isolation

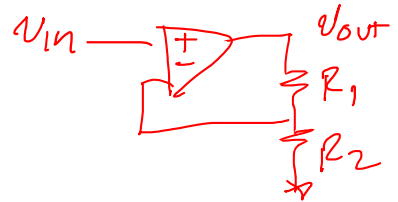


$$v_{out} = \left(\frac{R_1}{R_2} + 1 \right) v_{in}$$

$$= \frac{2k}{1k} + 1 = 3!$$

Speaker

DAC

Amplifier, Non-inverting Gain = 3

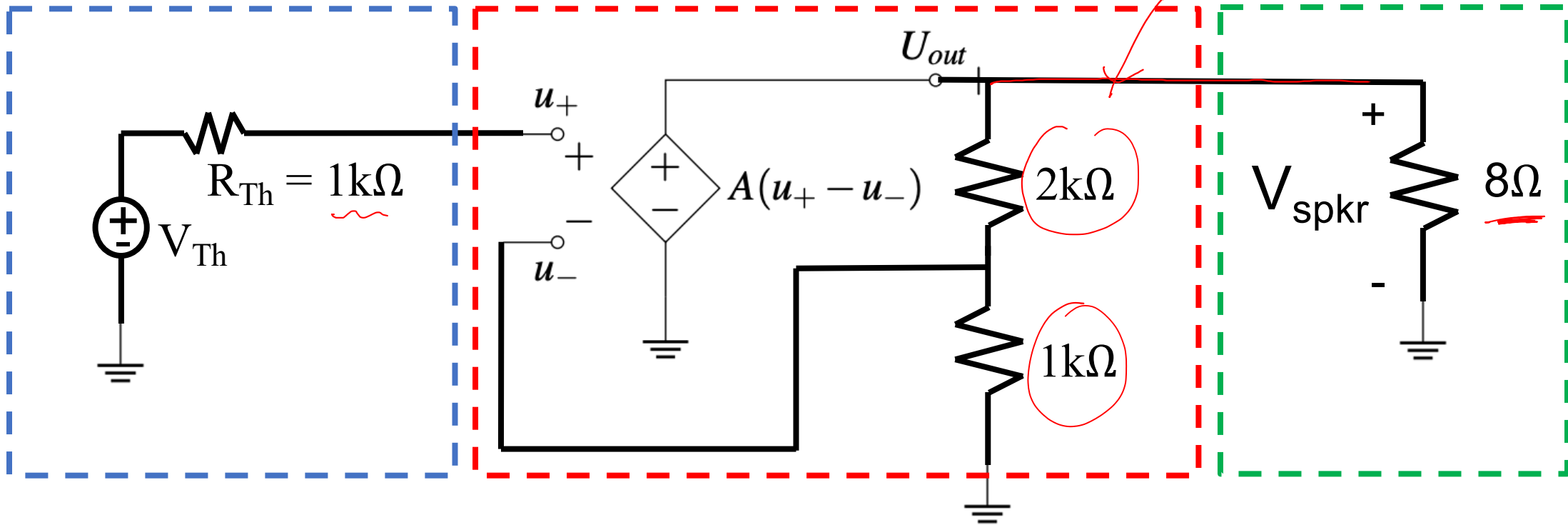


* attenuation
gain < 1

Why does this work?

+ amplifies

Why is 8Ω not attenuating?


The Golden Rules of (Ideal) Op Amps #1 ✓

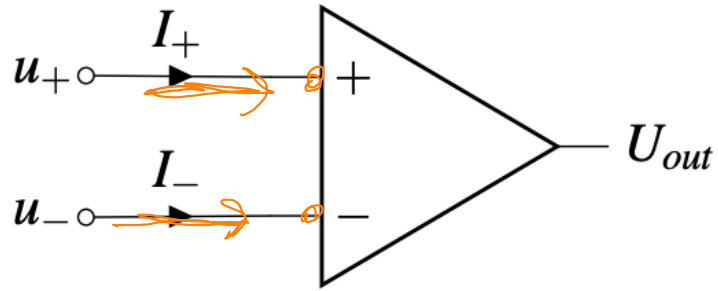

Inputs are open circuits

* $R_{in} = \infty$




#1: $I_+ = I_- = 0$

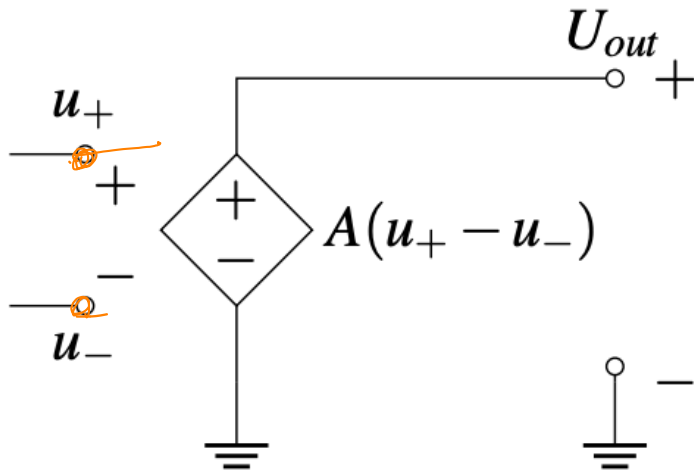

The Golden Rules of (Ideal) Op Amps #2

(applies to negative feedback)

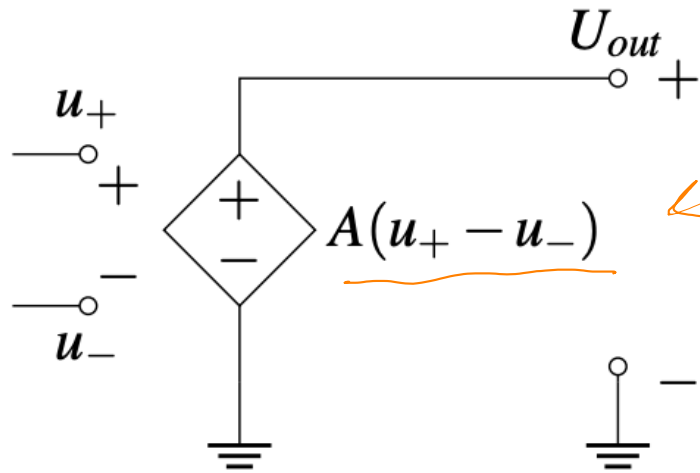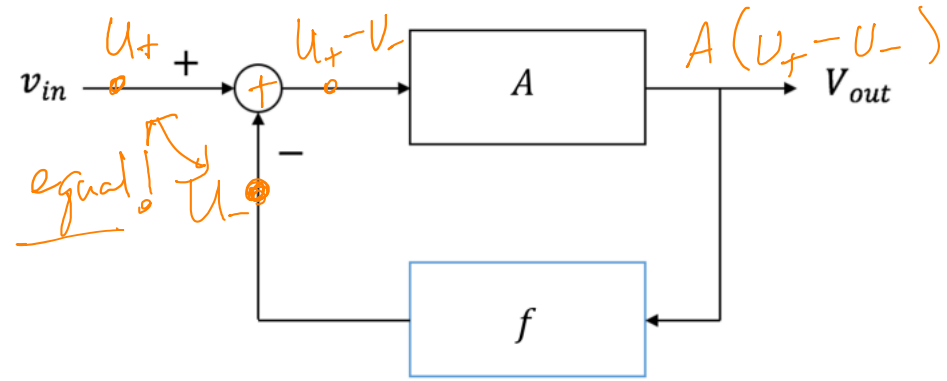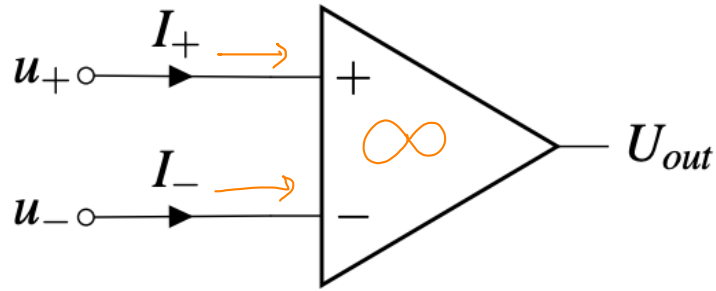* The gain of an ideal op amp is $A = \infty$ *



$$A(u_+ - u_-) = U_{out}$$

$$(u_+ - u_-) = \frac{U_{out}}{A} \rightarrow \infty \Rightarrow 0$$

$$\Rightarrow (u_+ - u_-) = 0$$


#2: $u_+ = u_-$
Only in negative feedback and $A = \infty$

An Extra Attribute of (Ideal) Op Amps


Golden rules

① $A = \infty$

② $R_{out} = 0 \Omega$

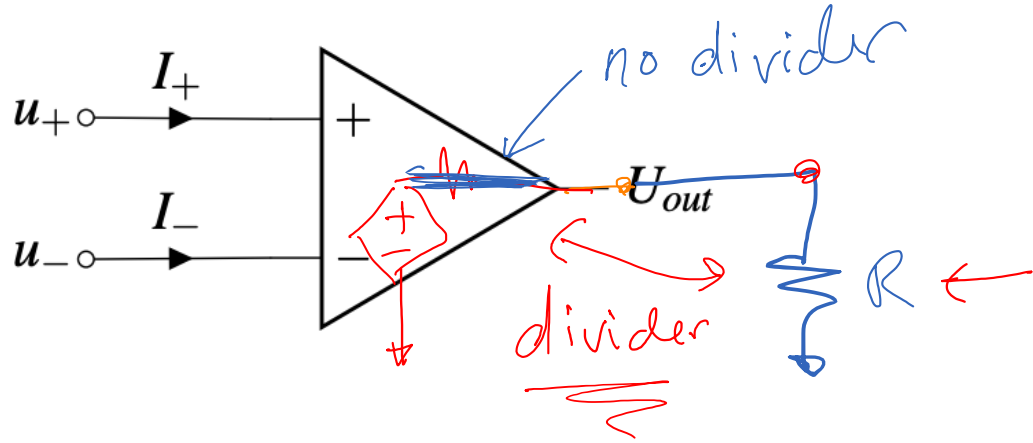

any output won't attenuate the signal

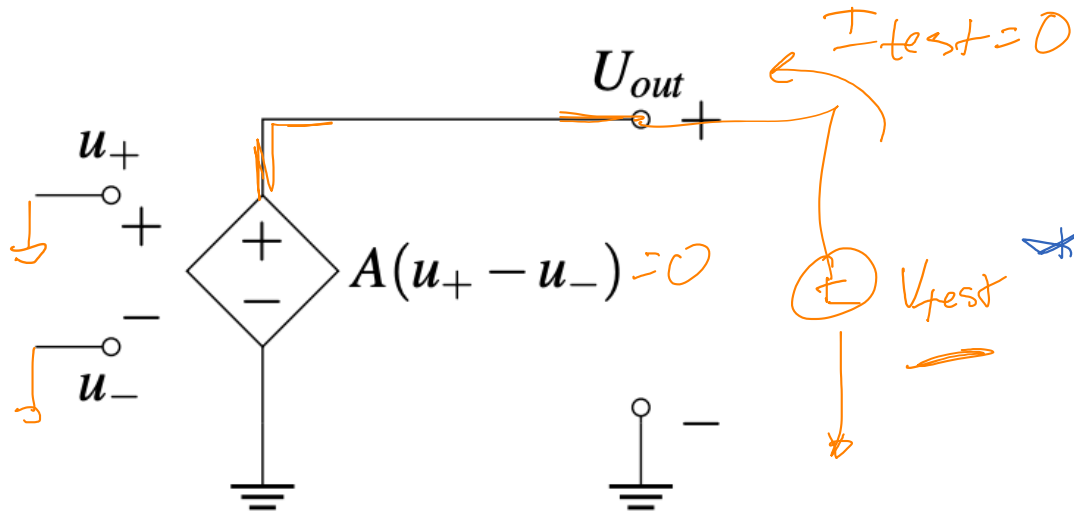

The output resistance of an op-amp is


$R_{out} = 0 \Omega$ (like a short circuit)

$\infty \cdot 0 \rightarrow$ finite

$V_{out} = A(u_+ - u_-) = 0$


Useful Configurations

* Inverting Amplifier

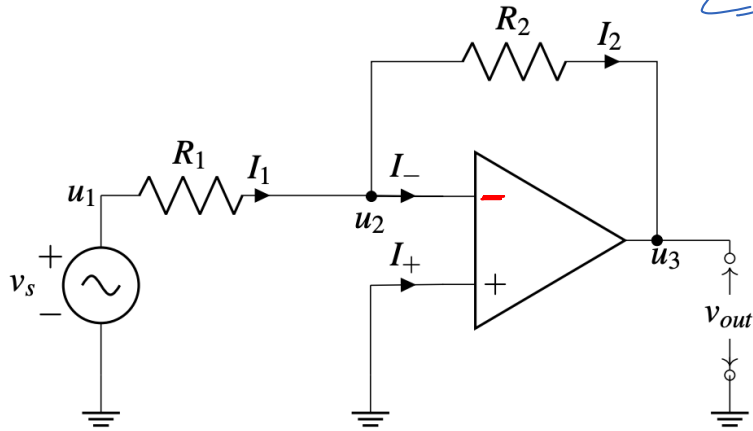


input $\rightarrow V$
 output $\rightarrow V$
 gain $\rightarrow -$

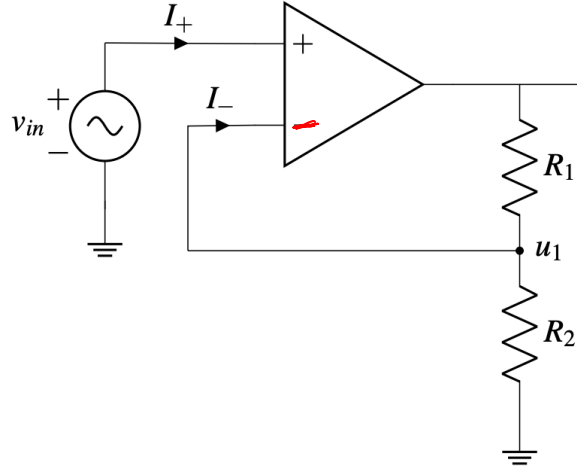* *good for speaker*
 Non-inverting Amplifier



input $\rightarrow V$
 output $\rightarrow V$
 gain $\rightarrow +$

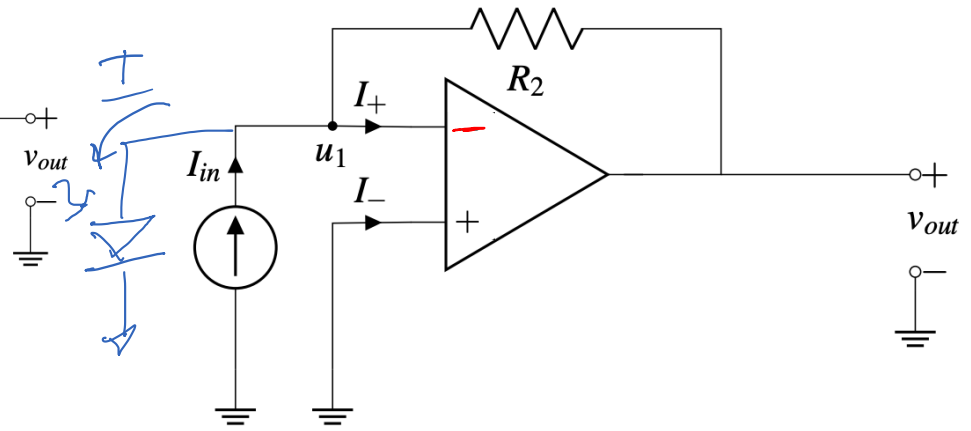
* Trans-impedance Amplifier
 * Trans-resistance Amplifier



input $\rightarrow I$
 output $\rightarrow V$
 gain $\rightarrow -$

Check for Negative Feedback

How do we check?
want negative feedback

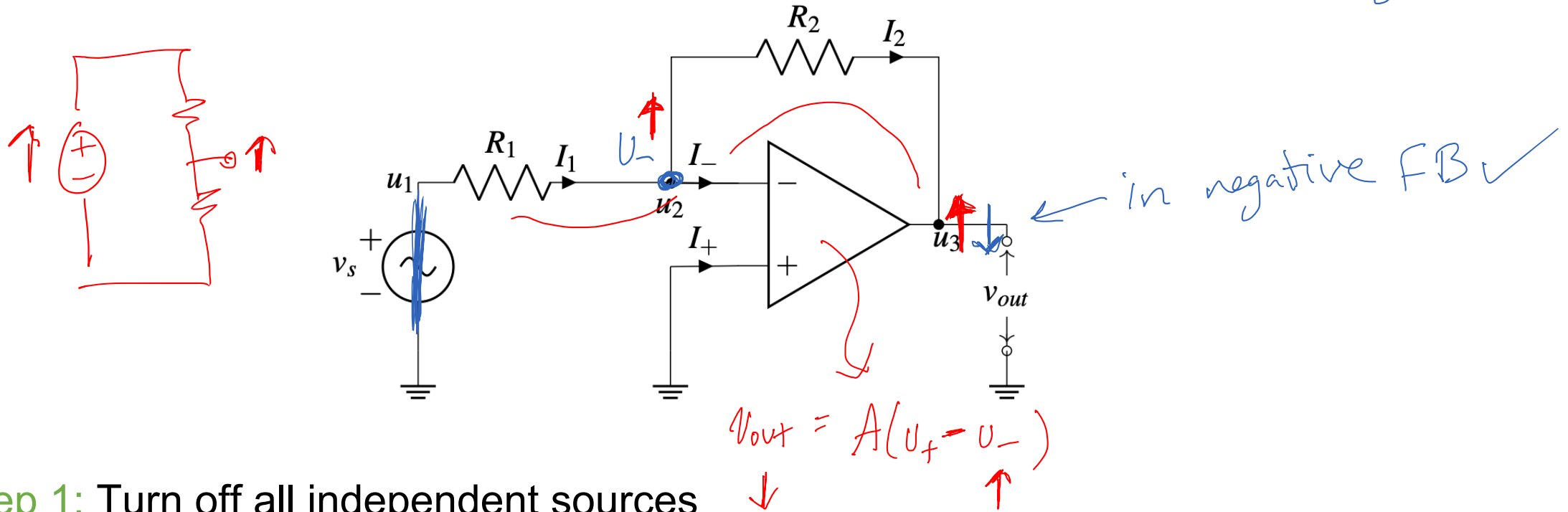


✓ **Step 1:** Turn off all independent sources

- Voltage source becomes wire; Current source becomes open

Step 2: Check how the feedback loop responds to a change in the output

- Negative feedback: Increase output, loop tries to decrease it
- Positive feedback: Increase output, loop tries to increase it further

Example 1: Inverting Amplifier

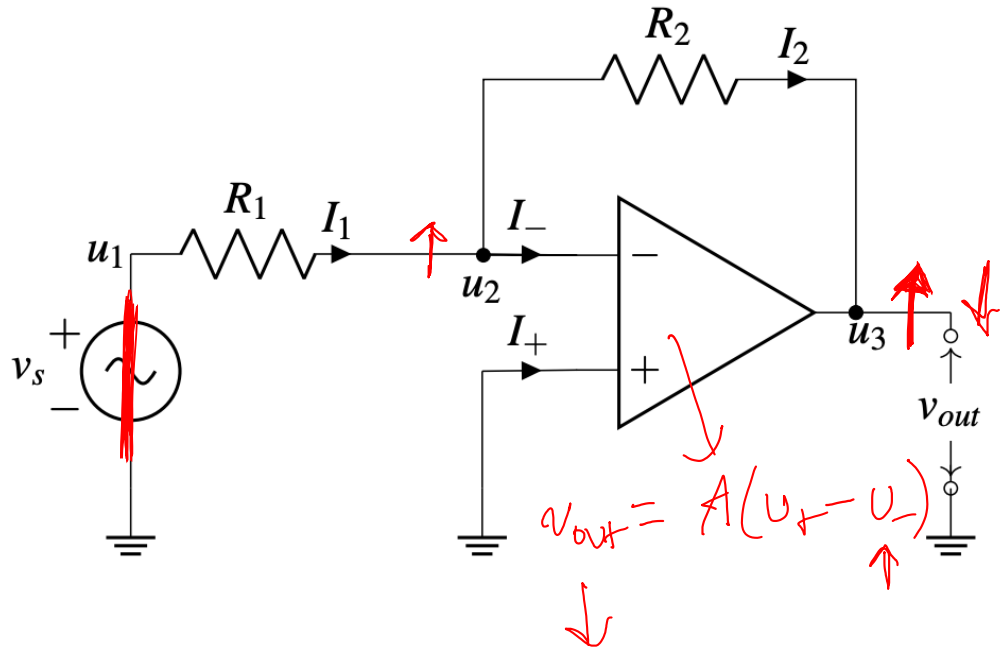


#1: $I_+ = I_- = 0$

#2: $u_+ = u_-$
Only in negative feedback and $A = \infty$

✓ $A = \infty$

✓ $R_{out} = 0$

Example 1: Inverting Amplifier

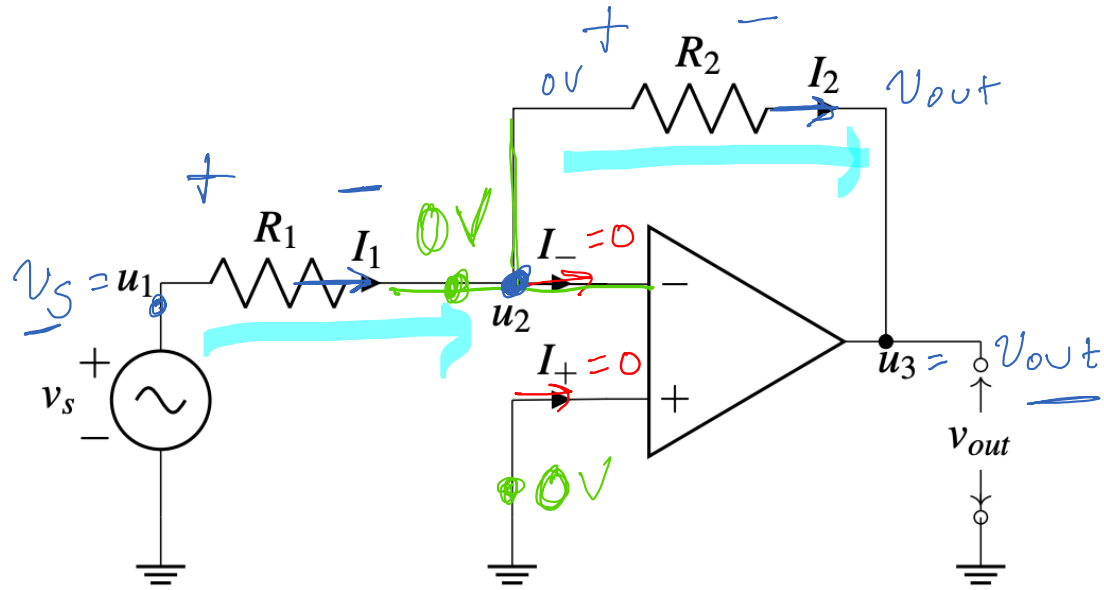

→ #1: $I_+ = I_- = 0$

→ #2: $u_+ = u_-$
Only in negative feedback and $A = \infty$

Looking for:

$$v_{out} = \alpha v_s$$

$$\frac{v_{out}}{v_s} = \alpha \left[\frac{V}{V} \right]$$

$A = \infty$

$R_{out} = 0$

KCL: $I_1 = I_2 + I_- \rightarrow 0$

① $I_1 = I_2$

Ohm's Law: $\frac{v_s - 0V}{R_1} = I_1$

$\frac{v_s}{R_1} = I_1$

$\frac{0V - v_{out}}{R_2} = I_2$


$-\frac{v_{out}}{R_2} = I_2$

$$\frac{v_s}{R_1} = \frac{-v_{out}}{R_2}$$

$$v_{out} = -\frac{R_2}{R_1} \cdot v_s$$

$$\frac{v_{out}}{v_s} = -\frac{R_2}{R_1} *$$

Example 2: Trans-resistance Amplifier

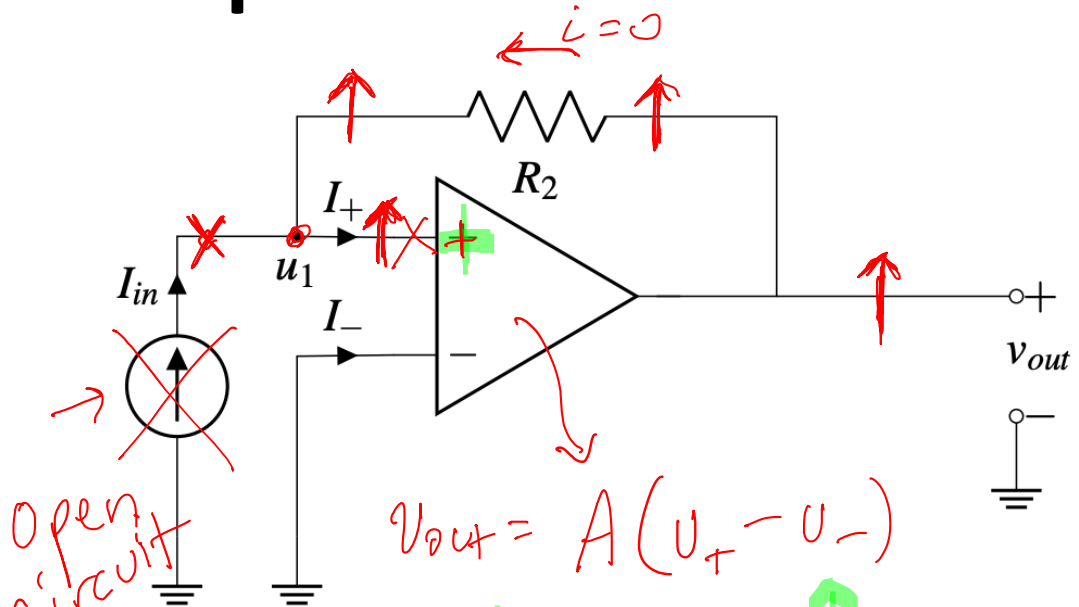

Open circuit

$$V_{out} = A(u_+ - u_-)$$




positive feedback!


doesn't work!!!

#1: $I_+ = I_- = 0$

#2: $u_+ = u_-$
Only in negative feedback and $A = \infty$

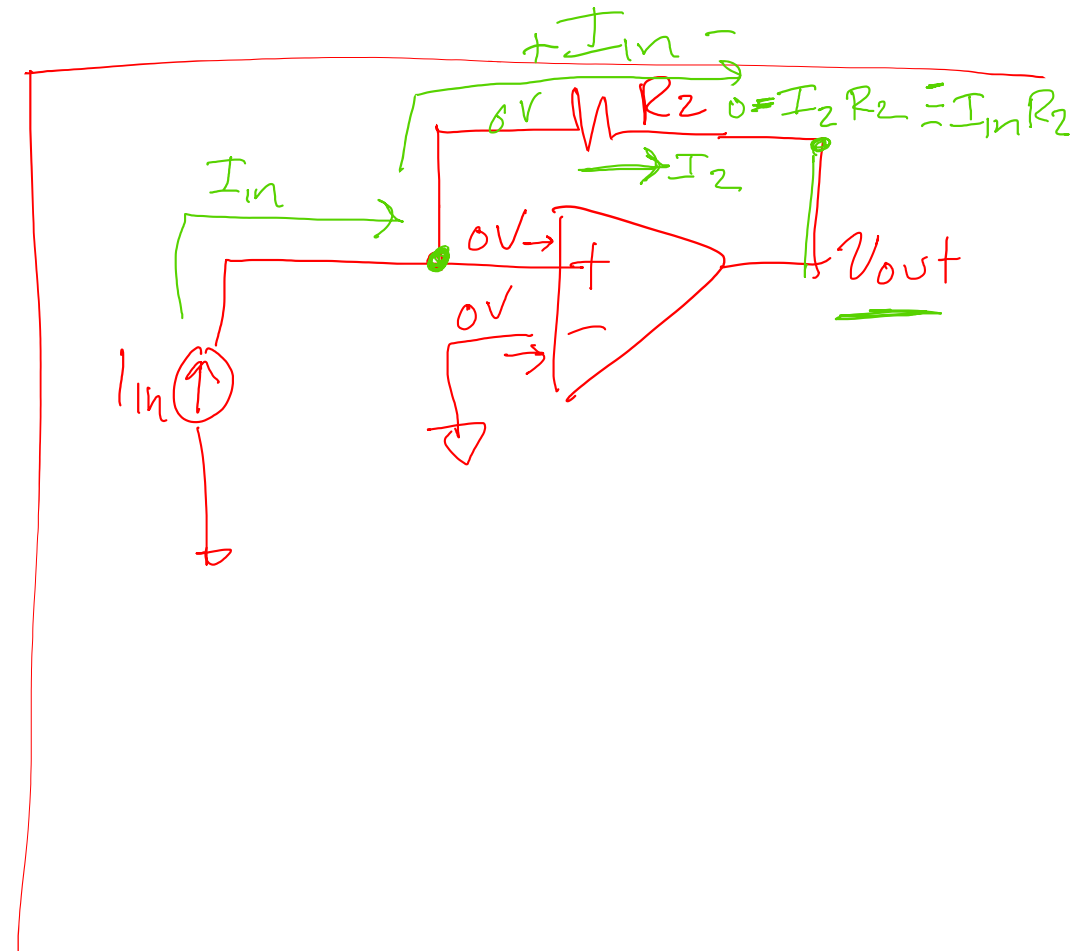

Example 2: Trans-resistance Amplifier

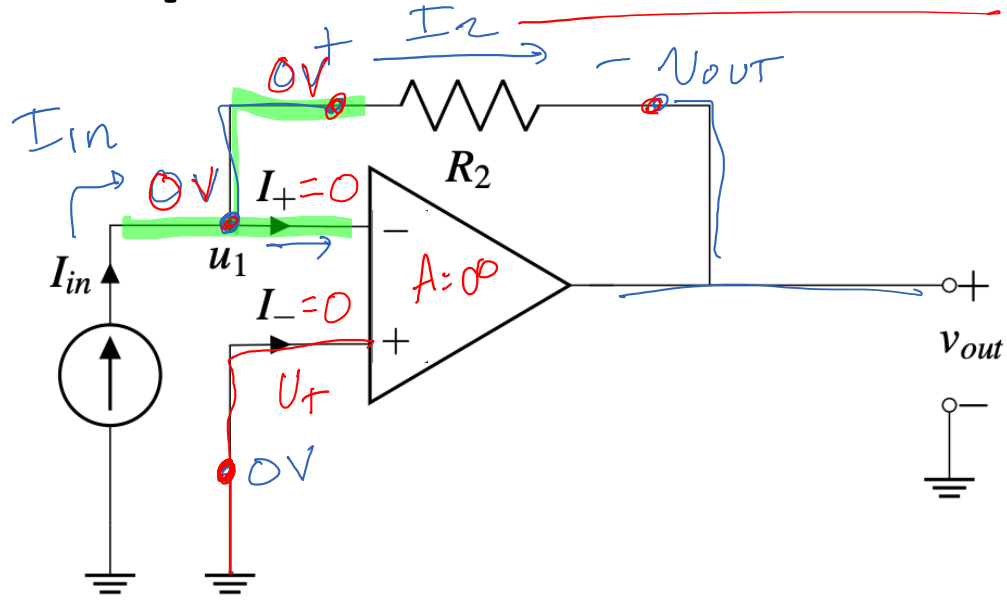

✓ #1: $I_+ = I_- = 0$

⇒ #2: $u_+ = u_-$
Only in negative feedback and $A = \infty$

looking for:

$$V_{out} = \alpha I_{in}$$

$$\frac{V_{out}}{I_{in}} = \alpha \left[\frac{V}{A} \right] = [R^-] \leftarrow \text{resistance!}$$

KCL: $I_{in} = I_2 + I_+$

① $I_{in} = I_2$

Ohm's Law: $\Rightarrow \frac{0V - V_{out}}{R_2} = I_2$



② $-\frac{V_{out}}{R_2} = I_2$

$$-\frac{V_{out}}{R_2} = I_2 = I_{in}$$

$$V_{out} = -R_2 I_{in}$$

$$\boxed{\frac{V_{out}}{I_{in}} = -R_2} \quad \checkmark$$

Example 3: Non-Inverting Amplifier

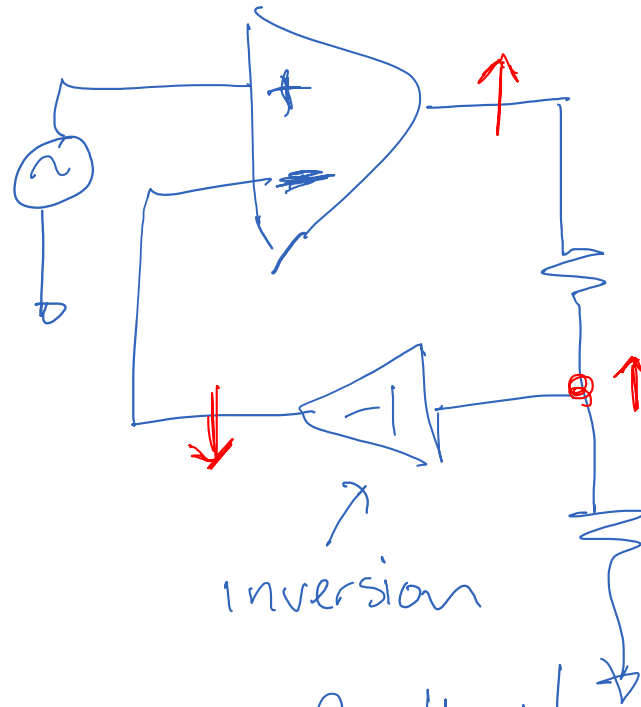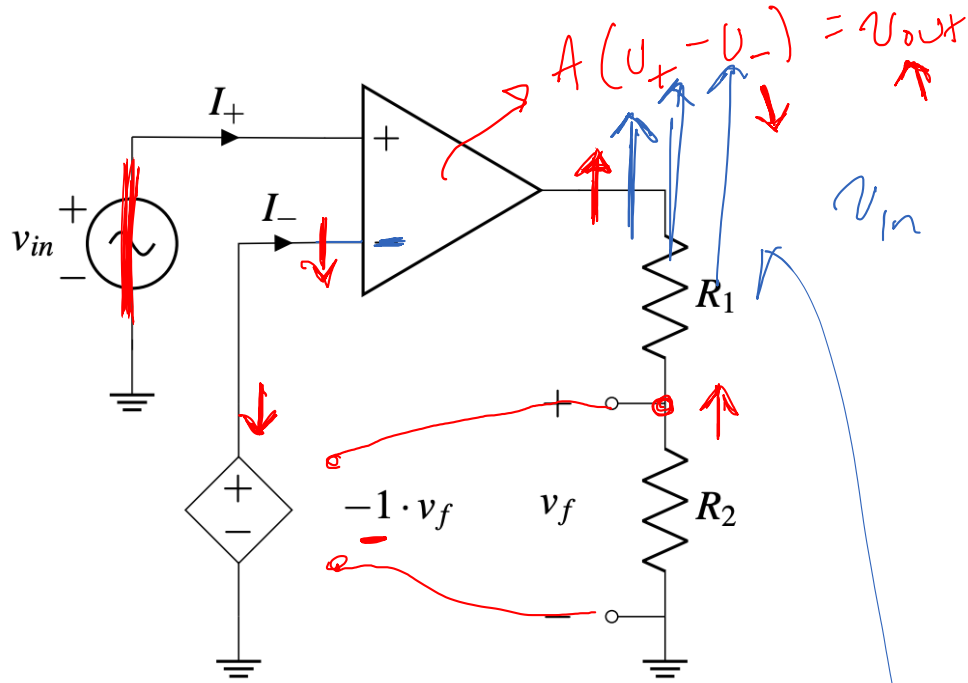

positive feedback!
doesn't work

#1: $I_+ = I_- = 0$

#2: $u_+ = u_-$
 Only in negative feedback and $A = \infty$


Need to Gain and Isolation

No attenuation

DAC

Amplifier, Non-inverting Gain = 3

Speaker

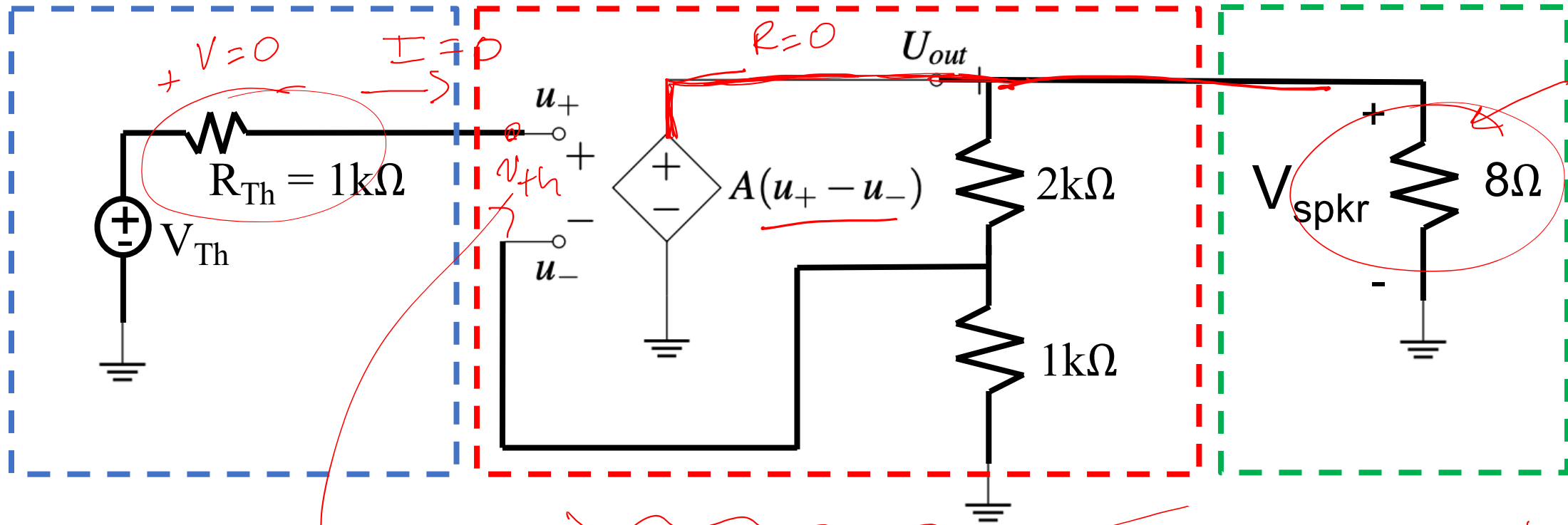

don't lose signal!

$R_{in} = \infty$


$R_{out} = 0$

Why does this work?

supplied directly from V source


Summary of Useful Configurations

Inverting Amplifier

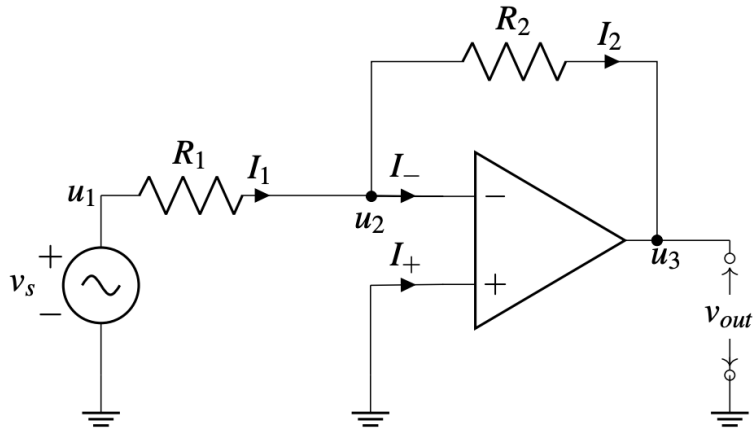


$$v_{out} = -\frac{R_2}{R_1} \cdot v_{in}$$

Non-inverting Amplifier

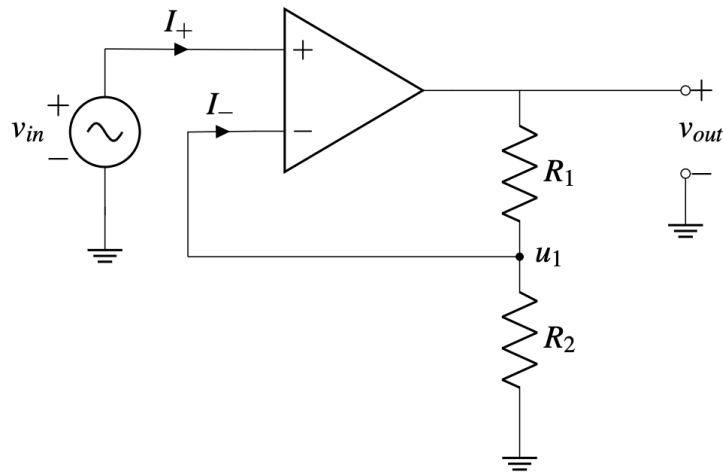

$$v_{out} = \left(1 + \frac{R_1}{R_2}\right) \cdot v_{in}$$

Trans-resistance Amplifier

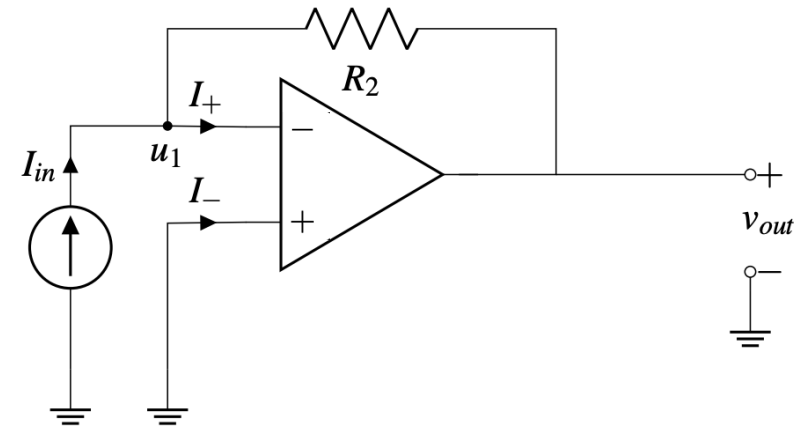

$$v_{out} = -R_2 \cdot I_{in}$$