
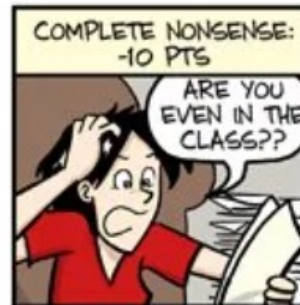
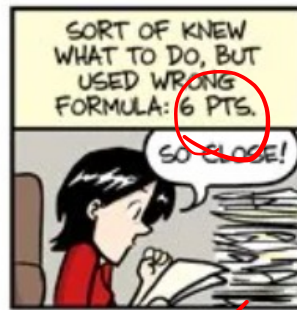
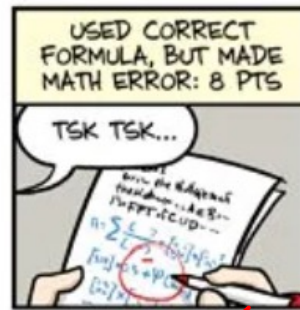


# EECS 16A

Spring 2023 - Profs. Muller & Waller  
Power and I/V Measurement

## GRADING RUBRIC

→ PROBLEM 1 (TOTAL POINTS: 10)

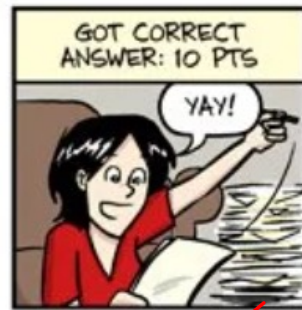

JORGE CHAM © 2010



# Midterm is Tomorrow! 7-9pm

PRINT your student ID: \_\_\_\_\_

PRINT AND SIGN your name: \_\_\_\_\_, \_\_\_\_\_, \_\_\_\_\_  
(last name) (first name) (signature)

PRINT the time of your discussion section and your GSI(s) name: \_\_\_\_\_

PRINT the student IDs of the person sitting on your right: \_\_\_\_\_ and left: \_\_\_\_\_

## General Notes

- This exam has a combination of multiple choice, fill-in-the-blank, and free-response questions.
- **You must adhere to the following format to receive full credit:**
  - For fill in the blank questions, **legibly write your final answer entirely in the provided boxes.**
  - For questions with **circular bubbles**, select exactly *one* choice, by filling the bubble ●.
    - You must choose either this option.      ○ Or this one, but not both!
  - For questions with **square boxes**, you may select *multiple* choices, by filling the squares ■.
    - You could select this choice.      ■ You could select this one too!
  - For free-response questions please show your work in the provided empty boxes. Doing so enables us to reward you partial credit where applicable.

# Midterm is Tomorrow! 7-9pm

## 1. HONOR CODE

Please read the following statements of the honor code, and sign your name (you don't need to copy it).


*I will respect my classmates and the integrity of this exam by following this honor code. I affirm:*

- *I have read the instructions for this exam. I understand them and will follow them.*
- *All of the work submitted here is my original work.*
- *I did not reference any sources other than my unlimited printed resources.*
- *I did not collaborate with any other human being on this exam.*

Other admin:

\* I will take over office hours Wednesday 11am– 12pm in my office 564 Cory Hall
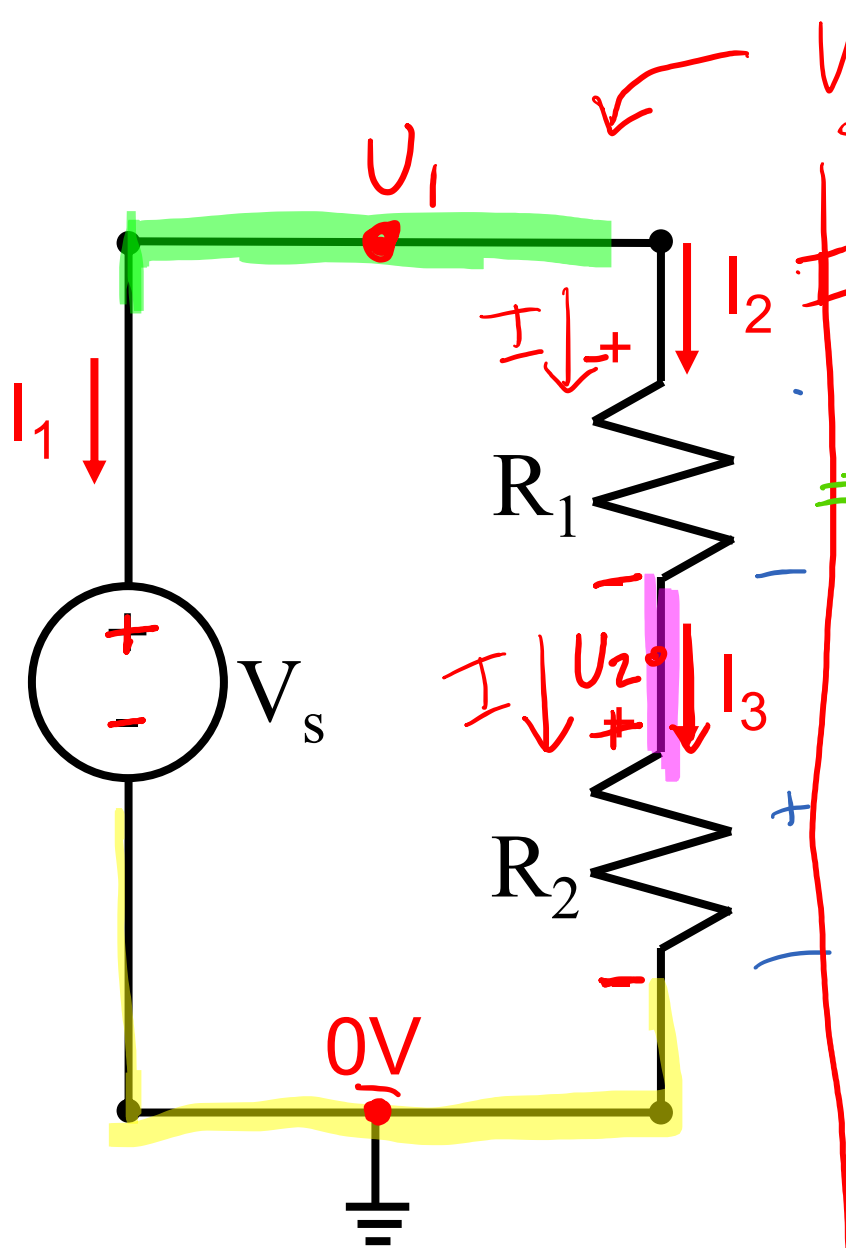
# Last Lecture: Kirchoff's Current Law (KCL)




Voltage divider

KCL



$$I_1 + I_2 = 0$$

$$I_2 = -I_1 = I$$

$$I_2 = I_3 = I$$

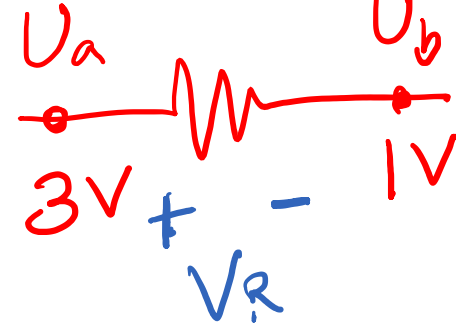


$$V_R = U_a - U_b = 3V - 1V = 2V$$

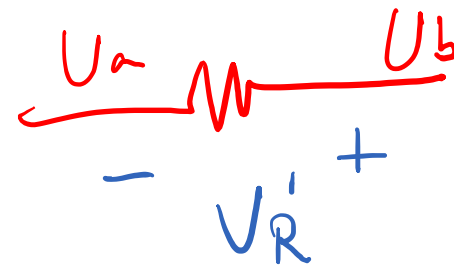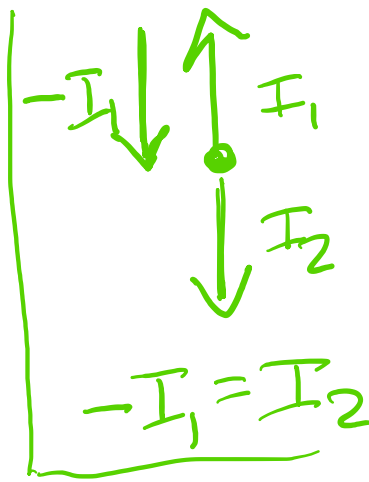


$$V_R' = U_b - U_a = 1V - 3V = -2V$$
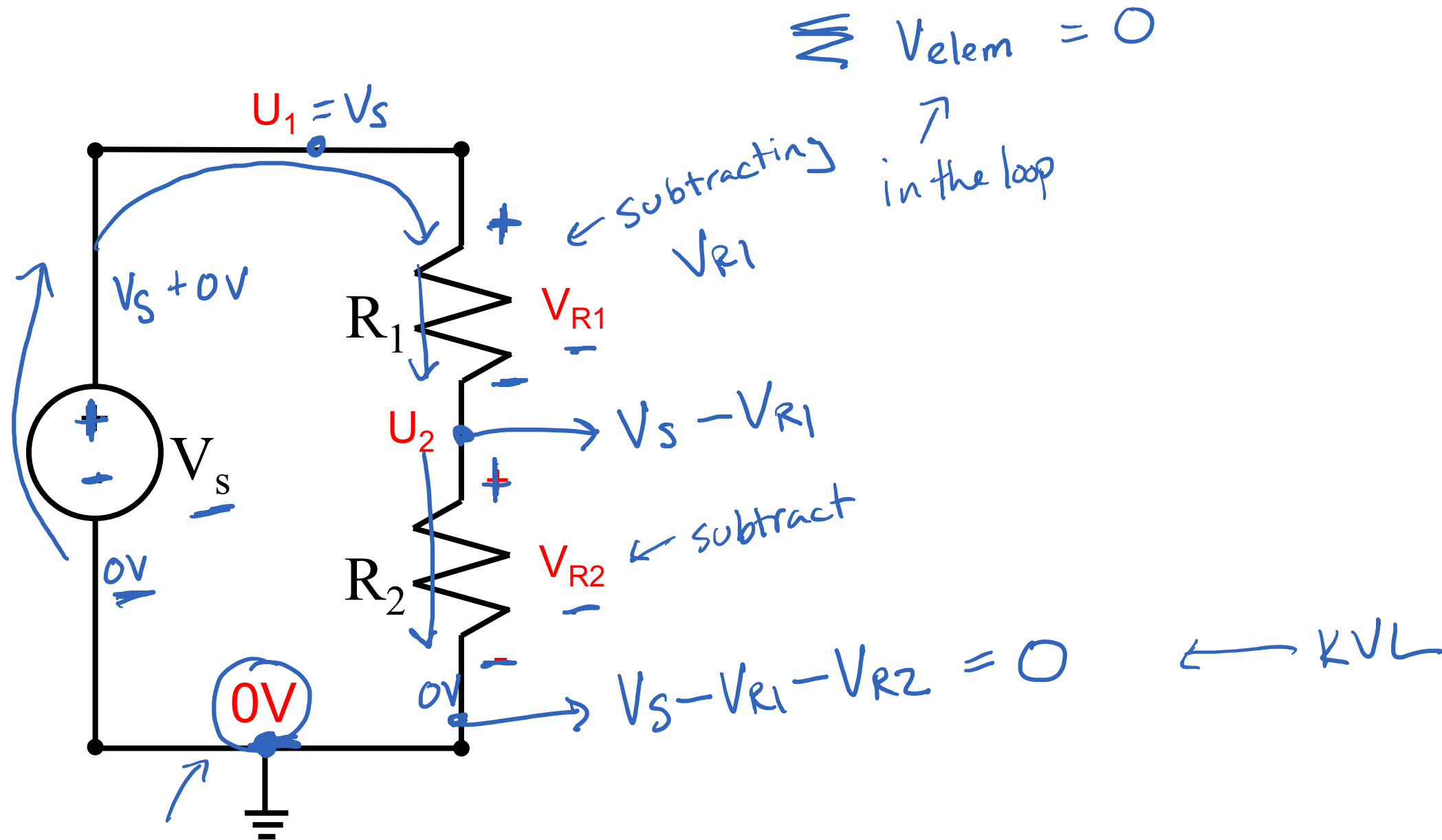
# Last Lecture: Kirchoff's Voltage Law (KVL)



# Last Lecture: Ohm's Law

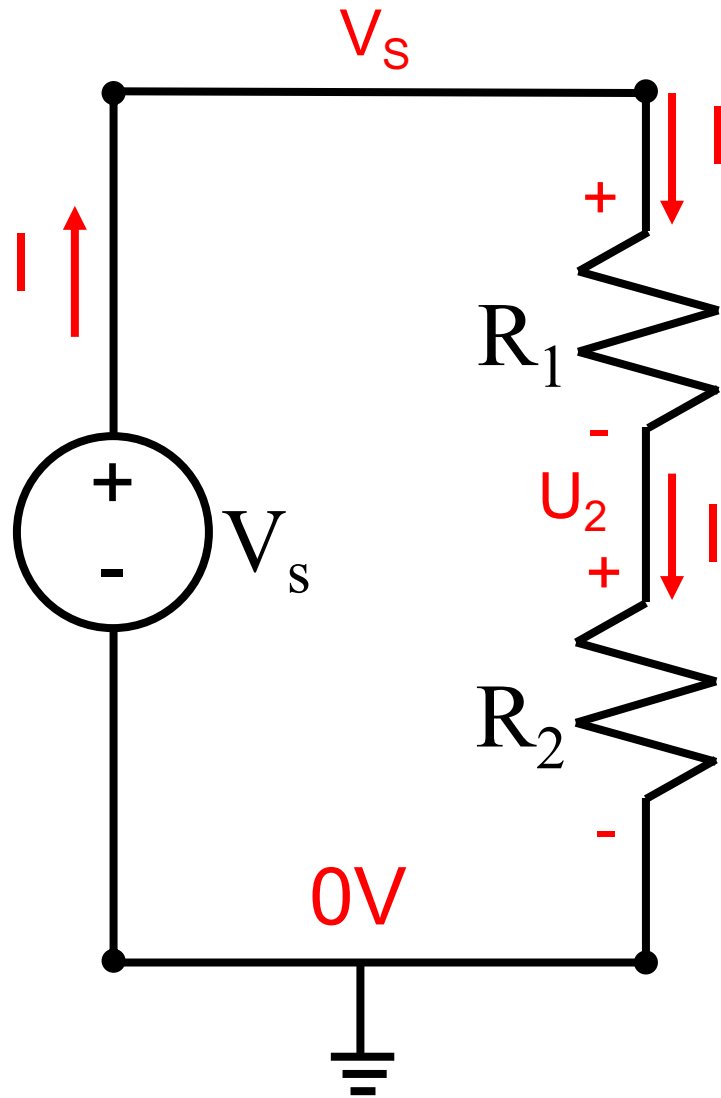


Is the system of equations complicated? Linear Algebra can help!  $A\vec{x} = \vec{b}$

$$\rightarrow IR_1 + U_2 = V_s$$

$$\rightarrow IR_2 - U_2 = 0$$

$$\rightarrow \begin{bmatrix} R_1 & 1 \\ R_2 & -1 \end{bmatrix} \begin{bmatrix} I \\ U_2 \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$$

# Voltage Divider Observations

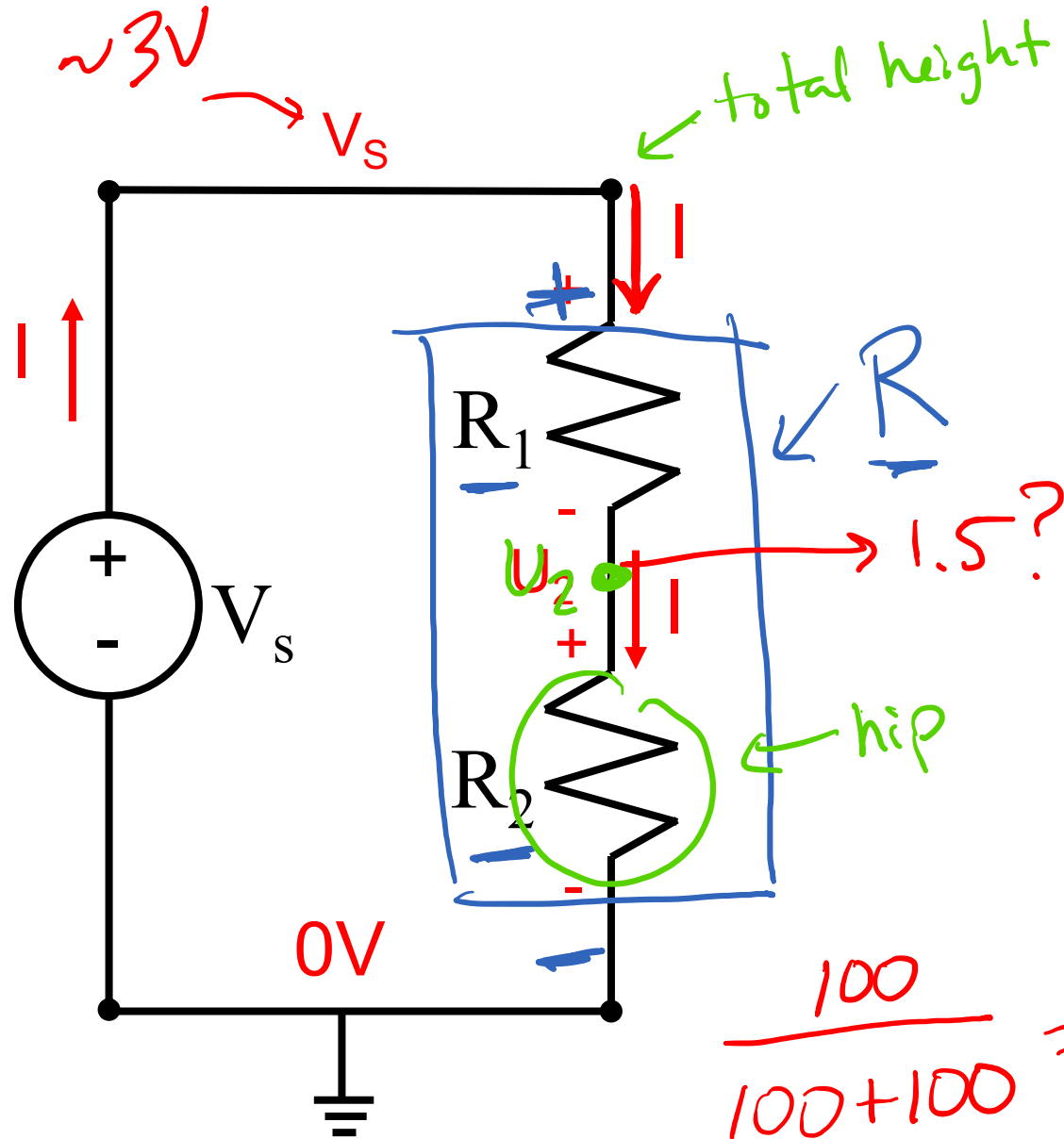

$$RI = V$$

$$I = (V_s - 0) / R \quad I = \frac{V_s}{R}$$

$$I = \frac{V_s}{(R_1 + R_2)}$$

resistance add in series

$$U_2 = \frac{V_s R_2}{R_1 + R_2} = V_s \left( \frac{R_2}{R_1 + R_2} \right)$$

divides the voltage

ratio =  $\frac{1}{2}$

$$\frac{100}{100 + 100} = \frac{1}{2}$$



# Power and Energy in Circuits

**Current:** flow of charges (electrons moving from point A → B inside a material)

$$I = \frac{dQ}{dt}$$



**Voltage:** provides the **energy** [Joules] to move charge from A → B.  
1 Volt provides 1 Joule of energy to 1 Coulomb of charge.


$$V_{AB} = \frac{dE}{dQ}$$

**Power** [Watts]: the rate at which **energy** is transferred

$$P = \frac{dE}{dQ} \cdot \frac{dQ}{dt} = \frac{dE}{dt} = \boxed{V_{AB} \cdot I}$$




# Power in an Element

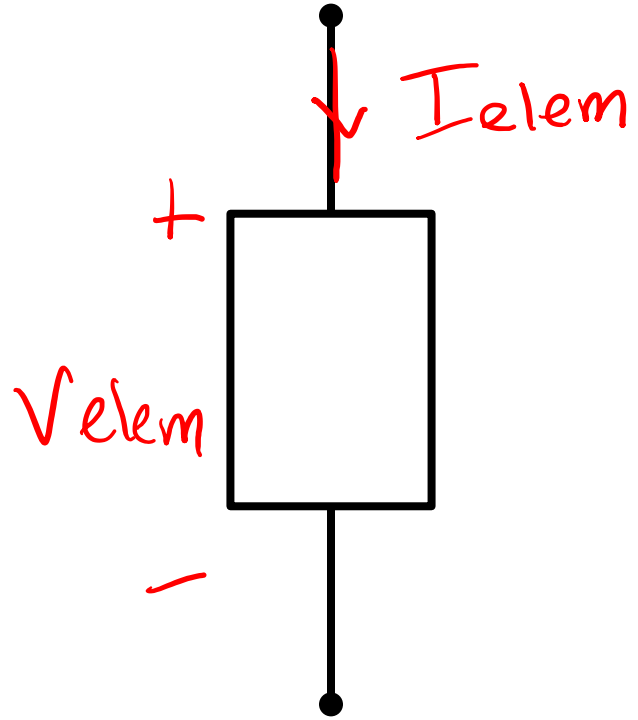

$$P_{elem} = V_{elem} \cdot I_{elem}$$

# Power in a Resistor

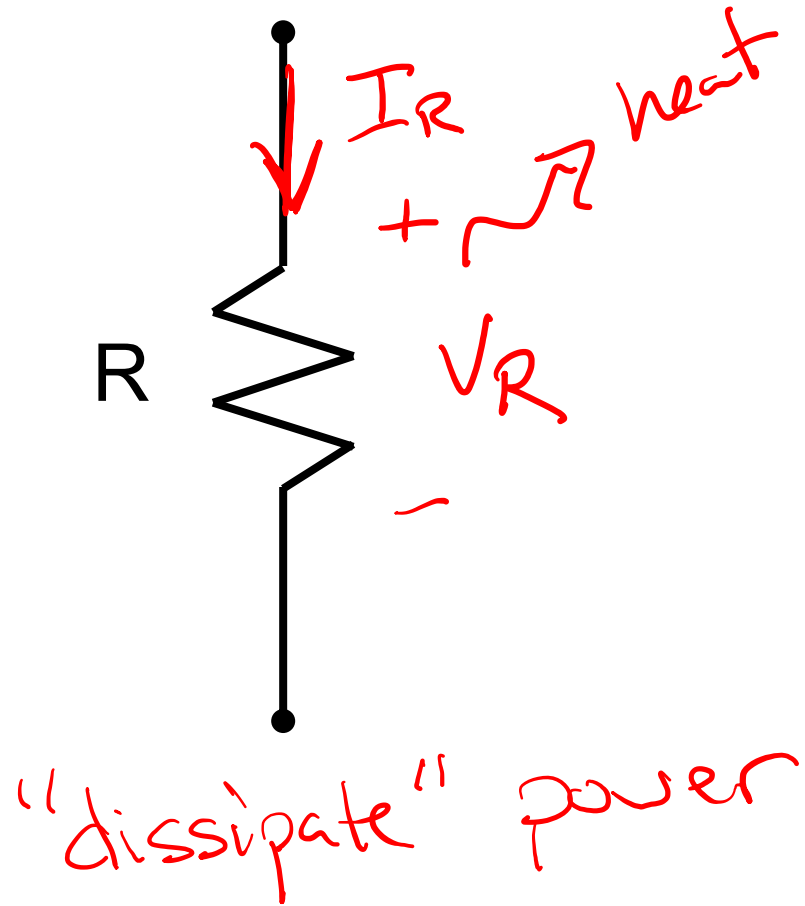

$$\text{Power [watts]} = V_R \cdot I_R$$

$$I_R = \frac{V_R}{R}$$


$$\text{Power} = V_R \cdot \frac{V_R}{R} = \frac{V_R^2}{R}$$

$$V_R = I_R R$$


$$\text{Power} = I_R \cdot R \cdot I_R = I_R^2 \cdot R$$

always +

# Power in Wires and Open Circuits

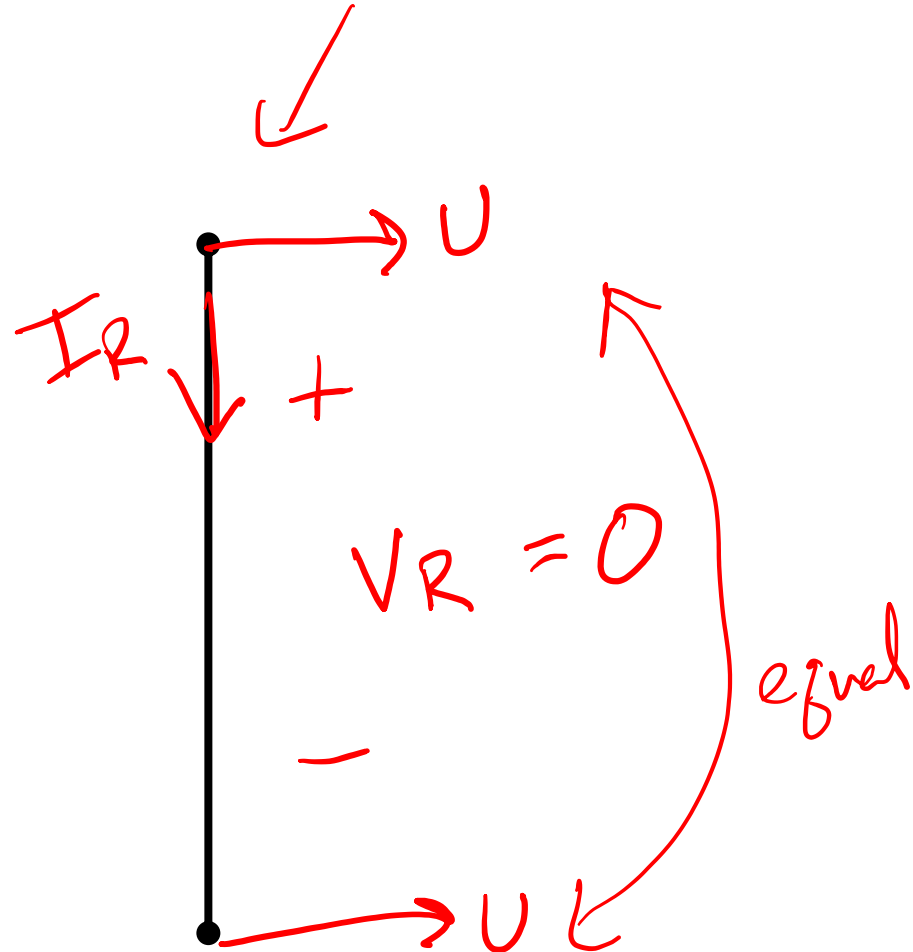

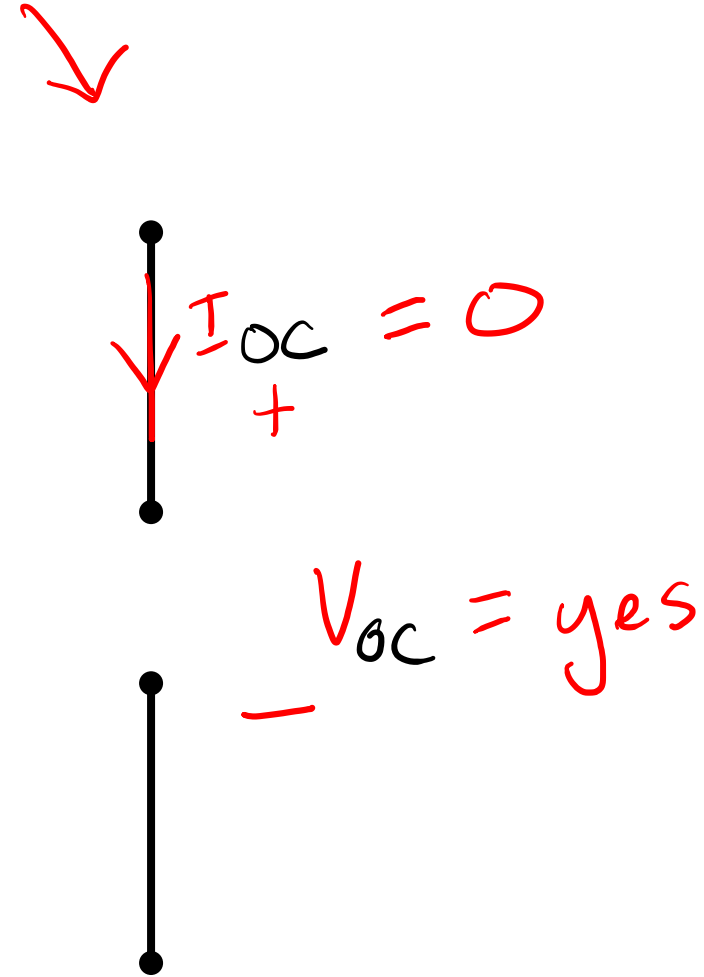
$$\text{Power} = I_R V_R \overset{0}{=} 0$$



$$\text{Power} = V_{OC} \cdot \cancel{I_{OC}} \overset{0}{=} 0$$

# Example

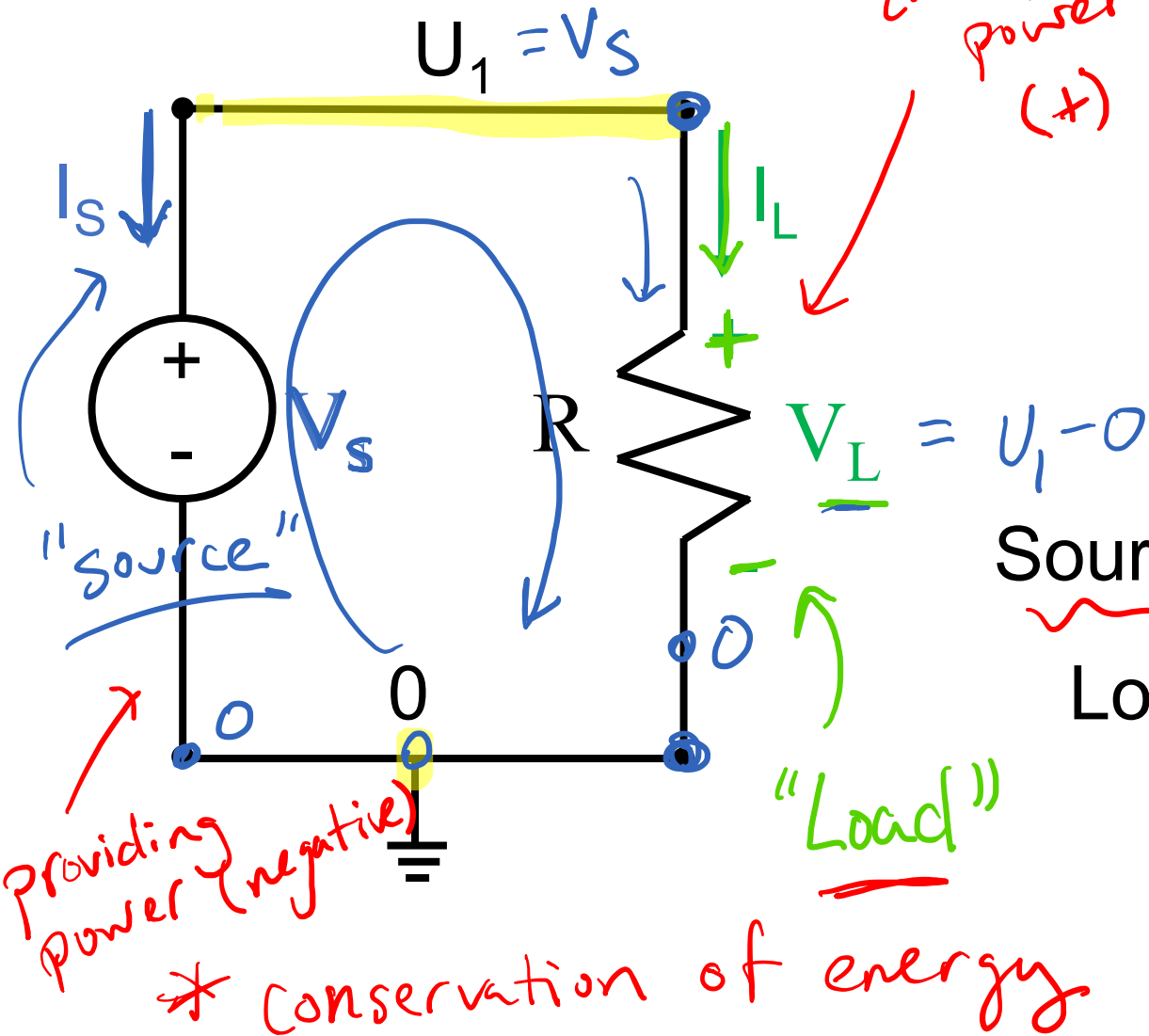

KCL:  $I_s + I_L = 0$

$-I_s = I_L$

KVL:  $V_s - V_L = 0$

$V_s = V_L = U_1 - 0$


Source Power:  $P_s = I_s V_s$

Load Power:  $P_L = I_L V_L$   
 $= I_L V_s$

How are these related?

\*  $P_L = -I_s V_s = -P_s$   
 equal and opposite!

# How to measure Voltage?

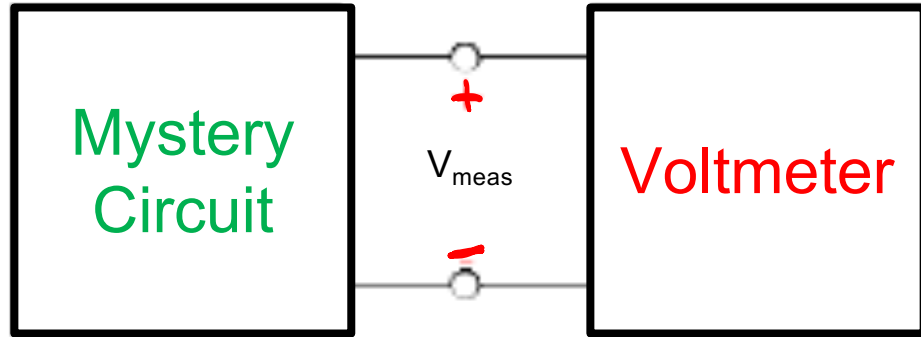

Goal:  $V_{meas} = V_S$


KVL:  $V_S - V_R - V_{meas} = 0$

$V_S - V_R = V_{meas}$


← open circuit! \*  $V_R = 0$

$V_R = I_R R = 0$

$I_R = 0$

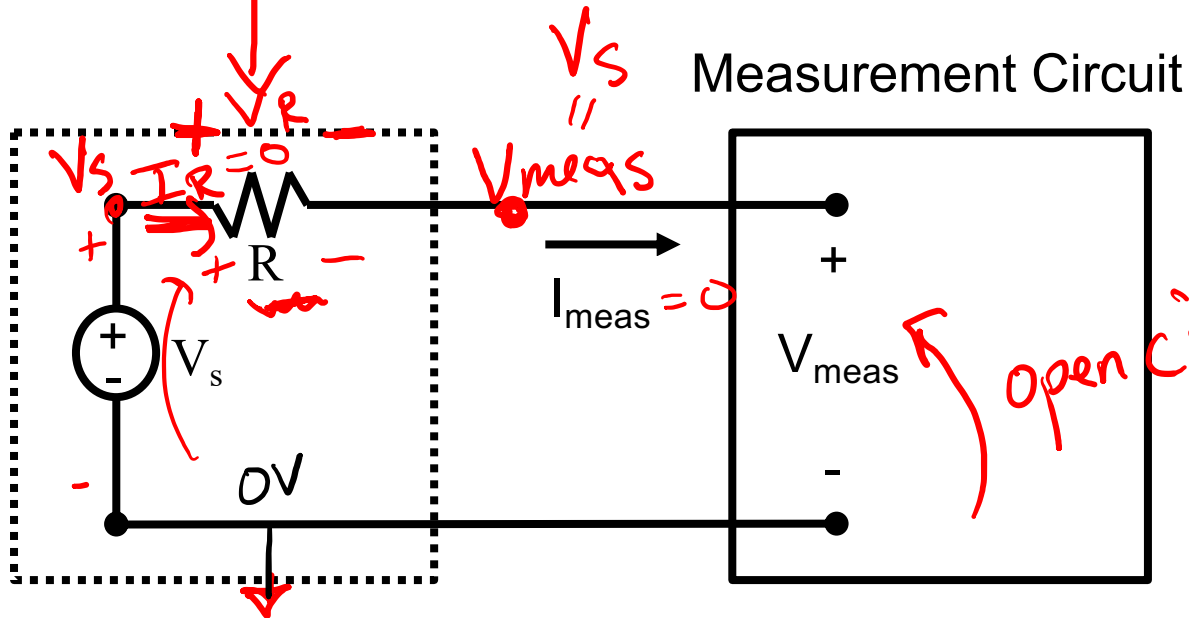

# How to measure Current?

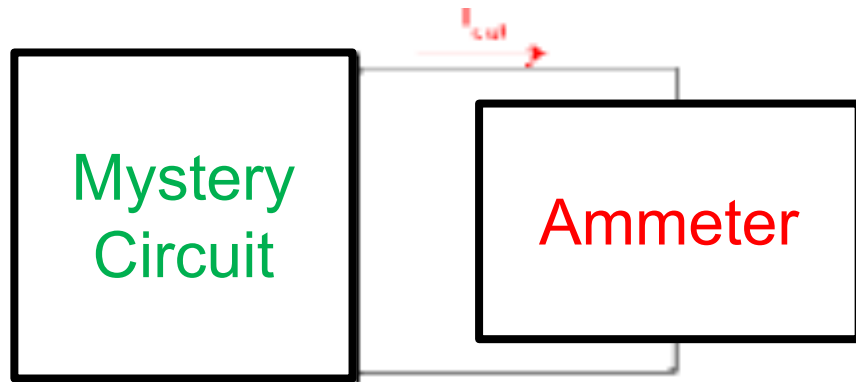


Goal:  $I_{meas} = I_s$

KCL:  $I_s = I_R + I_{meas}$


$I_R = 0$

$V_R = I_R R = 0$


$V_R = 0$

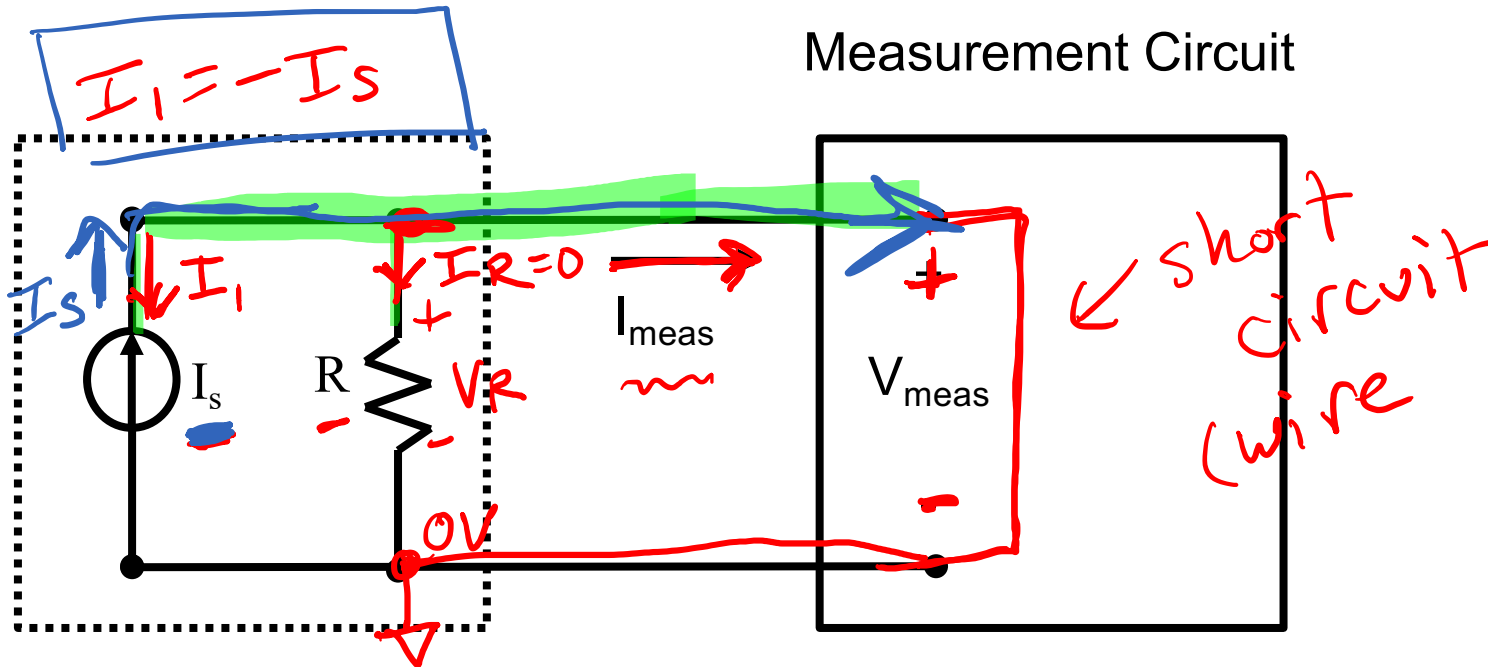

# How to measure Resistance?

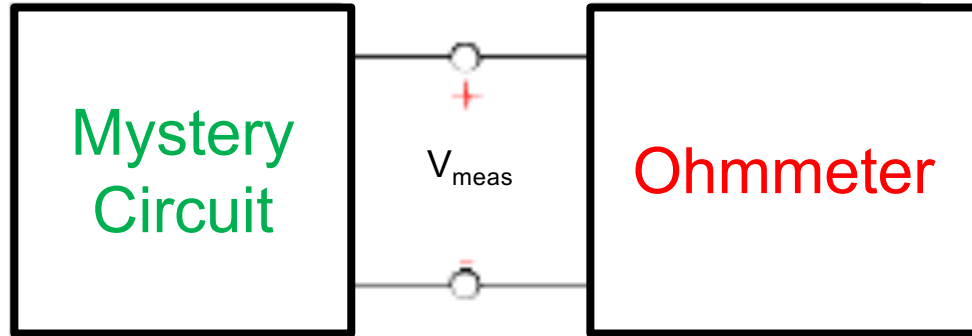

Measurement Circuit

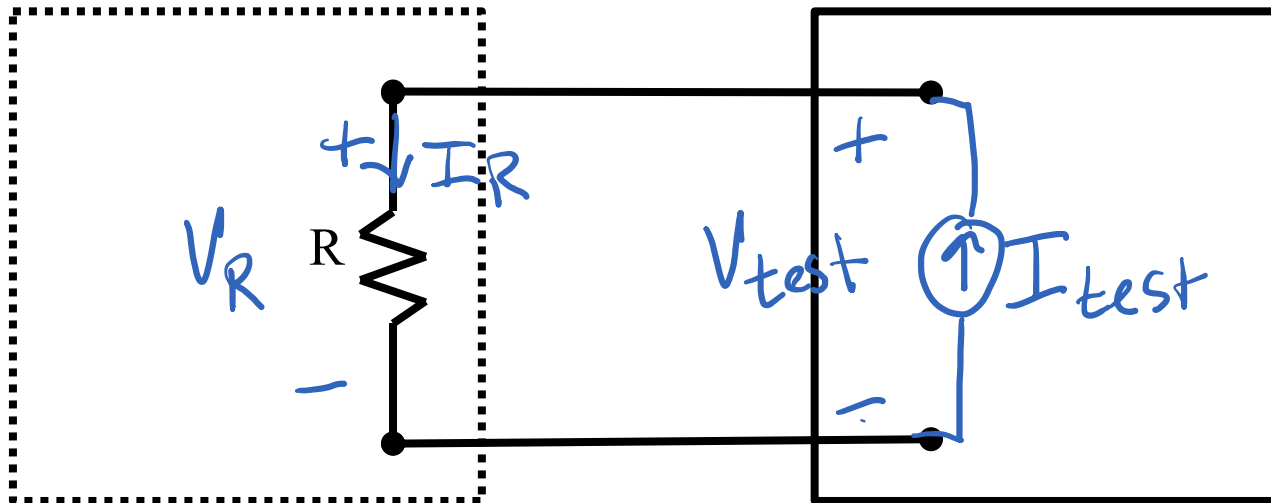

Ohm's Law

$$V_R = I_R R$$

$$R = V_R / I_R$$

$$R = \frac{V_{\text{test}}}{I_{\text{test}}}$$





**Demo!**