

TOUCH SCREEN

EECS 16A

Spring 2023 - Profs.
Muller & Waller
Resistors & Resistive
Touchscreen



YOU'RE DOING IT WRONG

Admin



Module 1 and midterm are complete!

Recap

* **Power** [Watts]: the rate at which **energy** is transferred

$$P = IV$$

\downarrow \rightsquigarrow heat

large R
small R



large \downarrow small

$$V = IR$$

constant


$$P = V \cdot I \uparrow$$

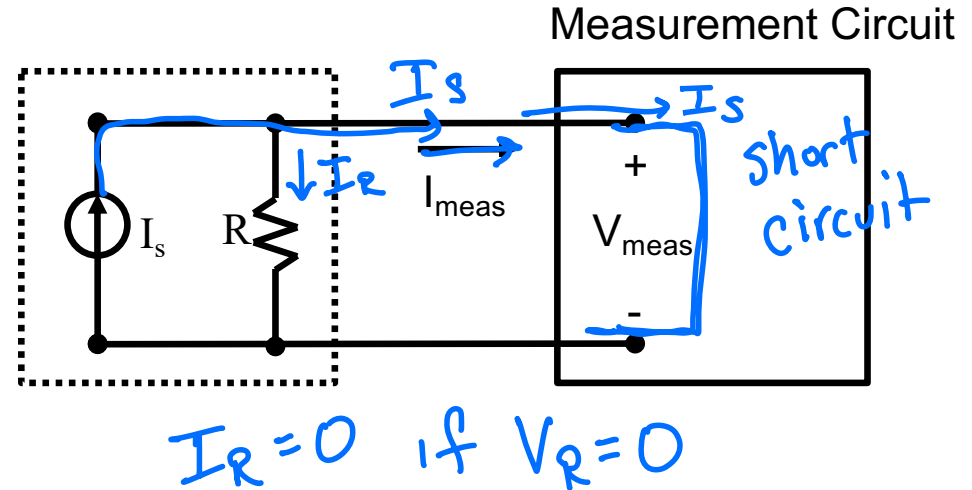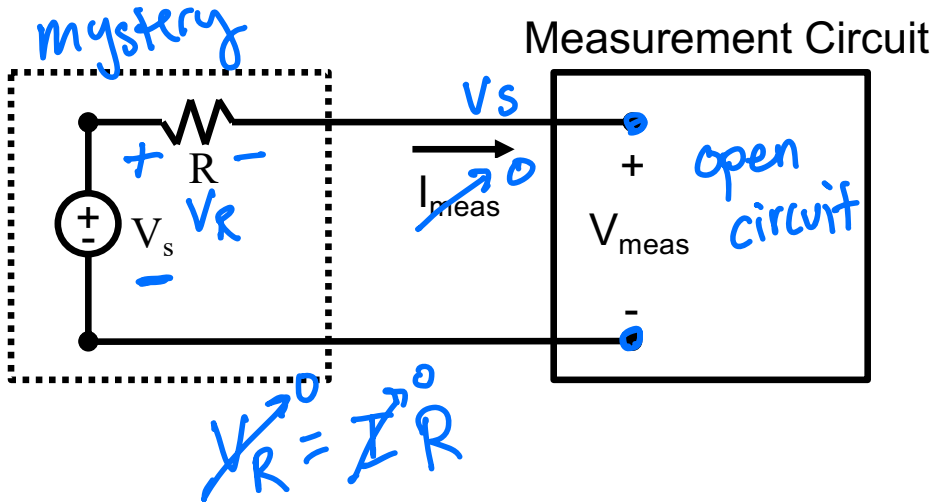Power is dissipated in a resistor as heat
Supplies provide power to the circuit



Tool For Today's Lecture: The Voltage Divider

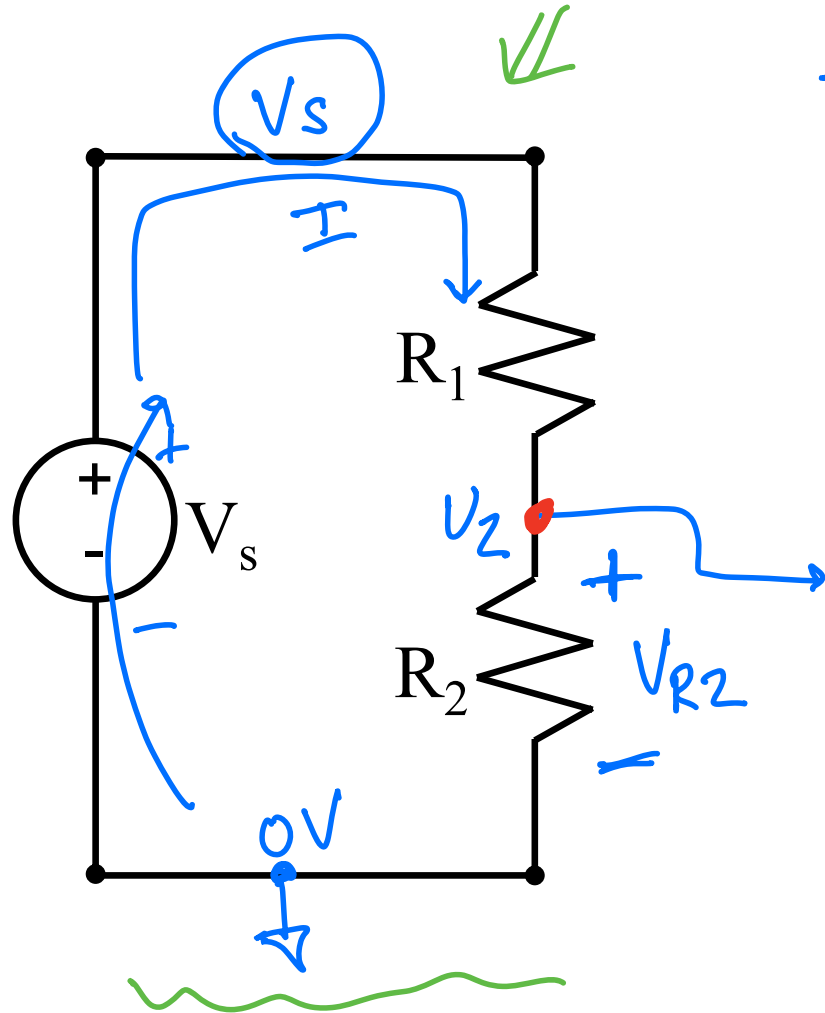- ① the voltage divider
- ② KVL / KCL
- ③ Ohm's Law




$$I = \frac{V_s}{R_1 + R_2}$$

$$U_2 = \frac{V_s R_2}{R_1 + R_2}$$

$$V_s \left(\frac{R_2}{R_1 + R_2} \right)$$

Resistive Touch Screen

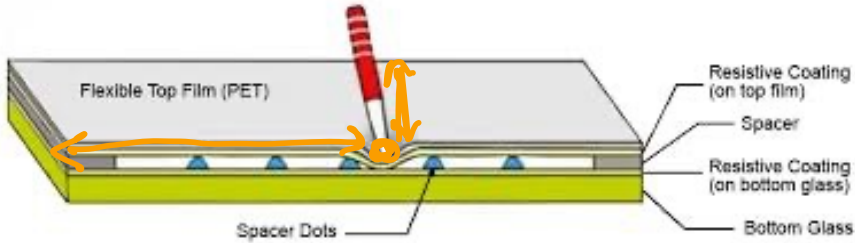


$$\text{Conductance} = \frac{1}{\text{Resistance}}$$

want $\downarrow R$ $\uparrow C$



Mechanical Actuation

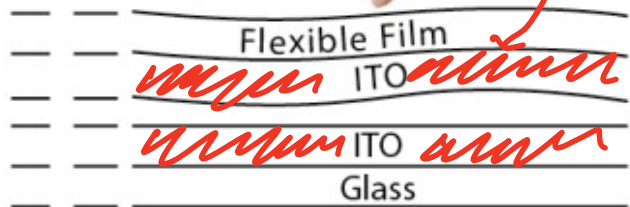



flexible conductor \rightarrow ITO

flexible

Indium Tin Oxide

Rigid base

Resistive Touch Screen

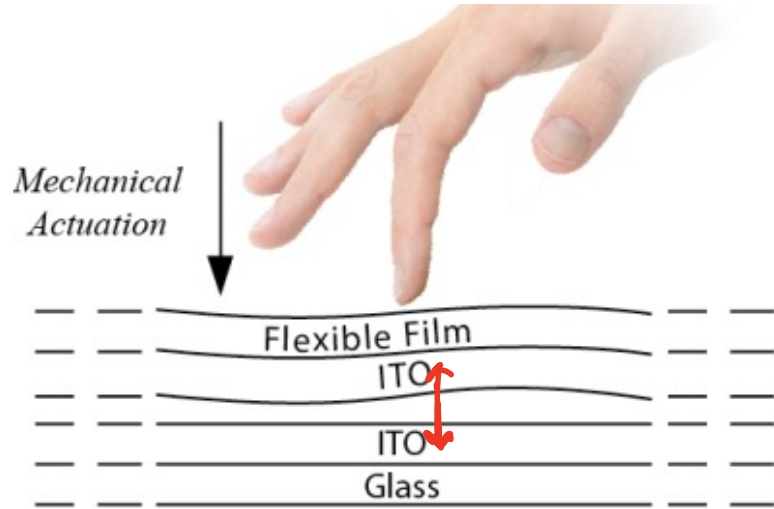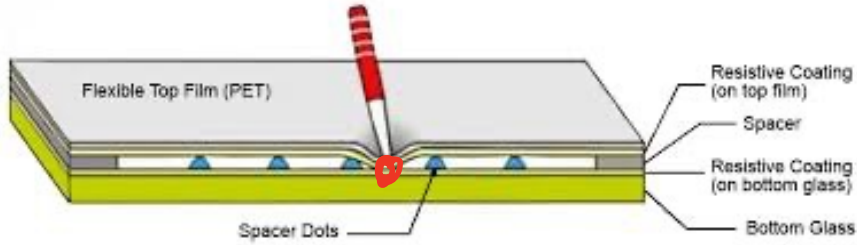


how much light passes through


want low R

$$V = IR \uparrow$$

$$\downarrow P = V \cdot I \downarrow$$

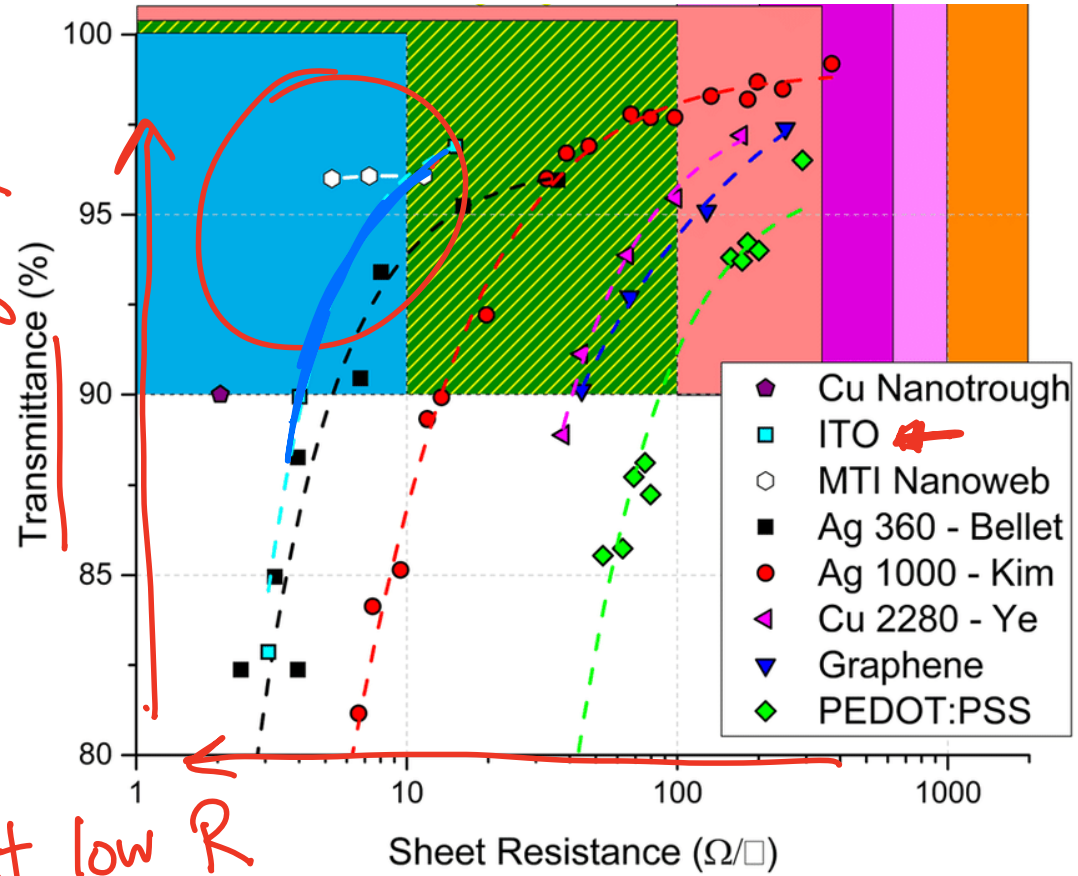


Resistive Touch Screen

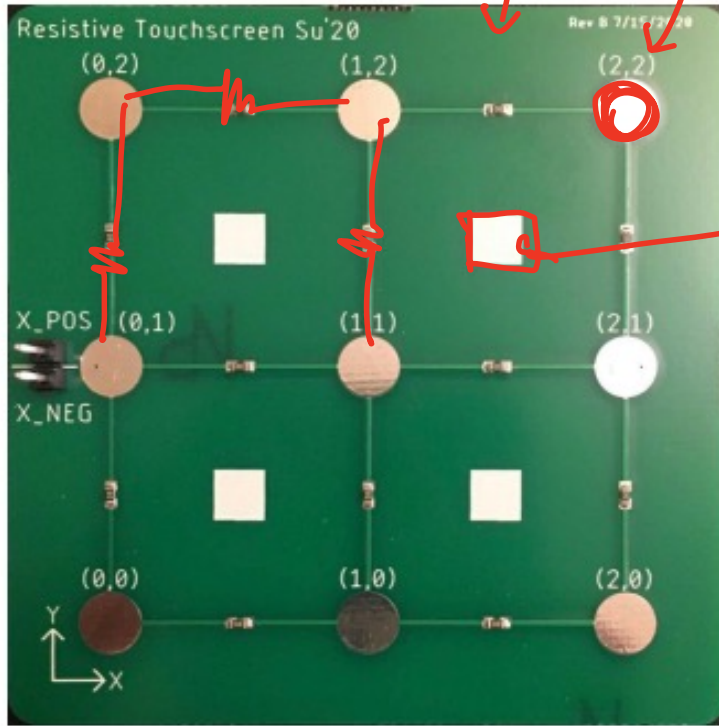

Bottom Layer: Resistive Layer

Top Layer: Flexible Resistive Layer

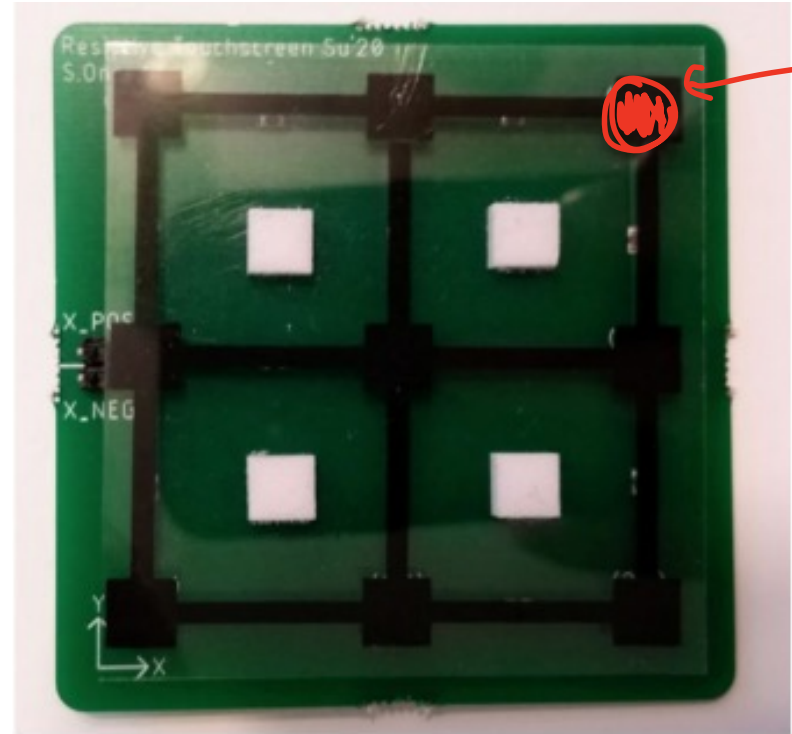


Rigid touchpoint

spacer

flex

Resistance, Resistivity, Conductivity – Properties of Materials

Note 12

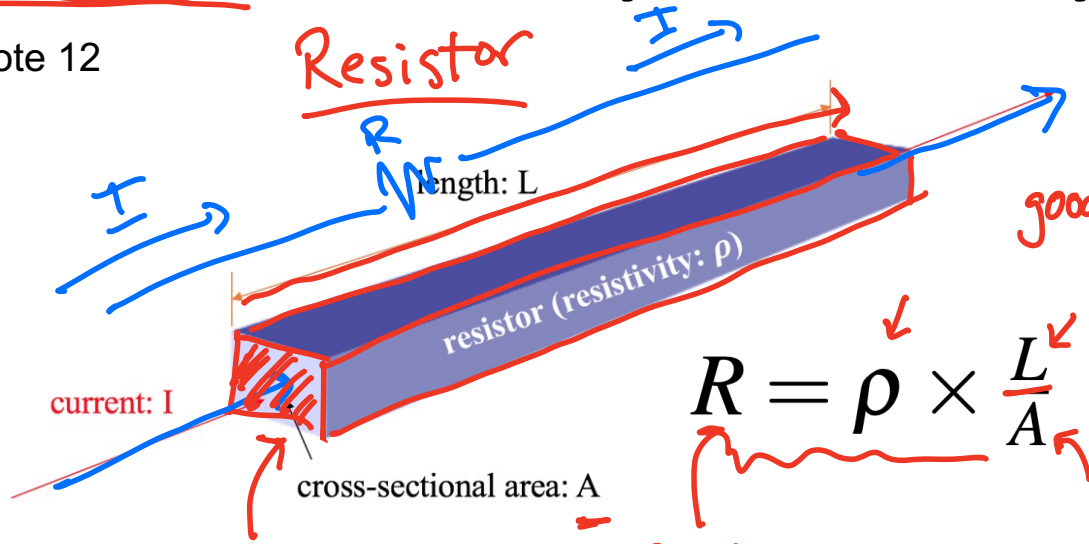

$\frac{L}{A}$: geometric parameters
 → properties of wire/elem (R)

Wide wires → low R

longer wires → more E is lost


Material	Electrical characteristics	
	Electrical Resistivity ($\Omega \times \text{cm}$)	Electrical Conductivity ($\Omega^{-1} \times \text{cm}^{-1}$)
Cu	0.034 x 10 ⁻⁵	29 x 10 ⁵
Fe	32.54 x 10 ⁻⁵	0.031 x 10 ⁵
Ag	0.36 x 10 ⁻⁵	2.8 x 10 ⁵
Al	0.03 x 10 ⁻⁵	33.3 x 10 ⁵
Ni	0.046 x 10 ⁻⁵	21.7 x 10 ⁵
Cu-Fe	33.37 x 10 ⁻⁵	0.030 x 10 ⁵
Cu-Ag	2.71 x 10 ⁻⁵	0.37 x 10 ⁵
Al-Ni	0.564 x 10 ⁻⁵	1.77 x 10 ⁵

Resistivity (ρ) [$\Omega\text{-cm}$]
 → property of the material

Conductivity (σ) [$\Omega\text{-cm}$]⁻¹
 $\sigma = \frac{1}{\rho}$
 - property of material

Resistive Touch Screen

Problem: Find the location of touch


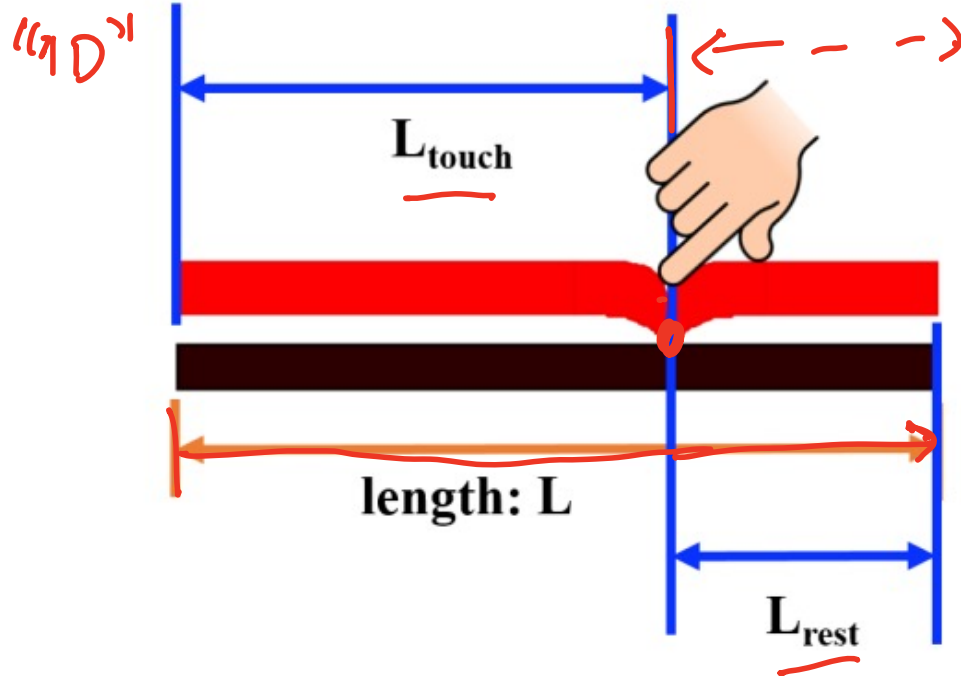


Go from **mechanical** to **electrical** quantity


Want to measure $\frac{L_{\text{touch}}}{L}$

L_{touch} is unknown

Resistive Touch Screen – First model

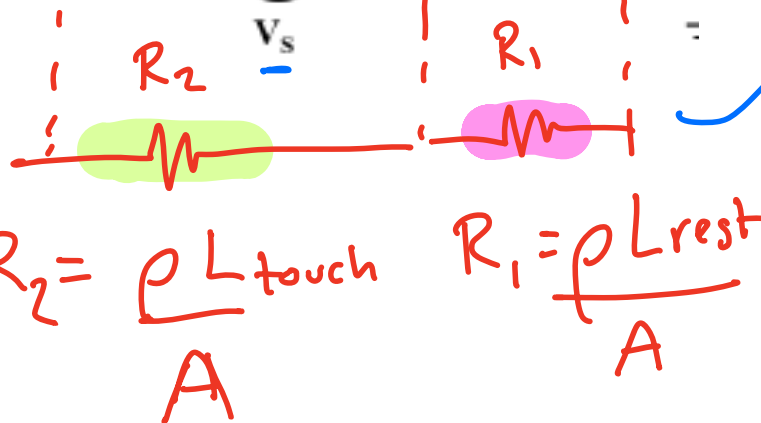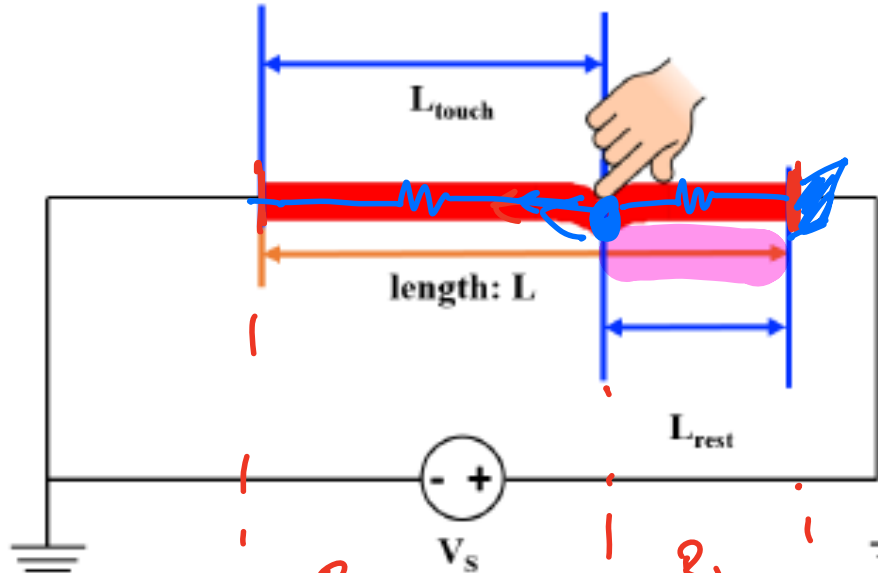
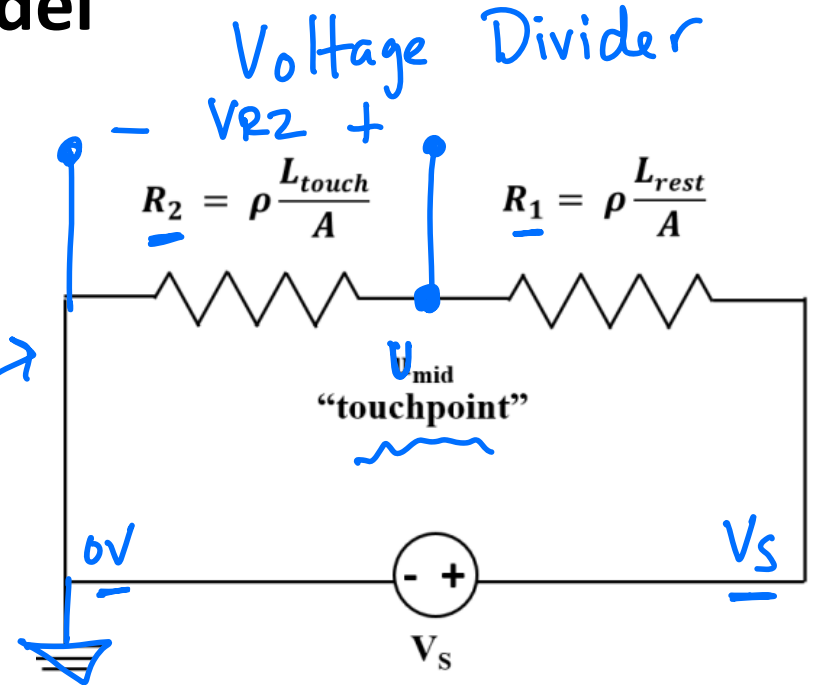
$$R_2 = \frac{\rho L_{touch}}{A} \quad R_1 = \frac{\rho L_{rest}}{A}$$



Voltage Divider



$$R_2 = \rho \frac{L_{touch}}{A} \quad R_1 = \rho \frac{L_{rest}}{A}$$

$$V_{mid} = V_s$$

$$V_{R2} = V_{mid} - 0$$

$$\Rightarrow V_{mid} = V_s \frac{R_2}{R_1 + R_2}$$

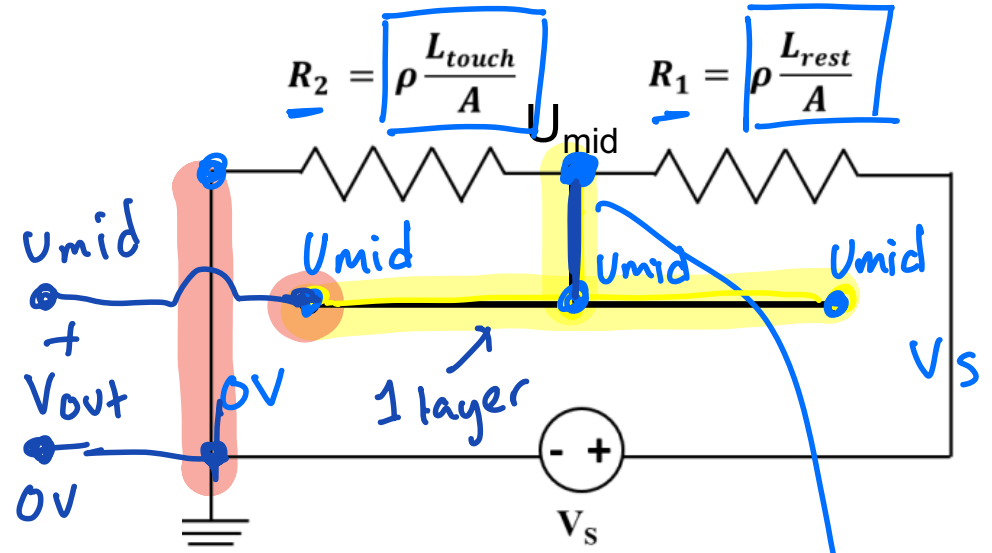
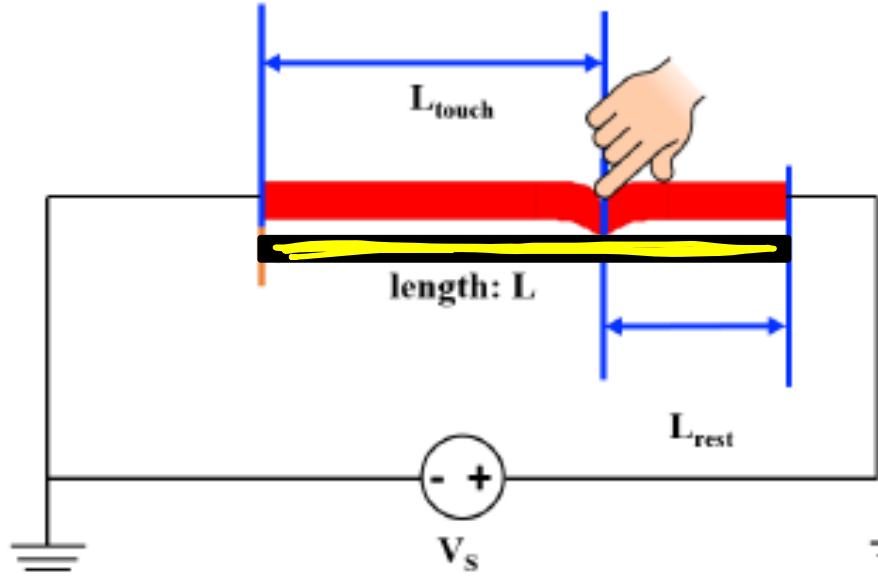
Resistive Touch Screen – More realistic model




$$U_{mid} = V_s \left(\frac{R_2}{R_1 + R_2} \right)$$

$$* U_{mid} = V_s \left(\frac{\rho L_{touch}/A}{\rho L_{rest}/A + \rho L_{touch}/A} \right) = V_s \left(\frac{L_{touch}}{L_{rest} + L_{touch}} \right) = \frac{V_s L_{touch}}{L}$$


$V_{out} = U_{mid}$ (open circuit)

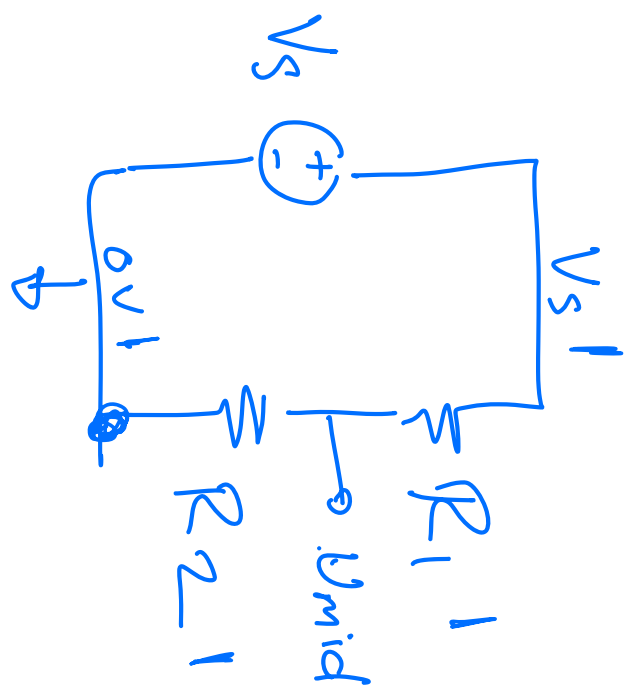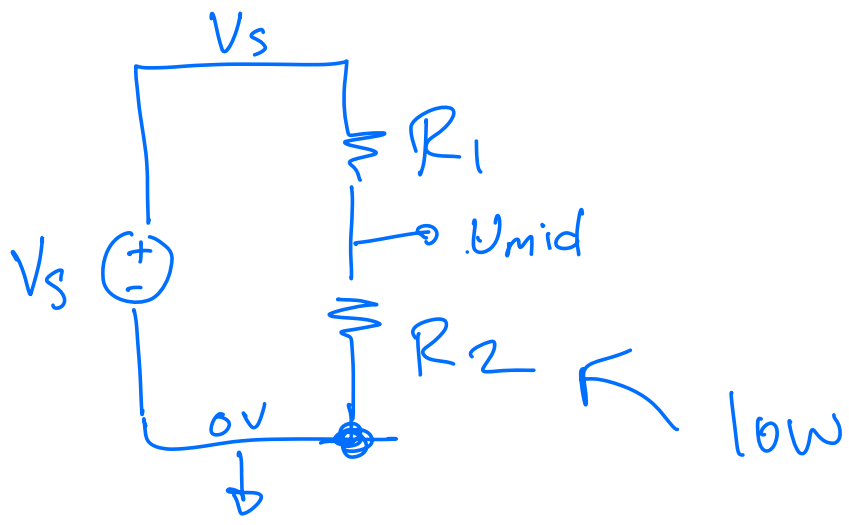

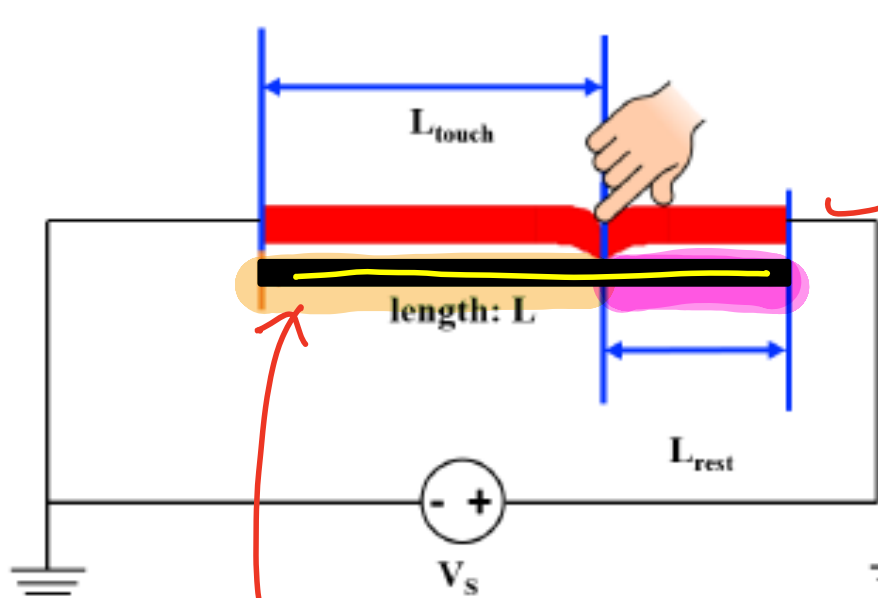Resistive Touch Screen – Most realistic model




represents bottom plate

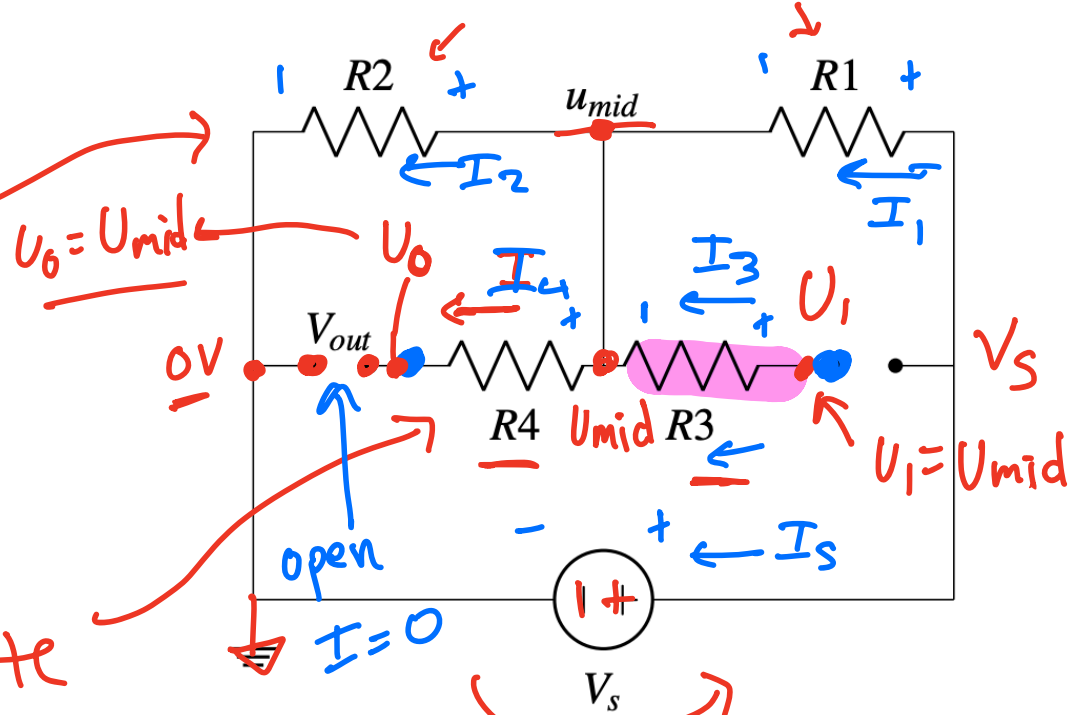


KCL: $I_4 = 0$

$I_3 = 0$

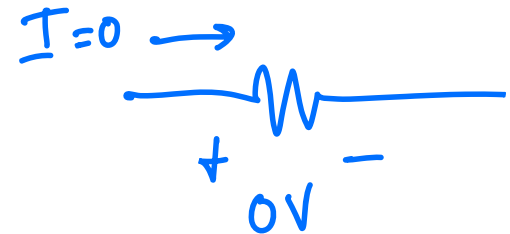


$V_{out} = U_{mid}$

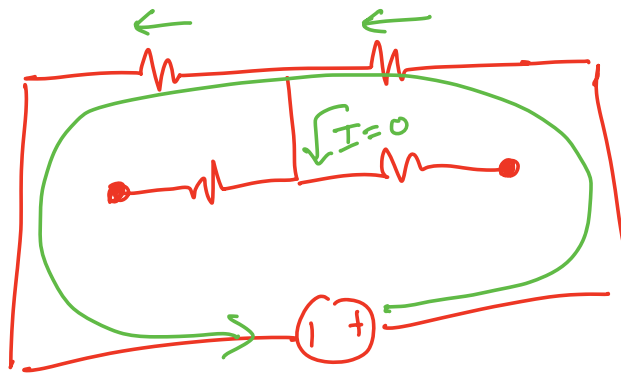


An Interesting Circuit *

What are U_2 ? U_3 ?

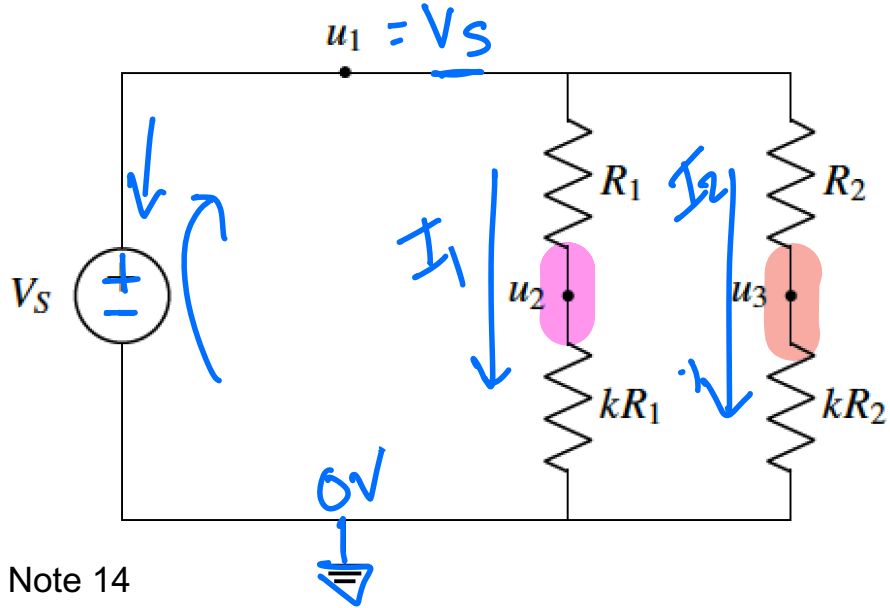

Note 14

* tool box

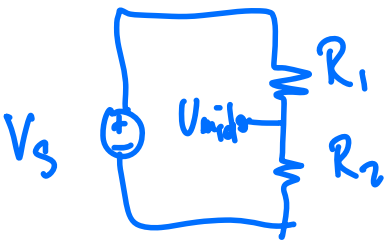

$$U_{mid} = V_S \left(\frac{R_2}{R_1 + R_2} \right)$$