

EECS 16A

Spring 2023 - Profs.
Muller & Waller
2D Resistive
Touchscreens


TOUCH SCREEN




YOU'RE DOING IT WRONG

Toolbox

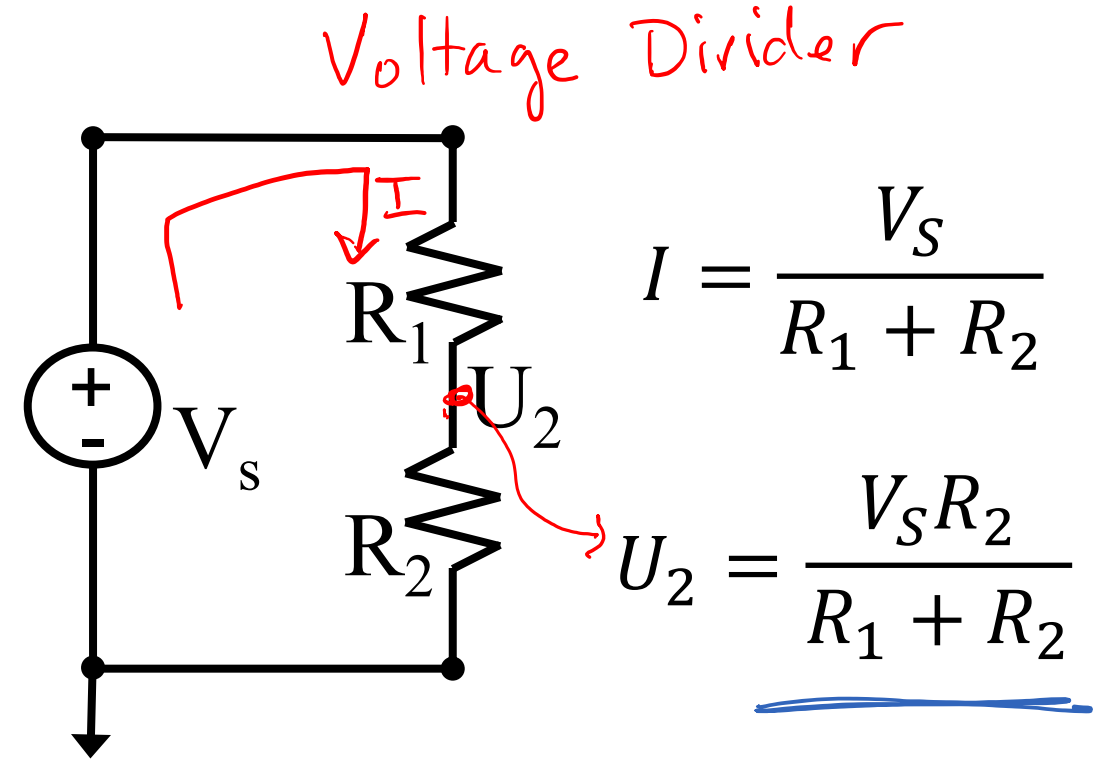
- ✓ *KVL: Voltage drops around a loop sum to 0*
- ✓ *KCL: All currents coming out of a node sum to 0*
- ✓ $V = IR$
- ✓ $P = IV$
- $R = \rho L/A$





V Measurement Circuit

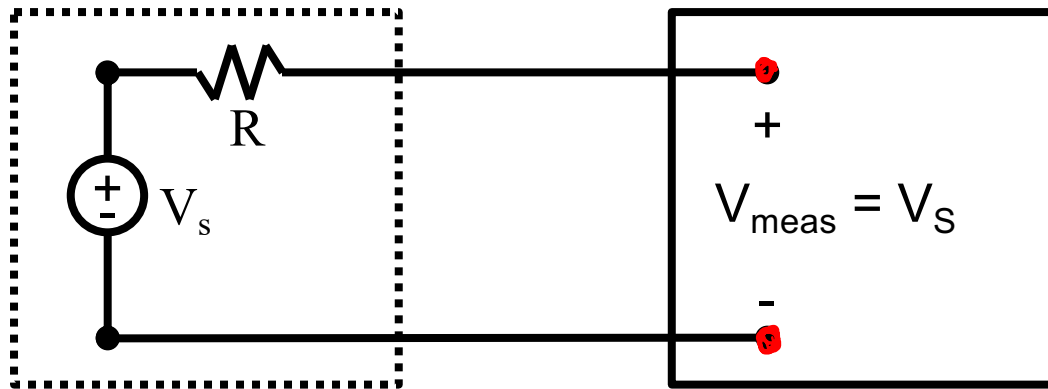

I Measurement Circuit

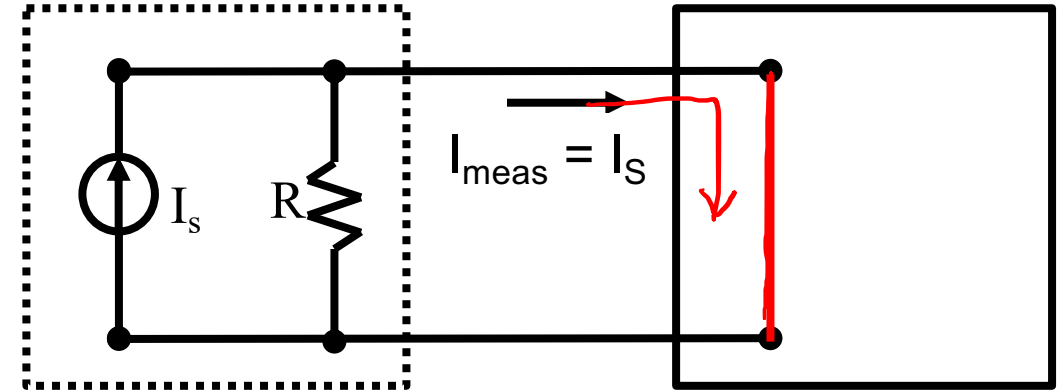

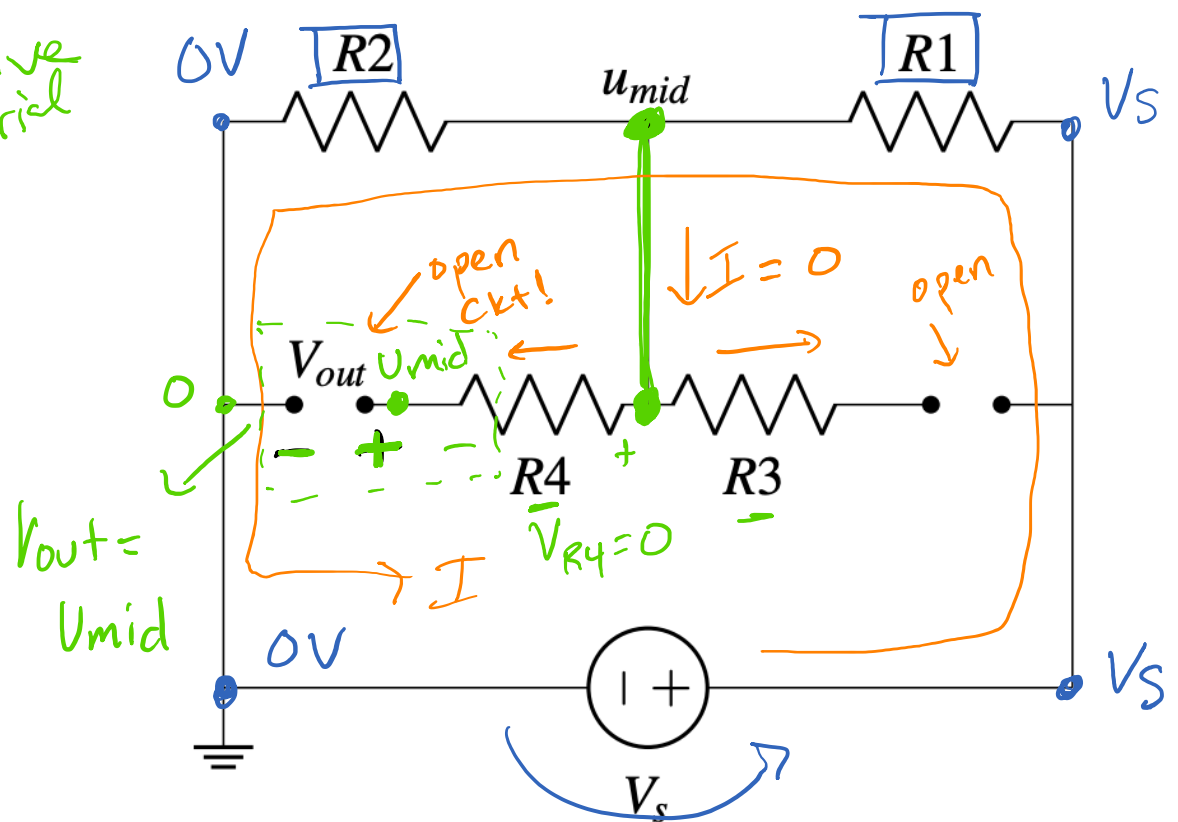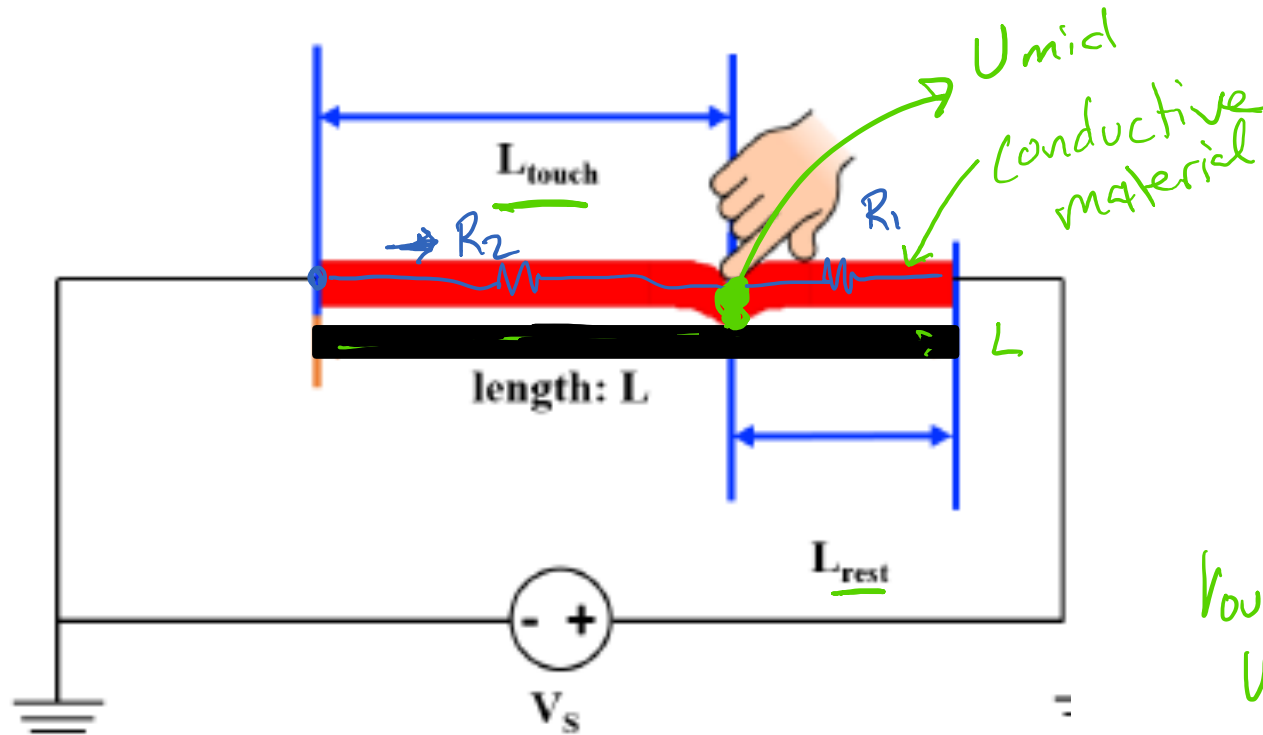Recap: Resistive Touch Screen – More realistic model



$$R = \frac{\rho L}{A}$$

$$L = L_{touch} + L_{rest}$$

$$R_2 = \frac{\rho L_{touch}}{A}$$


$$R_1 = \frac{\rho L_{rest}}{A}$$

Voltage Divider

$$U_{mid} = V_s \cdot \frac{R_2}{R_1 + R_2} = \frac{V_s \cdot \frac{\rho L_{touch}}{A}}{\frac{\rho L_{rest}}{A} + \frac{\rho L_{touch}}{A}}$$

$$= \frac{V_s L_{touch}}{L}$$

An Interesting Circuit

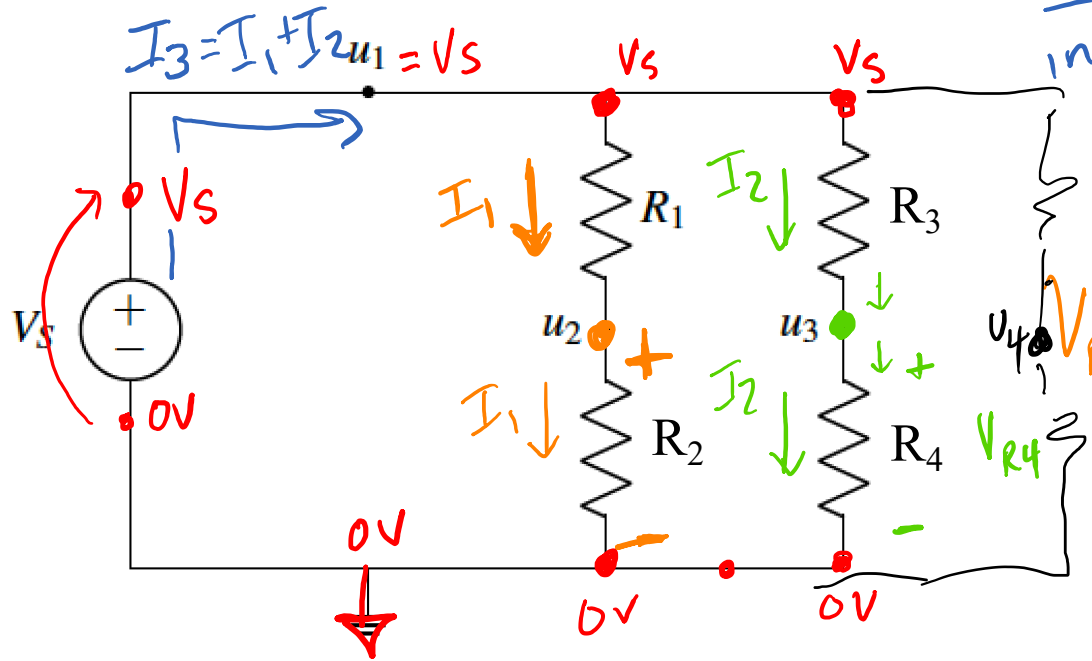

$$\frac{I_3}{\text{in}} = \frac{I_1 + I_2}{\text{out}}$$

$$I_1 = \frac{V_s}{R_1 + R_2}$$


$$I_2 = \frac{V_s}{R_3 + R_4}$$

$$V_{R4} = U_3 - 0 = I_2 R_4$$

$$V_{R2} = U_2 = \frac{V_s R_2}{R_1 + R_2}$$

$$U_3 = \frac{V_s R_4}{R_3 + R_4}$$

Note 14

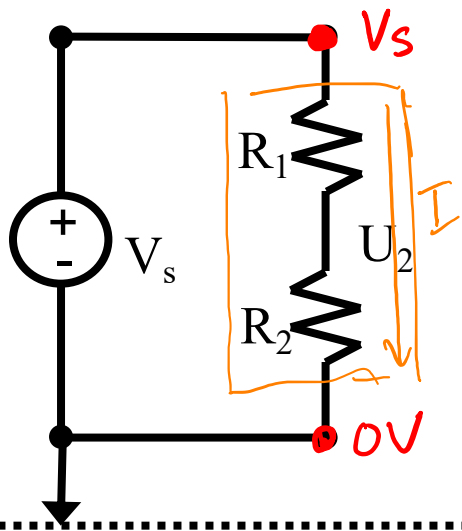

$$I = \frac{V_s}{R_1 + R_2}$$

$$U_2 = \frac{V_s R_2}{R_1 + R_2}$$


same!

same!

more branches? no problem

solve U_4 same way

An Interesting Circuit

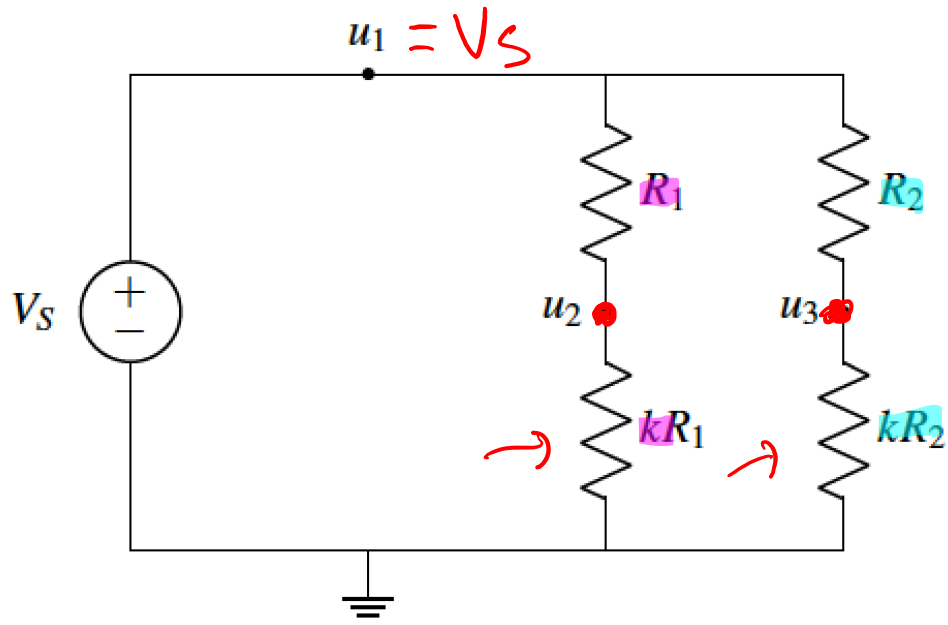

Note 14

$$U_2 = \frac{V_S \cdot kR_1}{kR_1 + R_1}$$

$$U_3 = \frac{V_S \cdot kR_2}{kR_2 + R_2}$$

$$U_2 = V_S \cdot \frac{k}{k+1}$$


$$U_3 = \frac{V_S k}{k+1}$$

* independent of resistance value

→ only ratio is important

* $U_2 = U_3$!!!

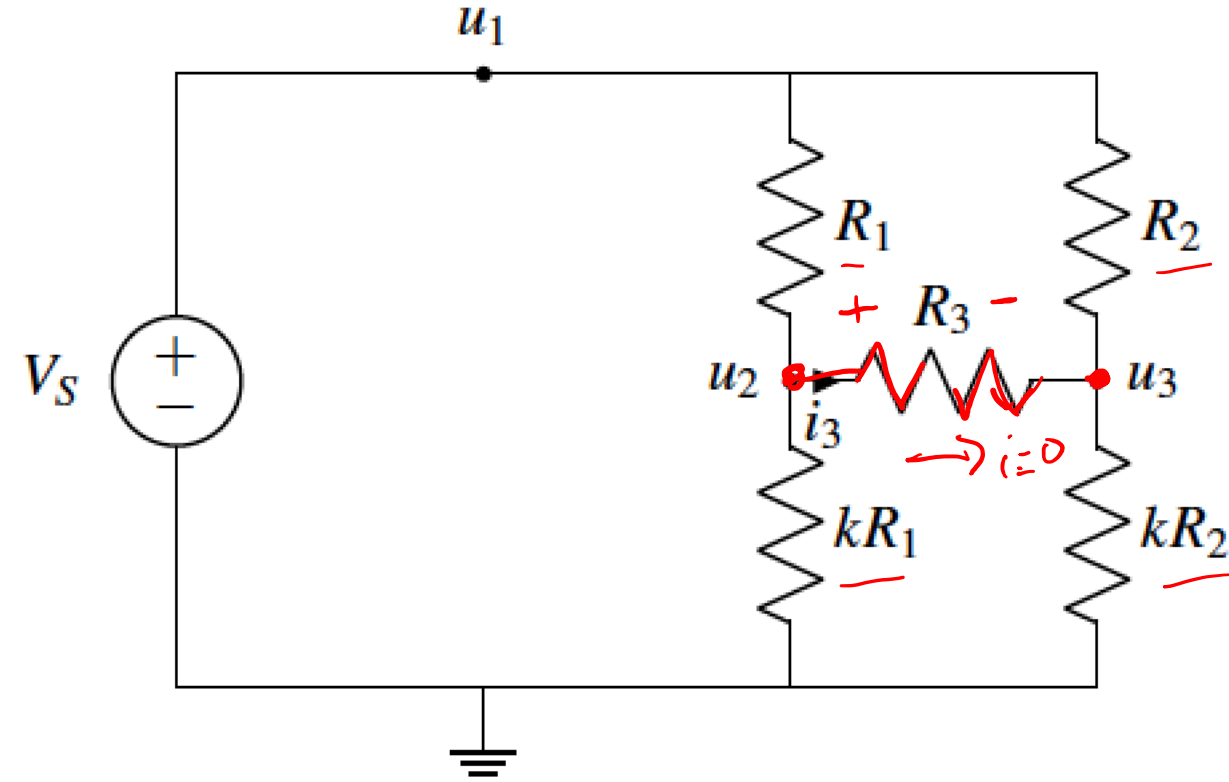Let's add one more resistor – what is i_3 ?





$$U_2 = U_3$$

$$i_3 = ?$$

$$V_{R3} = U_2 - U_3 = i_3 R_3$$
$$= 0$$


$$\therefore i_3 = 0$$

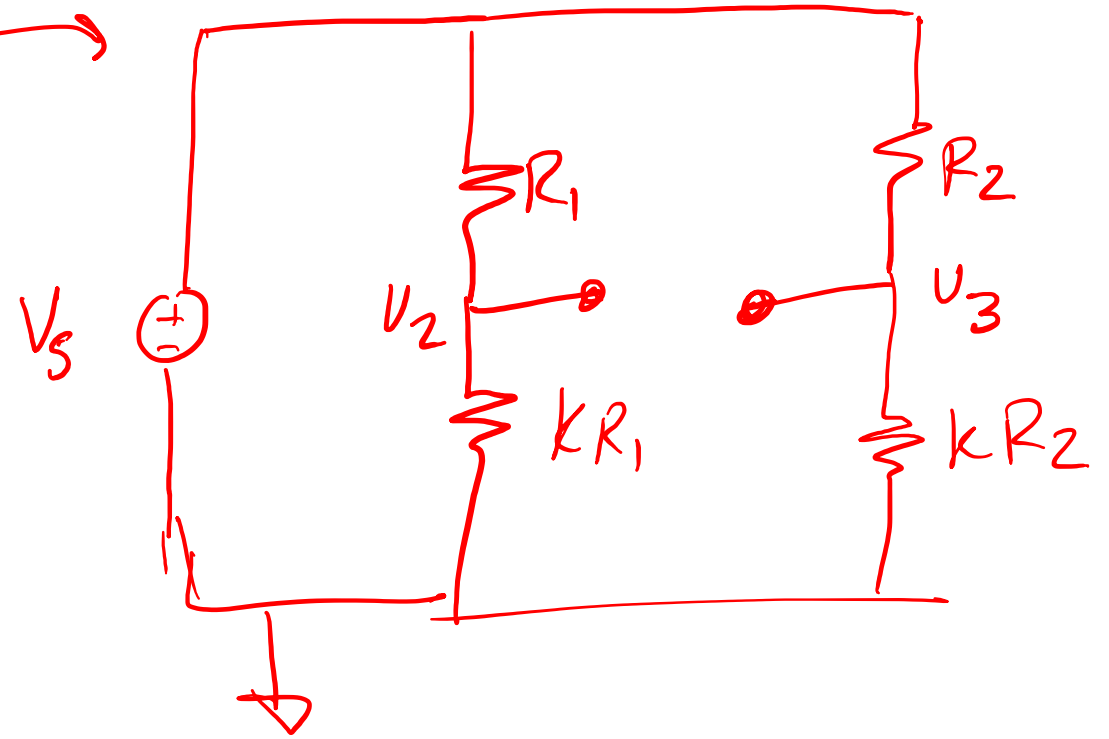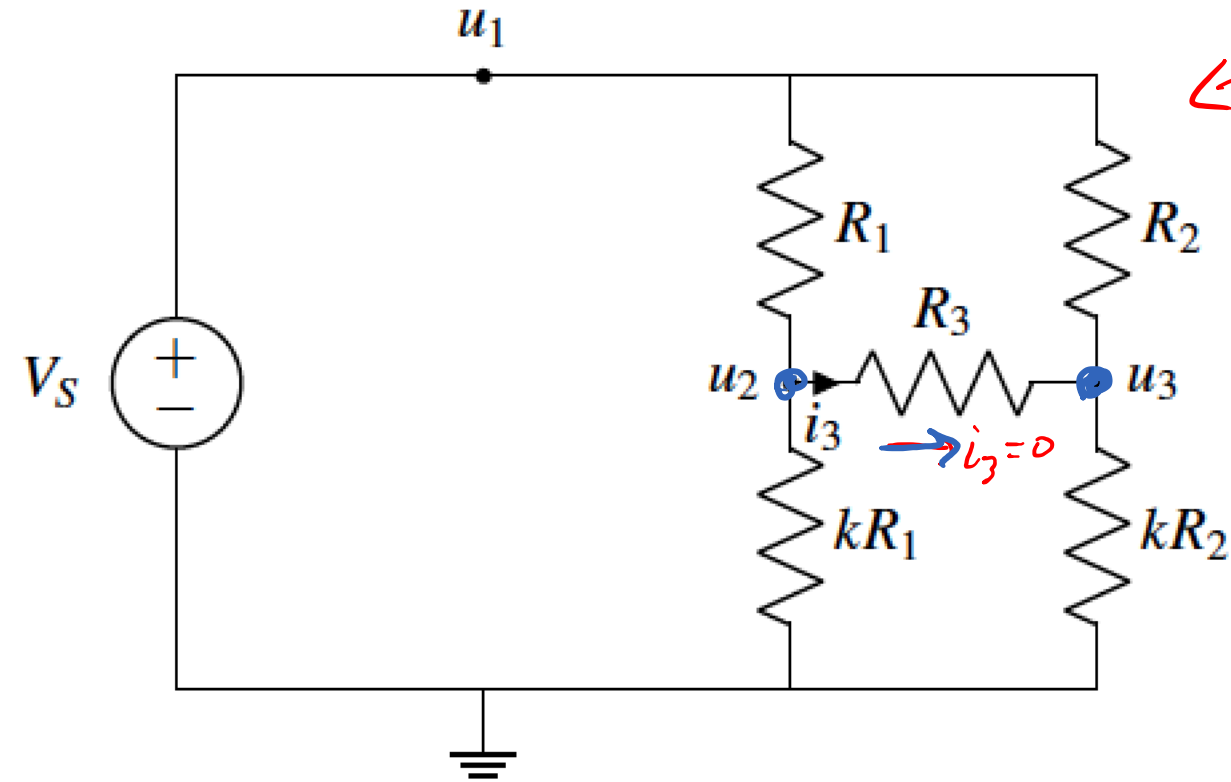Let's add one more resistor – equivalent circuit



an open circuit also has $i = 0$
functionally these circuits are equivalent

Who's willing to be R3?

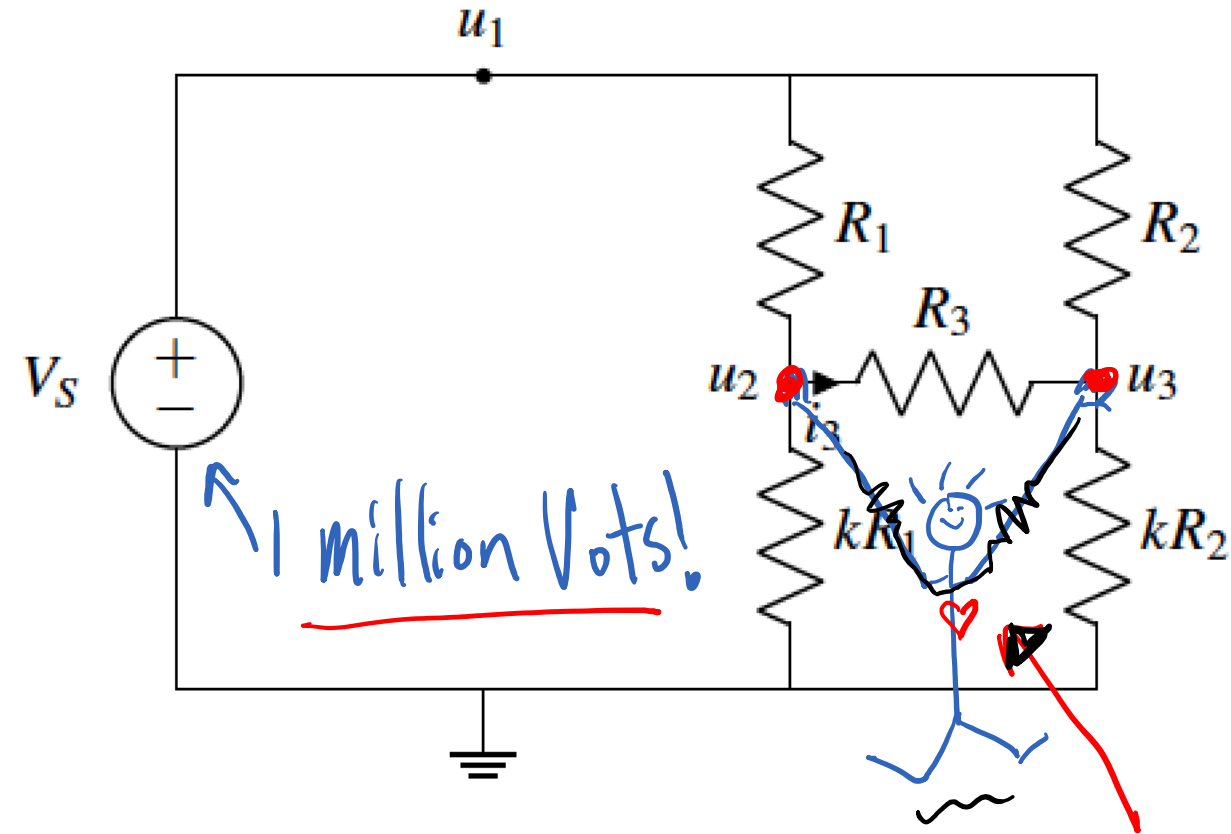




Resistor tolerance?

$\sim 1\%$




$\sim 100 \text{ mA}$ to stop a human heart!
 $= 0.1 \text{ A}$

$V_{R3} \Rightarrow 10,000 \text{ Volts!}$ ← what's the resistance of a human?


2D Touch Screen

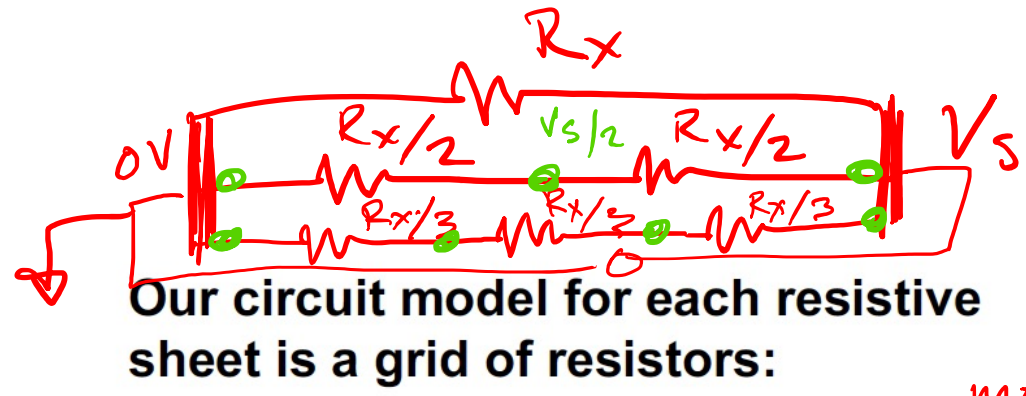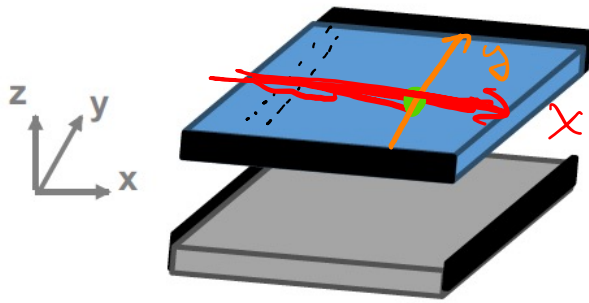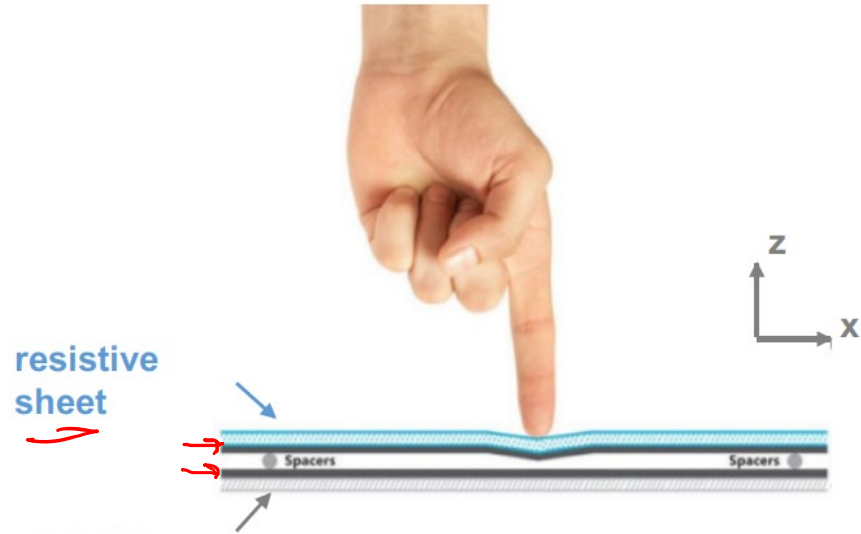

model of ITO

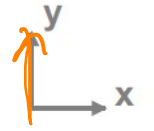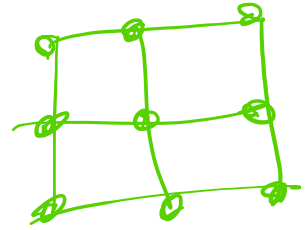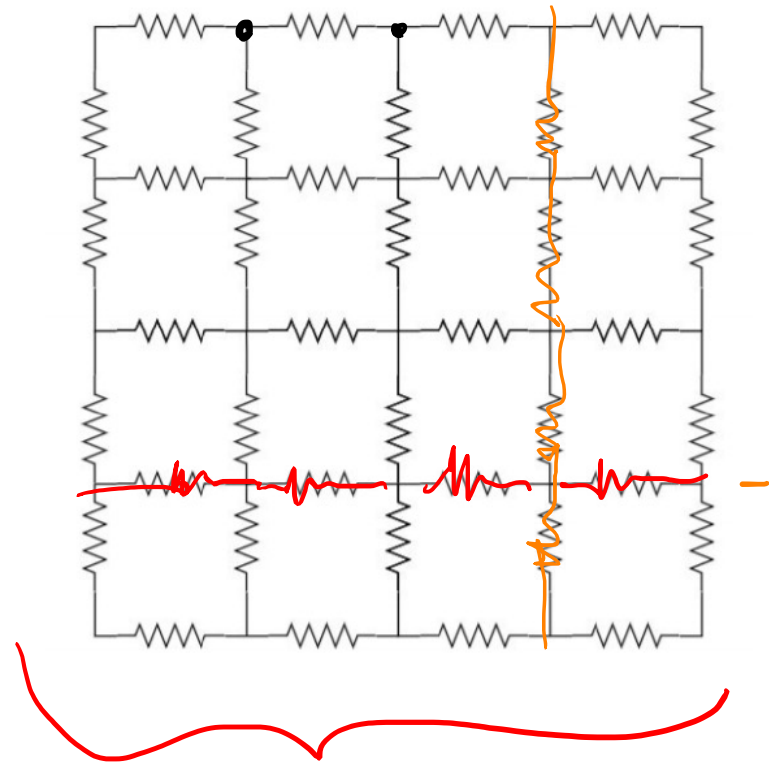



2D Touch Screen

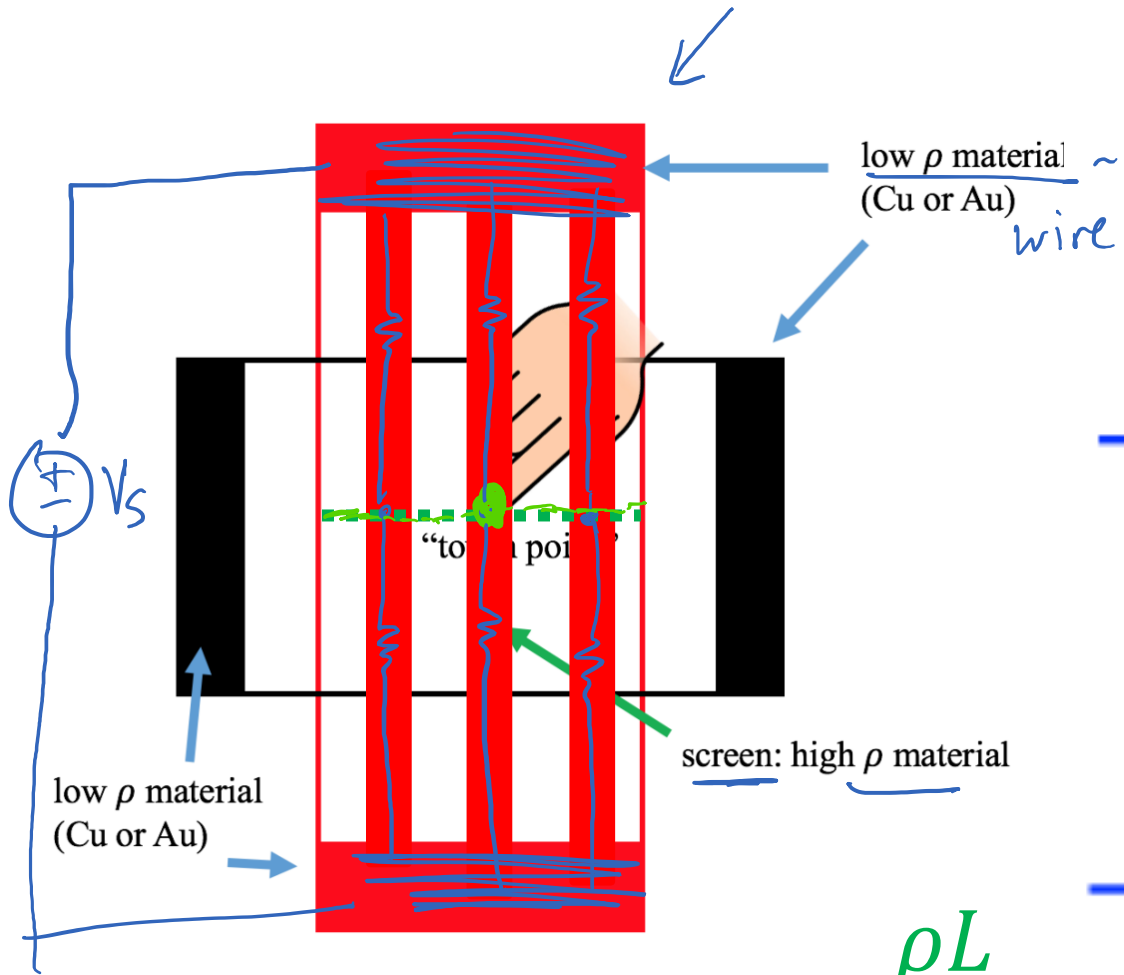


$$R = \frac{\rho L}{A}$$

$$L = L_{touch} + L_{rest}$$

(Same)

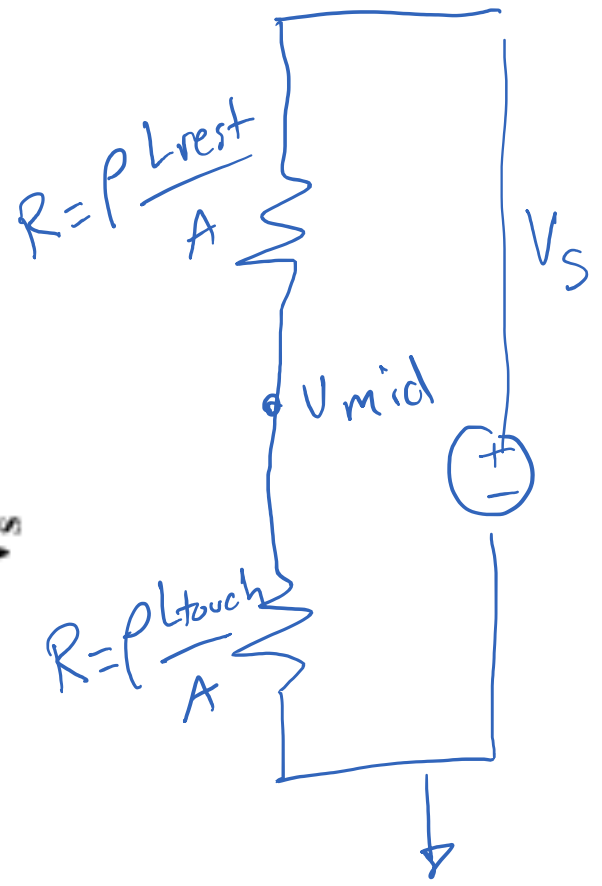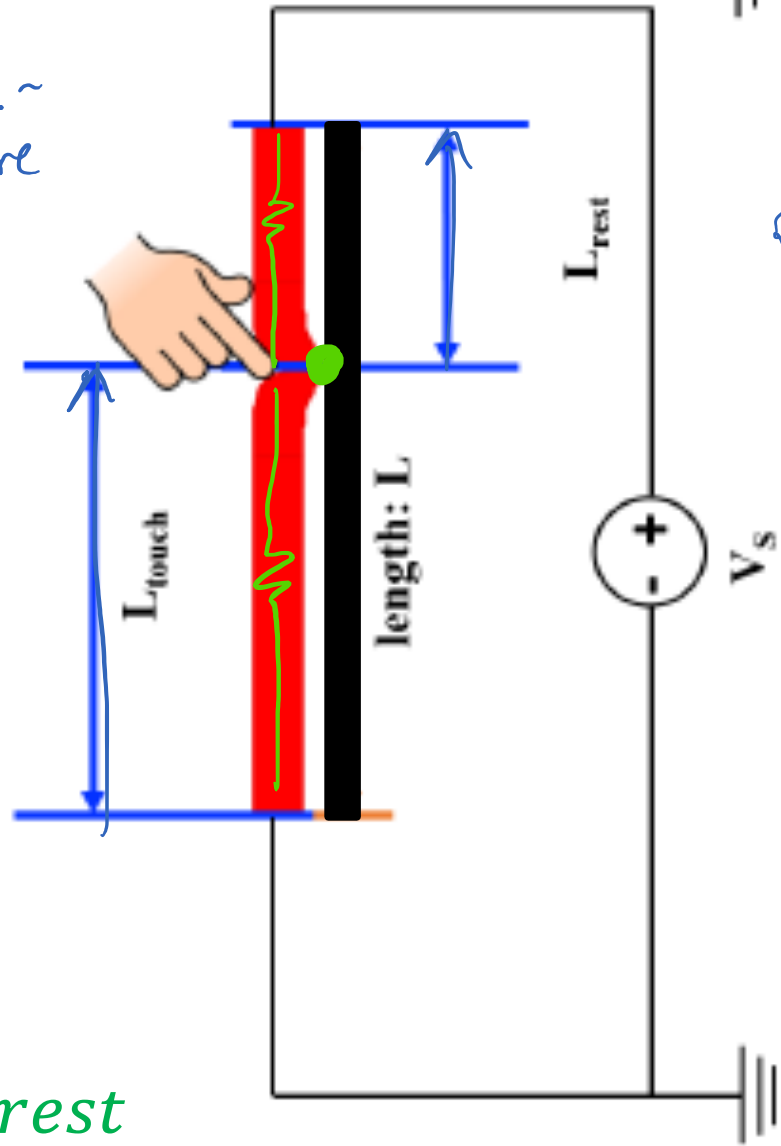

Top Plate Circuit Model

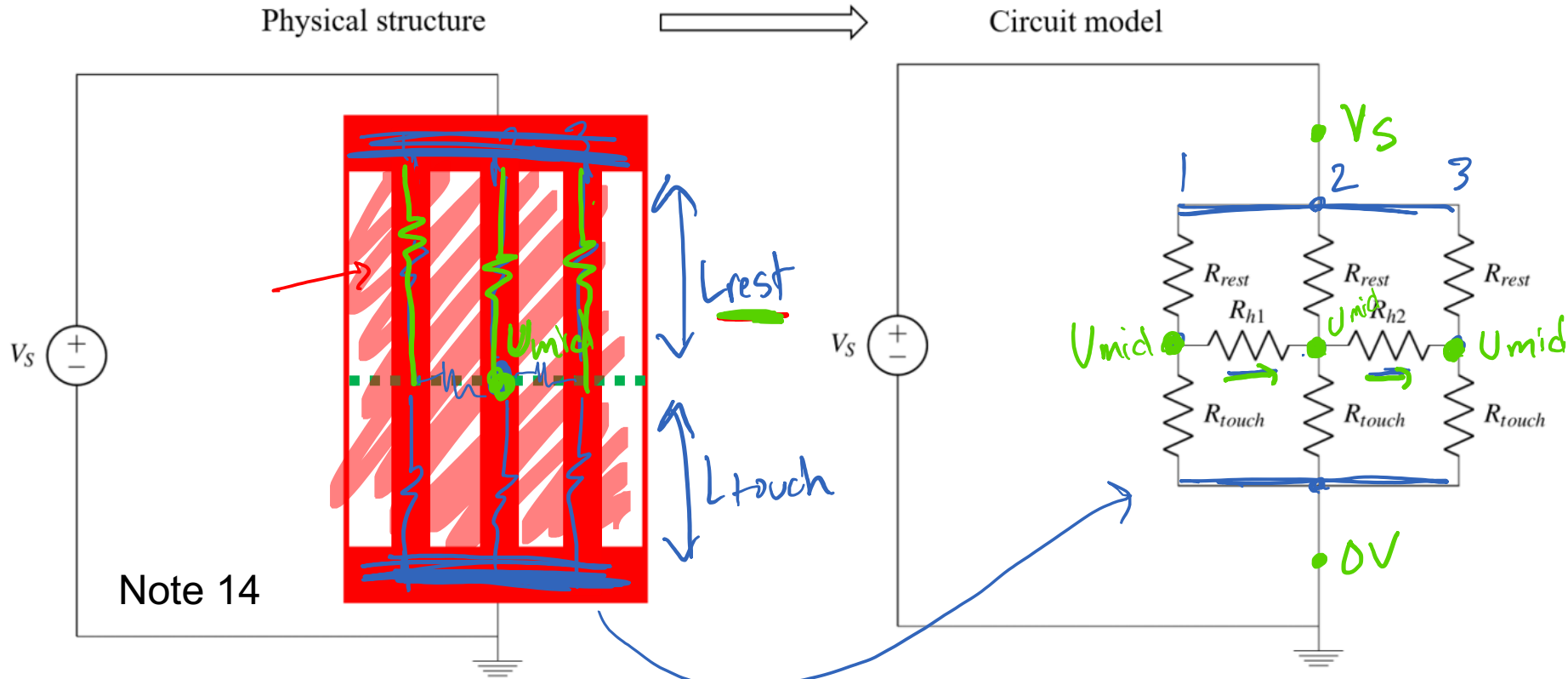

Note 14

Why R_{h1}, R_{h2} ?
(Volt. divider)

$$V_{mid} = \frac{V_s \cdot R_{touch}}{R_{touch} + R_{rest}}$$


$$i_{Rh1} = 0 \quad V_{Rh1} = 0$$

$$R = \frac{\rho L}{A}$$

$$L = L_{touch} + L_{rest}$$

$$V_{mid} = V_s \cdot \frac{\rho L_{touch} / A}{\rho L_{touch} / A + \rho L_{rest} / A} = \frac{V_s L_{touch}}{2}$$

Bottom Plate Model


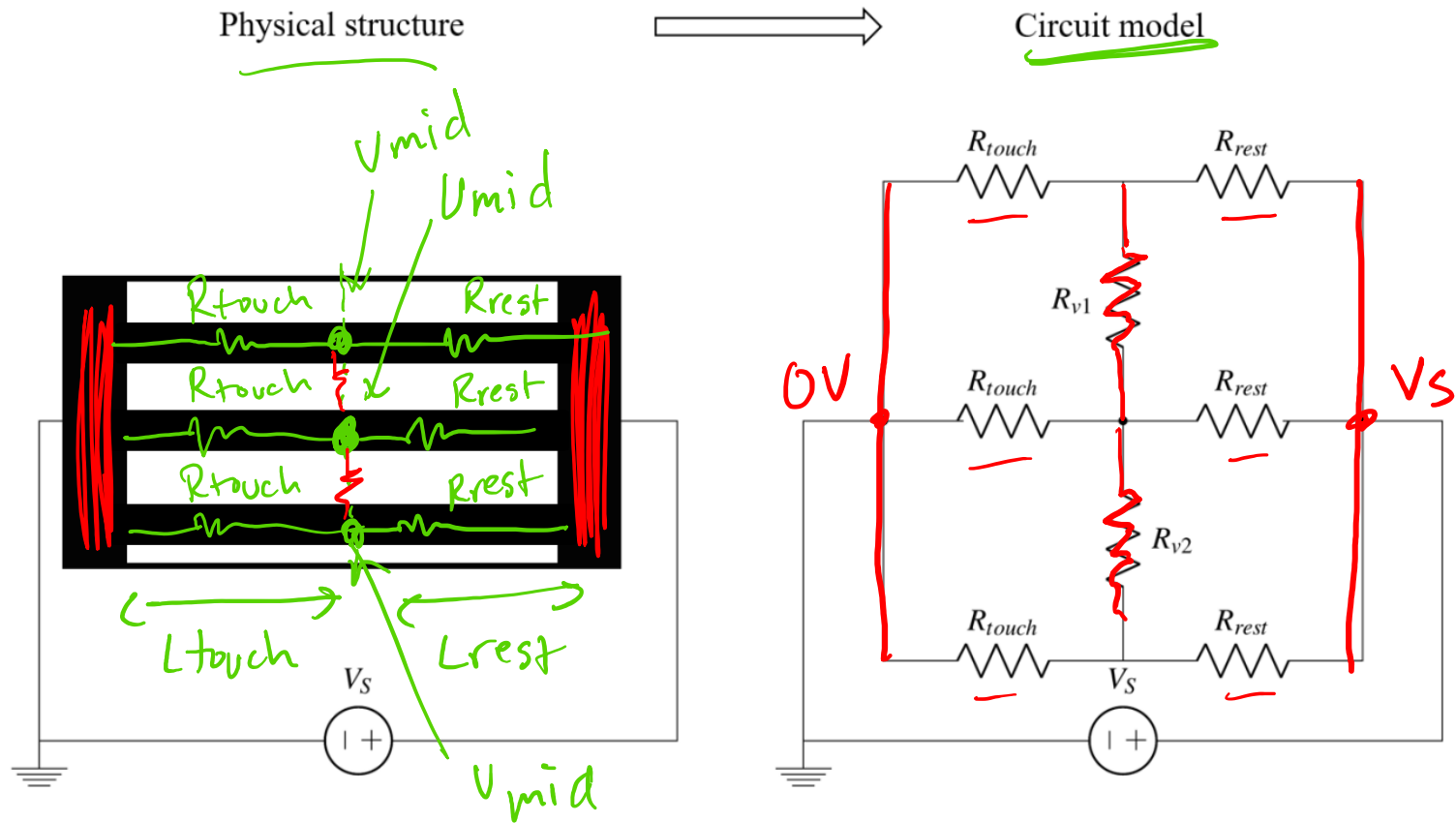


Note 14

$\longrightarrow X$

Touchscreen Readout

rotate 90°

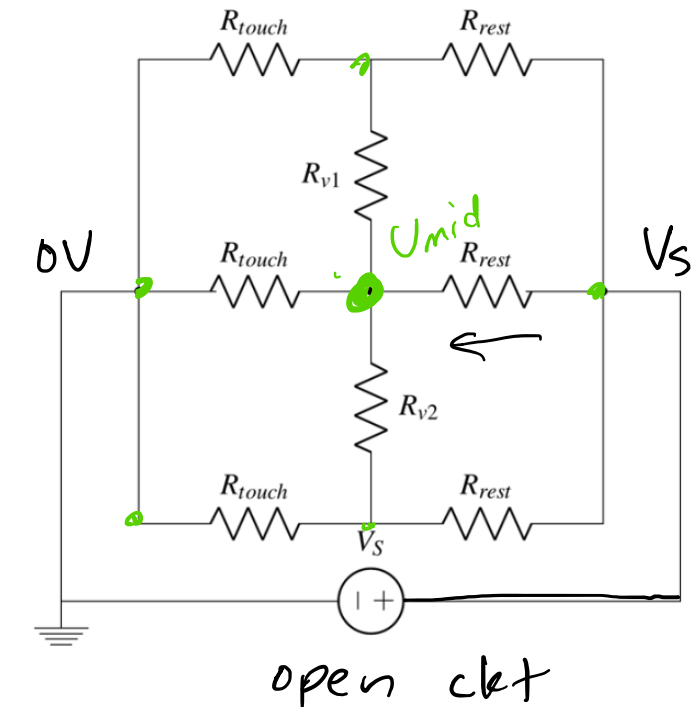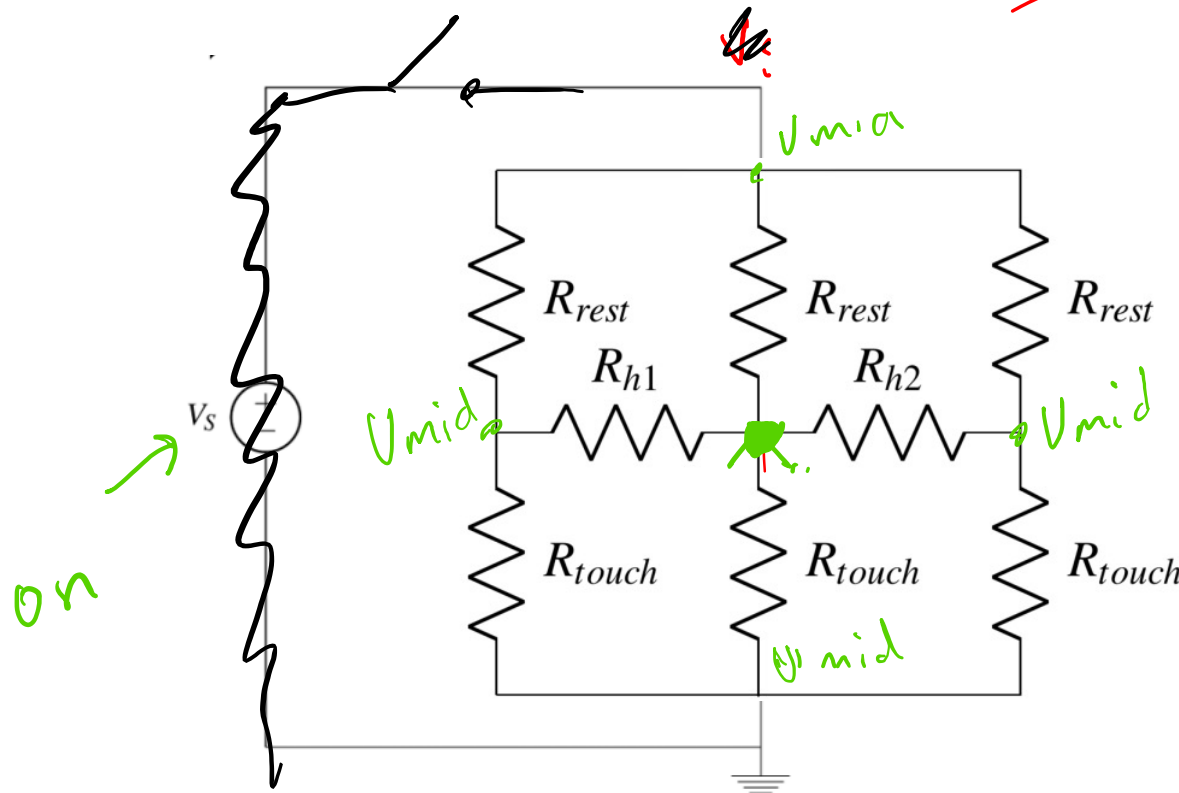

$$V_{mid} = \frac{V_s L_{touch}}{2}$$


1st - power vertical
Vertical Measurement
y-touch position →

Horizontal Measurement
x-touch position →

1st


2nd
ping pong

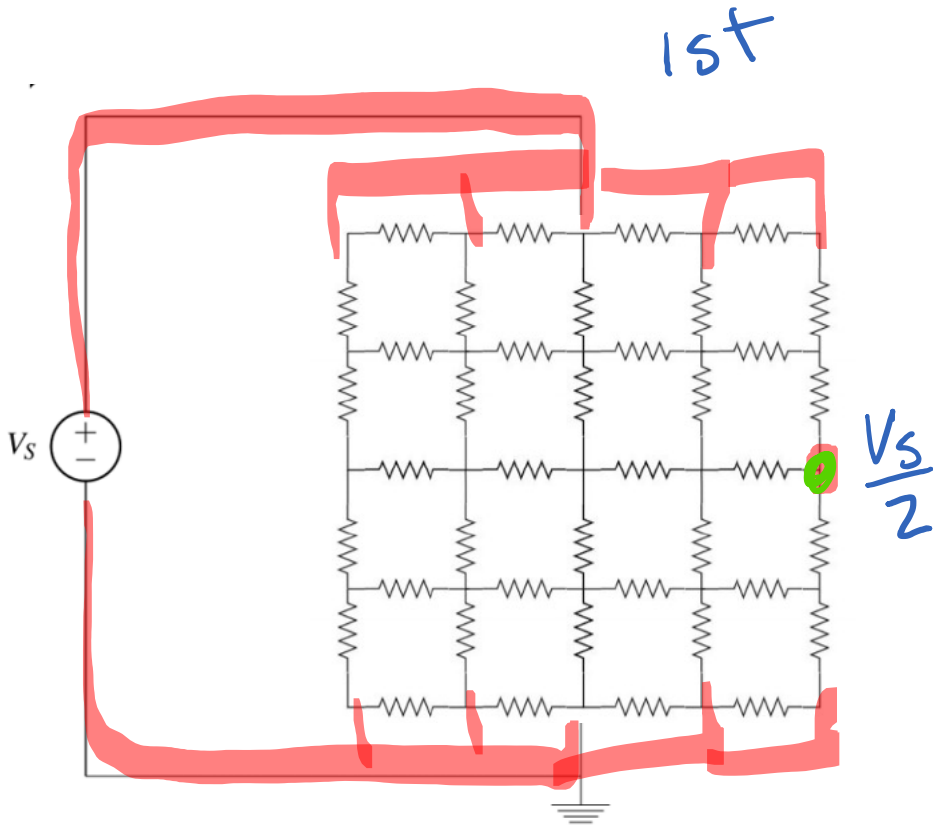Touchscreen Readout – More realistic model



Vertical Measurement
y-touch position

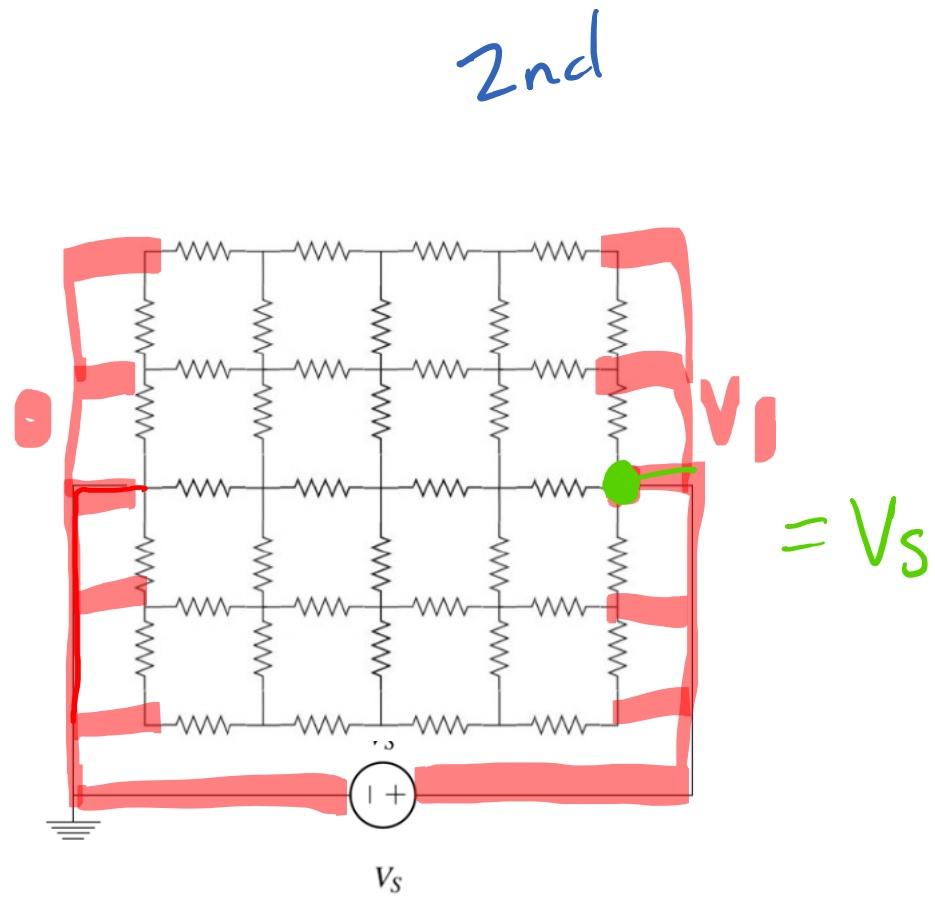$\rightarrow \frac{V_s}{2} = \frac{y_{max}}{2}$




Horizontal Measurement
x-touch position

$V_s = x_{max}$

Equivalence



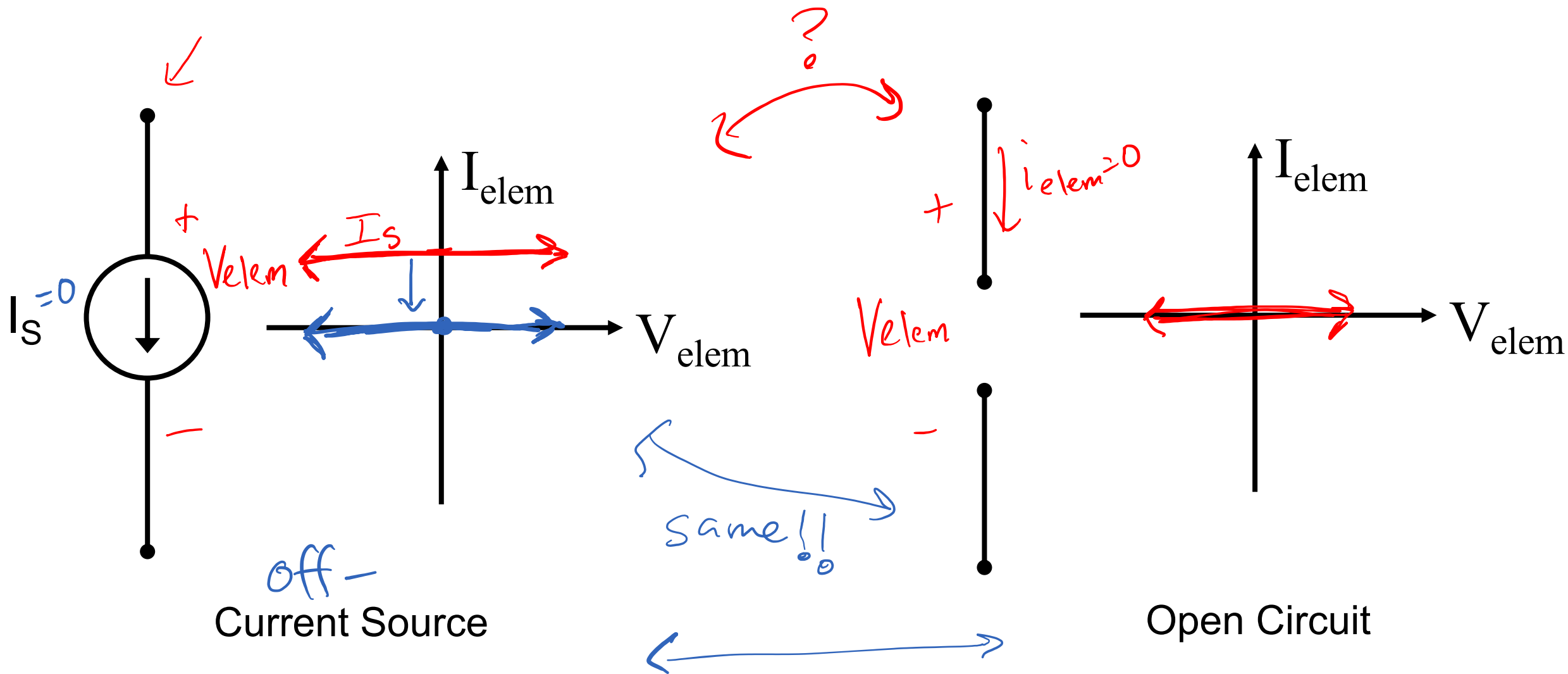* Two circuits are equivalent if they have the same IV relationship



Equivalence

allows circuit simplification

Two circuits are equivalent if they have the same IV relationship

