



Danger
Electric shock
risk



EECS 16A
Spring 2023 - Profs. Muller & Waller
Lecture 8B –
Capacitors & Capacitive Touchscreens

Toolbox

KVL: Voltage drops around a loop sum to 0



KCL: All currents coming out of a node sum to 0

$$V = IR$$


$$P = IV \quad R = \frac{\rho L}{A}$$

V_{source} (off) \rightarrow short

I_{source} (off) \rightarrow open

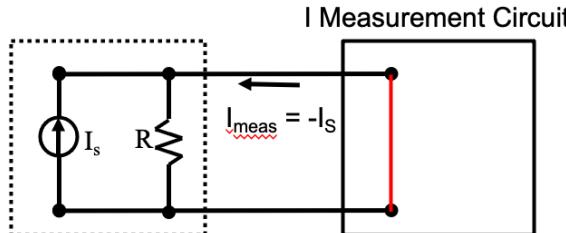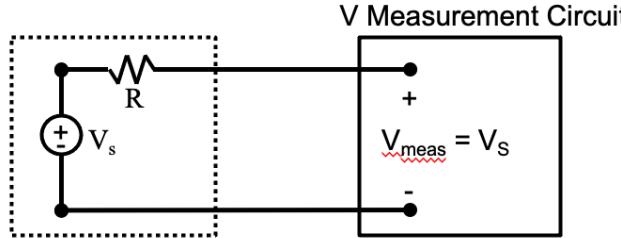

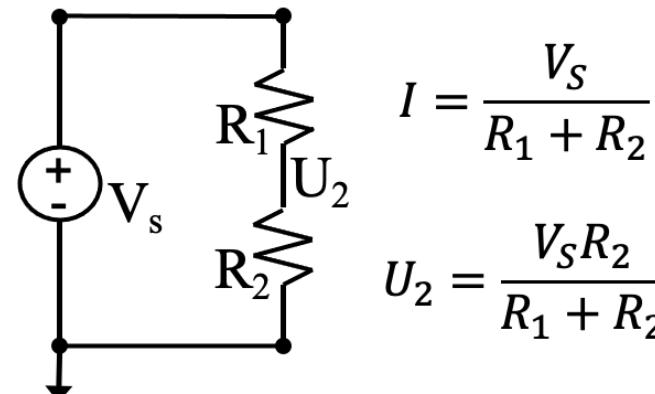
$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$




$$R_{\text{Th}} = V_{\text{Th}} / I_N$$

Thevenin Equivalent Circuit

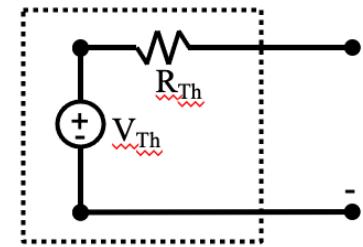


Norton Equivalent Circuit

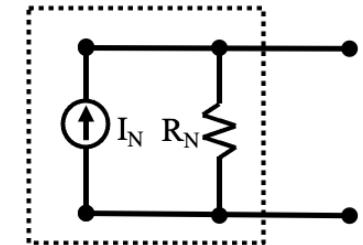

Last Time

Capacitance C in [Farads] or [F]

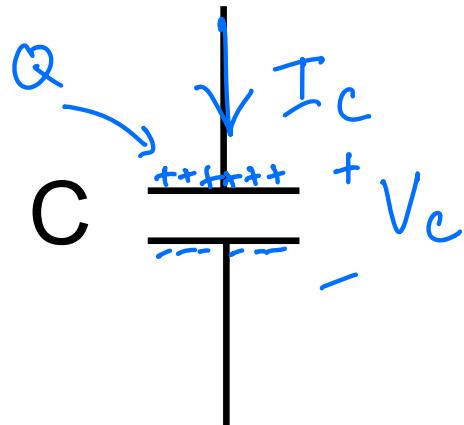


① $\frac{\partial}{\partial t}$ ②

$$Q = CV$$
$$I = C \frac{dV}{dt} * \text{I-V relation}$$

③


$$C = \frac{\epsilon A}{d}$$

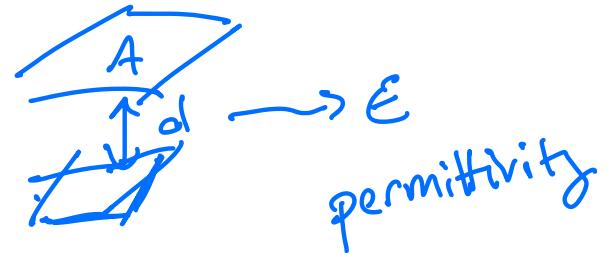

Circuit Example 1

Find the current in the capacitor I_C .

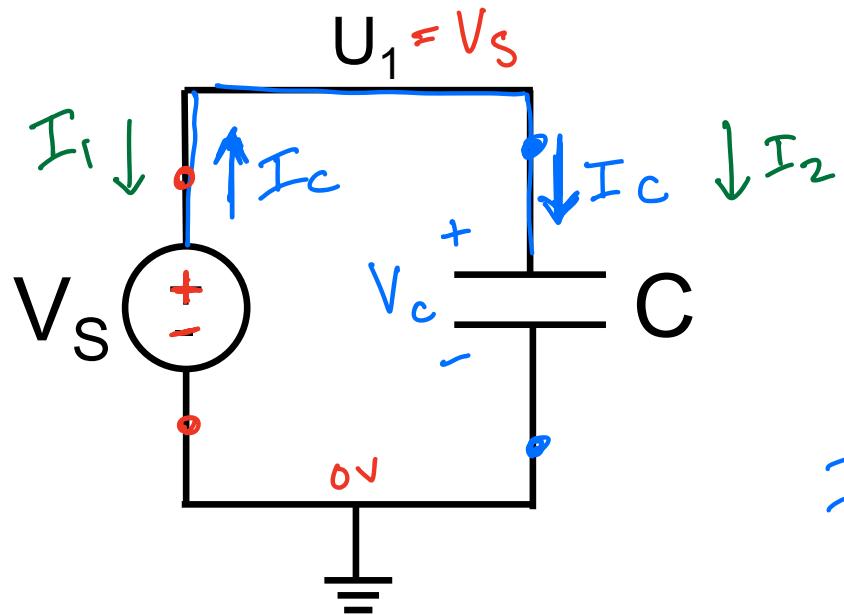→ V_C hasn't changed in a long time. (steady state)




$$\begin{aligned} \text{KCL: } I_1 + I_2 &= 0 \\ I_1 &= -I_2 \end{aligned}$$

Unknowns : I_c

I - V relation for C :

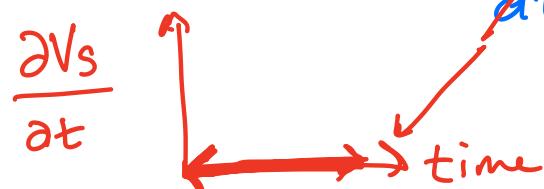
$$* I_c = C \frac{dV_c}{dt} = 0 \quad V_c = U_1 - 0 = V_s$$



$$* I_c = 0$$

Circuit Example 2

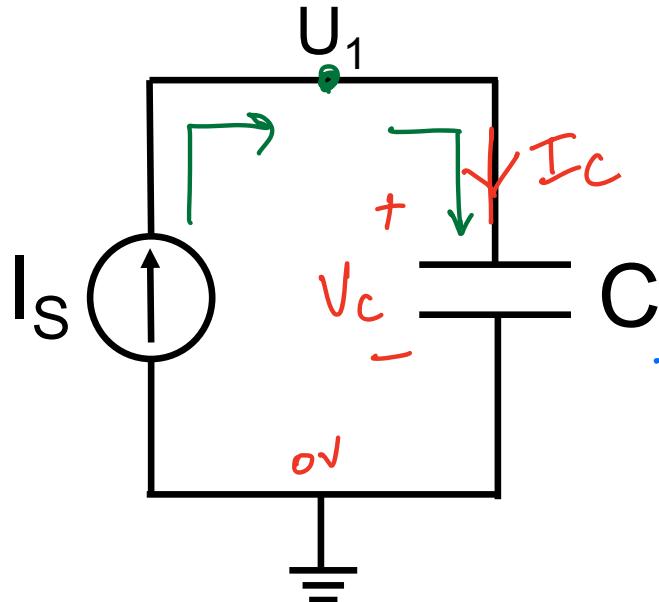At time $t = 0$, $\underline{U}_1 = \cancel{\underline{U}_1(0)}$ Volts
 Plot \underline{U}_1 vs. time ↑ cap is discharged



$$\underline{U}_1(0) = 0$$

$$KVL: V_c = U_1 - 0 = U_1 \Rightarrow V_c(t=0) = 0$$

$$KCL: I_s = I_c$$

$$\text{Unknown: } V_c = U_1$$


I-V

$$I_c = C \frac{dV_c}{dt} \Rightarrow I_s = C \frac{dU_1}{dt}$$

$$\frac{I_s}{C} dt = \frac{dU_1}{dt} \quad \int dU_1 = \int_0^t \frac{I_s}{C} dt$$

Circuit Example 2

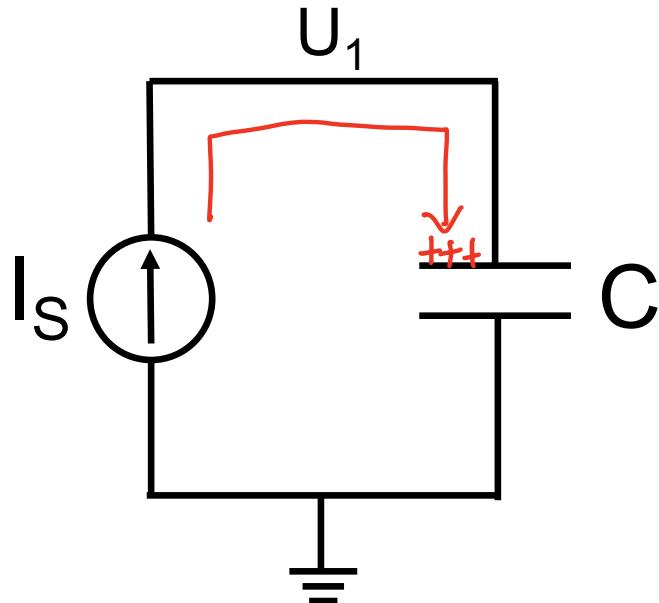At time $t = 0$, $U_1 = U_1(0)$ Volts
Plot U_1 vs. time




$$\int_{U_1(0)}^{U_1(t)} dU_1 = \int_0^t \frac{I_s}{C} dt$$

$$U_1 \Big|_{U_1(0)}^{U_1(t)} = \frac{I_s}{C} t \Big|_0^t$$

$$U_1(t) - U_1(0) = \frac{I_s}{C} t - I_s(0)$$


$$U_1(0) = 0$$

$$U_1(t) = \frac{I_s}{C} t$$

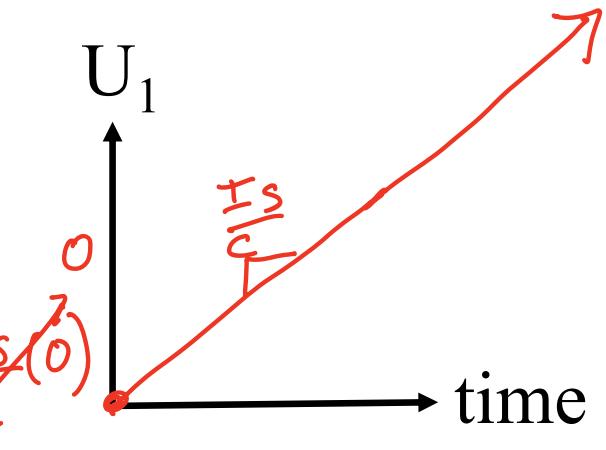

Circuit Example 3

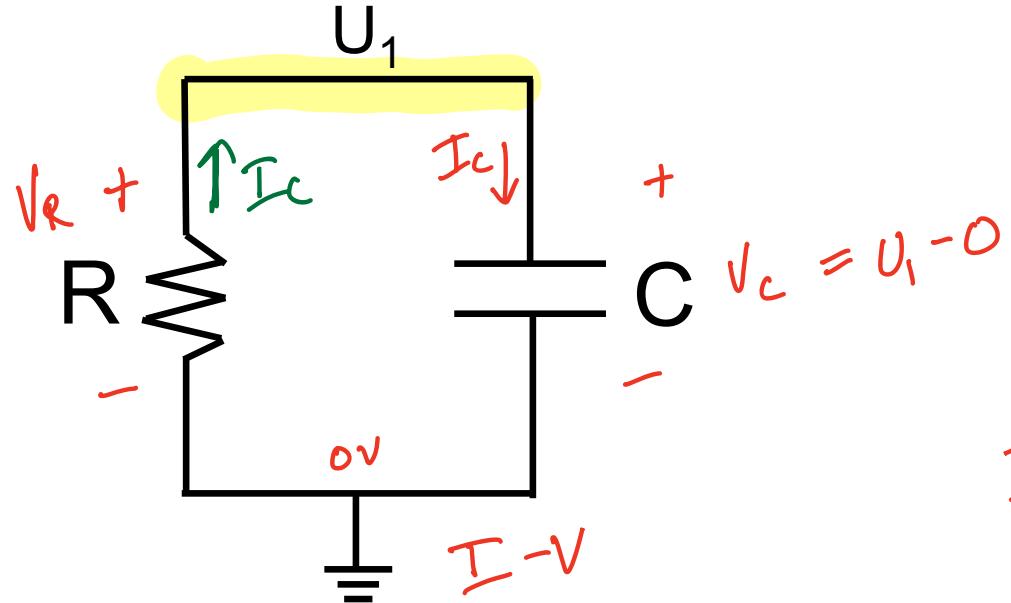*What is the steady-state potential U_1 ?
waited forever



$$KVL: V_c = U_1$$

$$\begin{aligned} KCL: \quad &I_R + I_c = 0 \\ &\underline{I_R} = -\underline{I_c} \end{aligned}$$

Unknowns: U_1, I_c

I-V relations:

$$V_R = I_R R$$

$$V_R = U_1 - 0$$

$$V_R = -I_c R$$

$$\textcircled{1} * U_1 = -I_c R$$

$$- \qquad \qquad \qquad \sqrt{ }$$

$I - V$ relation:

$$\textcircled{2} \quad I_c = C \frac{dV_c}{dt} = C \frac{dU_i}{\cancel{dt}}$$

know U_i doesn't change

$$I_c = 0$$

$$\therefore V_R = 0 \Rightarrow U_i = 0$$

If you have a V_c that doesn't change
there's no current






$$I = C \frac{dV}{dt} \quad Q = CV$$

Equivalent Circuits with Capacitors

*Capacitor – only circuits

$$I_C = C \frac{dV_C}{dt}$$

Capacitive Circuit

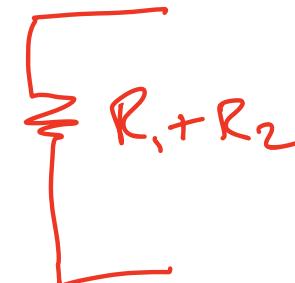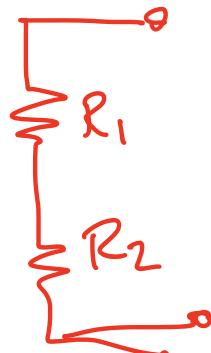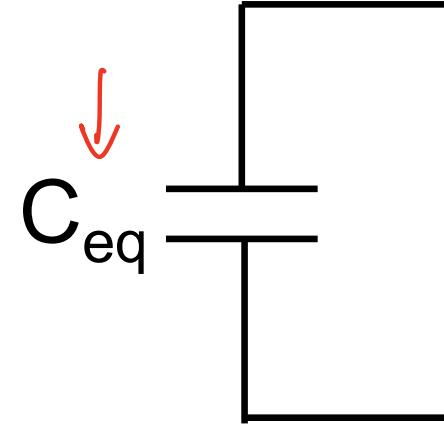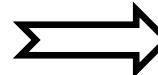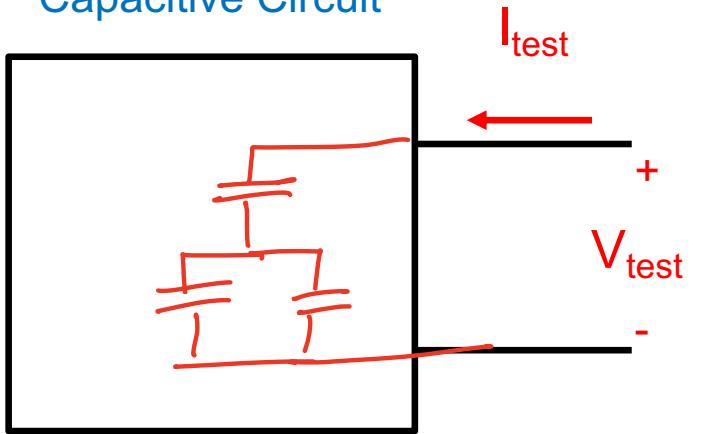



Resistor

$$V = I R$$

$$R = \frac{V}{I}$$

Two Methods

$$I_C = C \frac{dV_C}{dt}$$

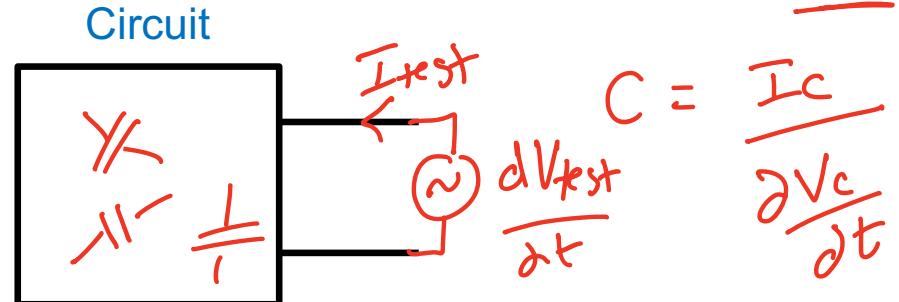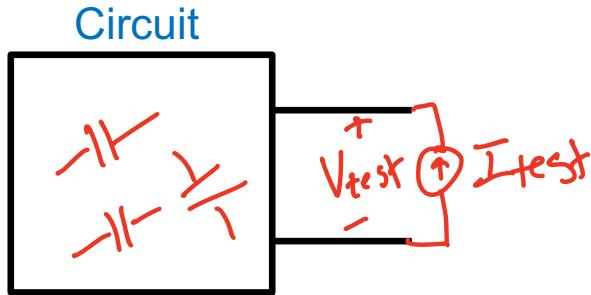

① Method 1:

Apply I_{test}

Measure $\underline{\underline{dV_{\text{test}}/dt}}$


Method 2:

Apply dV_{test}/dt

Measure I_{test}

find: $\underline{\underline{\frac{I_{\text{test}}}{dV_{\text{test}}/dt}}} = C_{\text{eq}}$

Equivalence Example 1

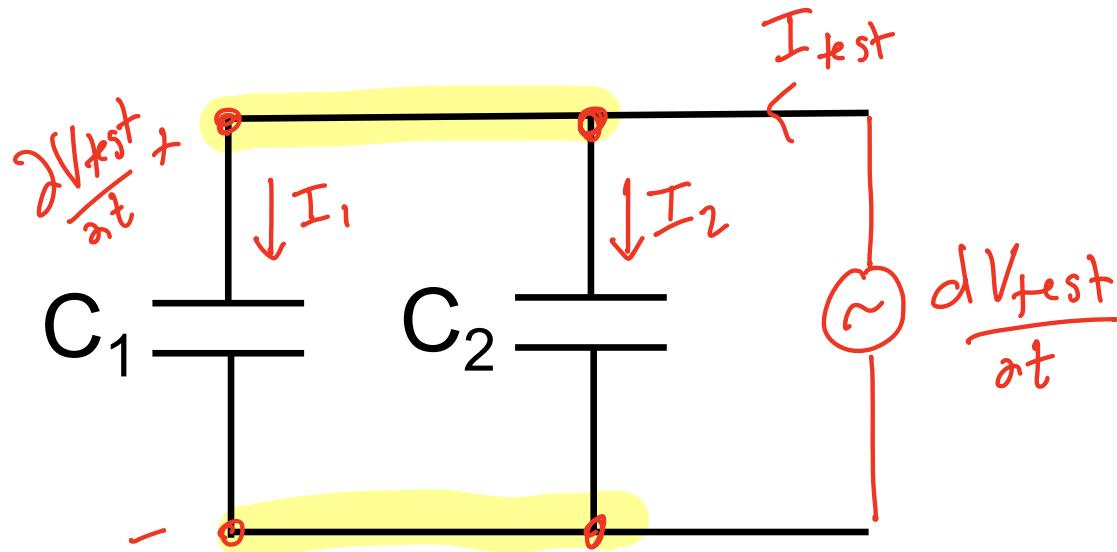

$$I_C = C \frac{dV_C}{dt}$$

$$\text{KCL: } I_{\text{test}} = I_1 + I_2$$

$I - V:$

$$I_1 = C_1 \frac{dV_{\text{test}}}{dt}$$


$$I_2 = C_2 \frac{dV_{\text{test}}}{dt}$$

② Method 2:

Apply dV_{test}/dt

Measure I_{test}

Equivalence Example 1

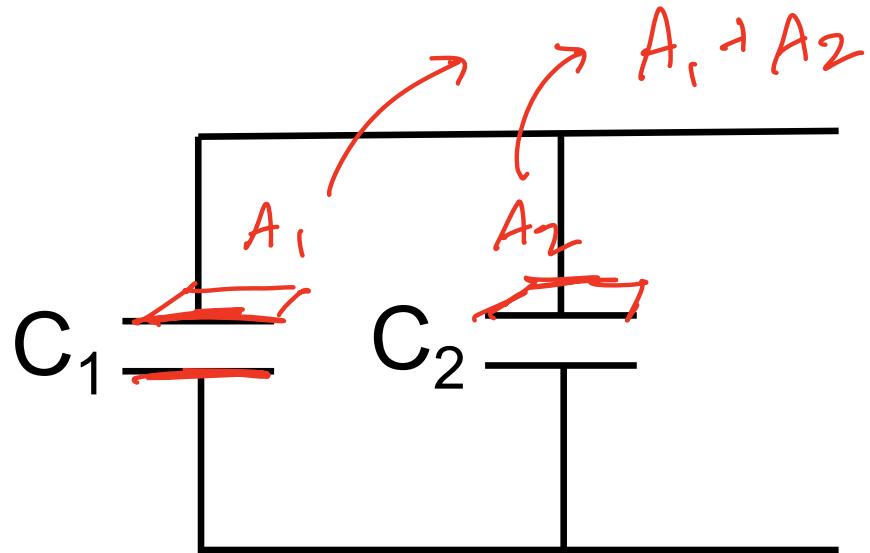

$$I_C = C \frac{dV_C}{dt}$$

$$\begin{aligned} I_{\text{test}} &= I_1 + I_2 \\ &= C_1 \frac{dV_{\text{test}}}{dt} + C_2 \frac{dV_{\text{test}}}{dt} \end{aligned}$$

$$I_{\text{test}} = (C_1 + C_2) \frac{dV_{\text{test}}}{dt}$$


$$\frac{I_{\text{test}}}{dV_{\text{test}}/dt} = C_{\text{eq}} = [C_1 + C_2]$$

Method 2:

Apply dV_{test}/dt

Measure I_{test}

Equivalence Example 2

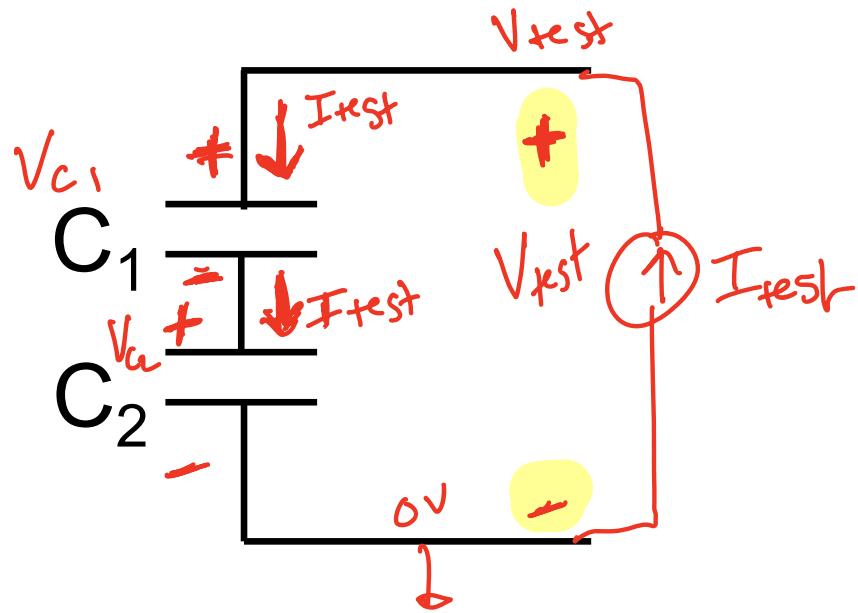

$$I_C = C \frac{dV_C}{dt}$$

$$\text{KVL} : V_{\text{test}} = V_{c1} + V_{c2}$$

$$\frac{\partial}{\partial t} V_{\text{test}} - V_{c1} - V_{c2} = 0$$

$$\textcircled{1} \quad \frac{\partial V_{\text{test}}}{\partial t} = \frac{\partial V_{c1}}{\partial t} + \frac{\partial V_{c2}}{\partial t}$$

$$\underline{I - V}$$

$$\textcircled{2} \quad I_{\text{test}} = C_1 \frac{\partial V_{c1}}{\partial t} = C_2 \frac{\partial V_{c2}}{\partial t}$$

$$\frac{\partial V_{c1}}{\partial t} = \frac{I_{\text{test}}}{C_1}$$


$$\frac{\partial V_{c2}}{\partial t} = \frac{I_{\text{test}}}{C_2}$$

① Method 1:

Apply I_{test}

Measure dV_{test}/dt

Equivalence Example 2

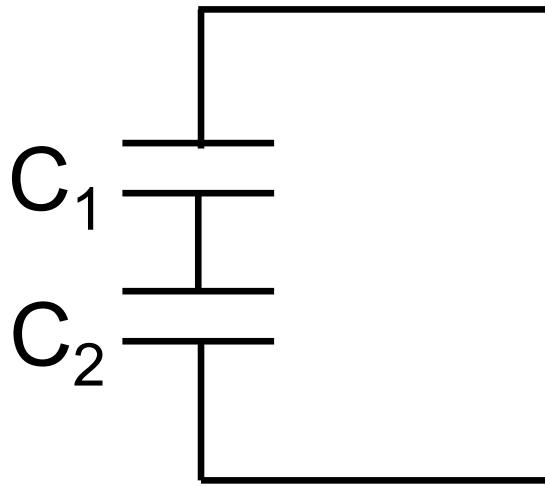

$$\frac{\partial V_{\text{test}}}{\partial t} = \frac{\partial V_{C_1}}{\partial t} + \frac{\partial V_{C_2}}{\partial t}$$

$$\frac{\partial V_{\text{test}}}{\partial t} = \frac{I_{\text{test}}}{C_1} + \frac{I_{\text{test}}}{C_2}$$

$$* C_{\text{eq}} = \frac{I_{\text{test}}}{\frac{\partial V_{\text{test}}}{\partial t}} = \left[\frac{1}{C_1} + \frac{1}{C_2} \right]^{-1}$$


Method 1:
Apply I_{test}
Measure $\frac{dV_{\text{test}}}{dt}$

$$\frac{\partial V_{\text{test}}}{\partial t} = I_{\text{test}} \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$


$$I_C = C \frac{dV_C}{dt}$$

Equivalent Capacitors Summary

Capacitors in Series

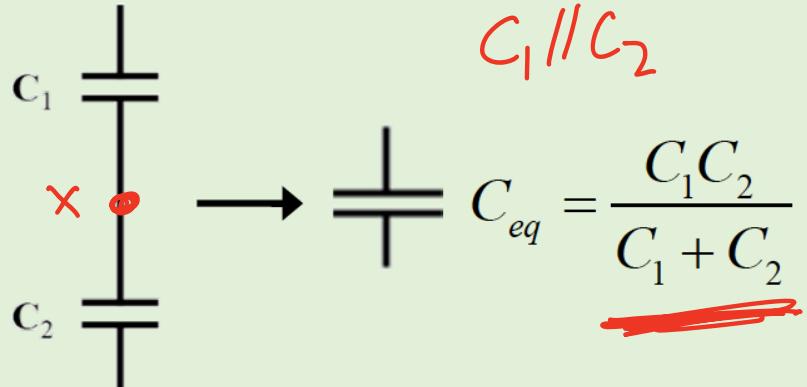


Capacitors in Parallel

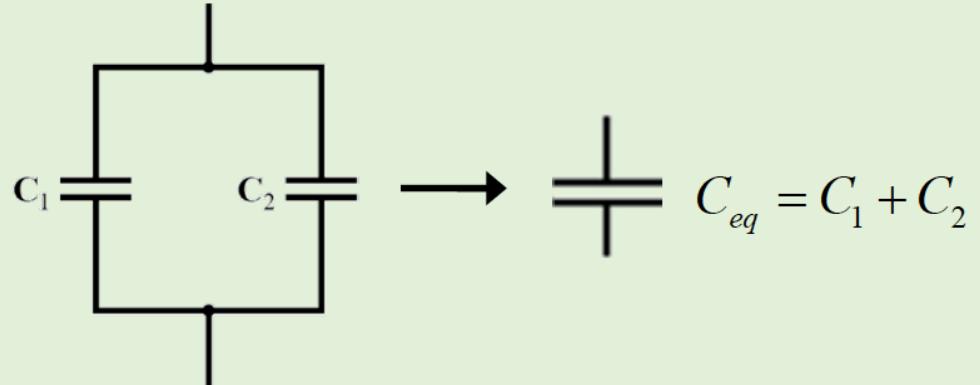


$$\frac{R_1 R_2}{R_1 + R_2}$$

R₁ // R₂

$$R_{eq} = R_1 + R_2$$

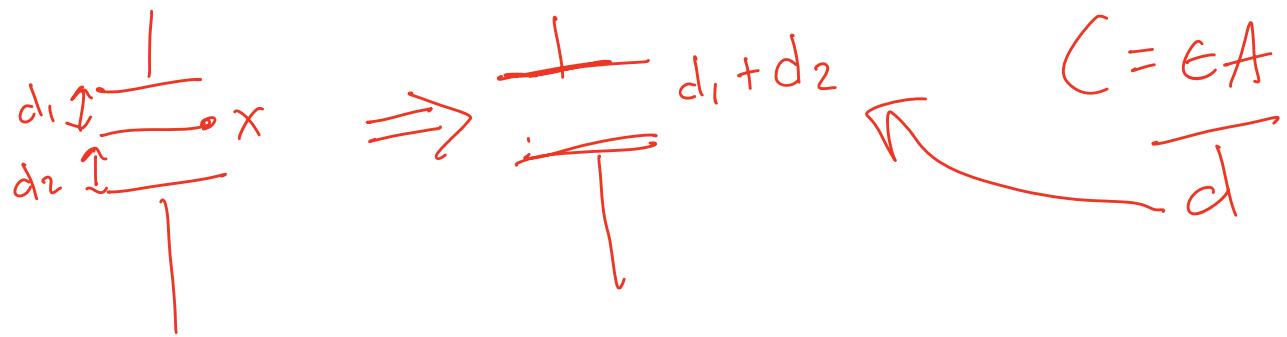


Capacitive Touchscreens

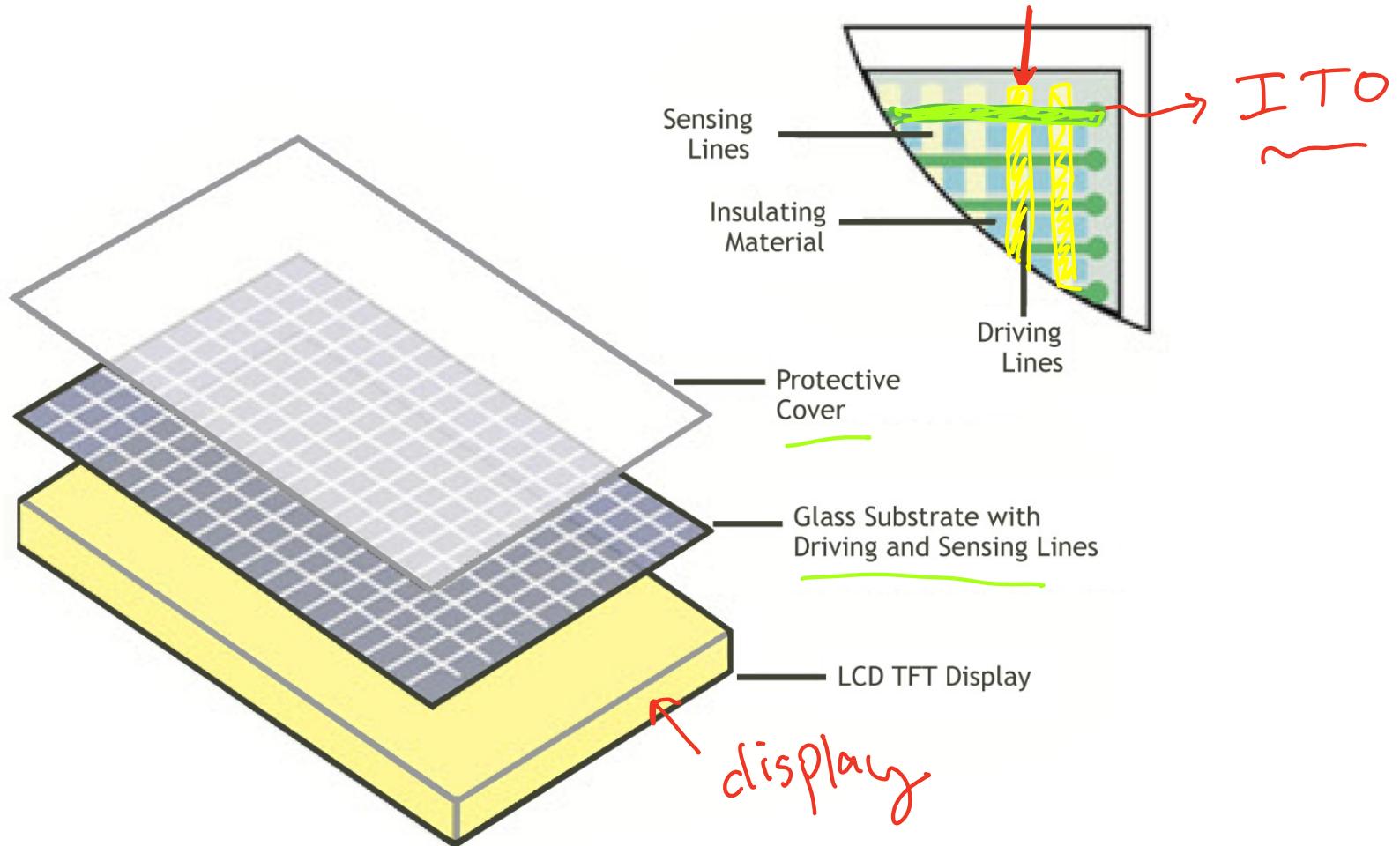

Capacitive Touchscreen – Model without Touch

$$C = \frac{\epsilon A}{d}$$

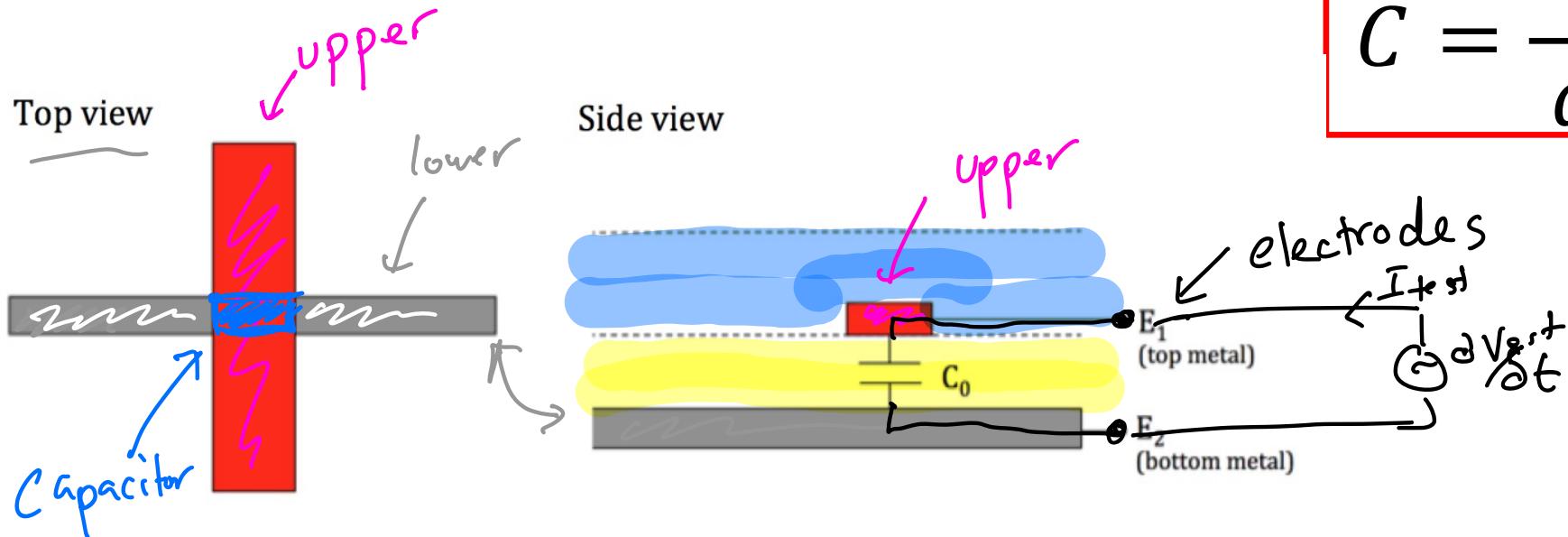


Capacitive Touchscreen – Model with Touch

$$* C = \frac{\epsilon A}{d}$$



Side view

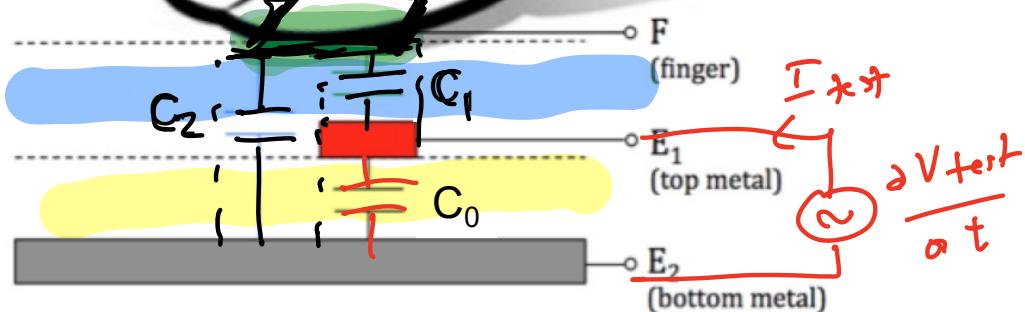


The finger forms a capacitor!


the measurement will change with a finger!

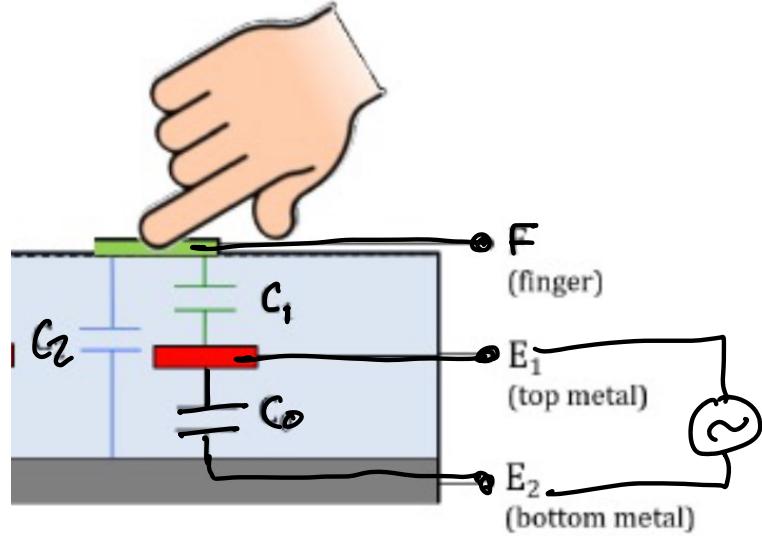* Problem: One of the terminals is a finger?!?



Capacitive Touchscreen – Model with Touch





No touch

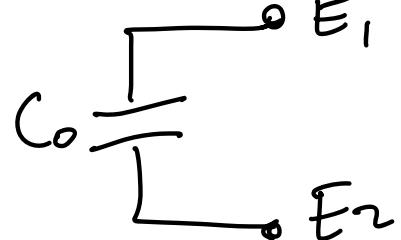

with touch

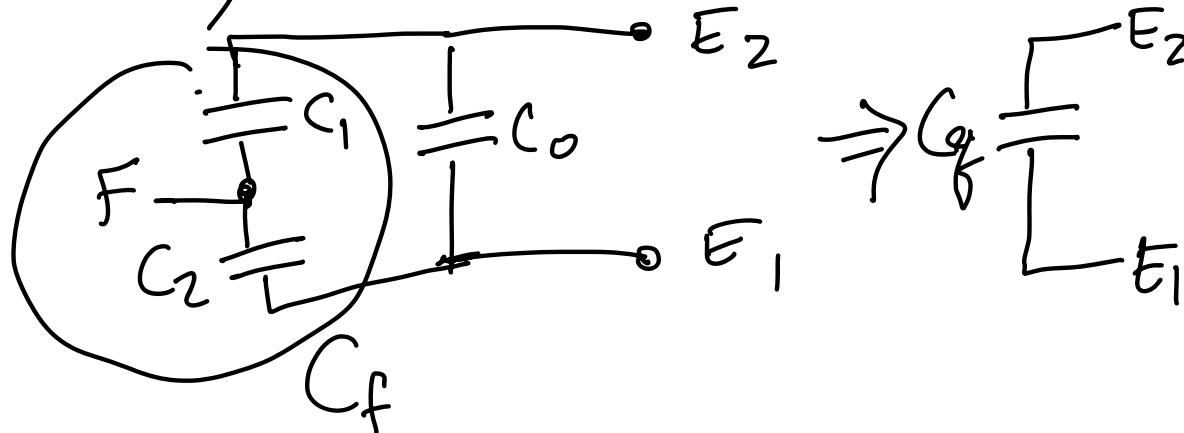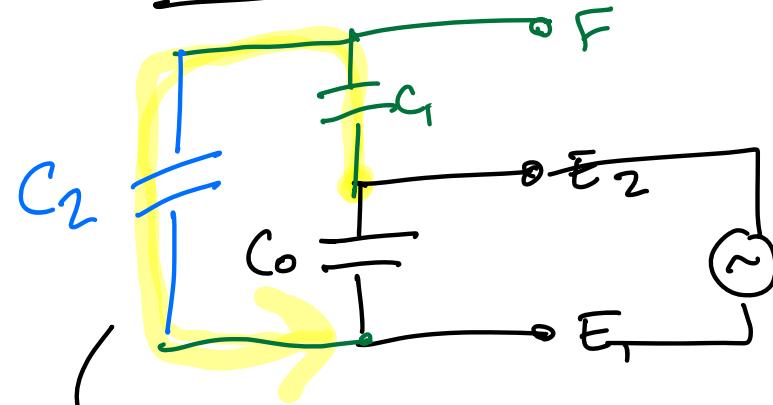

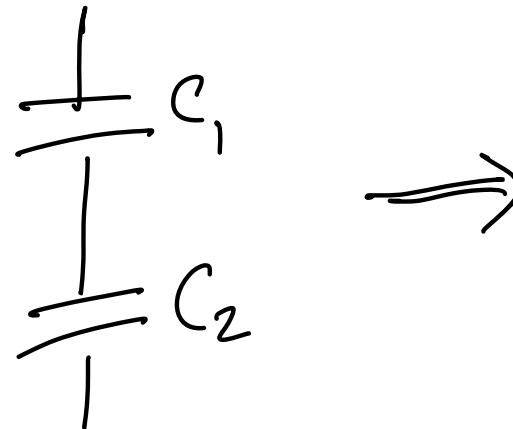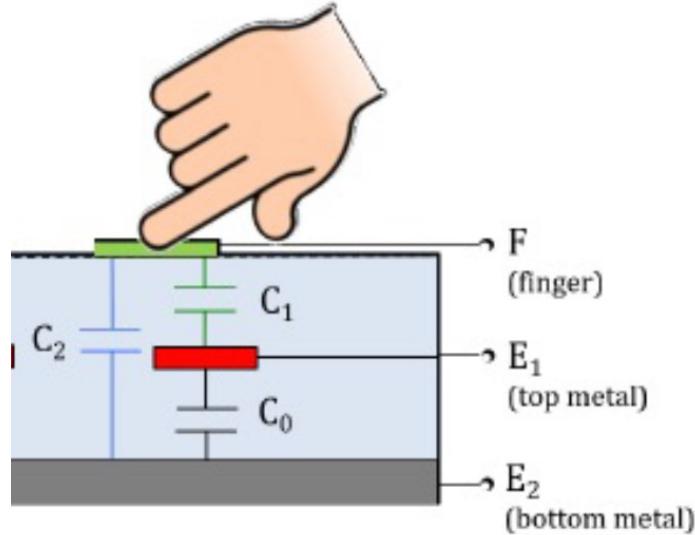Capacitive Touchscreen – Model with Touch



$$\frac{C_1 C_2}{C_1 + C_2} = C_f$$

w/finger
extra cap

