



EECS 16A

Spring 2023 - Profs. Muller & Waller
Lecture 9B – Op Amps & Negative Feedback

Toolbox

KVL: Voltage drops around a loop sum to 0

KCL: All currents coming out of a node sum to 0

$$V = IR$$


$$P = IV$$

$$R = \frac{\rho L}{A}$$

$V_{\text{source}}(\text{off}) \rightarrow \text{short}$


$I_{\text{source}}(\text{off}) \rightarrow \text{open}$

Thevenin Equivalent Circuit

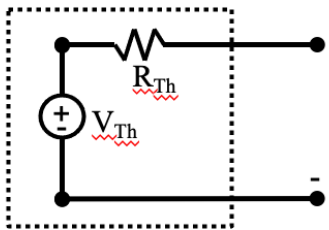



Measure V
with open

Norton Equivalent Circuit

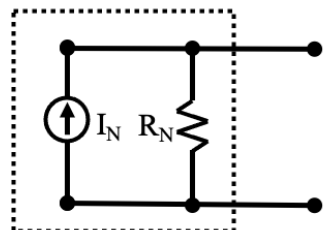

Measure I
with short
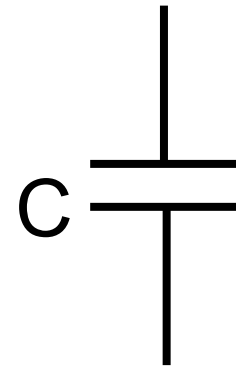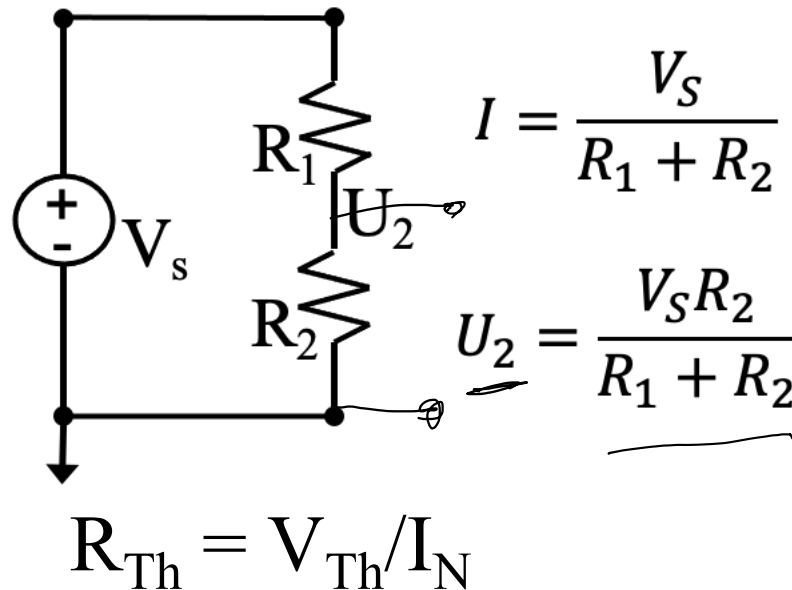
$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$




$$Q = CV$$


$$I = C \frac{dV}{dt}$$

$$C = \frac{\epsilon A}{d}$$


Capacitors in Series

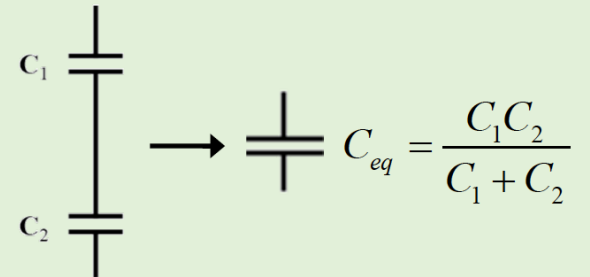

Capacitors in Parallel

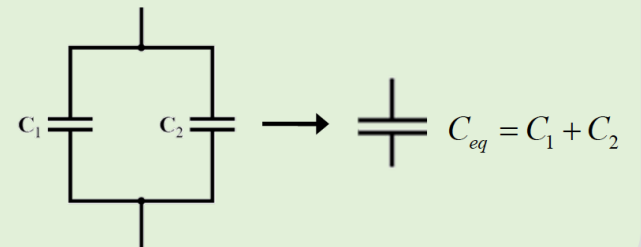


Last Time: Comparators!

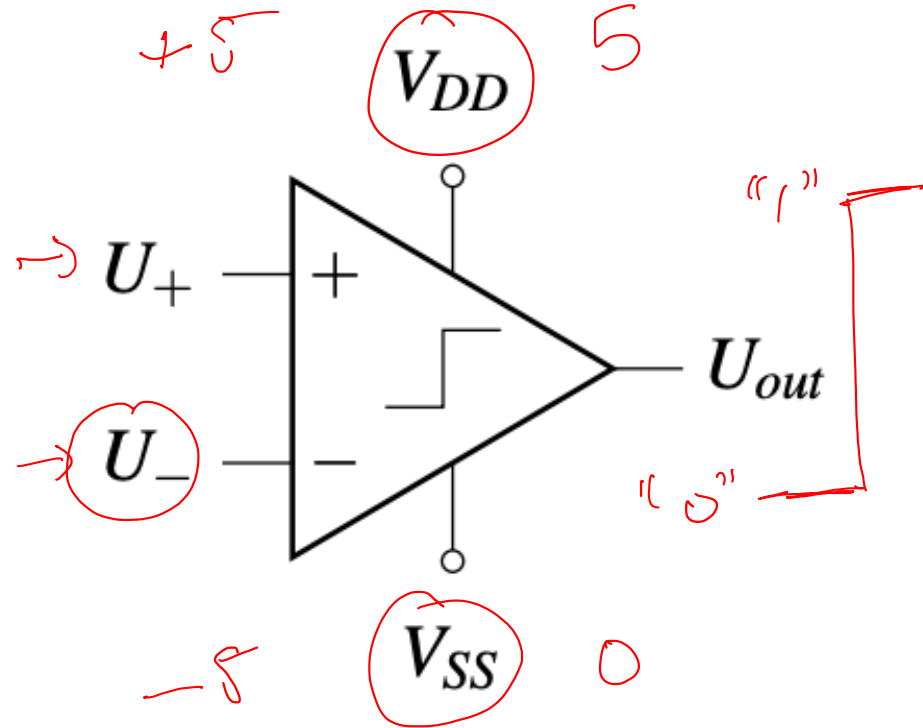





Comparators compare two values (inputs):

$$U_+ > U_- \rightarrow U_{out} = \text{"1"} \Rightarrow V_{DD}$$
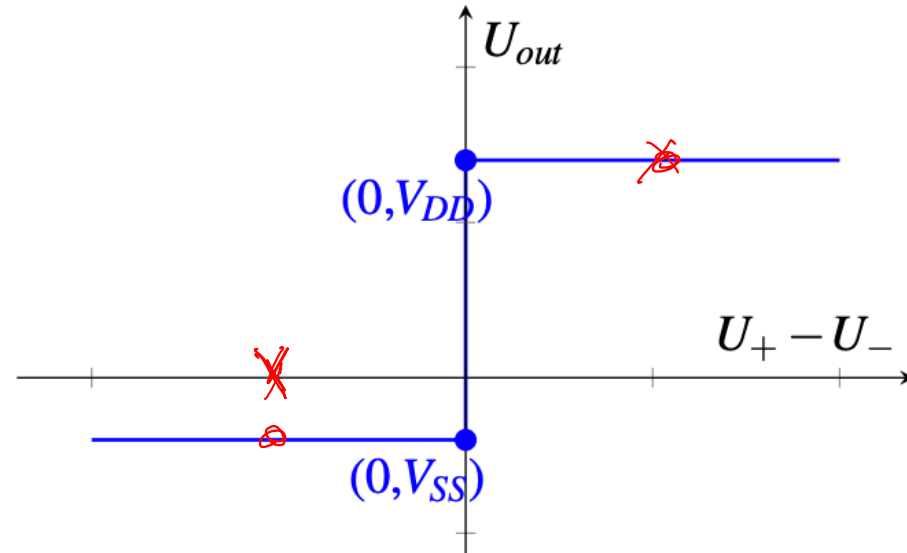
$$U_+ < U_- \rightarrow U_{out} = \text{"0"} \Rightarrow V_{SS}$$





New Elements with 2 Inputs and 2 Outputs

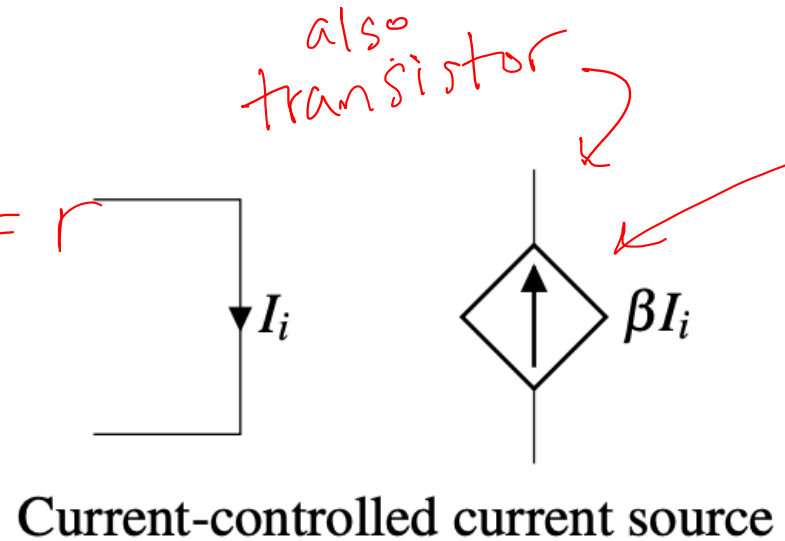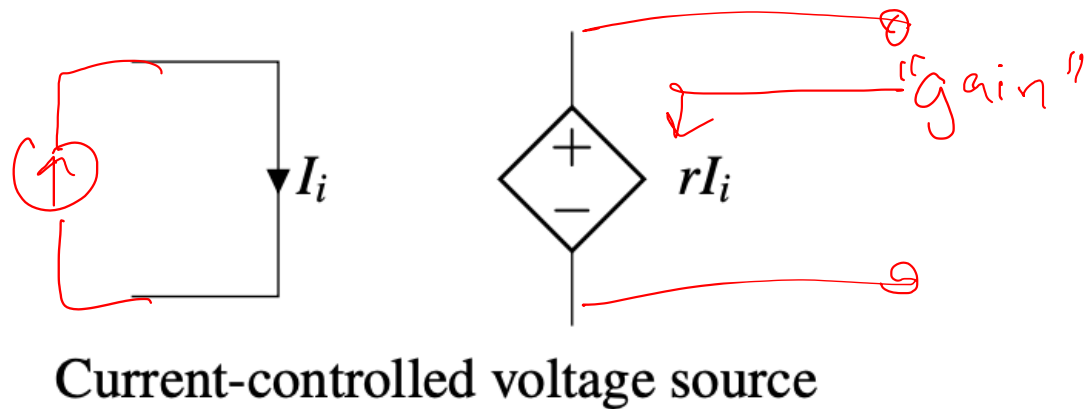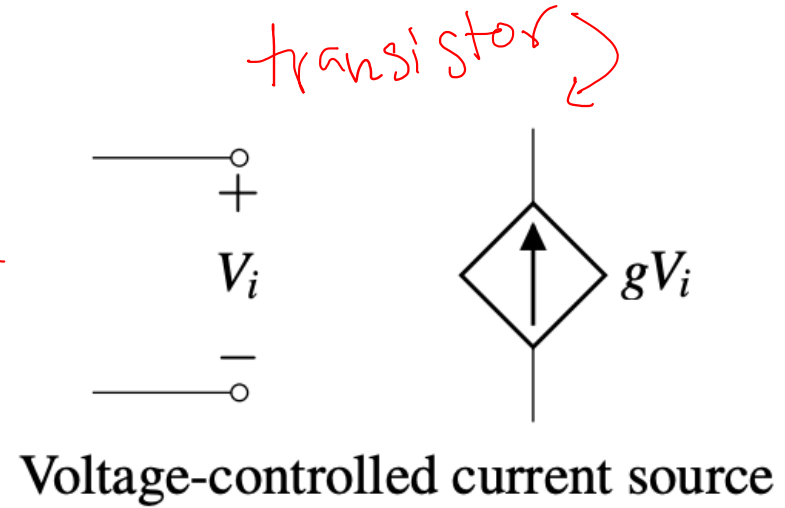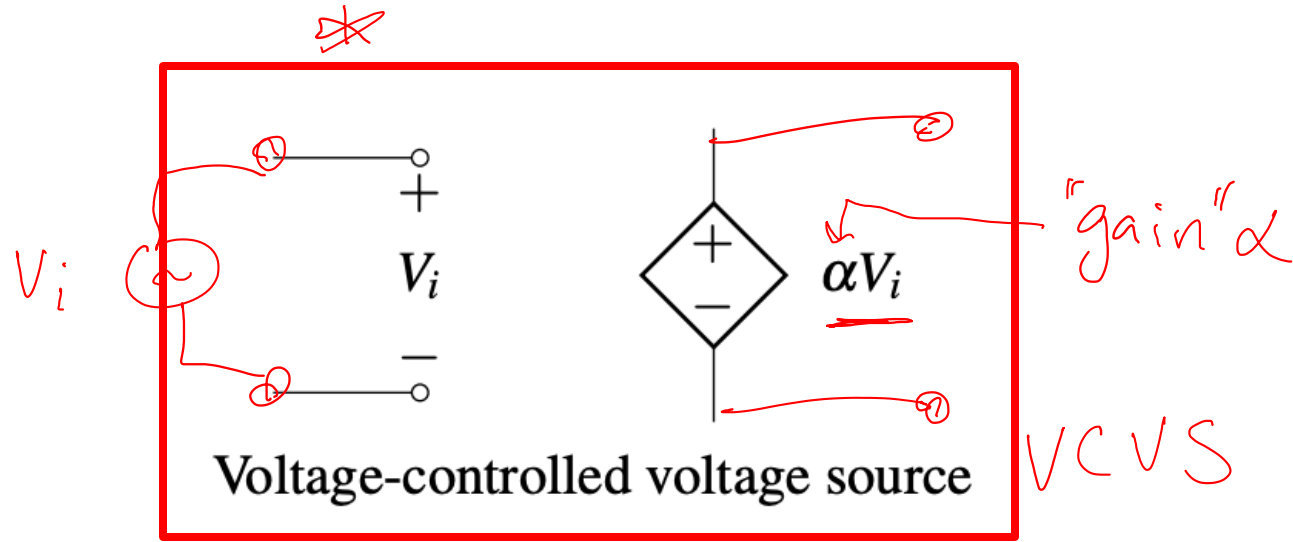

dependent sources



CCVS

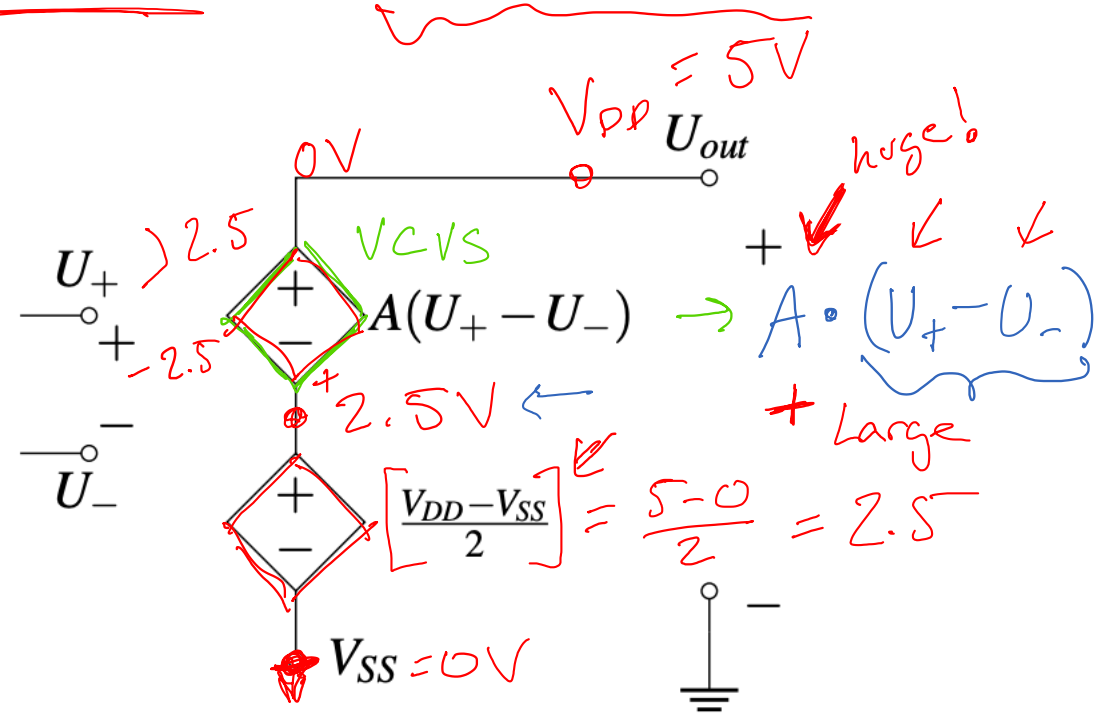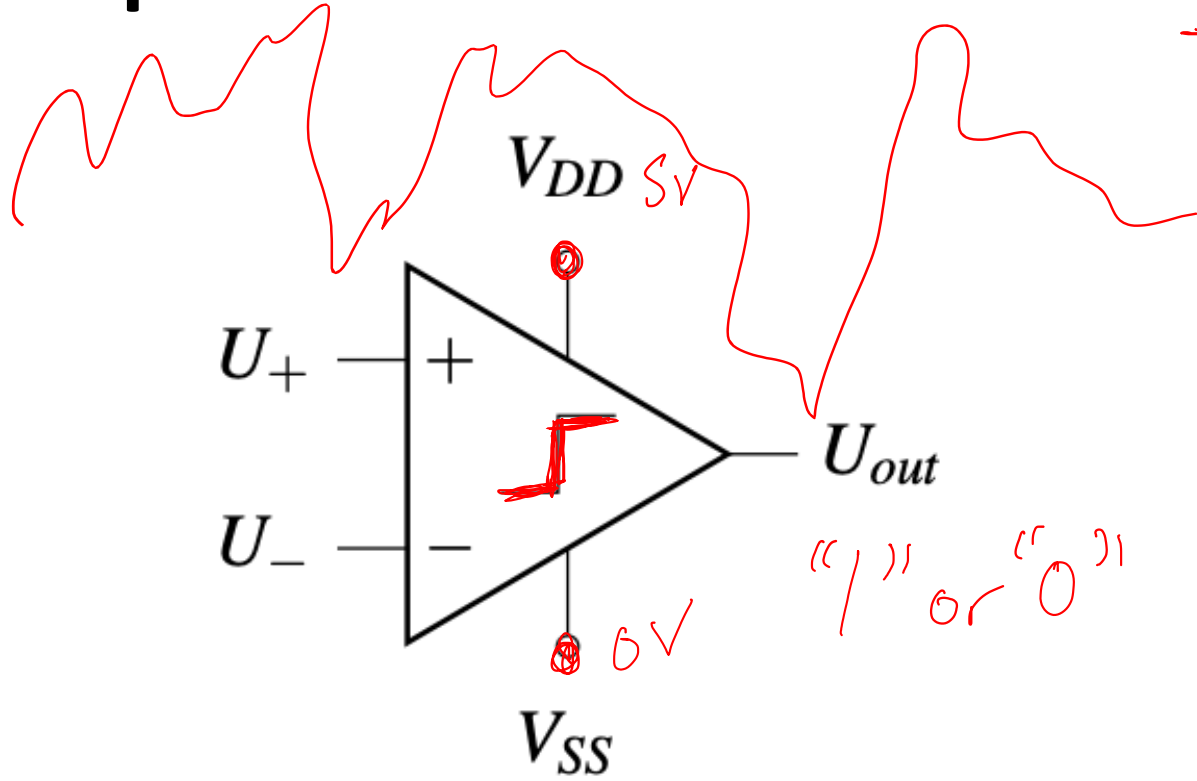Comparator Model – converts analog to 1-bit digital!




What's analog?

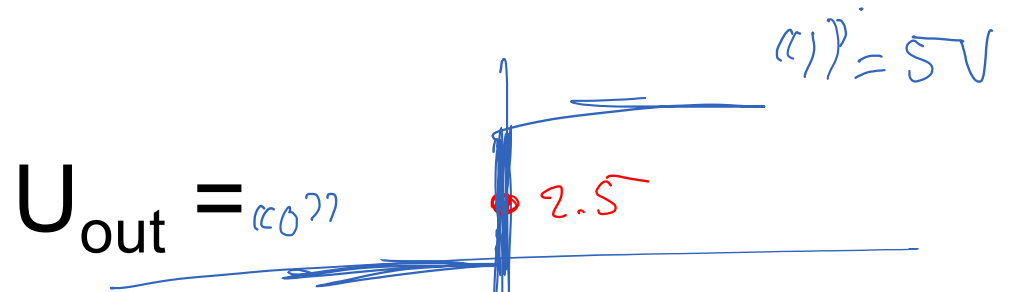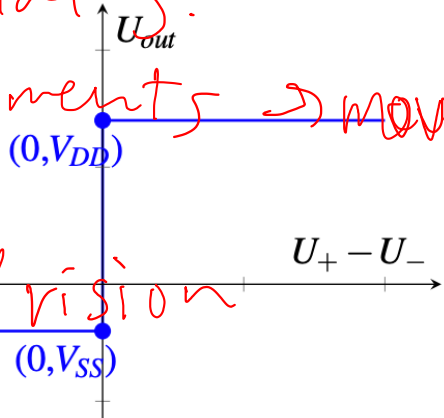- measurements → movement
- sound
- light/vision
- time





A is large in comparators!

From Last Lecture: How to Read Out Touch

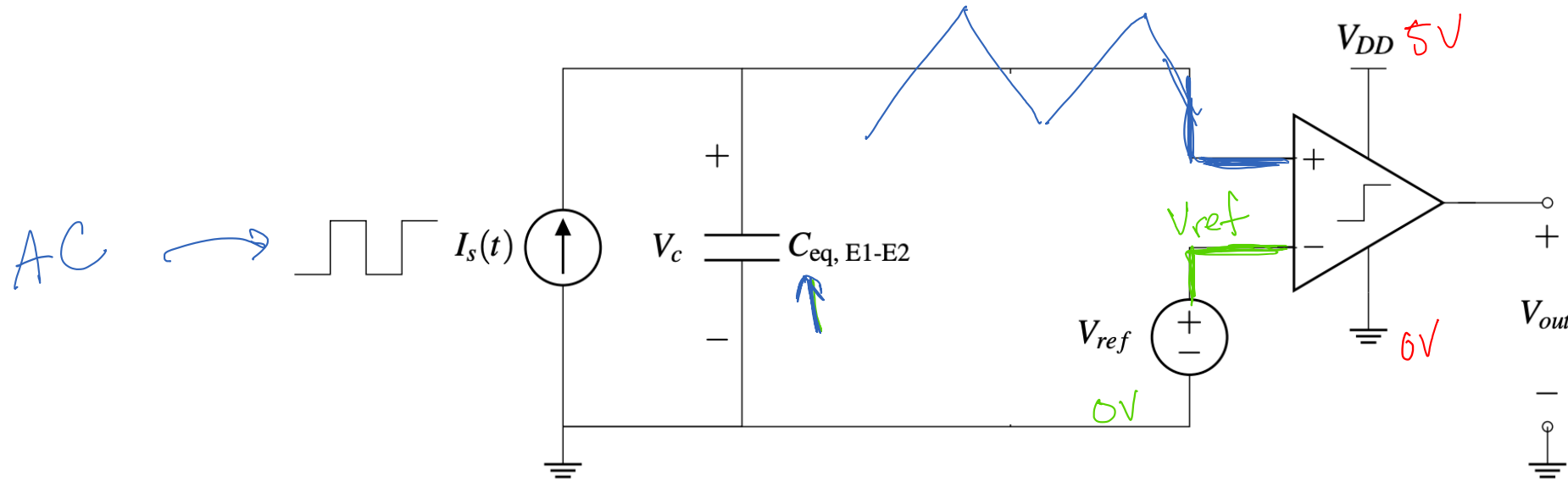

$V_{out} = 2.5 + A(U_+ - U_-)$


$V_{out} = 2.5 + A(V_c - V_{ref})$

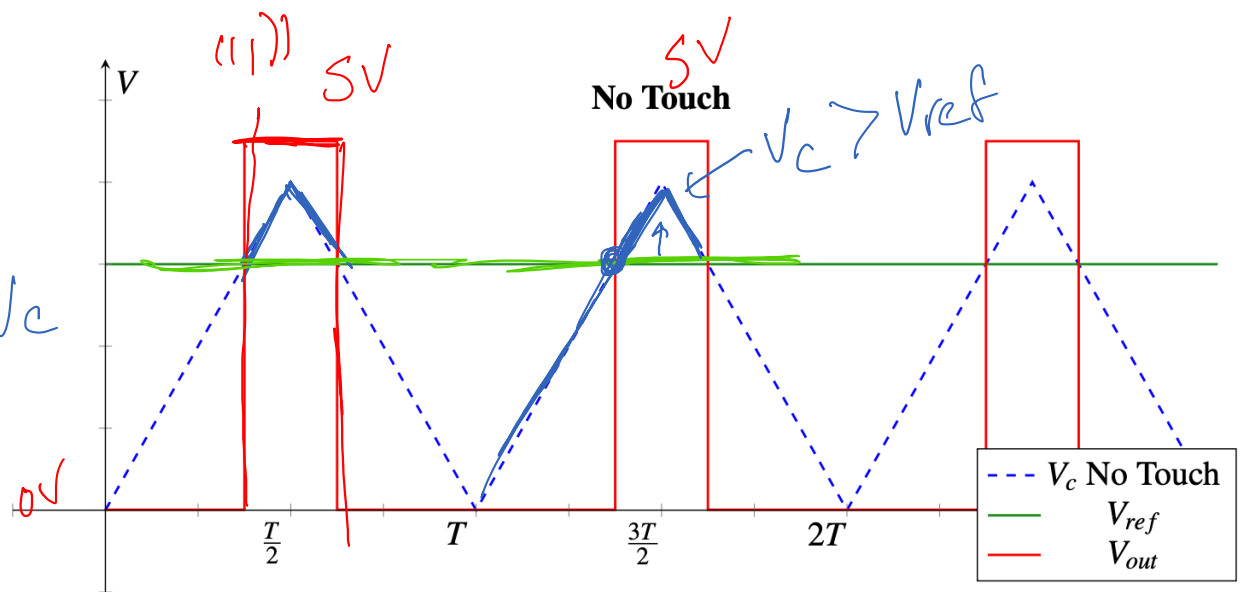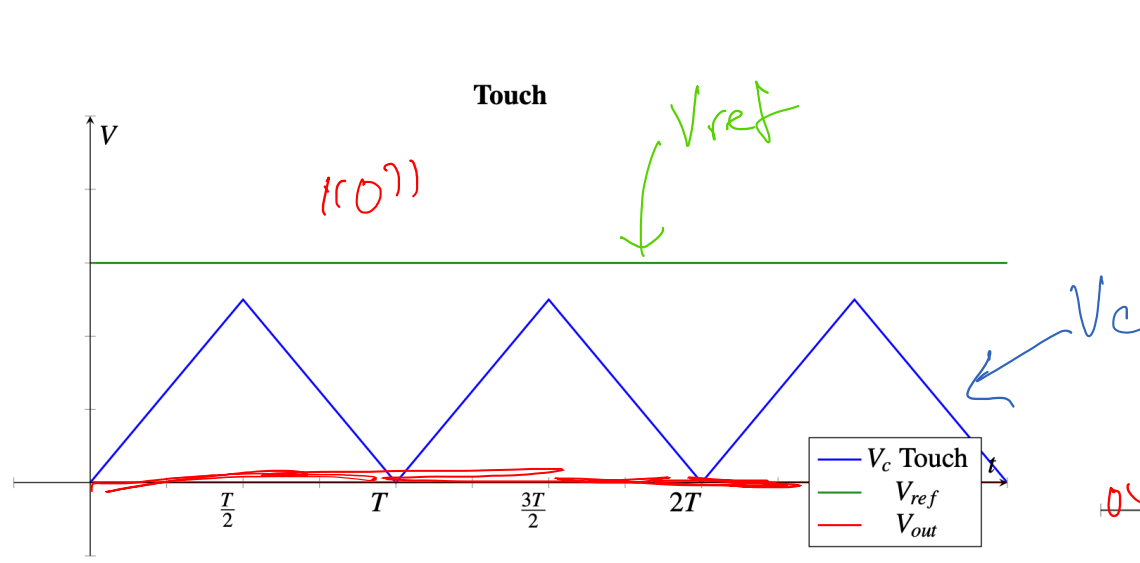

Operational Amplifier – Same Model!



(Different circuit – optimized for analog output)

→ amplify! → loading effects

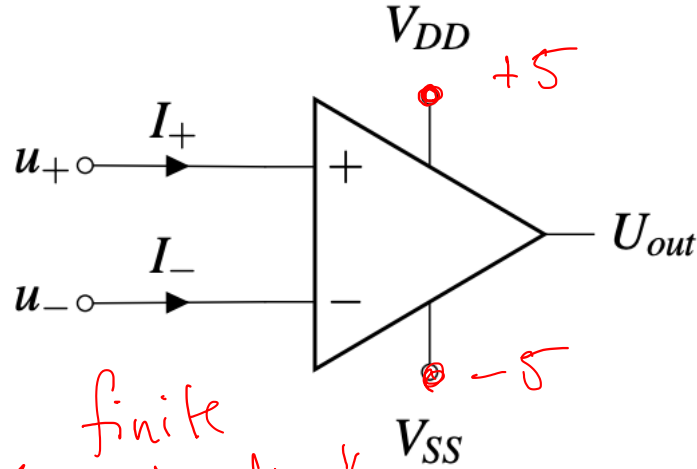

finite "bandwidth"



$$\frac{V_{DD} - V_{SS}}{2} = 5$$

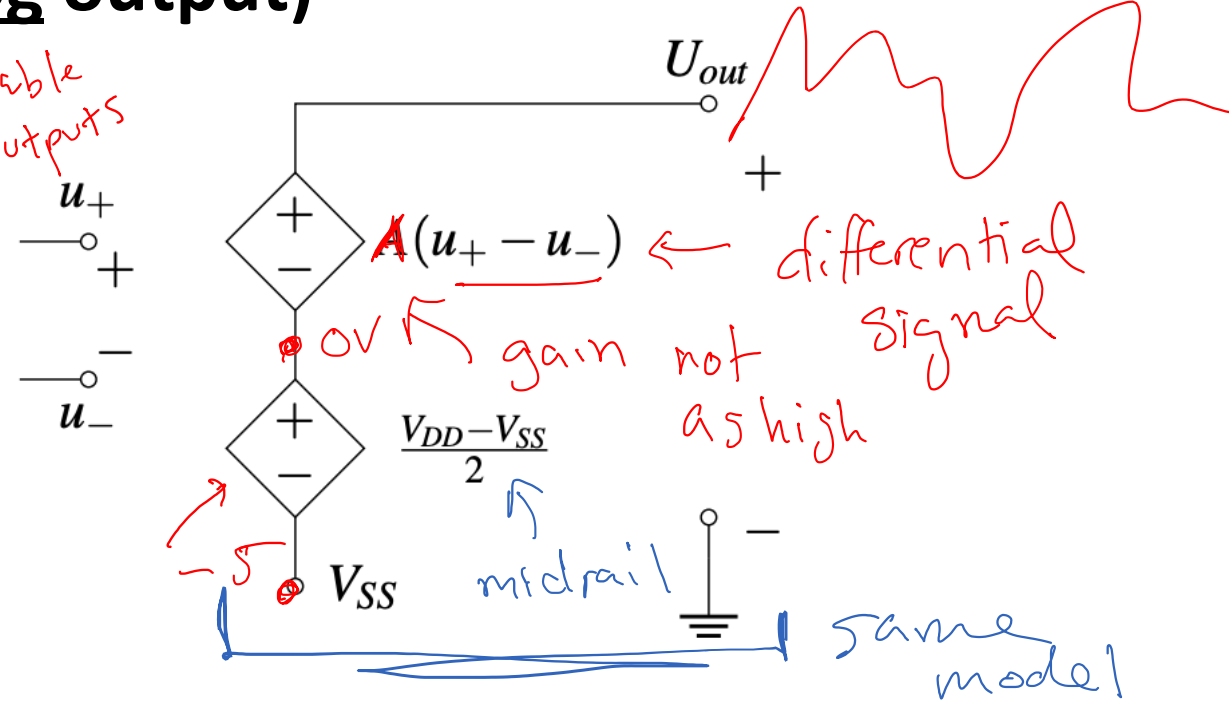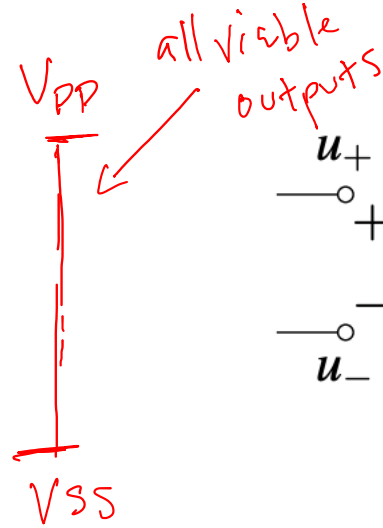

same model

If $V_{DD} = V_{SS}$ we can simplify! *←*

~~X~~

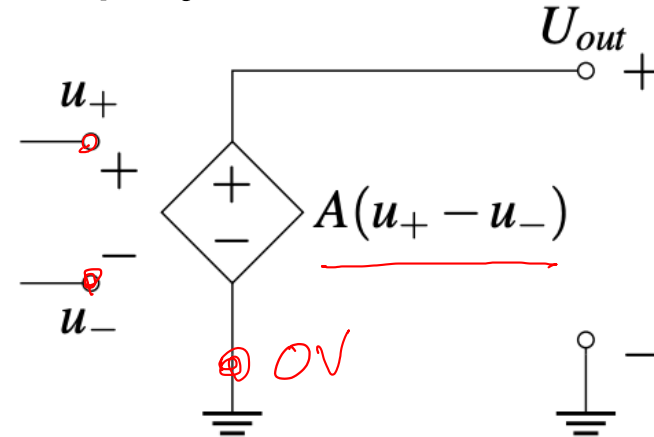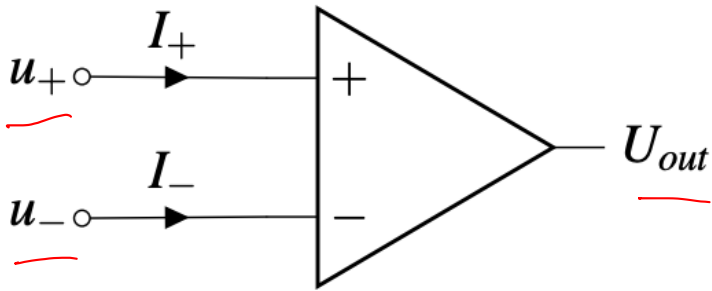


I got an internship at Bose this summer!

*First assignment: Design a circuit to play music – LOUD!

Music is analog!

Music is stored as digital

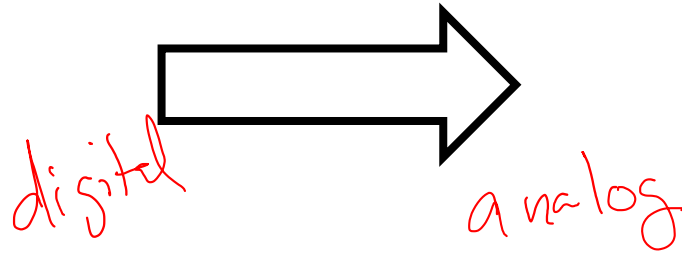



Music is analog!




Need to convert digital to analog?

Speaker takes 0 – 10 V


DAC: Digital to Analog Converter

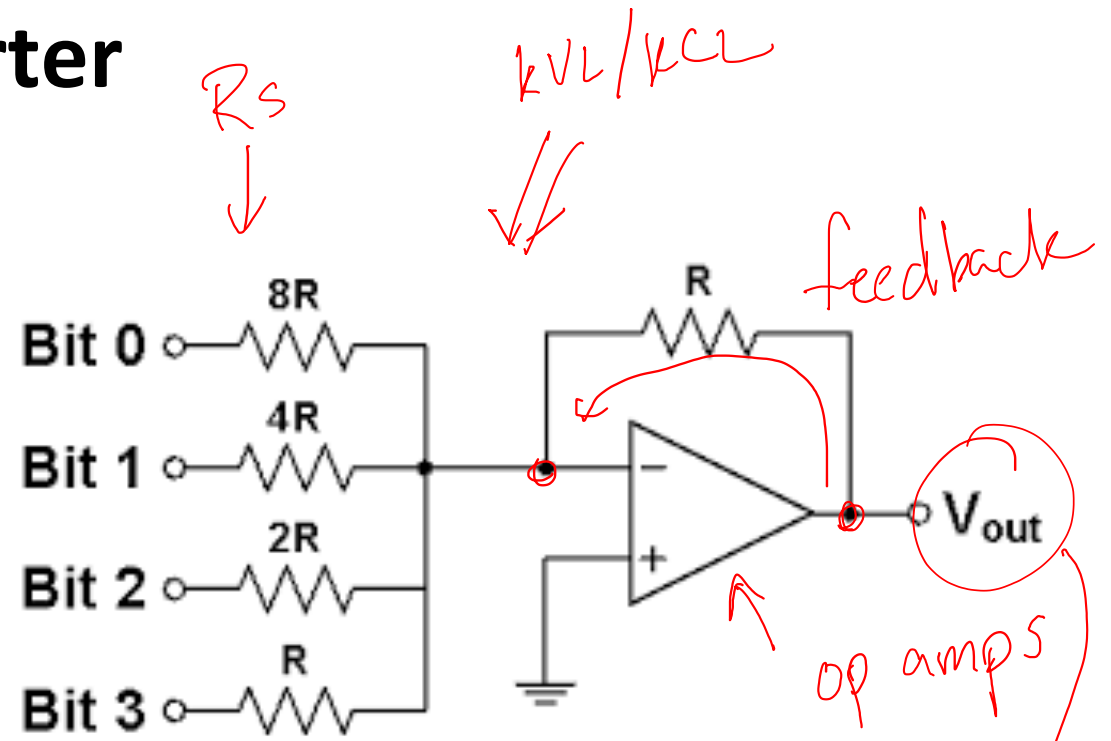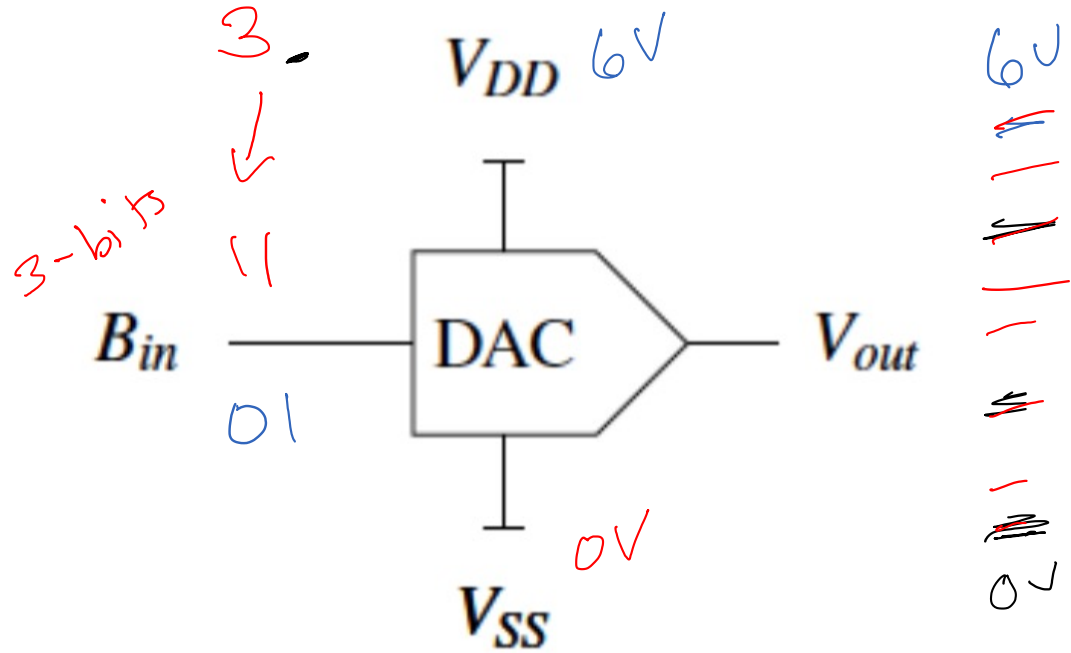

binary 1-bit

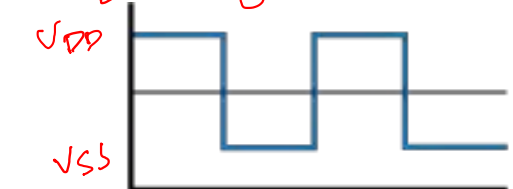


1-bit

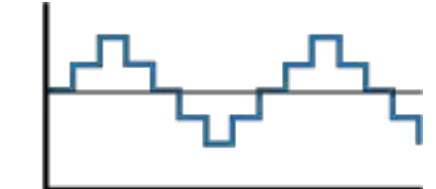


2-bit → 4 levels

sine wave

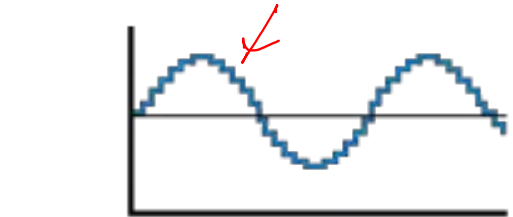

4-bit

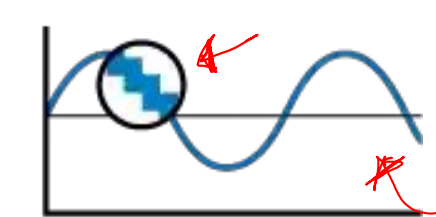


16-bit

| Decimal Number | Equivalent Binary Number | Decimal Number | Equivalent Binary Number |
|----------------|--------------------------|----------------|--------------------------|
| 0 | 0000 | 8 | 1000 |
| 1 | 0001 | 9 | 1001 |
| 2 | 0010 | 10 | 1010 |
| 3 | 0011 | 11 | 1011 |
| 4 | 0100 | 12 | 1100 |
| 5 | 0101 | 13 | 1101 |
| 6 | 0110 | 14 | 1110 |
| 7 | 0111 | 15 | 1111 |



16 Bit/44.1 kHz

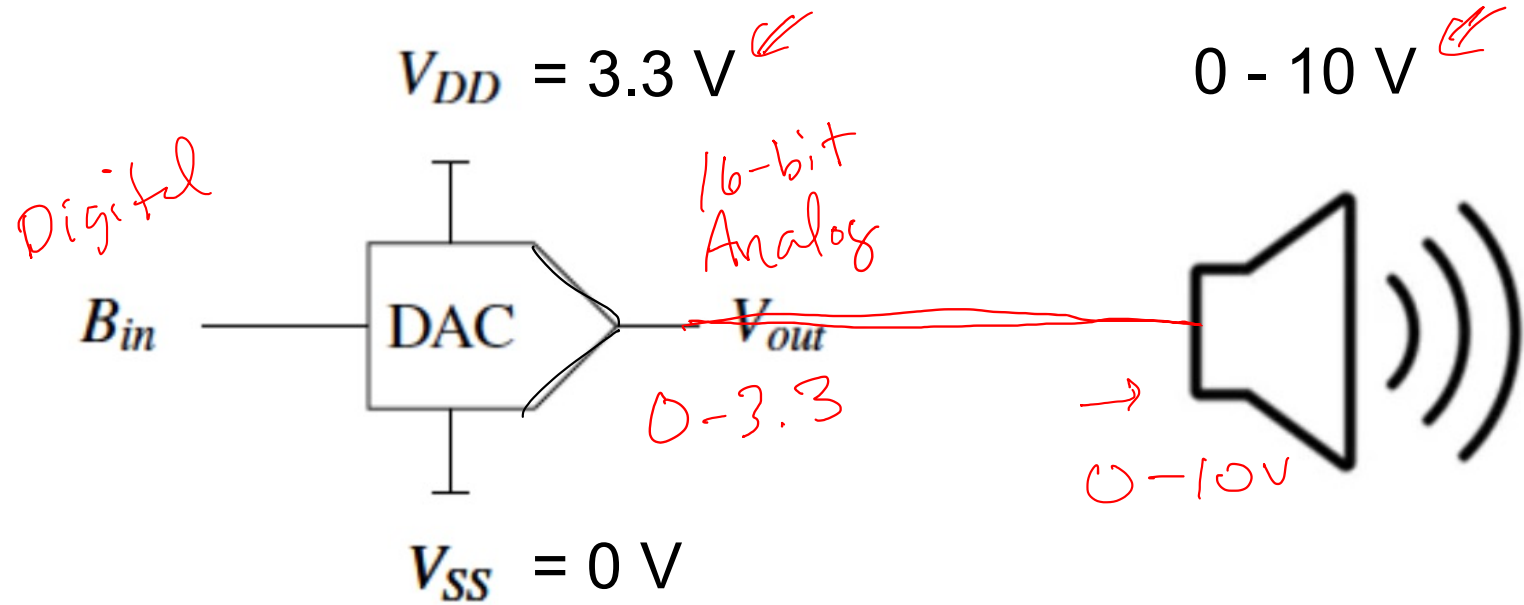Can We Connect the DAC Directly to a Speaker?




$$V_{\text{speaker}} = V_{\text{th}} \cdot \frac{R_{\text{sp}}}{R_{\text{sp}} + R_{\text{th}}}$$

$$= \frac{V_{\text{th}} \cdot 8}{8 + 10000}$$

$$= V_{\text{th}} \cdot \frac{8}{10008}$$

Thevenin Equivalent Circuit


Thevenin Equivalent Circuit

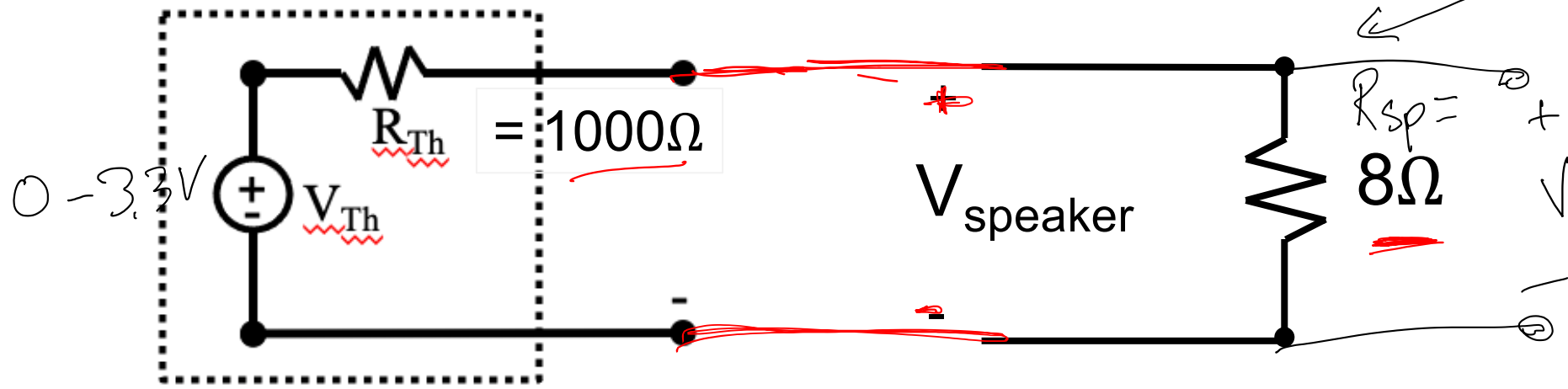


$$V_{\text{speaker}} = V_{\text{th}} \cdot 0.0079$$

$$V_{\text{th, max}} = 3.3\text{ V}$$

Need to Isolate DAC and Speaker!

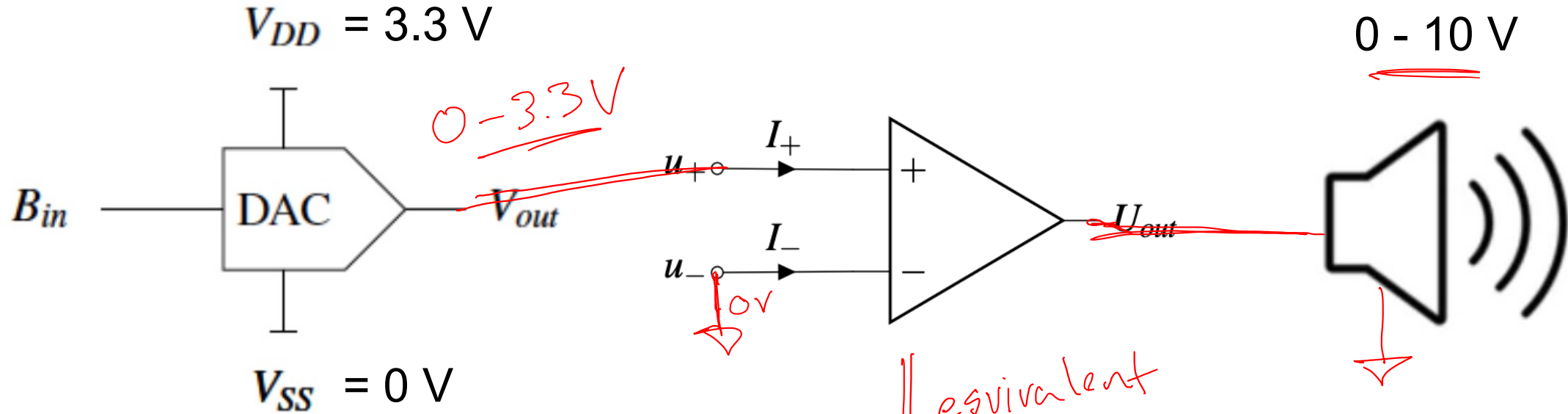


Thevenin Equivalent Circuit

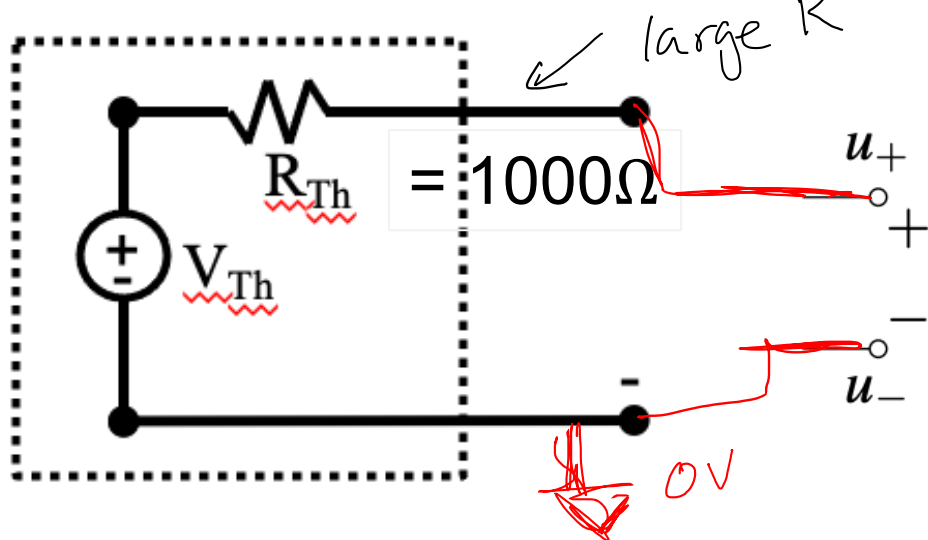


equivalent model

Thevenin Equivalent Circuit

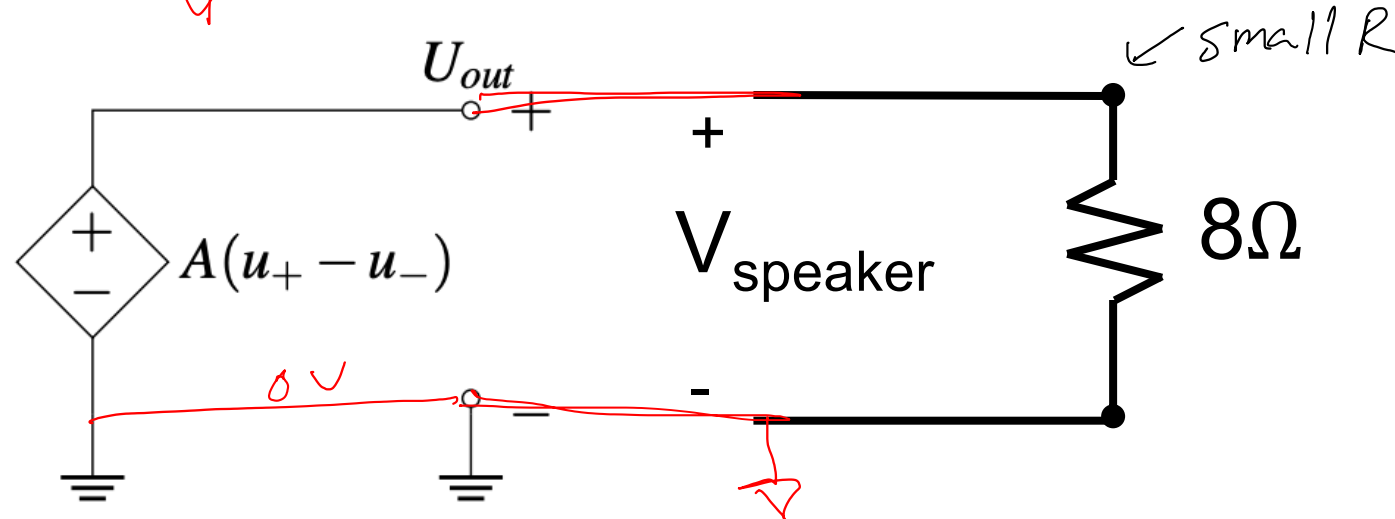

Solve for V_{speaker} !

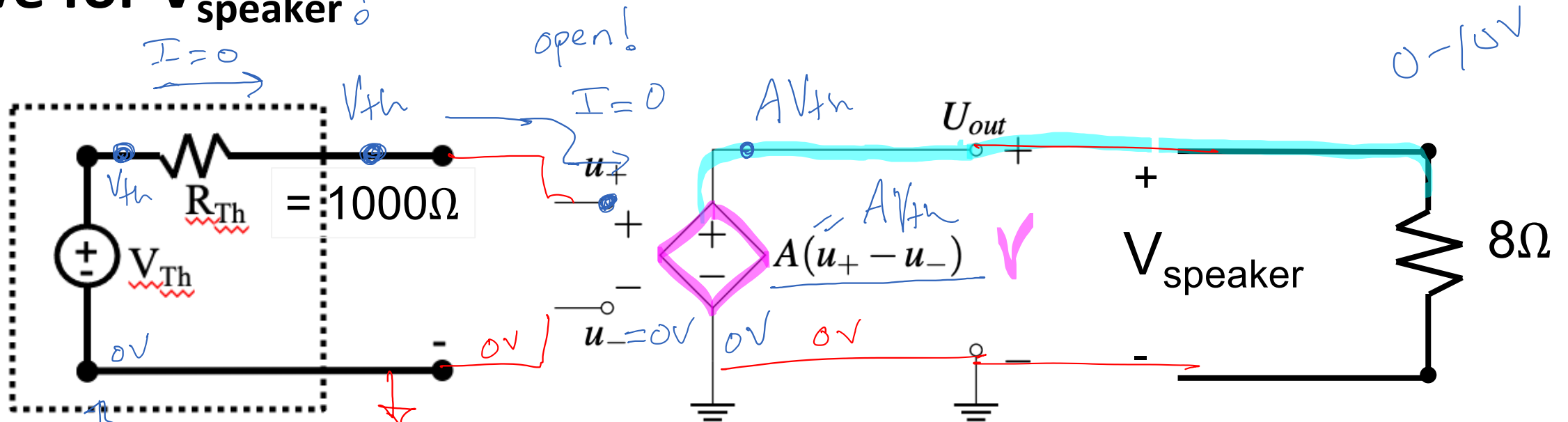

0-3.3


$$u_+ = V_{Th}$$

$$\begin{aligned}
 & A(u_+ - u_-) \\
 &= A(V_{Th} - 0) \\
 &= AV_{Th}
 \end{aligned}$$

$$\begin{aligned}
 V_{\text{speaker}} &= U_{out} \\
 &= [AV_{Th}]
 \end{aligned}$$

* Want $A=3!$ V/V
 ↑ unitless

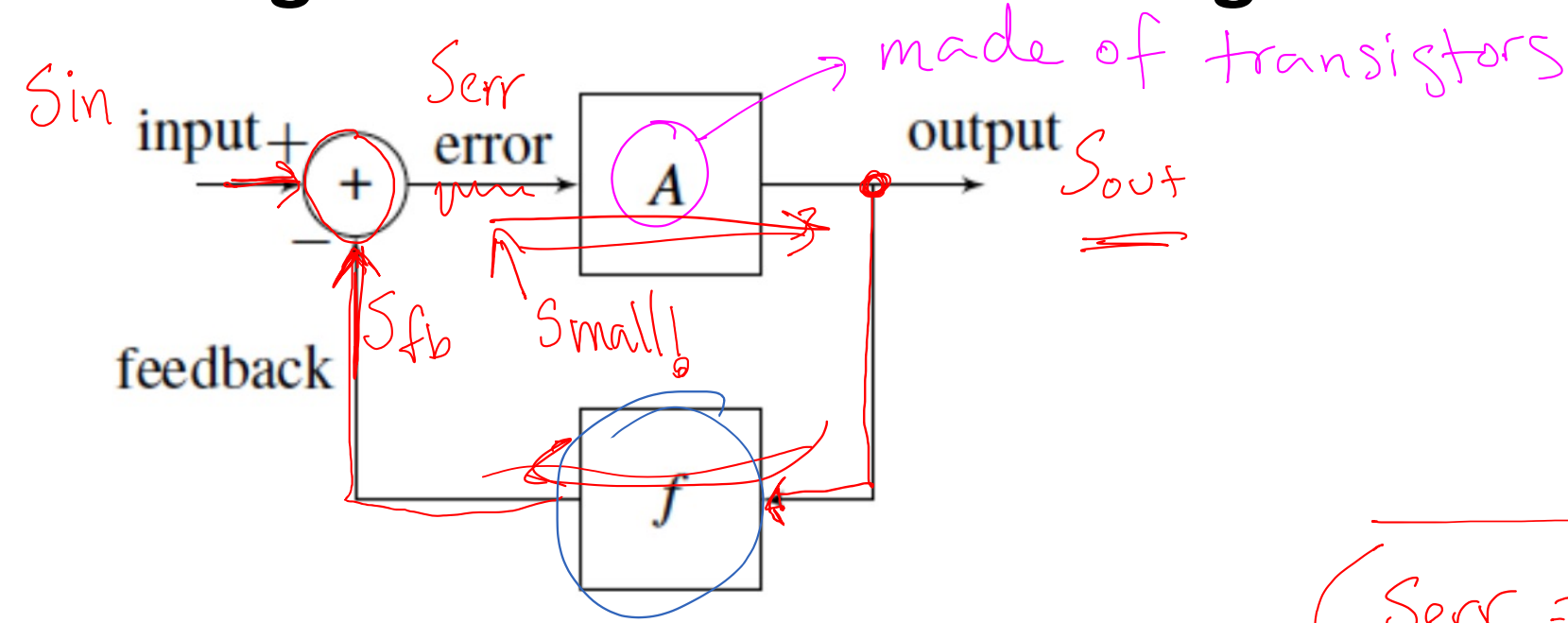Setting a Reliable Gain with Negative Feedback!



transistors are unreliable for gain

S_{nm}

Make small adjustments to correct the output
Basis of Control Theory
Used all the time in circuits!

solve!

$$\begin{cases} S_{err} = S_{in} - S_{fb} \\ S_{out} = A S_{err} \\ S_{fb} = f S_{out} \end{cases}$$

→ What are some examples from daily life?

- thermostat!
- Grades
-

transfer function

$$\frac{S_{out}}{S_{in}} = \frac{A}{1 + Af}$$


Setting a Reliable Gain with Negative Feedback!

Black's formula

$$\frac{S_{out}}{S_{in}} = \frac{A}{1 + Af}$$

Describes the input-output relationship:
*The Transfer Function
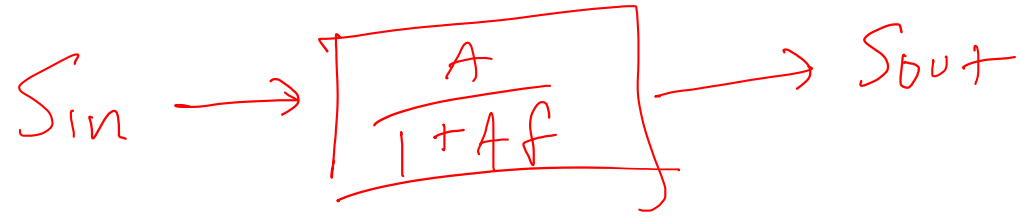
$$S_{out} = \left[\frac{A}{1 + Af} \right] S_{in}$$




$$\frac{A \rightarrow \infty}{1 + Af \rightarrow \infty} \approx \frac{\infty}{\cancel{1 + \infty f}}$$

A is unreliable \rightarrow vary



A \rightarrow really large A $\rightarrow \infty$
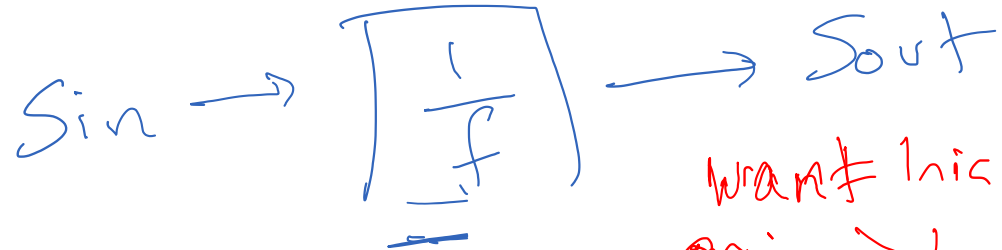
$$\approx \frac{\infty}{\cancel{\infty f}} \approx \frac{1}{f}$$




want high gain
gain > 1 $f < 1$

Apply Negative Feedback to an Op Amp!

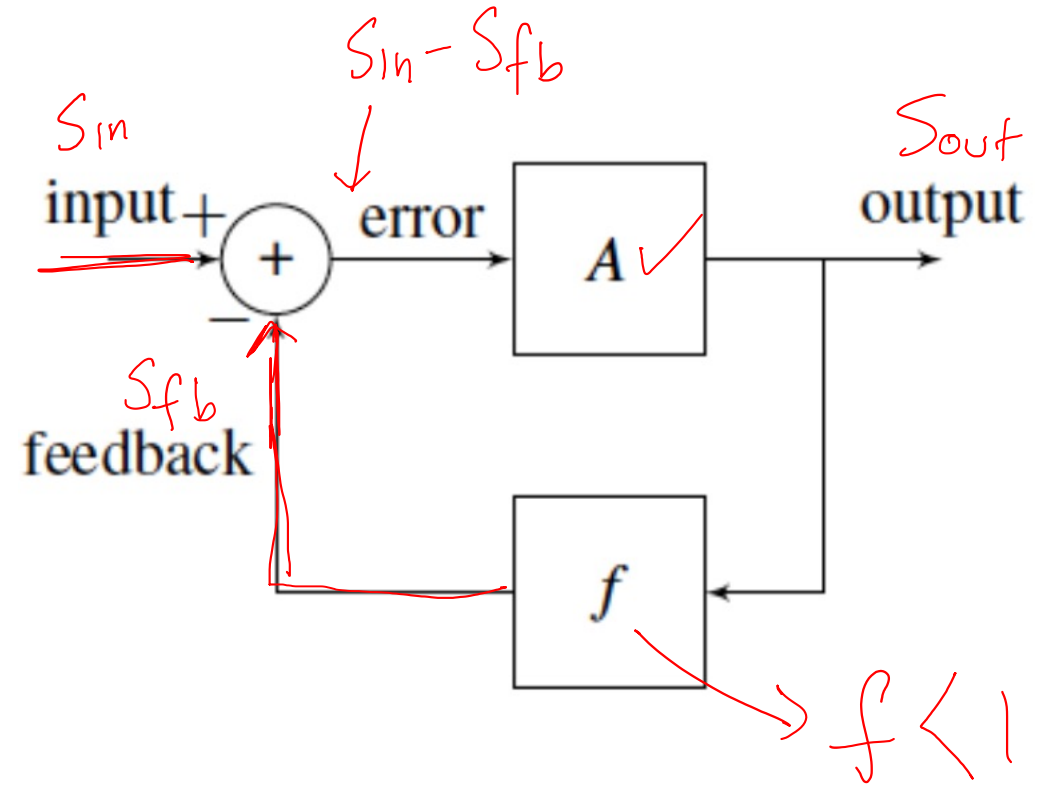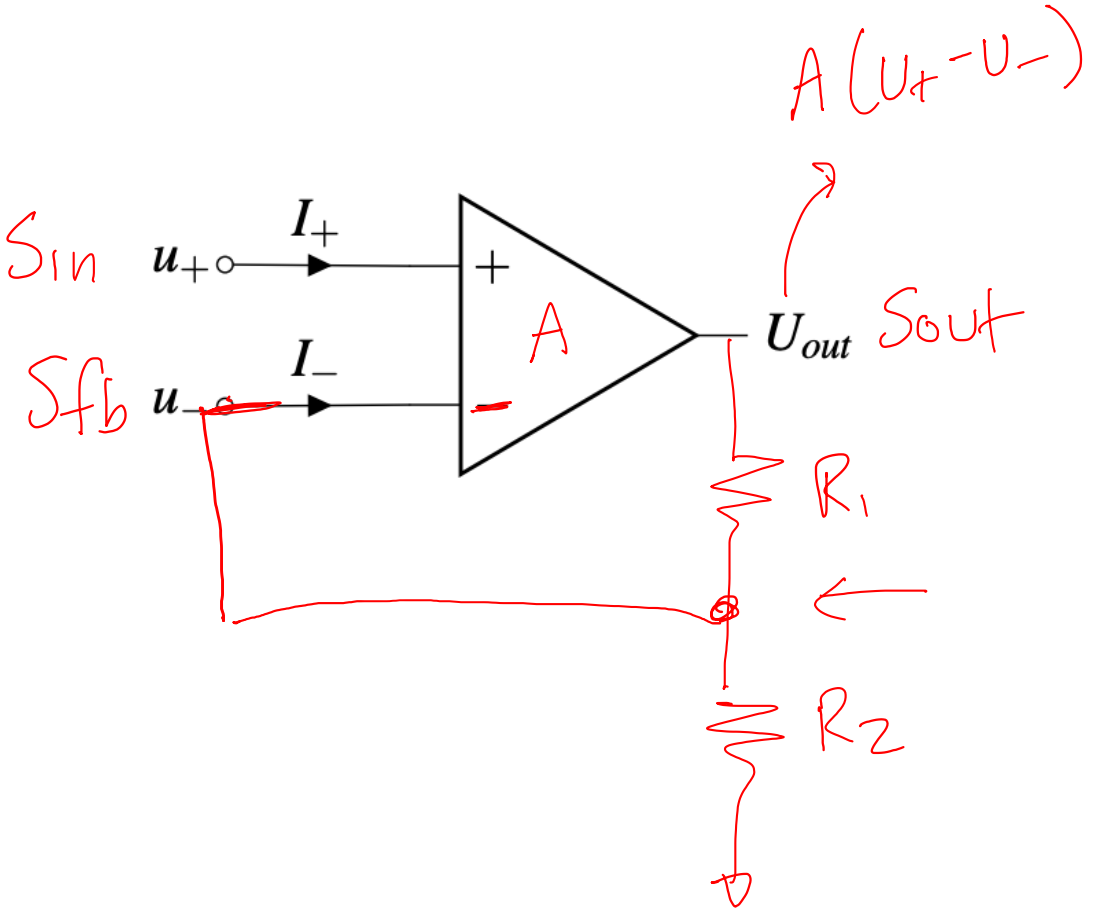

An Op Amp with Negative Feedback!
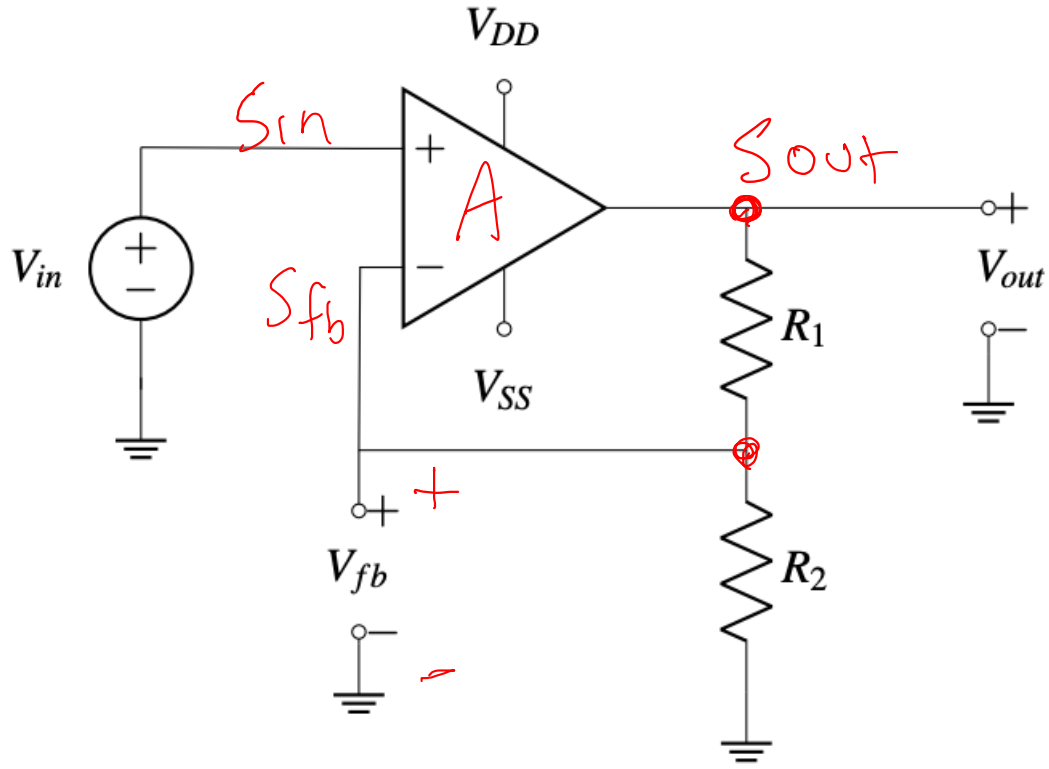
$$\frac{S_{out}}{S_{in}} = \frac{A}{1 + Af}$$



$$\underline{V_{fb}} = S_{fb} = \frac{S_{out} \cdot R_2}{R_2 + R_1}$$

$$f \cdot S_{out} = V_{fb} = \frac{R_2}{R_2 + R_1}$$

$$S_{out} = \frac{A \cdot S_{in}}{1 + A \left(\frac{R_2}{R_1 + R_2} \right)}$$

= 3!

$$S_{out} \approx \frac{R_1 + R_2}{R_2} \cdot S_{in}$$