

EECS 16A  
Spring 2022

Designing Information Devices and Systems I

Midterm 2

PRINT your student ID: \_\_\_\_\_

PRINT AND SIGN your name: \_\_\_\_\_,  
(last name) (first name) (signature)

PRINT the time of your discussion section and your GSI(s) name: \_\_\_\_\_

PRINT the student IDs of the person sitting on your right: \_\_\_\_\_ and left: \_\_\_\_\_

**1. HONOR CODE**

Please read the following statements of the honor code, and sign your name (you don't need to copy it).

*I will respect my classmates and the integrity of this exam by following this honor code. I affirm:*

- *I have read the instructions for this exam. I understand them and will follow them.*
- *All of the work submitted here is my original work.*
- *I did not reference any sources other than my one reference cheat sheet.*
- *I did not collaborate with any other human being on this exam.*




**2. Tell us about something that something you like about this class (1 point) All answers will be awarded full credit.**

PRINT your student ID: \_\_\_\_\_

### 3. KCL and KVL (3.5 points)

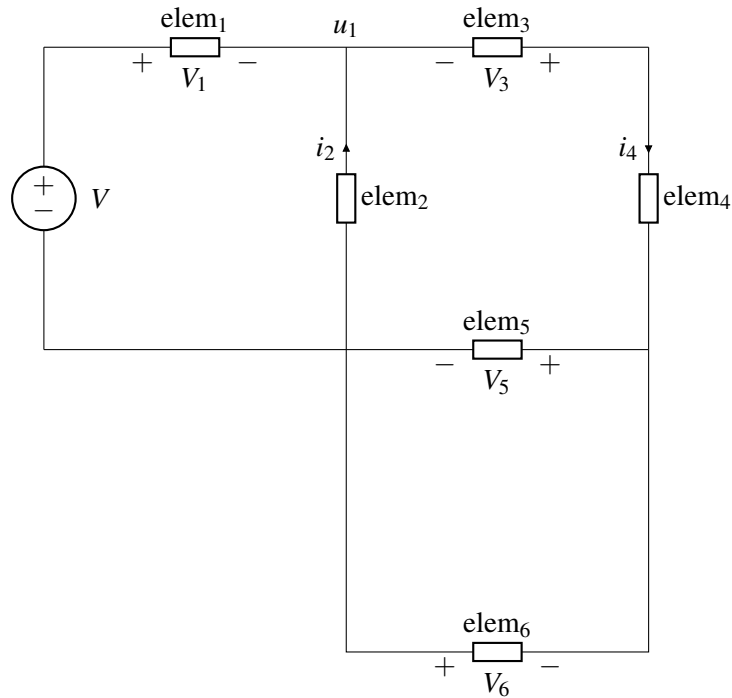- (a) (1.5 points) Given the circuit below, label all the missing **element** voltages and currents using passive sign convention. You do not need to label the voltage source or node voltages.




- (b) (1 point) Using your labeled voltages/currents, write the KCL equation for node  $u_1$ .

- (c) (1 point) Using your labeled voltages/currents, write the KVL equation for the loop containing  $\text{elem}_2$ ,  $\text{elem}_3$ ,  $\text{elem}_4$  and  $\text{elem}_5$ .

PRINT your student ID: \_\_\_\_\_

#### 4. Potentiometers (10 Points)

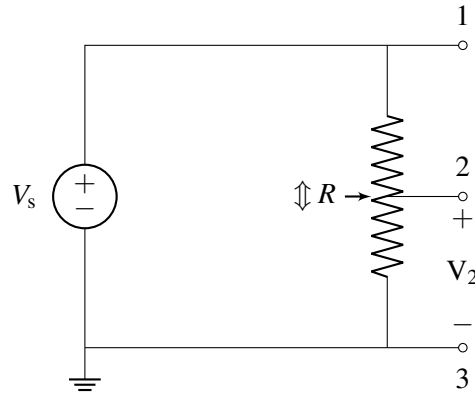- (a) (2 points) A potentiometer is a component that can provide variable resistance. As shown in the figure, terminals 1 and 3 of the potentiometer are fixed, and the resistance between them is always equal to  $R$ . By moving the wiper at terminal 2 up and down, the length between terminals 1 & 2 and 2 & 3 vary, changing  $R_{12}$  (the resistance between terminals 1,2) and  $R_{23}$  (The resistance between terminals 2,3).




In the figure, the potentiometer is connected to a voltage source. Express the output voltage,  $V_2$  (the voltage at terminal 2), as a function of the source voltage  $V_s$ ,  $R_{12}$ , and  $R_{23}$ .

PRINT your student ID: \_\_\_\_\_

- (b) (3 points) Now you are given a different type of variable resistor  $R_{var}$  with initial length  $L_0$  (mm), area  $A_0$  ( $\text{mm}^2$ ), and resistivity  $\rho$  ( $\Omega \cdot \text{mm}$ ). By squeezing the variable resistor, you decrease its length and increase its area: each squeeze of 1 mm will cause the *length* to decrease by 1 mm and the *area* to increase by 1/10 of  $A_0$ . Suppose the variable resistor is squeezed by  $d$  (mm), express the resistance  $R_{var}$  as a function of  $d$  and other variables in the problem.

PRINT your student ID: \_\_\_\_\_

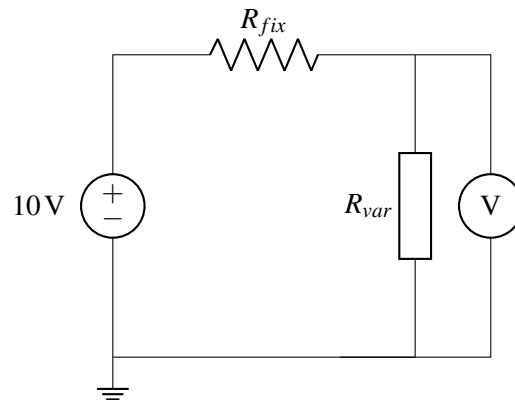
- (c) (5 points) You would like to use a variable resistor as a pressure sensor. To do so you must choose an  $R_{fix}$  and setup the following circuit to measure the voltage change across  $R_{var}$  with a voltmeter. Assume initially  $R_{var}$  is  $2\text{k}\Omega$ . When the pressure increases,  $R_{var}$  becomes  $3\text{k}\Omega$ . You only have resistors of three values:  $2\Omega$ ,  $2\text{k}\Omega$ ,  $2\text{M}\Omega$  to choose for  $R_{fix}$ . If your voltmeter can only detect changes larger than  $0.5\text{V}$ , which one of these resistors would you choose? Justify your answer mathematically.




PRINT your student ID: \_\_\_\_\_

**5. Physical Capacitors (5.5 points)**

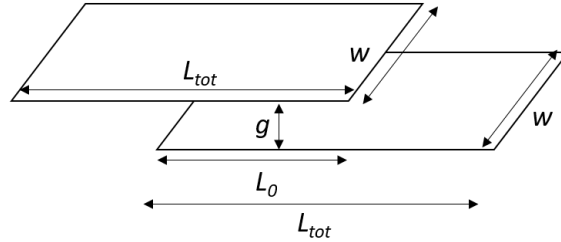- (a) (1.5 point) A parallel plate capacitor with area,  $A$ , separated by a gap,  $g$ , and contains an insulating layer with permittivity,  $\epsilon$ , is shown below. The plates are perfectly aligned in the  $w$  direction. Express the capacitance with the given variables.



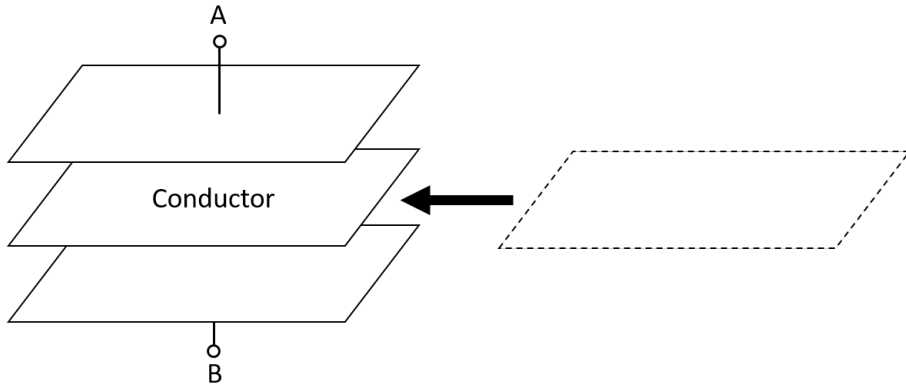
- (b) (4 points) For the capacitors in the following questions, assume air is between the plates, and permittivity of air is  $\epsilon$ . For each of the following statements, decide if it is true or false. Circle your answer and justify (intuitive arguments are valid) with a sentence or two.
- i. Inserting an **infinitely thin, uncharged, conductive** plate between a parallel plate capacitor changes the overall capacitance between A and B.



True      False

PRINT your student ID: \_\_\_\_\_

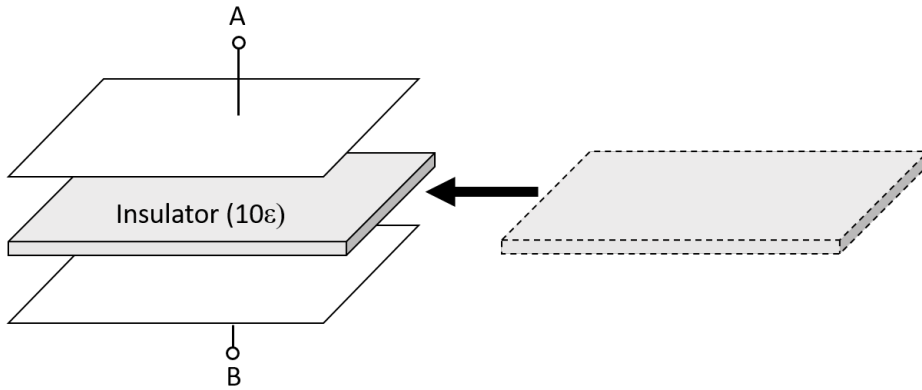- ii. Inserting a **finitely thick, uncharged, insulating** plate between a parallel plate capacitor changes the overall capacitance between A and B.




True    False

PRINT your student ID: \_\_\_\_\_

### 6. 2D Resistive Touch (11 points)

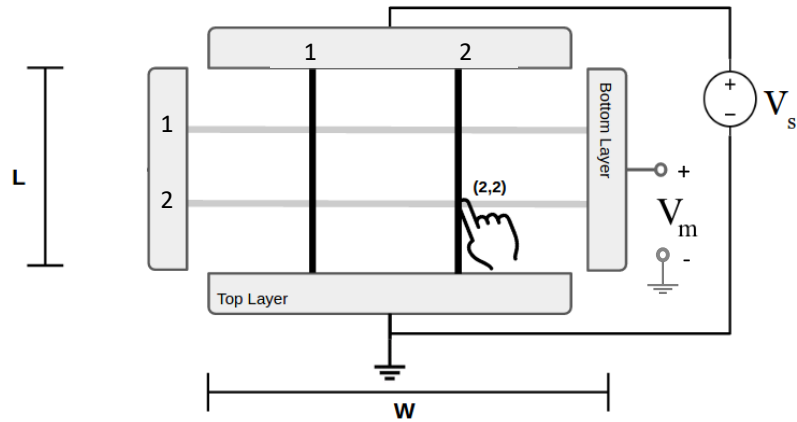
- (a) (3 points) Consider the 2x2 touchscreen below where the strips are equally spaced and connected by an ideal conducting plate on each end. There is no contact being made between overlapping strips except where the finger is touching. Draw an equivalent circuit diagram for when touch occurs at (2,2). Be sure to include  $V_s$ ,  $V_m$  in your diagram. You don't have to label the equivalent resistors.





PRINT your student ID: \_\_\_\_\_

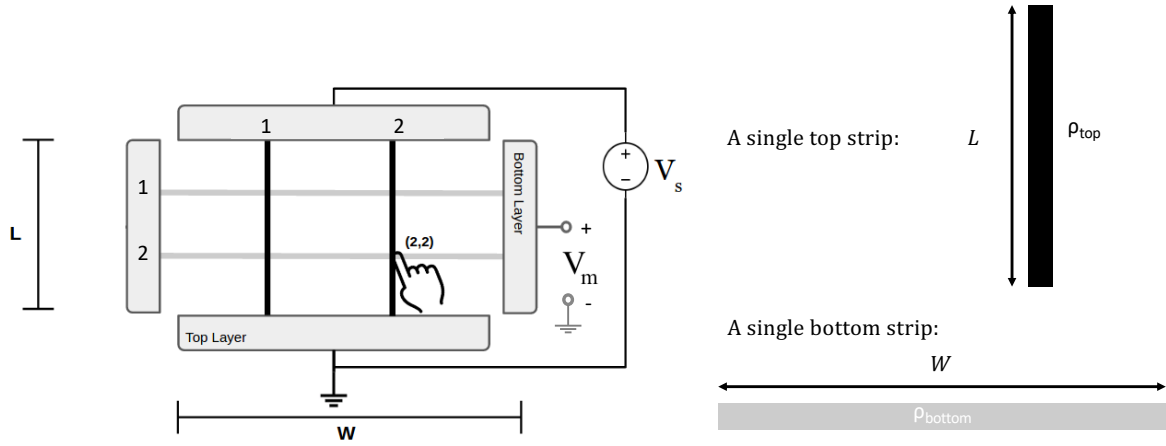
- (b) (3 points) In this resistive touchscreen, the top strips are made of a material with resistivity  $\rho_{top}$  and the bottom strips are made of a material with resistivity  $\rho_{bottom}$ .



What is  $V_m$  when touch occurs at (2,2)?

PRINT your student ID: \_\_\_\_\_

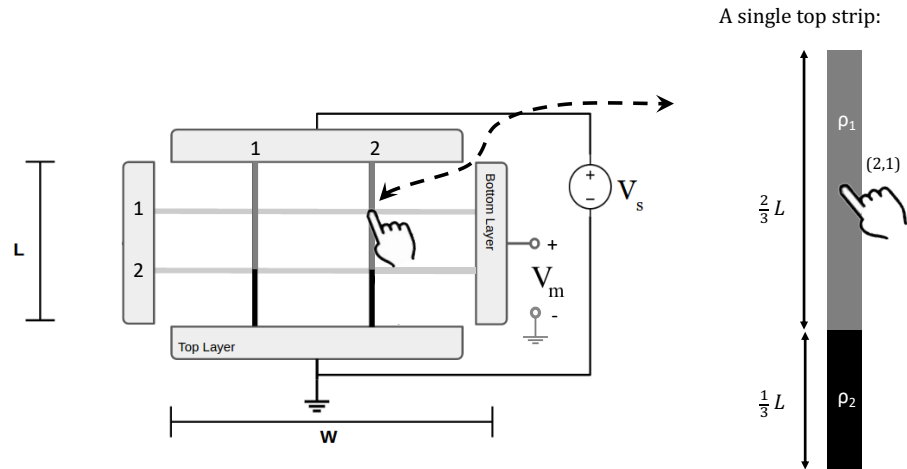
- (c) (5 points) Now consider that the bottom strips are made from not one, but two materials such that the first two thirds of the strip has resistivity  $\rho_1$  and the last third of the strip has resistivity  $\rho_2$  as shown. What is  $V_m$  when touch occurs at (2,1)? You may express your answer in terms of the following variables:  $L$ ,  $W$ ,  $\rho_1$ ,  $\rho_2$  and  $V_s$ .




PRINT your student ID: \_\_\_\_\_

### 7. Non-Ideal Measurement (20 points)

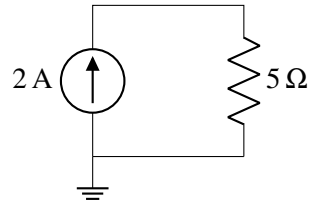- (a) (10 points) You are asked to find the power **supplied** by the current source in the circuit below. (Remember, the power supplied by an element to a circuit is the negative of the power dissipated by that element.)
- i. (2 points) Calculate the power supplied by the current source.



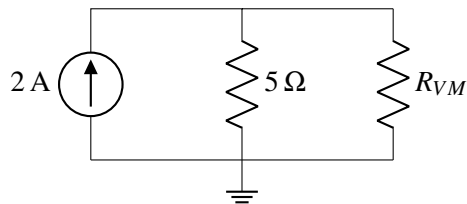- ii. (3 points) You would like to verify your calculation by measuring the voltage across the resistor. Unfortunately, you only have a **non-ideal** voltmeter. We will model the voltmeter as a resistor with resistance  $R_{VM}$ . If  $R_{VM}$  is  $5\Omega$ , how much power will the current source supply to the circuit?




PRINT your student ID: \_\_\_\_\_


- iii. (5 points) Let  $P_0$  be the power supplied by the source if the voltmeter is not present in the circuit (i.e. your answer from part (i)), and  $P_I$  the power supplied after adding the non-ideal voltmeter (as shown in part (ii)). We would like to ensure  $P_I \geq 0.8 * P_0$ . You may again assume that the voltmeter can be modeled as a resistance  $R_{VM}$ . What constraint should you put on the value of  $R_{VM}$ ?

PRINT your student ID: \_\_\_\_\_

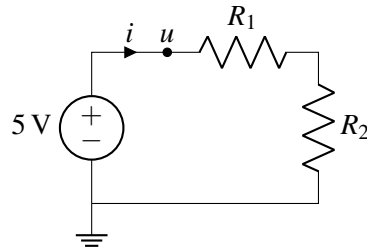(b) (4 points) You want to measure the voltage at node  $u$  in the following circuit:



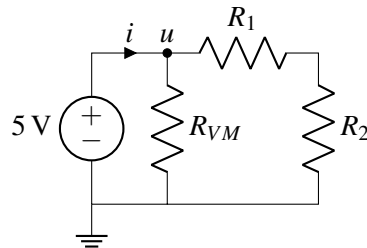You decide to attach a **non-ideal** voltmeter into the circuit below.




How will adding the voltmeter change the voltage at node  $u$  and the current  $i$ ? Circle your answer, and justify with math or a brief written explanation.

$u$  will:    Increase    Decrease    Stay the same


$i$  will:    Increase    Decrease    Stay the same

PRINT your student ID: \_\_\_\_\_

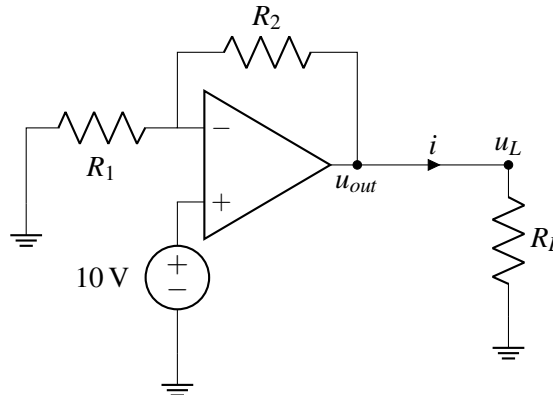(c) (6 points) Now you want to measure the current in the following circuit:



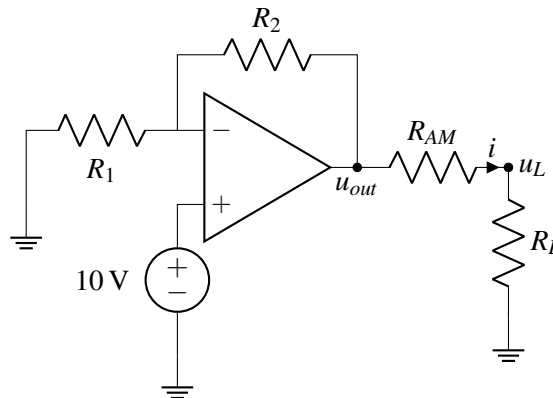You attach a **non-ideal** ammeter, which can be modeled as a resistor with some finite non-zero resistance  $R_{AM}$ , and the resulting circuit is shown below:



How will adding the ammeter change the following quantities? You may assume the op amp is ideal. Circle your answer and justify with math or a brief written explanation.

$u_{out}$ will:	Increase	Decrease	Stay the same
-----------------	----------	----------	---------------

PRINT your student ID: \_\_\_\_\_


$u_L$  will:    Increase    Decrease    Stay the same

$i$  will:    Increase    Decrease    Stay the same

PRINT your student ID: \_\_\_\_\_

### 8. Equivalence and Superposition (15 points)

(a) (12 points)

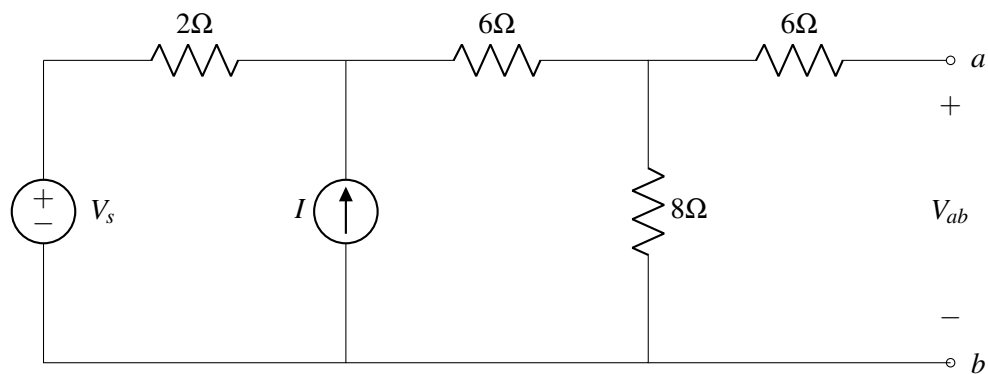


i. (4 points) Find the Thevenin equivalent resistance between terminals  $a$  and  $b$ .




PRINT your student ID: \_\_\_\_\_

 - ii. (8 points) Use superposition to find the Thevenin equivalent voltage between terminals  $a$ ,  $b$  as a function of  $I$  and  $V_s$ .




PRINT your student ID: \_\_\_\_\_

 

PRINT your student ID: \_\_\_\_\_

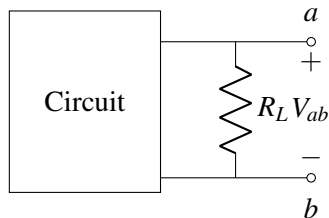
- (b) (3 points) Now you are given a new mystery circuit! You connect a load resistor  $R_L$  to your circuit, as shown below. You know that the Norton equivalent circuit from nodes  $a$  and  $b$  has  $I_{no} = 3A$  and  $R_{no} = 2\Omega$ . Find the value of  $R_L$  such that  $V_{ab} = 4V$ .



PRINT your student ID: \_\_\_\_\_


**9. Capacitors in the Wild (10 points)**

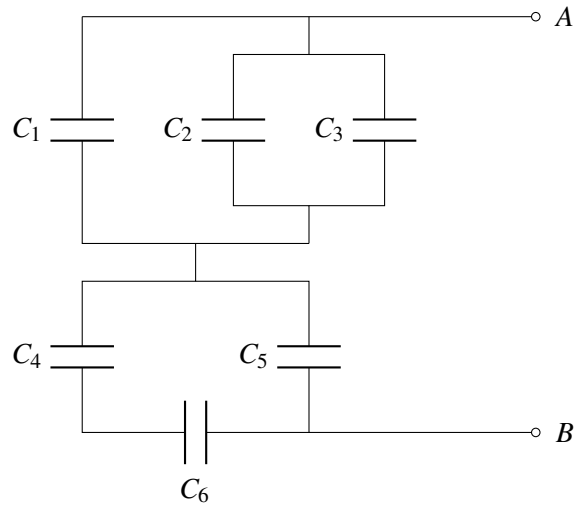- (a) (2 points) Find the equivalent capacitance between nodes  $A$  and  $B$  in terms of each of the capacitors,  $C_i$ . You can use the parallel operator ( $\parallel$ ) for simplification.




PRINT your student ID: \_\_\_\_\_

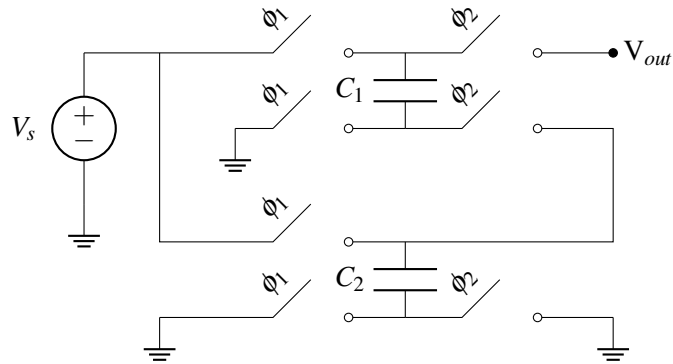- (b) (8 points) In the following circuit, switches labeled  $\phi_1$  are closed during phase 1 and open during phase 2; switches labeled  $\phi_2$  are closed during phase 2 and open during phase 1. Assume before phase 1 both capacitors are fully discharged. Each phase is long enough that the circuit reaches steady-state. Find  $V_{out}$  in phase 2 in terms of  $V_s$ ,  $C_1$  and  $C_2$ .




PRINT your student ID: \_\_\_\_\_

 

PRINT your student ID: \_\_\_\_\_


**10. Op-amps and Comparators (9 points)**

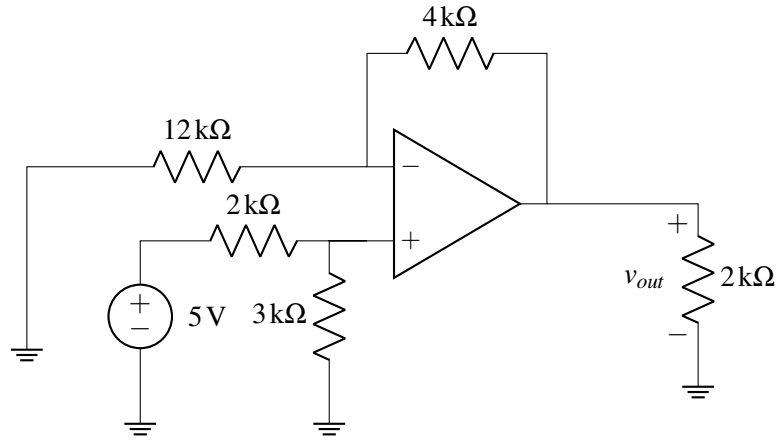(a) (3 points) You are given the following op-amp in negative feedback. Find  $v_{out}$ .



PRINT your student ID: \_\_\_\_\_

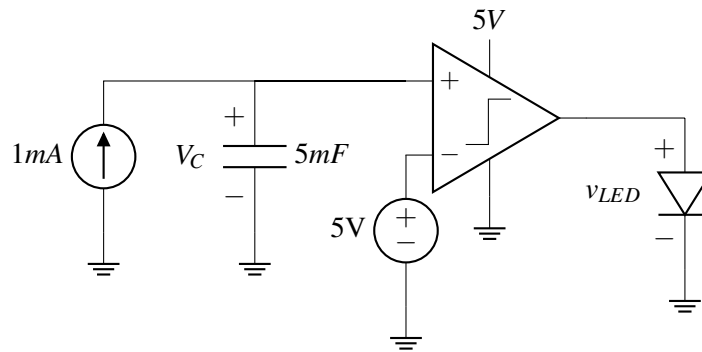- (b) (3 points) You are given the circuit below. The capacitor is initially uncharged. At time  $t = 0$ , the current source is turned on. Find  $V_C(t)$ .





PRINT your student ID: \_\_\_\_\_


- (c) (3 points) The LED turns on when the voltage across it is greater than 3.3V. Using the same setup as part (b), at what time  $t$  does the LED turn on?

PRINT your student ID: \_\_\_\_\_

### 11. Eigen Circuits (19 points)

(a) (7 points) You are given the following op-amp circuit in negative feedback.

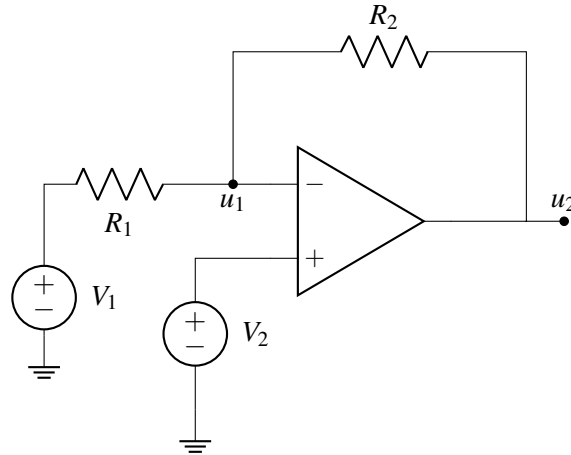i. (5 points) Express  $u_1$  and  $u_2$  in terms of  $V_1$ ,  $V_2$ ,  $R_1$  and  $R_2$ . Assume the op-amp is ideal.



PRINT your student ID: \_\_\_\_\_

- ii. (2 points) Write the above equations in the form of  $A\vec{x} = \vec{b}$ .  $\vec{x}$  is  $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$  and  $\vec{b}$  is  $\begin{bmatrix} u_1 \\ u_2 \end{bmatrix}$ .

PRINT your student ID: \_\_\_\_\_

- (b) (6 points) Assume that after plugging in values for  $R_1$  and  $R_2$ , the matrix  $\mathbf{A}$  you get is  $\begin{bmatrix} 0 & 1 \\ -2 & 3 \end{bmatrix}$ , find the eigenvalue(s) and the eigenvector(s) of this matrix.

PRINT your student ID: \_\_\_\_\_

- (c) (6 points) Assume you are given another linear circuit with inputs  $V_1$  and  $V_2$  and outputs  $u_1$  and  $u_2$ . The eigenvalues for this circuit are  $\lambda_1 = 1$  and  $\lambda_2 = 2$ . The corresponding eigenvectors are  $\vec{v}_1 = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$ ,  $\vec{v}_2 = \begin{bmatrix} 1 \\ 3 \end{bmatrix}$ . If we want  $u_1 = 3V$ ,  $u_2 = 7V$ , what would the input values be?

PRINT your student ID: \_\_\_\_\_

Extra page for scratchwork.  
**Work on this page will NOT be graded.**

PRINT your student ID: \_\_\_\_\_

Extra page for scratchwork.  
**Work on this page will NOT be graded.**