

# EECS 16B    Designing Information Devices and Systems II


## Fall 2021    Discussion Worksheet

# Discussion 1A

For this discussion, [Note 1](#) is helpful for background in transistors and RC circuits.

### 1. NAND Circuit

Let us consider a NAND logic gate. This circuit implements the boolean function  $\overline{(A \cdot B)}$ . The  $\cdot$  stands for the AND operation, and the  $\overline{\quad}$  stands for NOT; combining them, we get NAND!

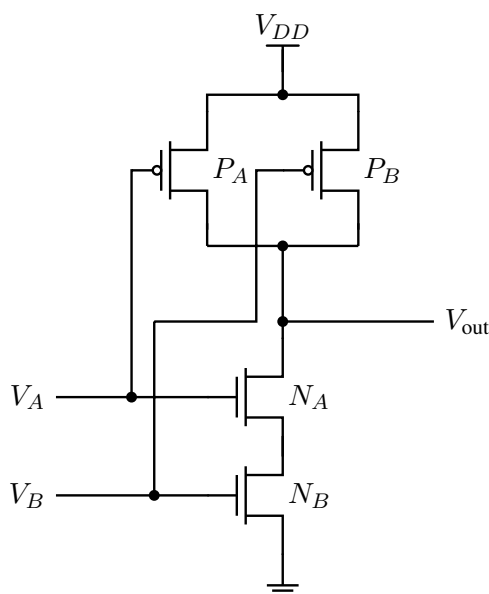

**Figure 1:** NAND gate transistor-level implementation.

$V_{tn}$  and  $V_{tp}$  are the threshold voltages for the NMOS and PMOS transistors, respectively. Assume that  $V_{DD} > V_{tn}$  and  $|V_{tp}| > 0$ .

(a) Label the gate, source, and drain nodes for the NMOS and PMOS transistors above.

(b) If  $V_A = V_{DD}$  and  $V_B = V_{DD}$ , which transistors act like open switches? Which transistors act like closed switches? What is  $V_{out}$ ?

(c) If  $V_A = 0V$  and  $V_B = V_{DD}$ , what is  $V_{out}$ ?

(d) If  $V_A = V_{DD}$  and  $V_B = 0V$ , what is  $V_{out}$ ?

(e) If  $V_A = 0V$  and  $V_B = 0V$ , what is  $V_{out}$ ?


(f) Write out the truth table for this circuit.

$V_A$	$V_B$	$V_{out}$
0	0	
0	$V_{DD}$	
$V_{DD}$	0	
$V_{DD}$	$V_{DD}$	

## 2. RC Circuits - Part I

In this problem, we will find the voltage across a capacitor over time in an RC circuit. In this part, we set up our problem by first defining four functions over time:  $I(t)$  is the current at time  $t$ ,  $V(t)$  is the voltage across the circuit at time  $t$ ,  $V_R(t)$  is the voltage across the resistor at time  $t$ , and  $V_C(t)$  is the voltage across the capacitor at time  $t$ .

Recall from 16A that the voltage across a resistor is defined as  $V_R = RI_R$  where  $I_R$  is the current across the resistor. Also, recall that the voltage across a capacitor is defined as  $V_C = \frac{Q}{C}$  where  $Q$  is the charge across the capacitor.

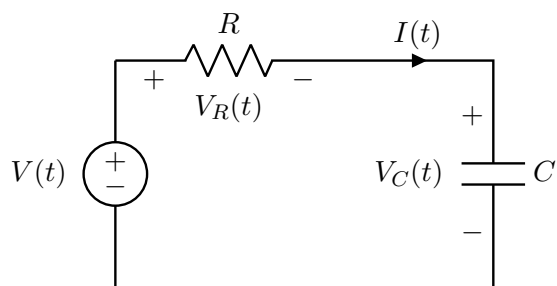

**Figure 2:** Example Circuit

(a) First, find an equation that relates the current across the capacitor  $I(t)$  with the voltage across the capacitor  $V_C(t)$ .

(b) Write a system of equations that relates the functions  $I(t)$ ,  $V_C(t)$ , and  $V(t)$ .

(c) So far, we have two relations between  $I(t)$  and  $V_C(t)$ . To solve this system of equations, we can remove

$I(t)$  from the equation using what we found in part (a). Rewrite the previous equation in part (b) in the form of a differential equation.

**Contributors:**

- Kumar Krishna Agrawal.
- Lev Tauz.
- Varun Mishra.
- Regina Eckert.