

EECS 16B Designing Information Devices and Systems II

Fall 2021 Discussion Worksheet

Discussion 1B

For this discussion, **Note 1** is helpful for the differential equations, and **Note j** covers the complex numbers fundamentals.

1. RC Circuits: Solving the Differential Equations

Recall that in **the last discussion**, we were tasked with analyzing an example RC circuit (in fig. 1) and using element equations (governing equations for resistors and capacitors) to formulate a differential equation. This equation describes the time-varying behavior of this circuit. Specifically, we had the following differential equation:

$$RC \frac{dV_C(t)}{dt} + V_C(t) = V(t) \quad (1)$$

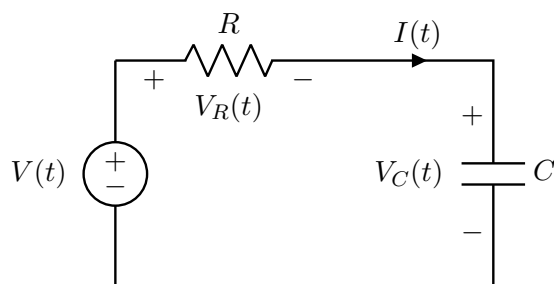


Figure 1: Sample RC Circuit

Our goal is to now solve this differential equation for the voltage across the capacitor, $V_C(t)$.

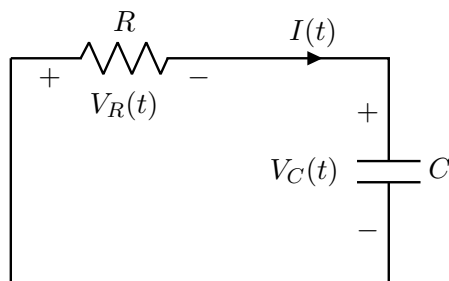


Figure 2: RC Circuit for part (a). Note that the voltage source has been turned off (0 V) for this subpart, and the initial voltage on the capacitor is V_{DD} .

- (a) Let's suppose that at $t = 0$, the capacitor is charged to a voltage V_{DD} ($V_C(0) = V_{DD}$). Let's also assume that $V(t) = 0$ for all $t \geq 0$ (voltage source is turned off). Solve the differential equation for $V_C(t)$ for $t \geq 0$.

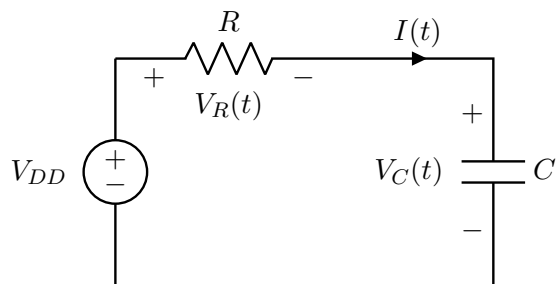


Figure 3: Circuit for part (b)

- (b) Now, let's suppose that we start with an uncharged capacitor $V_C(0) = 0$. We apply some constant voltage $V(t) = V_{DD}$ across the circuit for all $t \geq 0$. Solve the differential equation for $V_C(t)$ for $t \geq 0$.
- (c) We now want to combine the principles from the previous two subparts to understand the voltage waveform when a switch occurs at some time t . Specifically, suppose that at $t = 0$, $V(t) = 0$ V, $V_C(0) = V_{DD}$. Then, at some $t = t_{\text{switch}}$, the voltage source is turned on $V(t) = V_{DD}$ for $t \geq t_{\text{switch}}$. We want to find the equation for the overall capacitor voltage as a function of time (for times before and after t_{switch}).

2. Complex Algebra (Review)

(a) Express the following values in polar forms: -1 , j , $-j$, \sqrt{j} , and $\sqrt{-j}$. Recall $j^2 = -1$, and the complex conjugate of a complex number is denoted with a bar over the variable. The complex conjugate is defined as follows: for a complex number $z = x + jy$, the complex conjugate $\bar{z} = x - jy$.

(b) Represent $\sin(\theta)$ and $\cos(\theta)$ using complex exponentials. (*Hint: Use Euler's identity $e^{j\theta} = \cos(\theta) + j \sin(\theta)$.*)

For the next parts, let $a = 1 - j\sqrt{3}$ and $b = \sqrt{3} + j$.

(c) Show the number a in complex plane, marking the distance from origin and angle with real axis.

(d) Show that multiplying a with j is equivalent to rotating the magnitude of the complex number by $\frac{\pi}{2}$ or 90° in the complex plane.

(e) **(Practice)** For complex number $z = x + jy$ show that $|z| = \sqrt{z\bar{z}}$, where \bar{z} is the complex conjugate of z .

(f) **(Practice)** Express a and b in polar form.

(g) **(Practice)** Find ab , $a\bar{b}$, $\frac{a}{b}$, $a + \bar{a}$, $a - \bar{a}$, \overline{ab} , $\overline{a\bar{b}}$, and \sqrt{b} .

Contributors:

- Neelesh Ramachandran.
- Brian Kilberg.
- Kuan-Yun Lee.
- Maruf Ahmed.