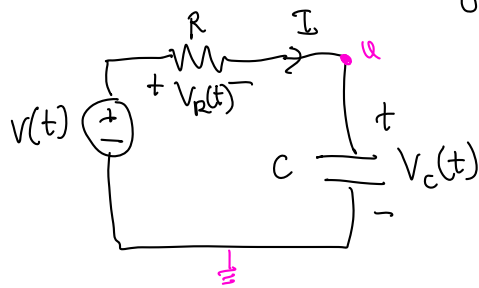


RC Circuits: Solving the Differential Equation



described by


$$RC \frac{dV_C(t)}{dt} + V_C(t) = V(t)$$

Differential equation

comes from doing NVA on circuit to the left @ u

Moses + Helen!
moseswon@
helenpeng@
Find me @
W2-4PM HWP
Feedback:
bit.ly/mw16bfb

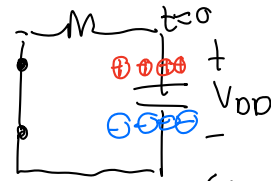- (a) (a) $t=0$, $V_C(0) = V_{DD}$ (initial charge)
 $V(t) = 0$, $t \geq 0$ (voltage source off)
 Solve for $V_C(t)$, $t \geq 0$



(prediction)
 $V_C(t) \rightarrow 0$
 $t \rightarrow \infty$

$$RC \frac{dV_C(t)}{dt} + V_C(t) = 0$$

$$RC \frac{dV_C(t)}{dt} = -V_C(t)$$

$$\left\{ \begin{aligned} \frac{dV_C(t)}{dt} &= -\frac{1}{RC} V_C(t) \\ V_C(0) &= V_{DD} \text{ (initial condition)} \end{aligned} \right.$$

$$V_{\text{guess}}(t) = a e^{bt} \quad t \geq 0$$


$$\frac{d}{dt} (V_{\text{guess}}(t)) = \frac{d}{dt} (a e^{bt}) = a \cdot b e^{bt} = b \cdot a e^{bt}$$

$$\frac{d}{dt} (V_{\text{guess}}(t)) = b \cdot V_{\text{guess}}(t)$$

$$V_{\text{guess}}(t=0) = a e^{b \cdot 0} = a e^{-\frac{1}{RC} \cdot 0} \Rightarrow b = ? \Rightarrow \boxed{b = -\frac{1}{RC}}$$

$$V_{\text{guess}}(0) = a e^0 = a \Rightarrow V_C(0) = V_{DD} \Rightarrow V_{\text{guess}}(0) = a \Rightarrow \boxed{a = V_{DD}}$$

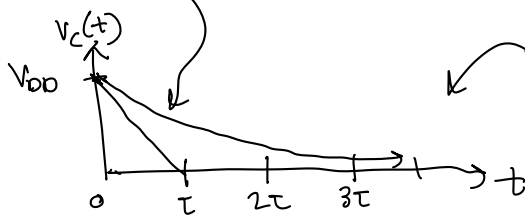
$$V_C(t) = V_{\text{guess}}(t) = V_{DD} e^{-\frac{1}{RC} t}, \quad t \geq 0$$



$\tau = RC$ (seconds)

$$\begin{aligned} \frac{dV_{\text{guess}}}{dt} &= \frac{d}{dt} \left(V_{DD} e^{-\frac{1}{RC} t} \right) \\ &= -\frac{1}{RC} V_{DD} e^{-\frac{1}{RC} t} \\ &= -\frac{1}{RC} V_{\text{guess}} \quad \checkmark \end{aligned}$$

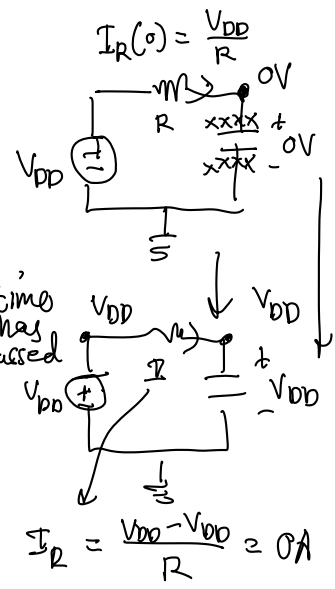① $t=0, V_c(0) = 0V$ (no charge on cap)
 $V(t) = V_{DD}, t \geq 0$ (voltage source on with V_{DD})
 solve for $V_c(t), t \geq 0$



$$RC \frac{dV_c(t)}{dt} + V_c(t) = V(t)$$

$$RC \frac{dV_c(t)}{dt} = V_{DD} - V_c(t)$$

$$\frac{dV_c(t)}{dt} = \frac{V_{DD} - V_c(t)}{RC}$$

$$\frac{du}{dt} = \frac{u}{RC}$$

What should u be?

$$u(t) = V_{DD} - V_c(t)$$

want our DE to look like an original one we know how to solve

$$\frac{d}{dt} u(t) = \frac{d}{dt} (V_{DD} - V_c(t))$$

$$= \frac{d}{dt} V_{DD} - \frac{d}{dt} V_c(t)$$

$$\frac{d}{dt} u(t) = -\frac{d}{dt} V_c(t)$$

$$-\frac{d}{dt} u(t) = \frac{d}{dt} V_c(t)$$

$$-\frac{d}{dt} u(t) = \frac{u(t)}{RC}$$

$$\frac{d}{dt} u(t) = -\frac{u(t)}{RC}$$

$$u(0) = V_{DD} - V_c(0)$$

$$\rightarrow u(0) = V_{DD}$$

$$u(0) = V_{DD} - V_c(0)$$

$$V_c(t) = V_{DD} e^{-\frac{1}{RC}t}$$

$$u(t) = a e^{bt}$$

$$= u(0) e^{-\frac{1}{RC}t}$$

Why is $a = u(0)$?

$$u(t=0) = a e^{b(0)}$$

$$= a e^0$$

$$= a \cdot 1$$

$$u(0) = a$$

$$u(t) = [V_{DD} - V_c(0)] e^{-\frac{1}{RC}t}, t \geq 0$$


$$V_{DD} - V_c(t) = [V_{DD} - V_c(0)] e^{-\frac{1}{RC}t}, t \geq 0$$

$$V_{DD} - [V_{DD} - V_c(0)] e^{-\frac{1}{RC}t} = V_c(t), t \geq 0$$


$$V_c(t) = V_{DD} - (V_{DD} - 0) e^{-\frac{1}{RC}t}$$

$$V_c(t) = V_{DD} - V_{DD} e^{-\frac{1}{RC}t}$$

$$\tau = RC$$

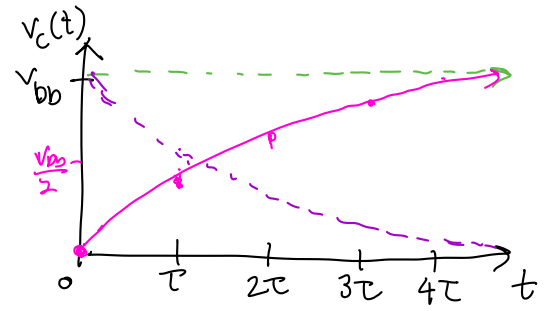

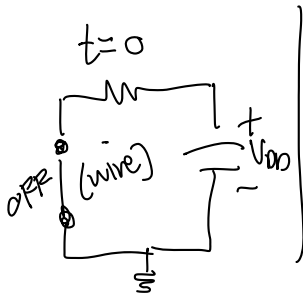(c) $0 \leq t \leq t_{\text{switch}}$
 $V_c(0) = V_{DD}$
 $V(t) = 0$
 ↑ voltage




$t > t_{\text{switch}}$
 $V(t) = V_{DD}$
 voltage source

Can we find $V_c(t)$, when the voltage source ($V(t)$) goes from OFF (0V) to on? (V_{DD})

$0 \leq t \leq t_{\text{switch}}$
 solved for this in (a)!

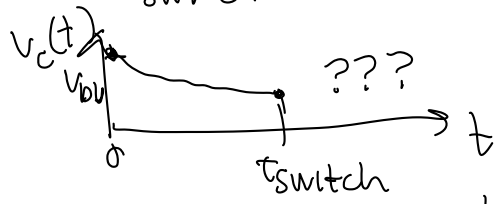$V_c(t) = V_{DD} e^{-\frac{1}{RC}t}$
 $t_{\text{switch}} \geq t \geq 0$



$V_c(t_{\text{switch}}) = V_{DD} e^{-\frac{1}{RC}t_{\text{switch}}}$

$t_s := t_{\text{switch}}$

$V_c(t_s) = V_{DD} e^{-\frac{1}{RC}t_s}$

$C \frac{dV_c}{dt} = I$
 $\frac{dV_c}{dt} = \frac{I}{C}$
 $\frac{dV_c}{dt} = \infty$
 $\frac{I}{C} = \infty?$
 Not possible

$V_c(t_s)$ should be that value
 $= V_{DD} e^{-\frac{1}{RC}t_s}$

$V_c(t) = \dots t \geq t_{\text{switch}}?$
 ~~$t \geq 0$~~

$t' := t - t_s$
 $t - t_{\text{switch}} \geq 0$
 $t' \geq 0$

$V_c(t'=0) = V_{DD} e^{-\frac{1}{RC}t_s}$
 $\Rightarrow t = t_s \quad t' \geq 0 \quad V(t') = V_{DD}$ (on)

Solved this in part (b)


$V_c(t') = V_{DD} - (V_{DD} - V_c(t')) e^{-\frac{1}{RC}t'}$

$V_c(t') = V_{DD} - (V_{DD} - V_{DD} e^{-\frac{1}{RC}t_s}) e^{-\frac{1}{RC}t'}$

$V_c(t) = V_{DD} - (V_{DD} - V_{DD} e^{-\frac{1}{RC}t_s}) e^{-\frac{1}{RC}(t-t_s)}$

$= V_{DD} (1 - e^{-\frac{1}{RC}(t-t_s)} + e^{-\frac{1}{RC}t})$
 $t' \geq 0 \Rightarrow t \geq t_s$

Algebra on next page

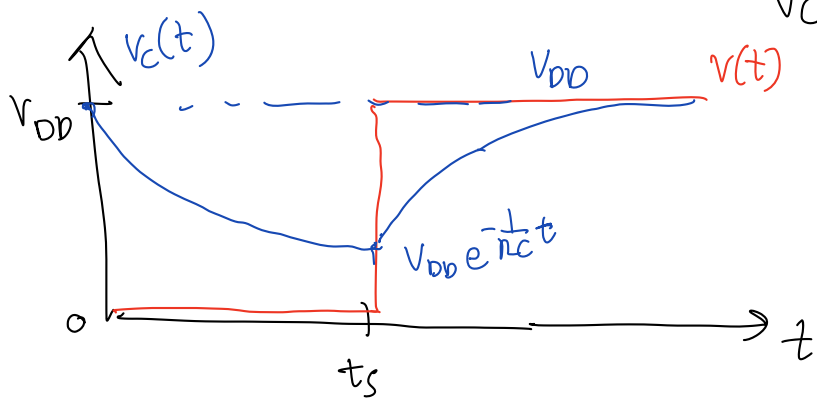

$$\textcircled{1} \textcircled{c} \quad V_c(t) = V_{DD} - (V_{DD} - V_{DD} e^{-\frac{1}{RC} t_s}) e^{-\frac{1}{RC} (t-t_s)}$$

Algebra
for steps
I skipped

$$\begin{aligned} &= V_{DD} - V_{DD} e^{-\frac{1}{RC} (t-t_s)} + V_{DD} e^{-\frac{1}{RC} (t-t_s)} e^{-\frac{1}{RC} t_s} \\ &= V_{DD} \left(1 - e^{-\frac{1}{RC} (t-t_s)} + e^{-\frac{1}{RC} (t-t_s)} e^{-\frac{1}{RC} t_s} \right) \\ &= V_{DD} \left(1 - e^{-\frac{1}{RC} (t-t_s)} + e^{-\frac{1}{RC} t + \frac{1}{RC} t_s - \frac{1}{RC} t_s} \right) \\ &= V_{DD} \left(1 - e^{-\frac{1}{RC} (t-t_s)} + e^{-\frac{1}{RC} t} \right) \end{aligned}$$

Footnote: Please, please, please try the $\boxed{2}$ Complex #'s practice problem even if you don't submit work for it in your discussion attendance. It will be good practice for HW and also later concepts you'll learn.