

# EECS16B DIS4B

Moses

Helen

✉ moseswon@

✉ helenpeng@


🕒 W, HWP 2-4PM

Anonymous feedback form  
bit.ly/mw16bfb

trying something different with questions today to not run over time. (question batching)

★ Cory 299 lecture Watch Party

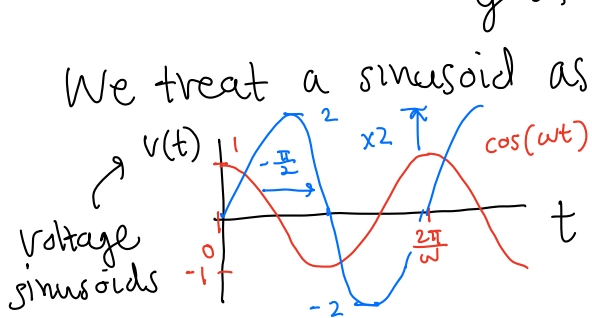Saw in lecture: Can we treat R, L, C as if they're all resistors? For circuits with sinusoidal voltages and currents yes! Can use NVA without pesky  $\frac{d}{dt}$ 's!



$$v(t) = \cos(\omega t) = \frac{1}{2}e^{j\omega t} + \frac{1}{2}e^{-j\omega t}$$

a constant

$$\tilde{V} = \frac{1}{2}e^{j\theta}$$

$$v(t) = 2\cos(\omega t - \frac{\pi}{2}) = e^{-j\frac{\pi}{2}}e^{j\omega t} + e^{j\frac{\pi}{2}}e^{-j\omega t}$$

twice as big! angle shift of  $-\frac{\pi}{2}$

## Learning objectives

- How to do Phasor analysis

**Step 1: Write sources as exponentials:  $\tilde{X}e^{j\omega t} + \tilde{X}e^{-j\omega t}$ .**

**Step 2: Transform circuits to phasor domain.**


(compute the numerical values of these impedances.)

**Step 3: Cast the branch and element equations in the phasor domain. (KVL, KCL, Ohm's)**

**Step 4: Solve for unknown variables**

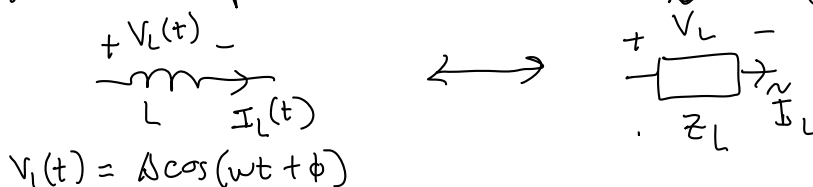**Step 5: Transform solutions back to time domain**


- Inductor impedance derivation (May not hit this one)
- If the inductor behaves like a resistor in phasor land what is its impedance  $Z_L$ ? (quantity analogous to resistance:  $\tilde{V}_L = Z_L \tilde{I}_L$ )



$$v_S(t) = 12 \sin\left(\omega t - \frac{\pi}{4}\right),$$

$$\omega = 1 \times 10^3 \frac{\text{rad}}{\text{s}}, R = \sqrt{3} \text{ k}\Omega, \text{ and } C = 1 \mu\text{F}.$$

Given  
this  
circuit:

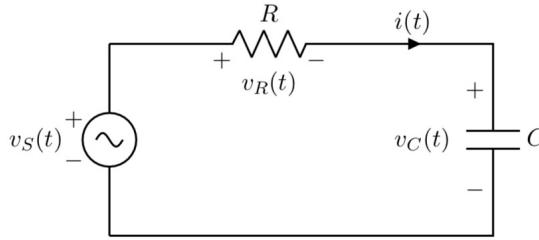

Goal: We seek to obtain a solution for  $i(t)$  with the sinusoidal voltage source<sup>1</sup>  $v_S(t)$ .

(a) **Step 1: Write sources as exponentials:**  $\tilde{X}e^{j\omega t} + \overline{\tilde{X}}e^{-j\omega t}$ .

All voltages and currents with known sinusoidal functions should be expressed in the standard exponential format. **Convert  $v_S(t)$  into an exponential and write down its phasor representation  $\tilde{V}_S$ .** Note that  $v_S(t)$  is given in terms of a sine wave, not a cosine wave.

$$v_S(t) = 12 \sin\left(\omega t - \frac{\pi}{4}\right)$$

$$\cos(\omega t) = \frac{e^{j\omega t} + e^{-j\omega t}}{2}$$

$e^{j\omega t} = \cos \omega t + j \sin \omega t$  & Purpose of phasor?

$$\cos(\square) = \frac{e^{j\square} + e^{-j\square}}{2}$$

$$\sin(\square) = \frac{-je^{j\square} + je^{-j\square}}{2}$$


$$v_S(t) = 12 \left( \frac{-je^{j(\omega t - \frac{\pi}{4})} + je^{-j(\omega t - \frac{\pi}{4})}}{2} \right)$$

$$= -6je^{j(\omega t - \frac{\pi}{4})} + 6je^{-j(\omega t - \frac{\pi}{4})}$$

$$-j = e^{-j\frac{\pi}{2}} \quad j = e^{j\frac{\pi}{2}}$$

$$v_S(t) = 6e^{-j\frac{\pi}{2}}e^{j\frac{\pi}{4}}e^{j\omega t} + 6e^{j\frac{\pi}{2}}e^{-j\frac{\pi}{4}}e^{-j\omega t}$$
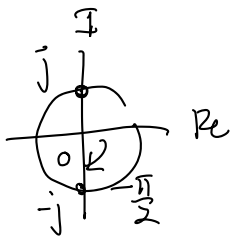
$$= 6e^{-j\frac{3\pi}{4}}e^{j\omega t} + 6e^{j\frac{3\pi}{4}}e^{-j\omega t}$$



### Questions

Q: Purpose of phasor?

A: Capture a sinusoidal V or I so that we can do NVA and compute other sinusoidal V's or I's w/o solving a DE.

Q: Could we use

$$\cos\left(\omega t - \frac{\pi}{2}\right) = \sin(\omega t)$$

A: Yes!

Voltage Phasor:  $\tilde{V}_S = 6e^{-j\frac{3\pi}{4}} \text{ V}$   
↑  
units


Voltage Phasor :  $\tilde{V}_S = 6e^{-j\frac{3\pi}{4}} V \leftarrow \text{units}$

(b) **Step 2: Transform circuits to phasor domain.** The voltage source  $v_S(t)$  is represented by its phasor  $\tilde{V}_S$ . Similarly,  $v_R(t)$  has phasor  $\tilde{V}_R$ , and  $v_C(t)$  has phasor  $\tilde{V}_C$ .

The current  $i(t)$  is related to its phasor counterpart  $\tilde{I}$  by

$$i(t) = \tilde{I}e^{j\omega t} + \bar{\tilde{I}}e^{-j\omega t}. \quad (3)$$

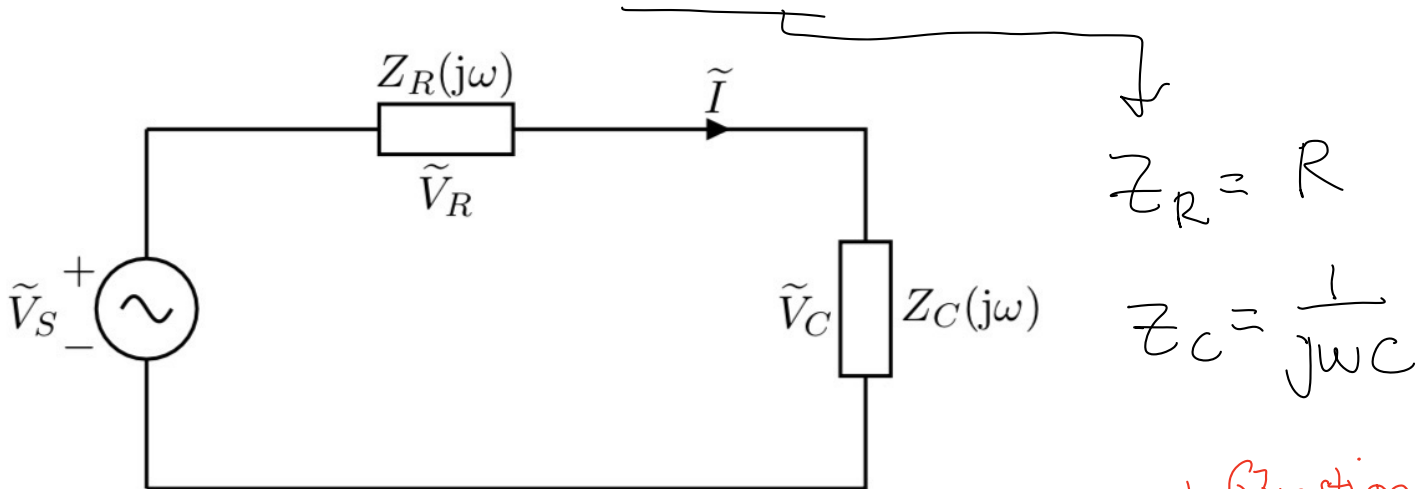Using the numbers given in the problem statement ( $\omega = 1 \times 10^3 \frac{\text{rad}}{\text{s}}$ ,  $R = \sqrt{3} \text{ k}\Omega$ , and  $C = 1 \mu\text{F}$ ), compute the numerical values of these impedances.



$$Z_R = R$$

$$Z_C = \frac{1}{j\omega C}$$


Figure 2: Circuit in "phasor domain"

$$Z_R = \sqrt{3} \text{ k}\Omega$$

$$Z_C = \frac{j \cdot 1}{j \cdot j \cdot (1 \frac{\text{krad}}{\text{s}}) (1 \mu\text{F})} \left[ \frac{\text{s}}{\text{F}} \right]$$

$$= -j \frac{10^6}{10^3} \Omega = -j1000 \Omega = -j1 \text{ k}\Omega$$

Labeled circuit:

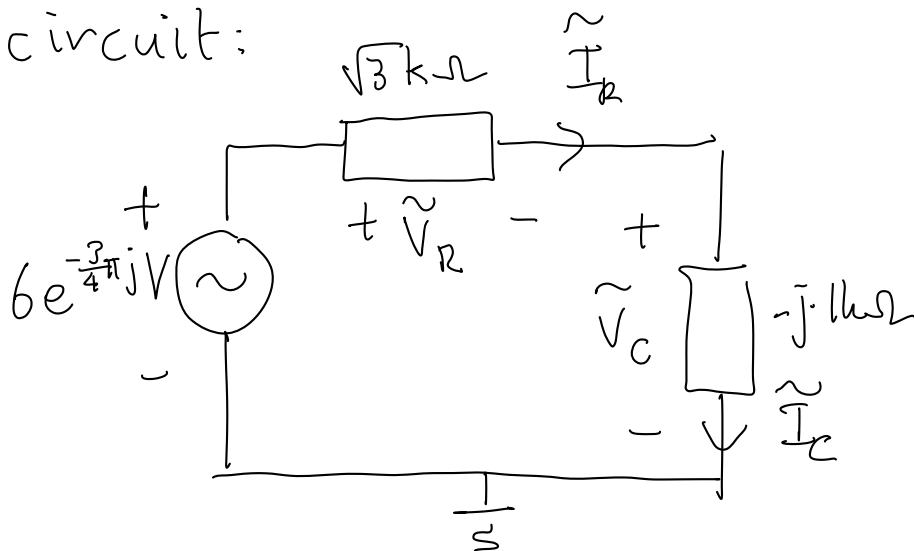

### Questions


Are all  $Z$ 's in units of ohms?  
 $\Rightarrow$  Yes

Why are  $Z_R$  &  $Z_C$  (later  $Z_L$ )

$\omega$  dependent?

$\Rightarrow$  Responds differently to changing voltages/currents of different speeds/rates (derivative of current/derivative of voltage in  $L$  &  $C$ )

Labeled circuit:

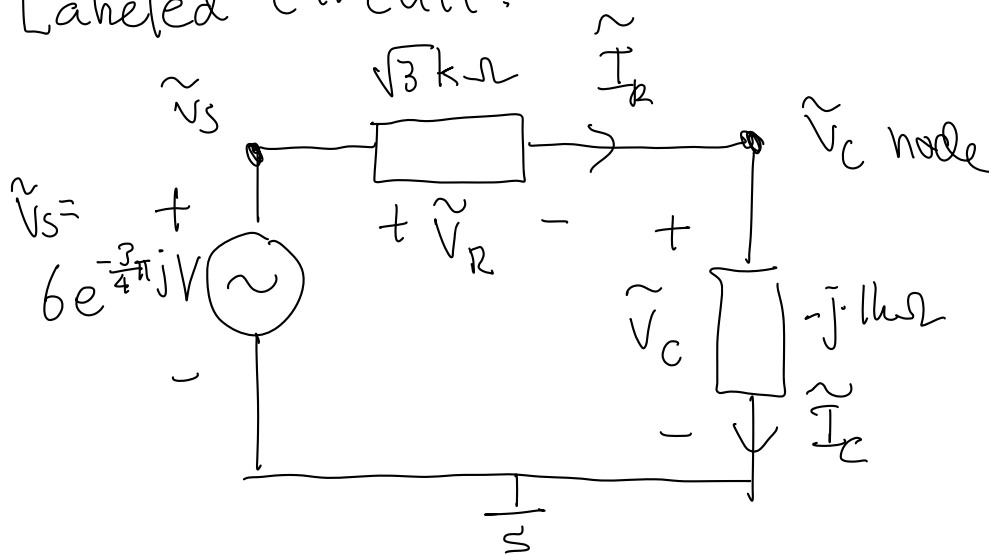

Questions

Q: Where is  $z_R, z_C$  from?

A: Derived in lecture, notes ( $z_C$  in 9/21/21 lecture)

Take as given that KCL, KVL applies (needs proof though)

(d) Step 3: Cast the branch and element equations in the phasor domain. (KVL, KCL, ohm's)

The previous subpart gave us a concrete relation we can use in the phasor domain to relate the voltages of the circuit elements. Specifically, we know that  $\tilde{v}_S = \tilde{v}_R + \tilde{v}_C$ .

Now, we must substitute in the voltage phasors corresponding to these terms, using the element impedances given in Step 2. At this point, feel free to leave the terms symbolic; in the next part, we will substitute in numbers.

KVL method  
(unknowns: current)

$$\tilde{v}_S = \tilde{v}_R + \tilde{v}_C$$

$$= z_R \tilde{i}_R + z_C \tilde{i}_C$$

"ohm's law"

(KCL @  $\tilde{v}_C$  node:  $\tilde{i}_R = \tilde{i}_C = \tilde{i}$ )

$$\tilde{v}_S = (z_R + z_C) \tilde{i}$$

$$\tilde{i} = \tilde{i}_C = \tilde{i}_R = \frac{\tilde{v}_S}{z_R + z_C} = \frac{6e^{-\frac{3}{4}\pi j} V}{\sqrt{3} k \Omega + (-j1 k \Omega)}$$

KCL method (NVA)  
(unknowns: node voltages)

KCL @  $\tilde{v}_C$  node:

$$\tilde{i}_R = \tilde{i}_C$$

$$\frac{\tilde{v}_S - \tilde{v}_C}{z_R} = \frac{\tilde{v}_C - 0V}{z_C}$$

$$\frac{\tilde{v}_S}{z_R} = \frac{\tilde{v}_C}{z_R} + \frac{\tilde{v}_C}{z_C} \quad \leftarrow \text{(usual NVA)}$$

Note 5 § 7.2 "Prove that KVL holds in phasor domain"

(c) [Practice] As an intermediate step to use in the next subpart, show that the fact that the first equation holds for all  $t$  implies the second equation:

Skipping this for time need this note!

$$v_S(t) = v_R(t) + v_C(t) \quad (6)$$

$$\tilde{v}_S = \tilde{v}_R + \tilde{v}_C \quad (7)$$



KVL equation

$$\tilde{V}_s = \tilde{V}_R + \tilde{V}_C$$

KCL equation

$$\frac{\tilde{V}_s - \tilde{V}_C}{z_R} = \frac{\tilde{V}_C - 0V}{z_C}$$

(e) Step 4: Solve for unknown variables

Solve the equation you derived in Step 3 for  $\tilde{I}$  and  $\tilde{V}_C$ . What is the polar form of  $\tilde{I}$  and  $\tilde{V}_C$ ? The polar form is given by  $Ae^{j\theta}$ , where  $A$  is a positive real number.

Hints:

$$\bullet \frac{\sqrt{3}}{2} - \frac{j}{2} = e^{-j\frac{\pi}{6}}$$

Note: did some work above, read KVL side

$$\begin{aligned} \tilde{I} &= \frac{6e^{-\frac{3}{4}\pi j} V}{\sqrt{3}k\Omega + (-j)k\Omega} = \frac{6e^{-\frac{3}{4}\pi j} V}{2 \cdot k\Omega \left(\frac{\sqrt{3}}{2} - \frac{j}{2}\right)} \\ (\tilde{I} = \tilde{I}_C = \tilde{I}_R) &= \frac{3mA e^{-\frac{3}{4}\pi j}}{e^{-j\frac{\pi}{6}}} \\ &= 3mA e^{-\frac{3}{4}\pi j} e^{j\frac{\pi}{6}} \\ &= 3mA e^{-\frac{9}{12}\pi j + \frac{2\pi}{12}j} \\ &= \boxed{3mA e^{-\frac{7}{12}j\pi}} \end{aligned}$$

$$\begin{aligned} \tilde{V}_C &= z_C \cdot \tilde{I}_C = z_C \tilde{I} \\ &= -j \cdot k\Omega \left( 3mA e^{-\frac{7}{12}j\pi} \right) \\ &= e^{j\frac{\pi}{2}} 3V e^{-\frac{7}{12}j\pi} \\ &= \boxed{3V e^{-\frac{13}{12}j\pi}} \end{aligned}$$

Polar form of  $\tilde{V}_C$ :  $\tilde{V}_C = 3V e^{-\frac{13}{12}j\pi}$

Polar form of  $\tilde{I}_C$ :  $\tilde{I}_C = 3mA e^{-\frac{7}{12}j\pi}$

Questions

Q: Why units (mA, V) before complex exponential?

A: I can carry them as a factor and multiplication is commutative

Q: Is this ckt a LPF? (low pass filter) - is that why our voltage on C has a lower amplitude?

A: Yes!

Q: Does what we did only apply to sinusoidal signals?

A: Yes, and to sums of sinusoidal signals.

Polar form of  $\tilde{V}_C$ :  $\tilde{V}_C = 3V e^{-\frac{13}{12}j\pi}$

Polar form of  $\tilde{I}_C$ :  $\tilde{I}_C = 3mA e^{-\frac{7}{12}j\pi}$

(f) **Step 5: Transform solutions back to time domain**

To return to time domain, we apply the relation between a sinusoidal function and its phasor counterpart. **What is  $i(t)$  and  $v_C(t)$ ? What is the phase difference between  $i(t)$  and  $v_C(t)$ ?**

$$\begin{aligned} V_C(t) &= \underbrace{3V e^{-\frac{13}{12}j\pi}}_{\tilde{V}_C} e^{j\omega t} + \underbrace{3V e^{+\frac{13}{12}j\pi}}_{\tilde{V}_C} e^{-j\omega t} \\ &= 3V \left( e^{j(\omega t - \frac{13}{12}\pi)} + e^{-j(\omega t - \frac{13}{12}\pi)} \right) \\ &= 3V \cdot 2 \cos\left(\omega t - \frac{13}{12}\pi\right) \end{aligned}$$

$$\omega = 1 \frac{\text{krad}}{\text{s}}$$

$$= \boxed{6V \cos\left(1 \frac{\text{krad}}{\text{s}} t - \frac{13}{12}\pi\right)}$$

$$i(t) = \boxed{6 \text{ mA} \cos\left(1 \frac{\text{krad}}{\text{s}} t - \frac{7}{12}\pi\right)}$$

$$-\frac{13}{12}\pi - \left(-\frac{7}{12}\pi\right) = \boxed{-\frac{\pi}{2}}$$

phase diff.

Questions

(g) Now, suppose that instead of wherever we analyzed the phasor as  $\tilde{X}$  (the coefficient associated with the  $e^{j\omega t}$  term), we had instead selected to work with  $\bar{X}$ , or we solved using both  $\tilde{X}$  and  $\bar{X}$ . **How would our answer or problem-solving procedure have changed?**

The answer @ the end doesn't change.

We'd need  $\bar{Z}$  for impedances but otherwise the process (translate, NVA, translate) is the same

## 2. Inductor Impedance

Given the voltage-current relationship of an inductor  $v(t) = L \frac{di(t)}{dt}$ , we want to show that its complex impedance is  $Z_L(j\omega) = j\omega L$ . We will perform this analysis in steps.

A sample inductor circuit is in fig. 3.

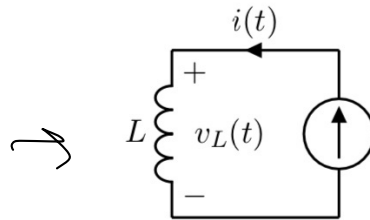


Figure 3: A simple inductor circuit.

- (a) Suppose that the input current source in fig. 3 has value  $i(t) = I_0 e^{st}$ , where  $I_0$  is some (not necessarily real) constant. **What is the corresponding  $s$ -phasor for the current?**

$$\tilde{I} = I_0 \leftarrow s\text{-phasor} \\ (\text{coeff. of } e^{st})$$

- (b) Now, using the governing voltage-current equation for an inductor, **derive the time-domain inductor voltage using the current expression and solve for the corresponding voltage  $s$ -phasor.**

Find  $\tilde{V}$  given that:  $L \frac{dI_L}{dt} = v_L$

$$v_L(t) = L \frac{d}{dt} (I_0 e^{st})$$

$$= L I_0 s e^{st}$$

$$v_L(t) \Rightarrow \tilde{V} = L I_0 s$$

- (c) Using the voltage and current  $s$ -phasors, **solve for the  $s$ -impedance of the inductor  $Z_L(s)$ .** (This is the ratio between these phasor quantities).

$$\frac{\tilde{V}}{\tilde{I}} = Z_L(s) = \frac{L I_0 s}{I_0} = \boxed{sL}$$

(d) Now, suppose that our current source value was instead  $i(t) = I_0 \cos(\omega t + \phi)$ , where  $\omega$  is the frequency of the cosine wave and  $\phi$  is the phase-offset.  $\phi = 0$  corresponds to the standard cosine centered at  $t = 0$ .

Using Euler's formula, represent  $i(t)$  as the sum of two complex exponentials. Using this, Find the new phasor  $\tilde{I}$  associated with the complex exponential  $e^{j\omega t}$ .

$$I_0 \cos(\omega t + \phi) = I_0 \left( \frac{1}{2} e^{j(\omega t + \phi)} + \frac{1}{2} e^{-j(\omega t + \phi)} \right)$$

$$\Downarrow$$

$$\frac{I_0}{2} e^{j\phi} e^{j\omega t} = \tilde{I} = \frac{I_0}{2} e^{j\phi}$$

(e) Same as before, use  $i(t)$  to derive  $v(t)$  and find the new phasor  $\tilde{V}$  associated with the complex exponential  $e^{j\omega t}$ .

$$v_L = L \frac{di_L}{dt} = L I_0 (-\sin(\omega t + \phi) \omega)$$

$$= -L I_0 \omega \sin(\omega t + \phi)$$

$$= -L I_0 \omega \left( \frac{-j}{2} e^{j(\omega t + \phi)} + \frac{j}{2} e^{-j(\omega t + \phi)} \right)$$

$$\Rightarrow L I_0 \omega \frac{j}{2} e^{j\phi} e^{j\omega t}$$

$$\tilde{V} = L I_0 \omega \frac{j}{2} e^{j\phi}$$

(f) Once again, using the voltage and current phasors, solve for the impedance of the inductor  $Z_L(s)$ . Is this the same quantity that we found in the earlier subpart, as expected?

$$Z_L(j\omega) = \frac{\tilde{V}}{\tilde{I}} = \frac{L I_0 \omega \frac{j}{2} e^{j\phi}}{\frac{I_0}{2} e^{j\phi}} = \boxed{j\omega L}$$

Got to here in section  $\downarrow$  read solutions for rest. notes below

