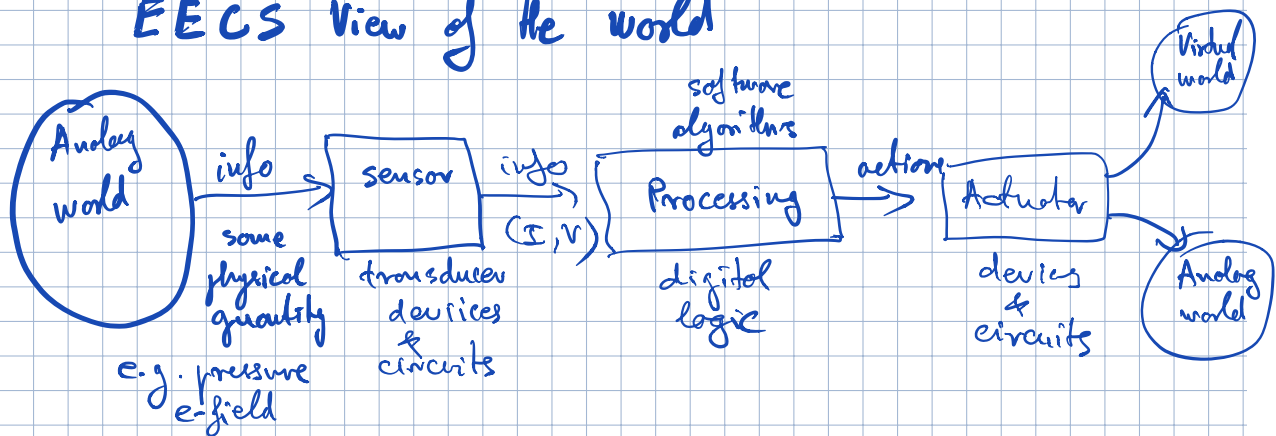



Lecture 1

- * EECS 16B Intro
- * Computing: Transistors & Logic
- * RC models
- * Solving RC circuits

EECS View of the world




16B examples:

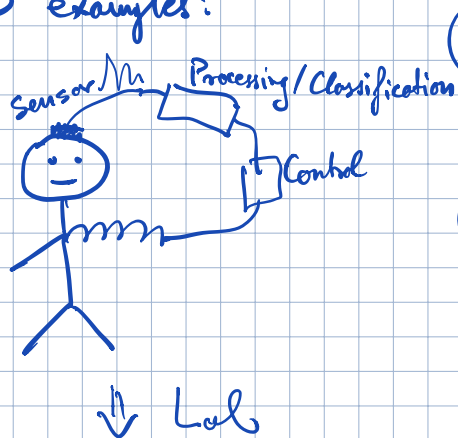

(M1) Sensor: Interface circuits / Diff. eqns

(M2) Control: Feedback

(M3) Processing: Classification SVD/PCA

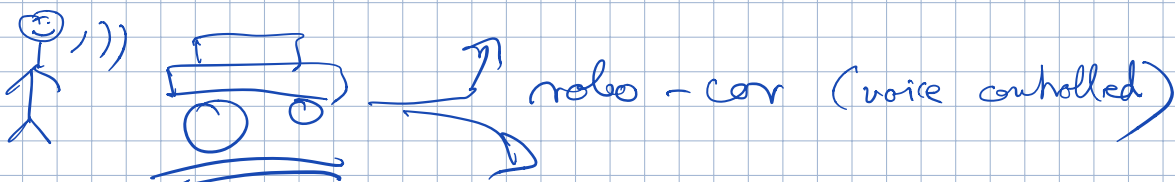


Processing

How do we implement computation?


digital logic \rightarrow distinct voltage levels (e.g. binary)
 logic 0 V_0 & logic 1 V_1

16A:






Switch

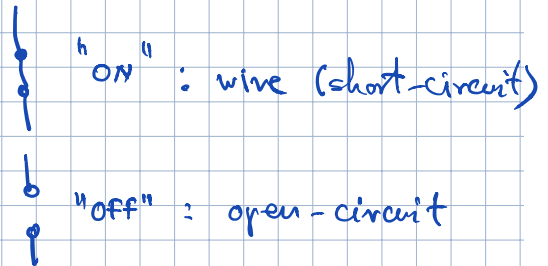

16B: Transistor

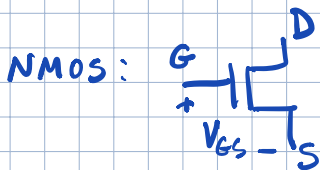

Simple model:

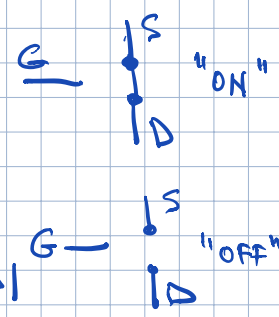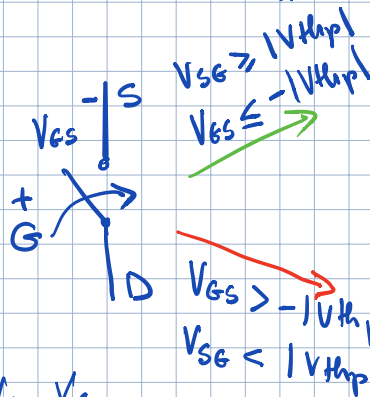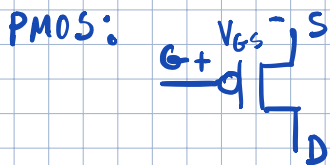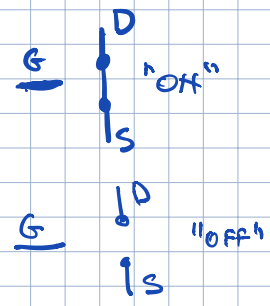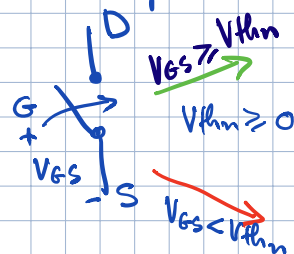


$V_{GS} = -V_{SG}$

$V_{GS} = V_G - V_S$; $V_{SG} = V_S - V_G$


Simplest logic gate :

an inverter

"logic symbol"

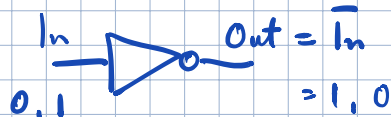


schematic :

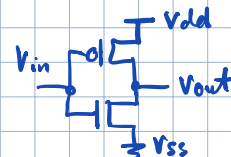

13

How does it work?

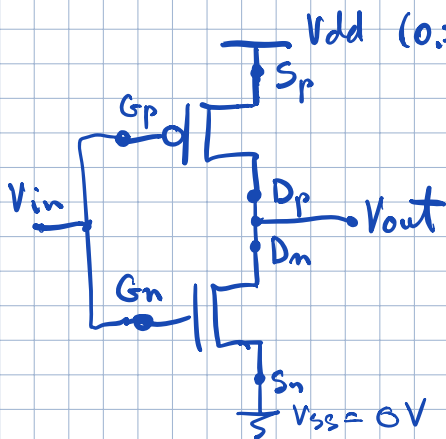


$$V_{thn} + |V_{thp}| \geq V_{dd} \quad (\text{1GB assumption})$$

$$0 \leq V_{thn} \leq V_{dd}$$

$$0 \leq |V_{thp}| \leq V_{dd}$$


Model:

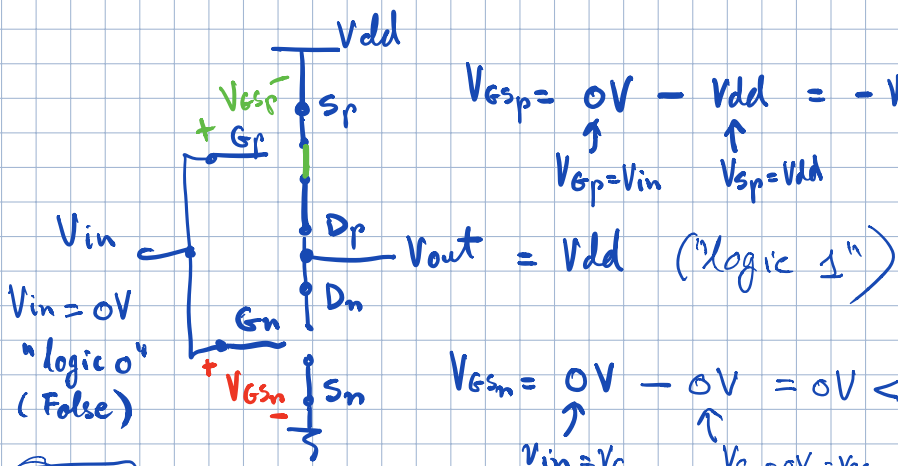

ON PMOS

OFF NMOS

CMOS

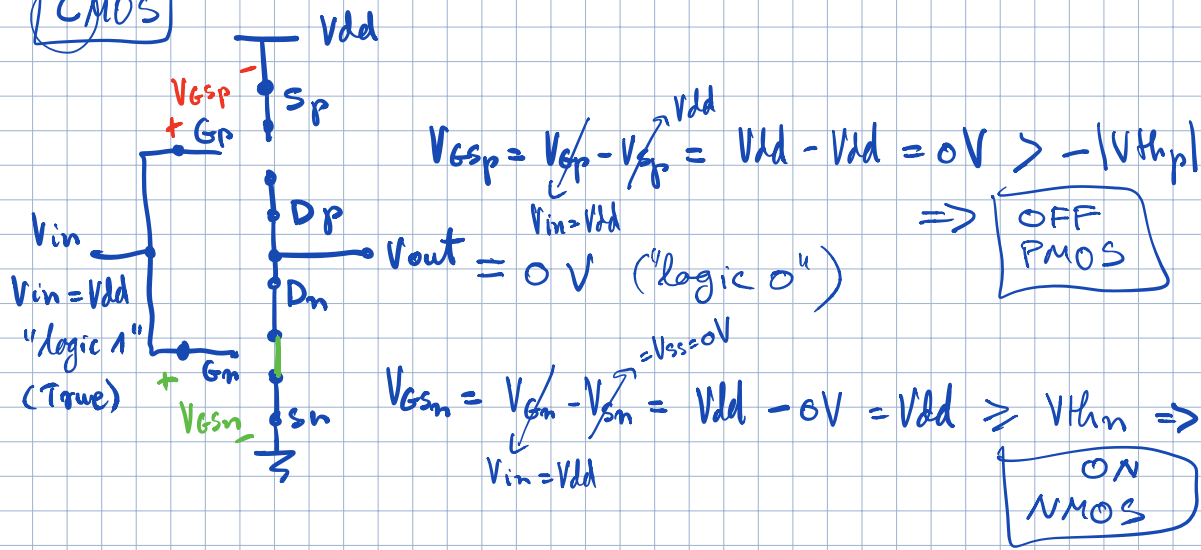

OFF PMOS

ON NMOS

Truth table:

| | V_{in} | V_{out} |
|-----------|-----------------|---------------------------|
| "logic 0" | 0V | V _{dd} (logic 1) |
| "logic 1" | V _{dd} | 0V (logic 0) |

Boolean math


| In | Out |
|----|-----|
| 0 | 1 |
| 1 | 0 |

inverter
out = \overline{In}


NAND , NOR
 Out = $\overline{A \cdot B}$ Out = $\overline{A + B}$

Let's make a processor : Cascading logic

Simple model:

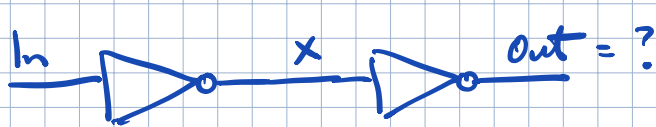

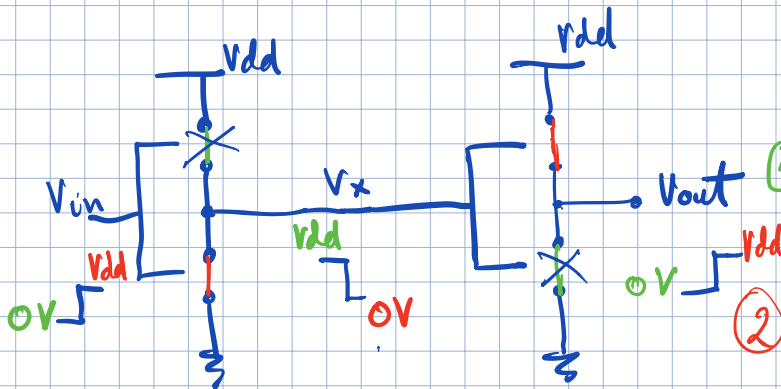$x = \overline{In}$
 Out = \overline{x}
 Out = $\overline{\overline{In}} = In$



State:

(1) $V_{in} = 0V \Rightarrow V_{p} = V_{dd} \Rightarrow V_{out} = 0V$

(2) $V_{in} = V_{dd} \Rightarrow V_{n} = 0V \Rightarrow V_{out} = V_{dd}$

It looks like this process is instantaneous!




Would make a super-fast processor & super cool!

Not real! ☹️

Need to look at how a device is made to make a better model.

ps

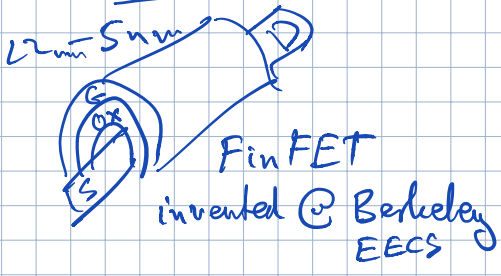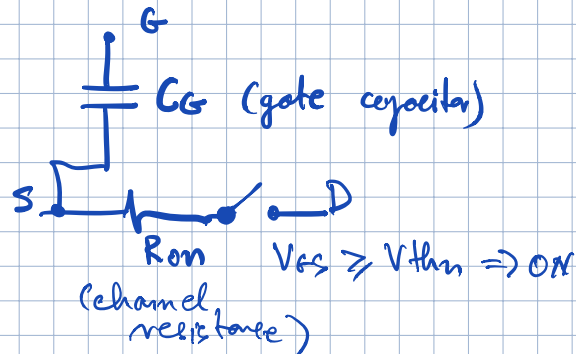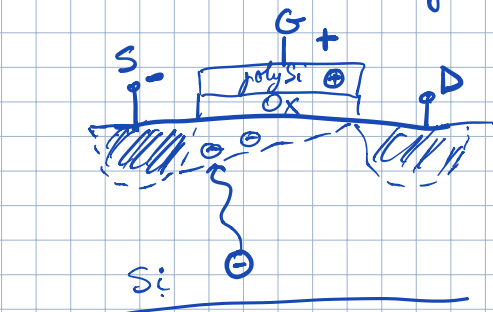NMOS (n-channel metal-oxide semiconductor field effect transistor)



To analyze this model
need to understand RC
circuits.