


## Lecture 2

\* Computing: Transistors & Logic

\* RC models

\* Solving RC circuits

\* RC transients

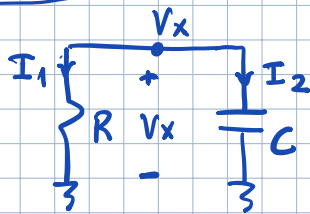

Elements:

$$I_2 = C \cdot \frac{dV_x}{dt}$$

$$V_x = I_1 \cdot R$$

KCL:

$$I_1 + I_2 = 0$$

$$I_1 = \frac{V_x}{R}, \quad I_2 = C \frac{dV_x}{dt} \quad \xRightarrow{\text{KCL}} \quad \frac{V_x}{R} + C \frac{dV_x}{dt} = 0$$

$t \geq 0$   
 $\Rightarrow$

$$\frac{dV_x}{dt} = -\frac{V_x}{RC} \quad (\text{differential equation})$$

① Guess:  $V_x(t) = a \cdot e^{bt}$

(educated guess based on the behavior/properties of the  $\frac{d}{dt} V_x$ )

$$V_x(0) = a \cdot e^{b \cdot 0} = a$$

↑  
initial state


$$\frac{d}{dt} V_x(t) = \frac{d}{dt} (a \cdot e^{bt}) = a \cdot b \cdot e^{bt} = b \cdot V_x(t)$$

$$\Rightarrow \frac{d}{dt} V_x(t) = -\frac{V_x(t)}{RC} \quad \text{and}$$

$$\frac{d}{dt} V_x(t) = b \cdot V_x(t)$$

$$\Rightarrow \boxed{b = -\frac{1}{RC}}$$
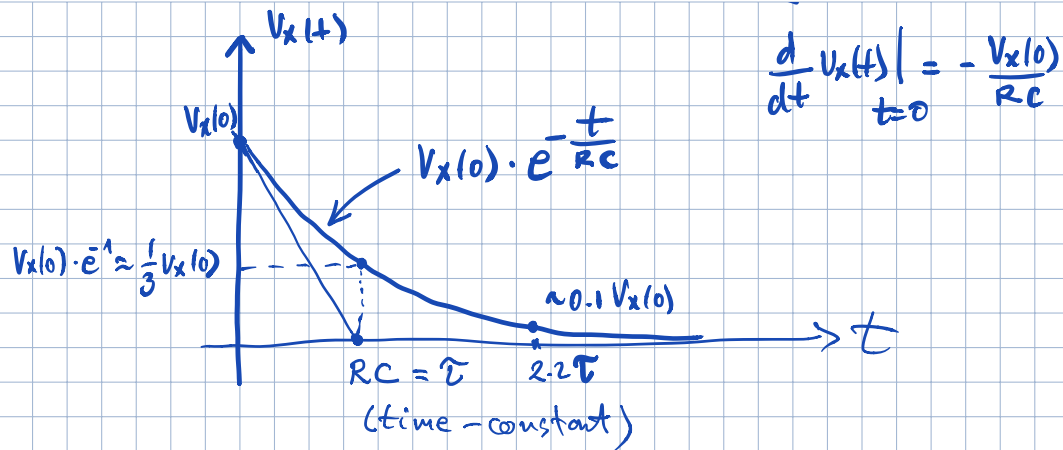
$$\boxed{V_x(t) = V_x(0) \cdot e^{-\frac{t}{RC}}}$$



② Check for uniqueness of the guess:

Suppose  $y(t)$  which also solves.

Shorter notation:  $x(0) = x_0$  (1)

$$\frac{d}{dt} x(t) = \lambda \cdot x(t) \quad (2) \quad \leftarrow$$

In ① Guesst & checked that  $x_d(t) = x_0 \cdot e^{\lambda t}$ ,  $t \geq 0$  satisfies (1) & (2).

Need to show  $y(t) = x_d(t)$ .

Either prove  $\frac{y(t)}{x_d(t)} = 1$  or  $y(t) - x_d(t) = 0$

$$\frac{y(t)}{x_d(t)} = \frac{y(t)}{x_0 \cdot e^{\lambda t}}$$

$$\left[ \frac{d}{dt} y(t) = \lambda \cdot y(t) \right]$$

since  $y(t)$  is also a solution

$$\frac{d}{dt} \left( \frac{y(t)}{x_d(t)} \right) = \frac{d}{dt} \left( \frac{y(t)}{x_0 e^{\lambda t}} \right) = \frac{1}{x_0} \frac{d}{dt} (y(t) e^{-\lambda t}) =$$

$$= \frac{1}{x_0} \left( \frac{d}{dt} y(t) \cdot e^{-\lambda t} + y(t) (-\lambda) \cdot e^{-\lambda t} \right)$$

$$= \frac{1}{x_0} \left( \lambda y(t) e^{-\lambda t} - \lambda \cdot y(t) \cdot e^{-\lambda t} \right) = 0$$

$$\frac{d}{dt} \left( \frac{y(t)}{x_d(t)} \right) = 0 \Rightarrow \boxed{\frac{y(t)}{x_d(t)} = a} \quad (\text{constant})$$

$t \geq 0$


From (1)  $x(0) = X_0$   
 $y(0) = X_0$  since  $y$  is also a solution

$$\frac{y(0)}{x_d(0)} = \frac{\cancel{y(0)} \rightarrow X_0}{\underset{\uparrow}{x_0} \cdot \cancel{e^{j\omega t}} = 1} = \boxed{1 = a}$$

$$\frac{y(t)}{x_d(t)} = 1 \quad x_d(t) = y(t)$$


( $x_d(t)$  is unique)

More complete proof in disc / hw.

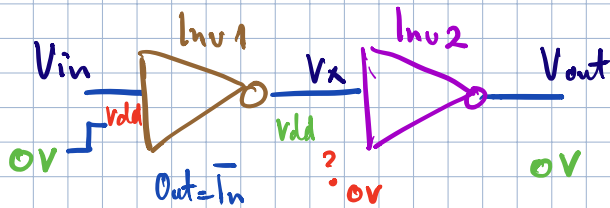




Logic view



↓ Schematic

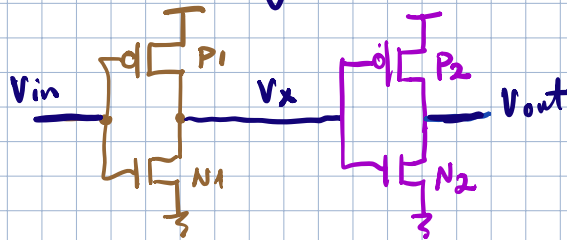


Implementation  
 Circuit (CMOS view)  
 more in IS1

↓ Model (RC)

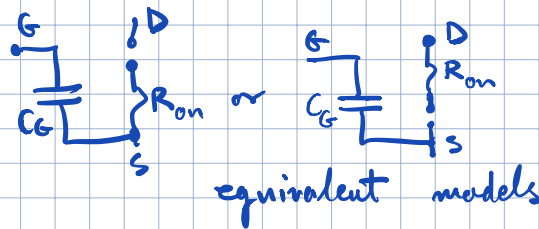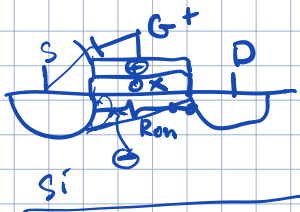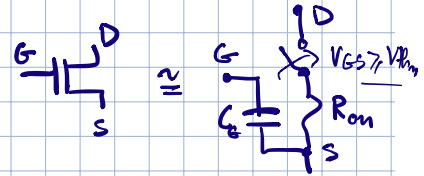

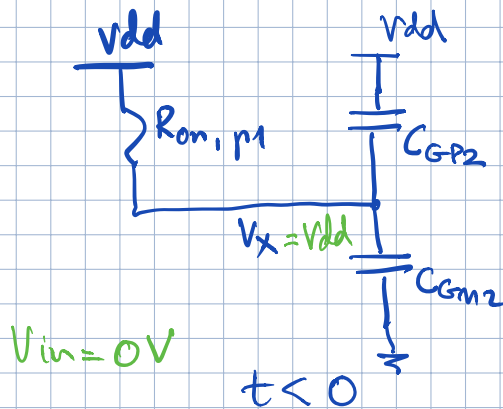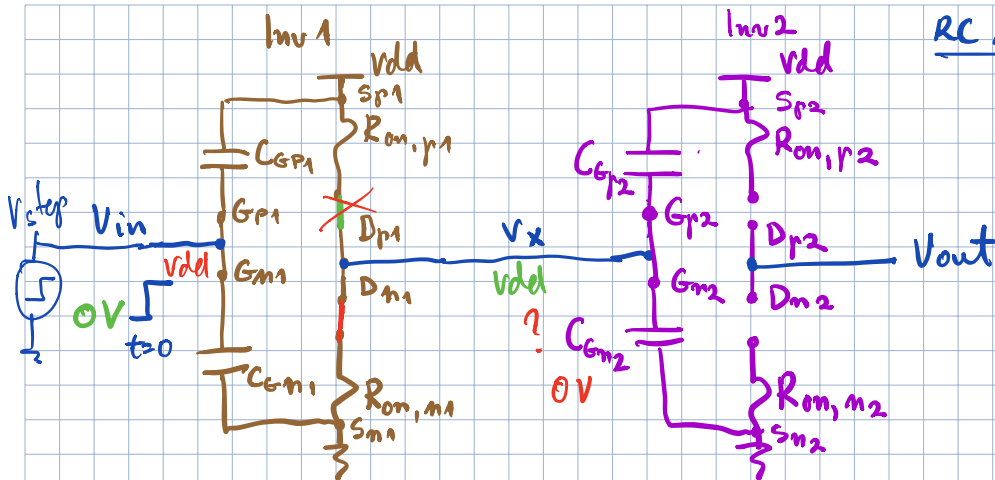

$\Rightarrow$   
 $t = 0$

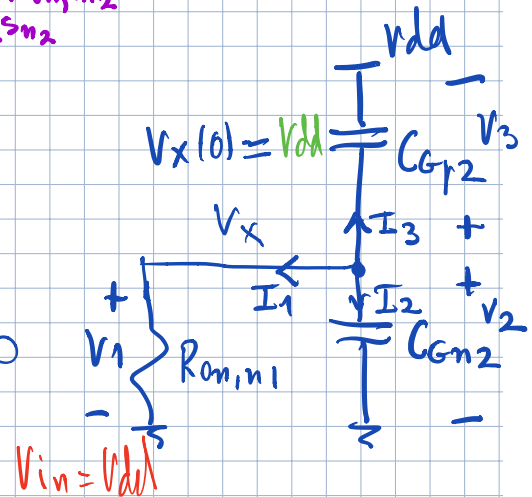

KCL:  $I_1 + I_2 + I_3 = 0$

Elements:  $V_1 = I_1 \cdot R_{on,m1}$

$$I_2 = C_{gm2} \cdot \frac{dV_2}{dt}$$

$$I_3 = C_{gp2} \cdot \frac{dV_3}{dt}$$

$$V_1 = V_x$$

$$V_2 = V_x$$

$$V_3 = V_x - V_{dd}$$

$$V_x(0) = V_{dd}$$

---

KCL:

$$\underbrace{\frac{V_1}{R_{on,m1}}}_{I_1} + \underbrace{C_{gm2} \frac{dV_2}{dt}}_{I_2} + \underbrace{C_{gp2} \frac{dV_3}{dt}}_{I_3} = 0$$

$$\frac{V_x}{R_{on, n1}} + C_{Gn2} \frac{dV_x}{dt} + C_{Gp2} \cdot \frac{d}{dt} (V_x - V_{dd}) = 0$$

$$\frac{V_x}{R_{on, n1}} + C_{Gn2} \frac{dV_x}{dt} + C_{Gp2} \frac{dV_x}{dt} = 0$$

$$\frac{V_x}{R_{on, n1}} + (C_{Gn2} + C_{Gp2}) \frac{dV_x}{dt} = 0$$


$$\frac{dV_x}{dt} = - \frac{V_x}{R_{on, n1} \cdot (C_{Gn2} + C_{Gp2})}$$

$$V_x(t) = V_x(0) \cdot e^{-\frac{t}{\tau}}, \quad \tau = R_{on, n1} \cdot (C_{Gn2} + C_{Gp2})$$

$$V_x(0) = V_{dd} \Rightarrow$$


$$V_x(t) = V_{dd} \cdot e^{-\frac{t}{\tau}}$$

$t \geq 0$

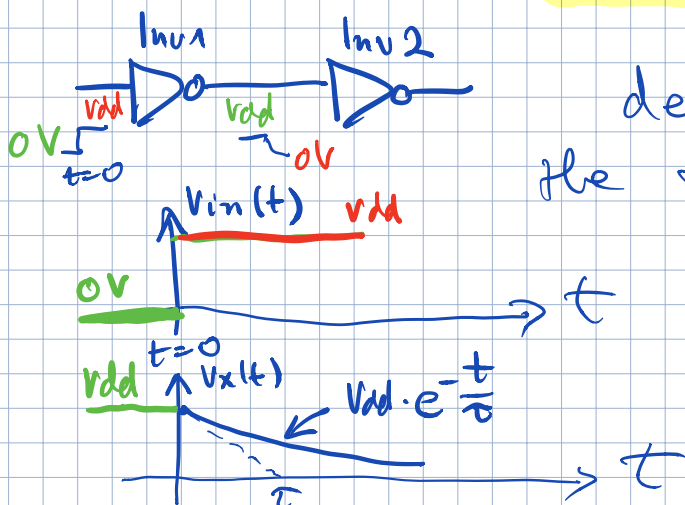

determines  
the speed of the transition

$$\tau_1 < \tau_2 < \tau_3$$

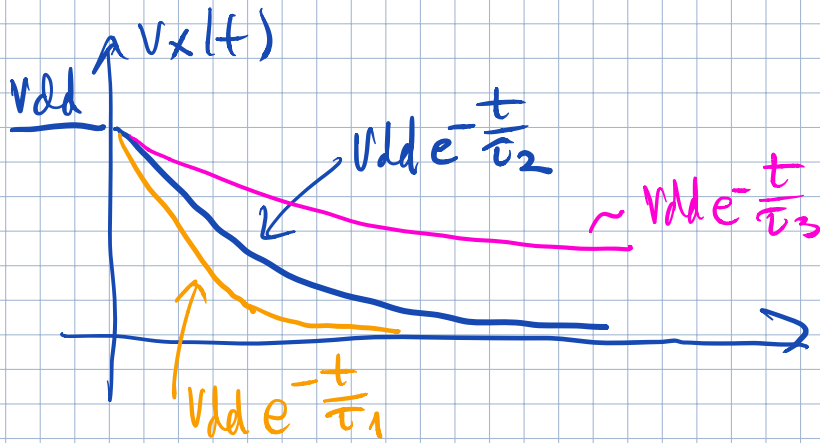

$$\tau = R_{on} \cdot (C_m + C_p)$$

For computer to be faster  $\tau \downarrow$   
Moore's law transistor scaling.