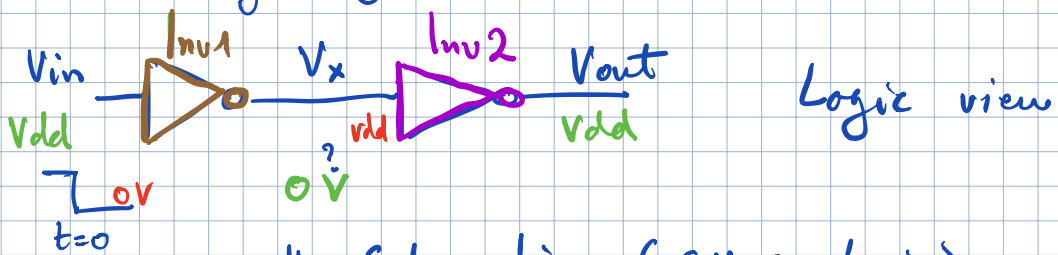



Lecture 3

- * Computing : Transistors & Logic
- * RC transients
- * Non-homogeneous diff. eqns
- * constant input
- * piece-wise constant input
- * Continuous input
- * sensing ←


Cascading logic example:





Schematic (CMOS logic)

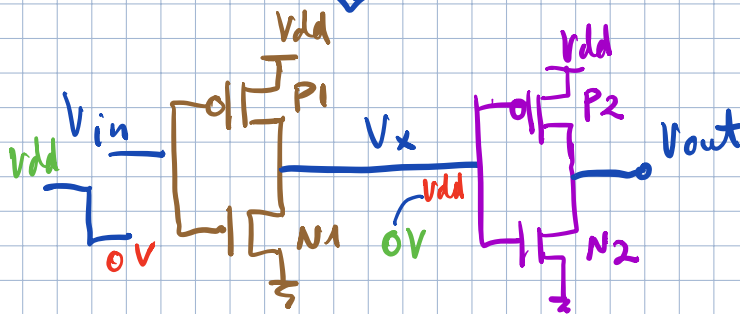

RC model

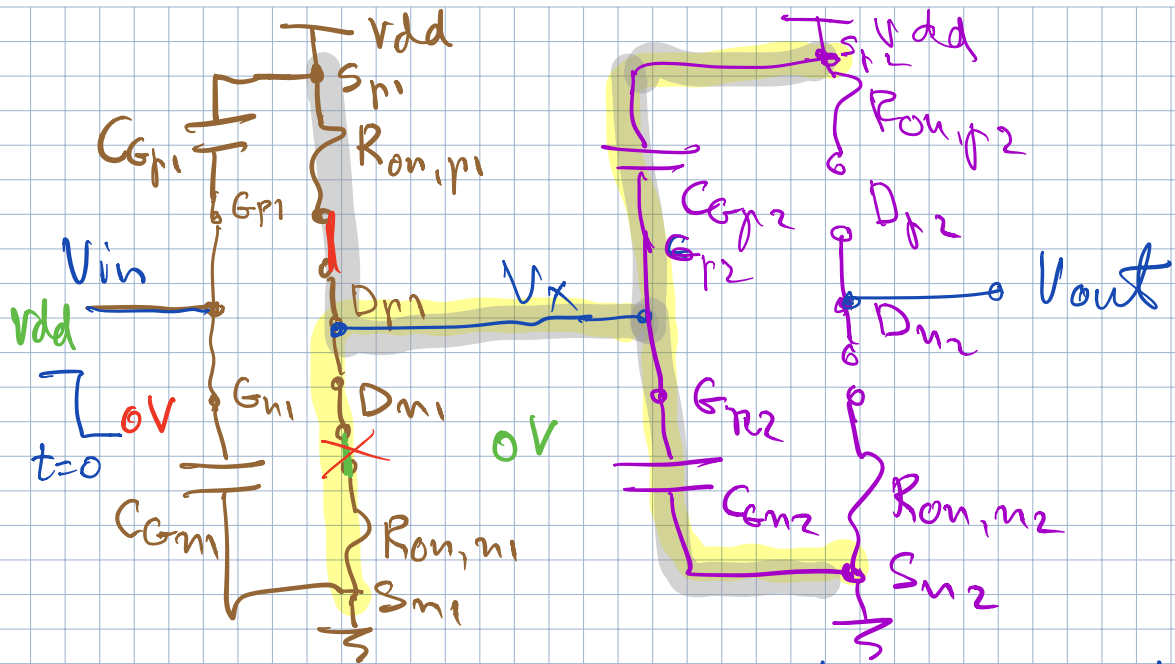

$V_{in} = V_{dd}$
 N_1 on
 P_1 off

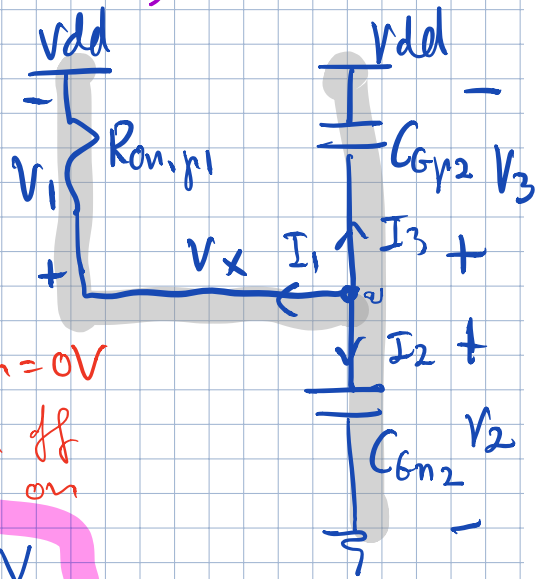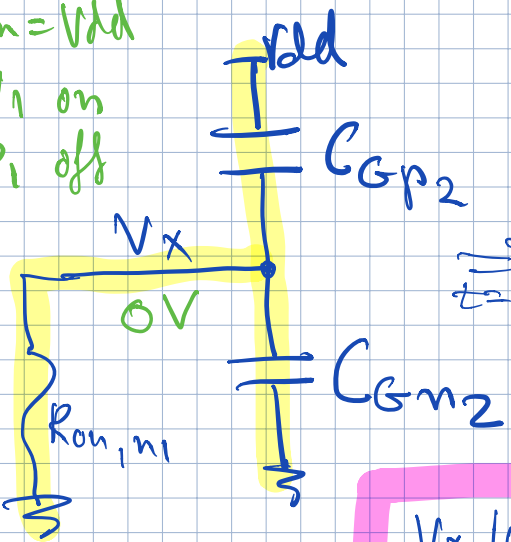

$V_{in} = 0V$
 N_1 off
 P_1 on
 $V_x(0) = 0V$

KCL: $I_1 + I_2 + I_3 = 0$

Elements :

$V_1 = I_1 \cdot R_{on,p1}$

$V_1 = V_x - V_{dd}$

$I_2 = C_{gn2} \cdot \frac{dV_2}{dt}$

$V_2 = V_x$

$I_3 = C_{gp2} \cdot \frac{dV_3}{dt}$

$V_3 = V_x - V_{dd}$

$$\frac{V_1}{R_{on, p1}} + C_{Gn2} \frac{dV_2}{dt} + C_{Gp2} \frac{dV_3}{dt} = 0$$

\uparrow \uparrow \uparrow
 I_1 I_2 I_3

$$\frac{V_x - V_{dd}}{R_{on, p1}} + C_{Gn2} \frac{dV_x}{dt} + C_{Gp2} \frac{d(V_x - V_{dd})}{dt} = 0$$

$$\frac{V_x - V_{dd}}{R_{on, p1}} + C_{Gn2} \frac{dV_x}{dt} + C_{Gp2} \frac{dV_x}{dt} = 0 \quad \left[\frac{d}{dt} V_{dd} = 0 \right]$$

$$(1) \quad \frac{V_x - V_{dd}}{R_{on, p1}} + (C_{Gn2} + C_{Gp2}) \frac{dV_x}{dt} = 0$$

$$\frac{dV_x}{dt} = - \underbrace{\frac{V_x}{R_{on, p1} (C_{Gn2} + C_{Gp2})}}_{\text{homogeneous term}} + \underbrace{\frac{V_{dd}}{R_{on, p1} (C_{Gn2} + C_{Gp2})}}_{\text{non-homogeneous}}$$

Form:

$$\frac{d}{dt} x(t) = \lambda x(t) + a \quad (\text{non-homogeneous})$$

$$\frac{d}{dt} x(t) = \lambda x(t) \quad (\text{homogeneous})$$

Going back to (1)

$$\frac{V_x - V_{dd}}{R_{on,p1}} + (C_{on2} + C_{op2}) \frac{d}{dt} (V_x - V_{dd}) = 0$$

$$\hat{V}_x = V_x - V_{dd}$$

$$\frac{\hat{V}_x}{R_{on,p1}} + (C_{on2} + C_{op2}) \frac{d}{dt} \hat{V}_x = 0$$

$$\frac{d\hat{V}_x}{dt} = - \frac{\hat{V}_x}{R_{on,p1} (C_{on2} + C_{op2})}$$

$$\tau = R_{on,p1} (C_{on2} + C_{op2})$$

homogeneous

diff. eqn.

to \Rightarrow I know how to solve it 😊

$$\hat{V}_x(t) = \hat{V}_x(0) e^{-\frac{t}{\tau}}$$





$$\hat{V}_x = V_x - V_{dd}$$

$$V_x(t) - V_{dd} = (V_x(0) - V_{dd}) e^{-\frac{t}{\tau}}$$


$$V_x(t) = V_{dd} (1 - e^{-\frac{t}{\tau}})$$

$$V_x(0) =$$

$$t \geq 0$$

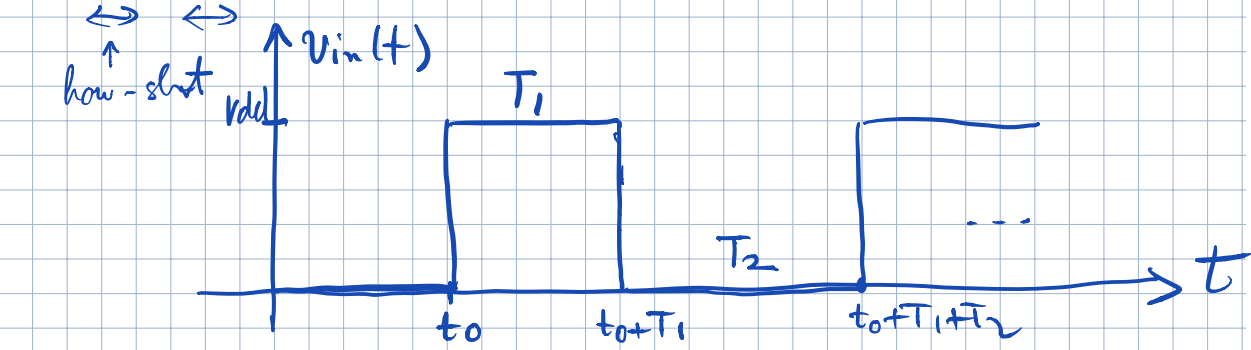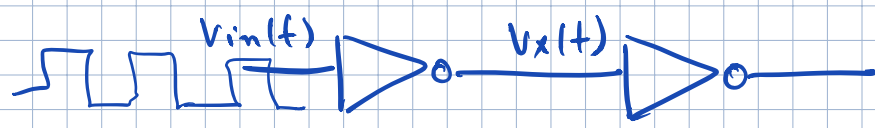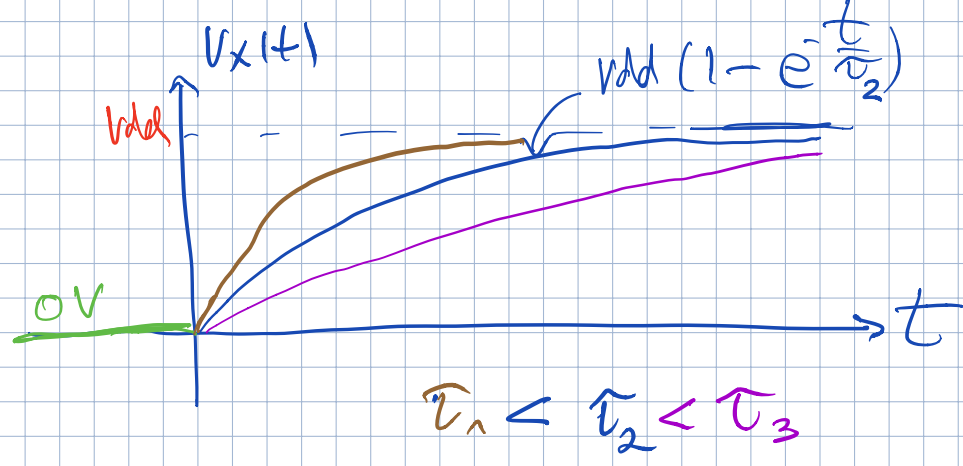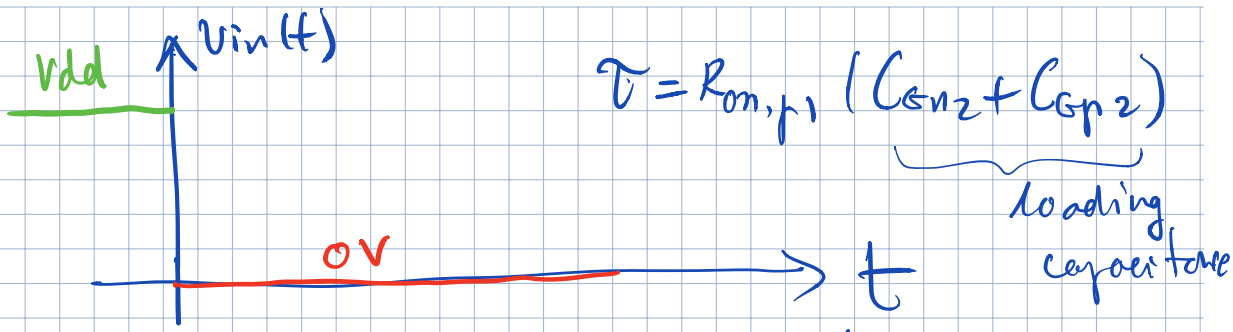

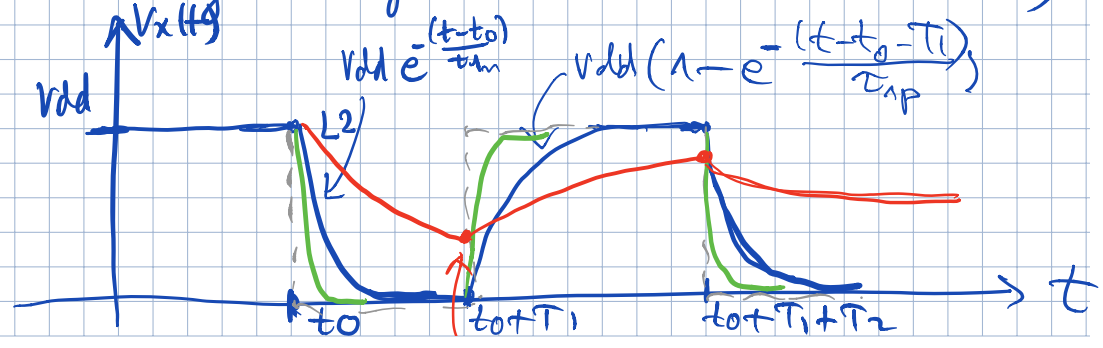Will $V_x(t)$ be able to follow these changes as a "logic" signal (to reach $0V$ or V_{dd})



$$\tau_{2m} < \tau_{1m} < \tau_{3m}$$

$$\tau_{2p} < \tau_{1p} < \tau_{3p}$$

limit condition is
 $v_x(t_0 + T_1)$ for $t \geq t_0 + T_1$
 $t_0 + T_1 + T_2$


Use the previous $v_x(t)$ solution as an initial value for the next interval.

Solutions for the piece-wise constant input.

Form:

$$\frac{d}{dt} x(t) = \lambda x(t) - \lambda u(t) \leftarrow \begin{matrix} \text{constant} \\ \text{or} \\ \text{piece-wise constant} \end{matrix}$$

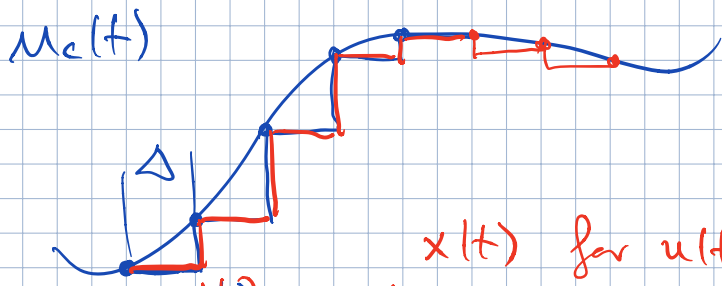want to solve for $u(t) = u_c(t)$
 ↑ continuous in time



$$u(t) \neq u_c(t)$$




$$u(t) \rightarrow u_c(t) \quad \Delta \rightarrow 0$$

$x(t)$ for $u(t)$
 $u(t) = \text{const}, t \in [t_0, t_0 + \Delta)$
 iterate & use the previous solution as initial condition ...
 in the end $\Delta \rightarrow 0$ (disc + hwr)

Why do we want to know

The response to continuous input?

EECS (16A/B) Pipeline

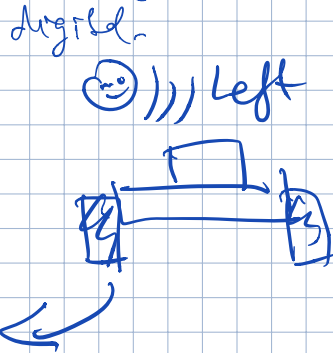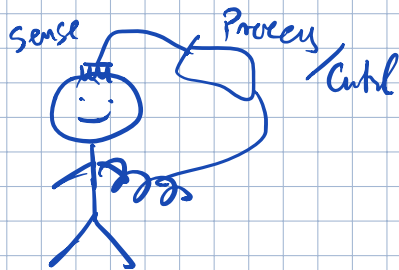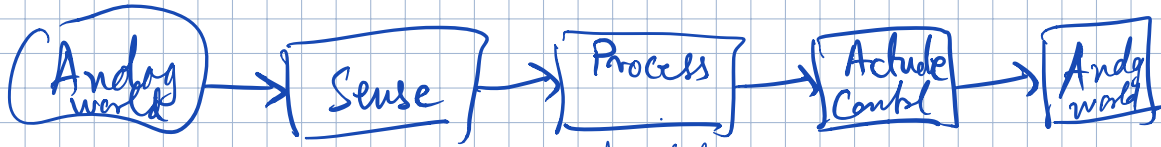

Sensing:

brain signals

or voice signals


signal of interest



+

interference

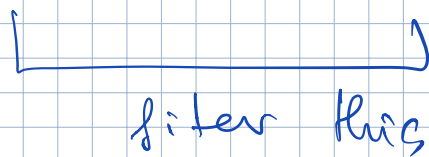~~(AC power, wifi/cellular
RF
FM radio ...
others speaking,
unwanted)~~



Goal: Filter (select) signals of interest

How can a circuit become a filter / process the signal?