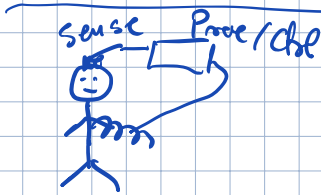


# Lecture 4

\* Sensing

\* Non-homogeneous diff. eqns.  
 & with continuous inputs



signals of interest



retain

+

~~interference~~


~~(AC power, wifi, cellubs, FM, AM ...)~~



~~filter-out~~

Goal: Filter (select) signals of interest

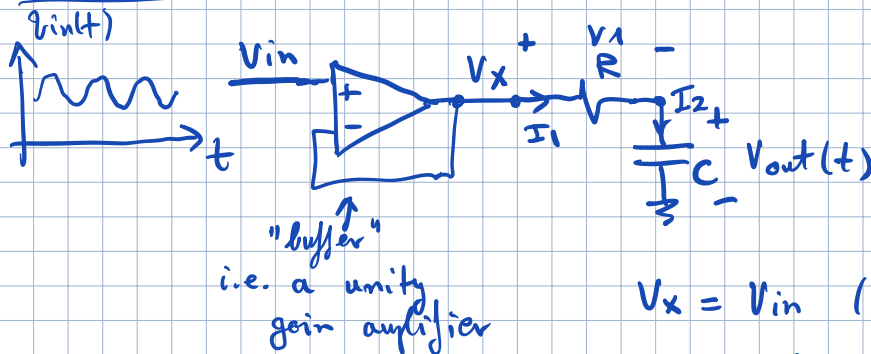How can a circuit do this "computation" ?



KCL:  $I_1 = I_2$

$V_x = V_{in}$  (buffer)

$V_1 = V_x - V_{out}$

$V_1 = I_1 \cdot R$

$I_2 = C \cdot \frac{dV_{out}}{dt}$

} Elements

$$\frac{V_{in} - V_{out}}{R} = C \frac{dV_{out}}{dt}$$

NVA  
nodal voltage  
analysis

$$\frac{dV_{out}(t)}{dt} = -\frac{V_{out}(t)}{RC} + \frac{V_{in}(t)}{RC}$$

continuous  
input  $\int_0^t$

In disc. & low:

$$V_{out}(t) = V_{out}(0) e^{-\frac{t}{RC}} + \frac{1}{RC} \int_0^t v_{in}(\theta) e^{-\frac{1}{RC}(t-\theta)} d\theta$$

homogeneous  
solution  
"response to init.  
condition"

non-homogeneous soln.  
"response to time-varying  
input"

The circuit "computes" this solution  $\int_0^t$

General form:  $\frac{d}{dt} x(t) = \lambda x(t) - \lambda u(t)$ ,  $\lambda = -\frac{1}{RC}$   
 $u(t) = v_{in}(t)$

Let's try to "compute" the response  
for some  $u(t)$ 's of interest.

Example 1:  $u(t) = e^{st}$

$$(1) \frac{d}{dt} x(t) = \lambda x(t) - \lambda u(t), \quad t \geq 0$$

$$s \neq \lambda$$

can solve:

$$\begin{aligned} x(t) &= x(0) e^{\lambda t} - \lambda \int_0^t u(\theta) e^{\lambda(t-\theta)} d\theta \\ &= x(0) e^{\lambda t} - \lambda e^{\lambda t} \int_0^t \underbrace{e^{s\theta} \cdot e^{-\lambda\theta}}_{e^{(s-\lambda)\theta}} d\theta \end{aligned}$$

⋮

or Guess & check:

$$x(t) = k \cdot e^{st}, \quad t \geq 0$$

$$\text{From (1)} \quad k \cdot s \cdot e^{st} = \lambda \cdot k e^{st} - \lambda \cdot e^{st}$$

$$ks = \lambda k - \lambda$$

$$k = -\frac{\lambda}{s-\lambda} \Rightarrow x(t) = \frac{-\lambda}{s-\lambda} \cdot e^{st}$$

To complete, add a homogeneous soln.

$$k_2 e^{\lambda t}$$

$$x(t) = k_2 e^{\lambda t} + \underbrace{k \cdot e^{st}} \leftarrow$$

$$x(0) = k_2 + k \Rightarrow k_2 = x(0) - k$$

$$x(t) = (x(0) + \frac{\lambda}{s-\lambda}) e^{\lambda t} - \frac{\lambda}{s-\lambda} e^{st}$$

Example 2:  $u(t) = \cos(\omega t)$

$$\frac{d}{dt} x(t) = \lambda x(t) - \lambda u(t)$$

Our RC system  
 $\lambda = -\frac{1}{RC}$

$$x(t) = x(0) e^{\lambda t} - \lambda \int_0^t u(\theta) e^{\lambda(t-\theta)} d\theta \quad \text{Formula}$$

$$= x(0) e^{\lambda t} - \lambda e^{\lambda t} \int_0^t u(\theta) e^{-\lambda \theta} d\theta$$

$$= x(0) e^{\lambda t} - \lambda e^{\lambda t} \int_0^t \cos(\omega \theta) e^{-\lambda \theta} d\theta$$

$$\int \cos(bx) \cdot e^{ax} dx = \frac{e^{ax}}{a^2 + b^2} (b \sin(bx) + a \cos(bx))$$

$$x(t) = x(0)e^{\lambda t} - \lambda e^{\lambda t} \left( \frac{e^{-\lambda t}}{\lambda^2 + \omega^2} (\omega \sin(\omega t) - \lambda \cos(\omega t)) - \frac{1}{\lambda^2 + \omega^2} (0 - \lambda) \right)$$

$$= x(0)e^{\lambda t} - \frac{\lambda}{\lambda^2 + \omega^2} (\omega \sin(\omega t) - \lambda \cos(\omega t)) - \frac{\lambda^2 e^{\lambda t}}{\lambda^2 + \omega^2}$$

$$x(t) = \underbrace{\left( x(0) - \frac{\lambda^2}{\lambda^2 + \omega^2} \right) e^{\lambda t}}_{\textcircled{1}} - \frac{\lambda (\omega \sin(\omega t) - \lambda \cos(\omega t))}{\lambda^2 + \omega^2}$$

$t \rightarrow \infty$   $\textcircled{1}$  (steady-state)  $\textcircled{2}$   $\lambda < 0$   $\lambda = -\frac{1}{RC}$

$\textcircled{1} \rightarrow 0$  b.c.  $\lambda < 0$ ,  $\lambda = -\frac{1}{RC}$

$$\textcircled{2} \quad \lambda = -\frac{1}{RC}$$

$$x(t) = \frac{\frac{1}{RC} \cdot \omega \sin(\omega t) + \left(\frac{1}{RC}\right)^2 \cos(\omega t)}{\left(\frac{1}{RC}\right)^2 + \omega^2}$$

$$= \frac{\omega RC \sin(\omega t) + \cos(\omega t)}{1 + (\omega RC)^2}$$

Case 1:  $\omega \gg \frac{1}{RC}$   
 $\Downarrow$   
 $\omega RC \gg 1$   
 $x(t) \approx 0$

Remember:

$$u(t) = \cos(\omega t)$$


$\omega$  - angular frequency

$$\omega = \frac{2\pi}{T} = 2\pi \cdot f$$

$T$  - period


Case 2:  $\omega \ll \frac{1}{RC}$   
 $\Downarrow$   
 $\omega RC \ll 1$

$$x(t) = \cos(\omega t + \theta)$$

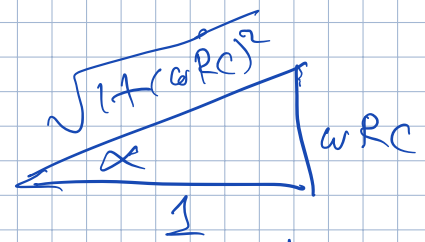

$$\alpha = \arctan(\omega RC, 1)$$

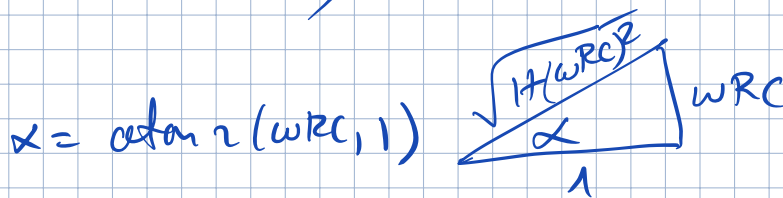"low-pass" filter because  
 it "passes" the low frequencies  
 and attenuates the high frequencies  
 (w.r.t.  $\frac{1}{RC}$ )



$$x(t) = \frac{1}{\sqrt{1+(\omega RC)^2}} \left( \underbrace{\frac{1}{\sqrt{1+(\omega RC)^2}} \cos(\omega t)}_{\cos(\alpha)} + \underbrace{\frac{\omega RC}{\sqrt{1+(\omega RC)^2}} \sin(\omega t)}_{\sin(\alpha)} \right)$$

$$= \frac{1}{\sqrt{1+(\omega RC)^2}} \left( \cos(\alpha) \cos(\omega t) + \sin(\alpha) \sin(\omega t) \right)$$

$$= \frac{1}{\sqrt{1+(\omega RC)^2}} \cos(\omega t - \alpha) \quad \begin{array}{l} \theta = -\alpha \\ \theta = -\arctan 2(\omega RC, 1) \end{array}$$

$$x(t) = \frac{1}{\sqrt{1+(\omega RC)^2}} \cdot \cos(\omega t + \theta)$$

Can also arrive here with a guess:

Guess:  $x(t) = A \cos(\omega t + \theta)$        $u(t) = V_{in} \cos(\omega t)$

System:  $\frac{d}{dt} x(t) = \lambda x(t) - \lambda u(t)$

$$-A\omega \sin(\omega t + \theta) = \lambda \cdot A \cos(\omega t + \theta) - \lambda V_{in} \cos(\omega t)$$

$$V_{in} \cos(\omega t) = A \cos(\omega t + \theta) + \frac{A\omega}{\lambda} \sin(\omega t + \theta)$$

$$= A \left( \cos(\omega t + \theta) + \frac{\omega}{\lambda} \sin(\omega t + \theta) \right)$$

$$\lambda = -\frac{1}{RC}$$

$$\frac{\sqrt{1+(\omega RC)^2}}{\alpha} \omega RC \quad \alpha = \arctan(\omega RC, 1)$$

$$V_{in} \cos(\omega t) = A (1 \cdot \cos(\omega t + \theta) - \omega RC \sin(\omega t + \theta))$$

$$V_{in} \cos(\omega t) = A \sqrt{1+(\omega RC)^2} \left( \frac{\overbrace{1 \cdot \cos(\omega t + \theta)}^{\cos(\alpha)}}{\sqrt{1+(\omega RC)^2}} - \frac{\overbrace{\omega RC \sin(\omega t + \theta)}^{\sin(\alpha)}}{\sqrt{1+(\omega RC)^2}} \right)$$

$$V_{in} \cos(\omega t) = A \sqrt{1+(\omega RC)^2} \cos(\omega t + \theta + \alpha)$$

$$V_{in} = A \sqrt{1+(\omega RC)^2} \Rightarrow A = \frac{V_{in}}{\sqrt{1+(\omega RC)^2}}$$

$$\theta + \alpha = 0 \Rightarrow \theta = -\alpha = -\arctan(\omega RC, 1)$$

$$\left. \begin{array}{l} \cos \alpha \cos \beta - \sin \alpha \sin \beta = \cos(\alpha + \beta) \end{array} \right\}$$

$$x(t) = V_{out}(t) = \frac{V_{in}}{\sqrt{1+(\omega RC)^2}} \cdot \cos(\omega t + \theta)$$

more general:

$$x(t) = x(t_0) e^{\lambda \cdot (t-t_0)} - \lambda \int_{t_0}^t u(\theta) e^{\lambda(t-\theta)} d\theta$$

$t \geq t_0$