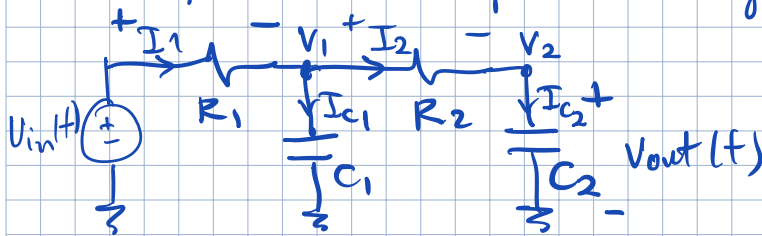


Lecture 5

- * Systems of differential equations
 - * Higher-order d.e.s
 - * Circuits w. multiple c's
 - * Vector DEs
- * Diagonalization

Going to more complex systems - circuits example
simplest two-capacitor example:



$$\text{KCL: } I_1 = I_2 + I_{C1}$$
$$I_2 = I_{C2}$$

$$V_{in} - V_1 = I_1 \cdot R_1$$

$$V_{out} = V_2 - 0 = V_2$$

$$V_1 - V_2 = I_2 \cdot R_2$$

$$I_{C1} = C_1 \frac{dV_1}{dt}, \quad I_{C2} = C_2 \frac{dV_2}{dt}$$

$$I_1 = I_{C2} + I_{C1}$$

from NVA
directly

$$\textcircled{1} \quad \frac{V_{in} - V_1}{R_1} = C_1 \frac{dV_1}{dt} + C_2 \frac{dV_2}{dt}$$

$$\textcircled{2} \quad \frac{V_1 - V_2}{R_2} = C_2 \frac{dV_2}{dt} \Rightarrow V_1 = V_2 + R_2 C_2 \frac{dV_2}{dt}$$

$$R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2} + (R_1 C_1 + R_1 C_2 + R_2 C_2) \frac{dV_2}{dt} + V_2 - V_{in} = 0$$

(2nd order diff. equation)

don't know how to solve it yet

$$\textcircled{1} \quad \frac{V_{in} - V_1}{R_1} = C_1 \frac{dV_1}{dt} + \frac{V_1 - V_2}{R_2}$$

$$\textcircled{2} \quad \frac{V_1 - V_2}{R_2} = C_2 \frac{dV_2}{dt}$$

$$\textcircled{1} \quad \frac{dV_1}{dt} = - \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} \right) V_1 + \frac{V_2}{R_2 C_1} + \frac{V_{in}}{R_1 C_1}$$

$$\textcircled{2} \quad \frac{dV_2}{dt} = \frac{1}{R_2 C_2} V_1 - \frac{1}{R_2 C_2} V_2$$

$$\frac{d}{dt} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} - \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} \right) & \frac{1}{R_2 C_1} \\ \frac{1}{R_2 C_2} & - \frac{1}{R_2 C_2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} \frac{1}{R_1 C_1} \\ 0 \end{bmatrix} V_{in}$$

only know how to solve

$$\frac{d}{dt} x(t) = \lambda x + u$$

Example: Assume: $R_1 = \frac{1}{3} \text{M}\Omega$, $R_2 = \frac{1}{2} \text{M}\Omega$;
 $C_1 = C_2 = 1 \mu\text{F}$

$$(a) \frac{d}{dt} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} 3 \\ 0 \end{bmatrix} v_{in}$$

How about some "magic":

$$(b) u_1 = v_2$$

$$(c) u_2 = v_1 + 2v_2$$

Assume:

$$v_{in} = 1V \quad t < 0$$

$$0V \quad t \geq 0$$

$$v_1(0) = 1V \quad \& \quad v_2(0) = 1V$$

Solving for $t \geq 0$

$$\frac{d}{dt} u_1 \stackrel{(b)}{=} \frac{d}{dt} v_2 \stackrel{(a)}{=} 2v_1 - 2v_2 \stackrel{(c)}{=} 2(u_2 - 2v_2) - 2v_2$$

$$= 2u_2 - 4v_2 - 2v_2 = 2u_2 - 6v_2 = 2u_2 - 6u_1$$

$$(d) \frac{d}{dt} u_1 = 2u_2 - 6u_1$$

$$\frac{d}{dt} u_2 \stackrel{(c)}{=} \frac{d}{dt} (v_1 + 2v_2) = \frac{d}{dt} v_1 + 2 \frac{d}{dt} v_2 \stackrel{(a)}{=}$$

$$= -5v_1 + 2v_2 + 2(2v_1 - 2v_2) =$$

$$= -5v_1 + 2v_2 + 4v_1 - 4v_2 =$$

$$= -v_1 - 2v_2 \stackrel{(c)}{=} -u_2 \quad \text{Whoa!}$$

$$(e) \frac{d}{dt} u_2 = -u_2 \quad (\text{homogenous}) \quad \text{Know how to solve } u_2.$$

$$\Rightarrow u_2(t) = u_2(0) e^{-t}, \quad t \geq 0$$

$$u_2(0) \stackrel{(c)}{=} V_1(0) + 2V_2(0) = 1V + 2 \cdot 1V = 3V$$

$$(f) \quad u_2(t) = 3 \cdot e^{-t}, \quad t \geq 0$$

$$(d) \quad \frac{d}{dt} u_1 = 2u_2 - 6u_1$$

$$\frac{d}{dt} u_1 = -6u_1 + 6e^{-t} \stackrel{s=-1}{}, \quad t \geq 0$$

$$\begin{array}{l} \swarrow \\ \lambda = -6 \\ \searrow \\ s = -1 \end{array}$$

Remember:

$$\frac{d}{dt} x(t) = \lambda x(t) - \lambda u(t)$$

where $u(t) = e^{st}$

$$x(t) = k_2 e^{\lambda t} - \frac{\lambda}{s-\lambda} e^{st}$$

$$x(0) = k_2 + \frac{\lambda}{s-\lambda} \quad \downarrow$$

$$u_1(t) = k_2 \cdot e^{-6t} + \frac{6e^{-t}}{-1+6}$$

$$u_1(0) = k_2 + \frac{6}{5}$$

$$u_1(0) \stackrel{(b)}{=} V_2(0) = 1V \Rightarrow k_2 = -\frac{1}{5}$$

$$(g) \quad u_1(t) = -\frac{1}{5} e^{-6t} + \frac{6}{5} e^{-t}$$

have solved for $u_1(t)$ & $u_2(t) \Rightarrow$
 \Rightarrow back-solve for $V_1(t)$ & $V_2(t)$

$$\begin{aligned}
 v_1(t) &\stackrel{(b) \& (c)}{=} u_2(t) - 2u_1(t) \stackrel{(1) \& (g)}{=} \\
 &= 3 \cdot e^{-t} - 2 \left(-\frac{1}{5} e^{-6t} + \frac{6}{5} e^{-t} \right) \\
 &= 3 \cdot e^{-t} + \frac{2}{5} e^{-6t} - \frac{12}{5} e^{-t}
 \end{aligned}$$

$$(h) \quad v_1(t) = \frac{3}{5} e^{-t} + \frac{2}{5} e^{-6t}$$

$$(i) \quad v_2(t) = -\frac{1}{5} e^{-6t} + \frac{6}{5} e^{-t}$$

$$(a) \quad \frac{d}{dt} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \underbrace{\begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix}}_A \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \underbrace{\begin{bmatrix} 3 \\ 0 \end{bmatrix}}_{\vec{b}} v_{in}$$

$$(b) \& (e) \quad \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 2 \end{bmatrix}}_{W^{-1}} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Leftrightarrow \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \underbrace{\begin{bmatrix} -2 & 1 \\ 1 & 0 \end{bmatrix}}_W \begin{bmatrix} u_1 \\ u_2 \end{bmatrix}$$

$$\frac{d}{dt} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \frac{d}{dt} \left(W^{-1} \cdot \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \right) = W^{-1} \frac{d}{dt} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} =$$

$$\stackrel{(a)}{=} \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 2 \end{bmatrix}}_{W^{-1}} \cdot \left(\underbrace{\begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix}}_A \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \underbrace{\begin{bmatrix} 3 \\ 0 \end{bmatrix}}_{\vec{b}} v_{in} \right)$$

$$\frac{d}{dt} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} \stackrel{(*)}{=} \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 2 \end{bmatrix}}_{W^{-1}} \underbrace{\begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix}}_A \underbrace{\begin{bmatrix} -2 & 1 \\ 1 & 0 \end{bmatrix}}_W \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} +$$

$$+ \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 2 \end{bmatrix}}_{W^{-1}} \cdot \underbrace{\begin{bmatrix} 3 \\ 0 \end{bmatrix}}_{\vec{b}} v_{in}$$

$$\frac{d}{dt} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \underbrace{\begin{bmatrix} -6 & 2 \\ 0 & -1 \end{bmatrix}}_{W^{-1}AW} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} + \underbrace{\begin{bmatrix} 0 \\ 3 \end{bmatrix}}_{W^{-1}\vec{b}} v_{in}$$

↑
upper-triangular

⇒ so, we can peel-back the solutions through GE.

Summary: Systems of differential equations

$$(1) \frac{d}{dt} \vec{x}(t) = A \vec{x}(t) + B \vec{u}(t), \quad \vec{x}(0)$$


$\vec{x}(t) = ?$
for $t \geq 0$.

Native \vec{x} coordinates: Variables

"Nice" coordinates $\vec{\tilde{x}}$:

$$(2) \vec{x}(t) = V \vec{\tilde{x}}(t)$$
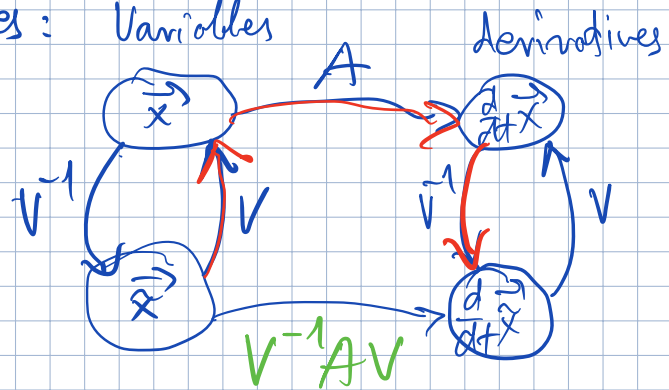
$$(3) \vec{\tilde{x}}(t) = V^{-1} \vec{x}(t)$$



$$\frac{d}{dt} \vec{\tilde{x}}(t) = \frac{d}{dt} (V^{-1} \vec{x}(t)) = V^{-1} \frac{d}{dt} \vec{x}(t) \stackrel{(1)}{=} \vec{v}$$

$$= V^{-1} (A \vec{x}(t) + B u(t)) = V^{-1} A \vec{x}(t) + V^{-1} B u(t) \stackrel{(2)}{=} \vec{w}$$

$$= V^{-1} A V \vec{\tilde{x}}(t) + V^{-1} B u(t)$$

$$(4) \frac{d}{dt} \vec{\tilde{x}}(t) = \underbrace{V^{-1} A V}_{\text{want this matrix to be "nice"}} \vec{\tilde{x}}(t) + V^{-1} B u(t)$$

e.g. upper-triangular \Rightarrow G.E.

or even better \Rightarrow diagonal

$\begin{bmatrix} \bullet & & \\ & \bullet & \\ & & \bullet \end{bmatrix}$ homogeneous. \Rightarrow know how to solve.

