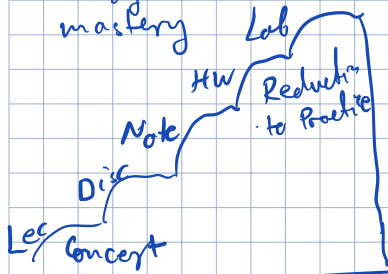


16B Mountain of mastery

Lecture 7



* Intro to inductors

* 2nd order systems with complex eigenvalues

Capacitor

$C \frac{dV}{dt} = I$ $I(t) = C \frac{dV(t)}{dt}$


* "resists a change in voltage"

* stores energy in electric field

$E = \frac{1}{2} CV^2$

C - unit Farad [F]

* at DC: acts as an open circuit

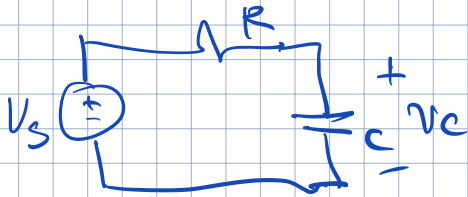

$V_c \sim e^{-\frac{t}{RC}}$


$\tau = RC$
time-constant

Inductor

$L \frac{dI}{dt} = V$ $V(t) = L \frac{dI(t)}{dt}$

* "resists a change in current"


* Stores energy in magnetic field:

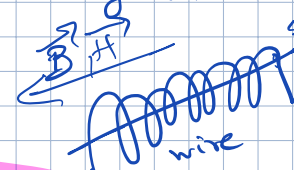

$E = \frac{1}{2} LI^2$

* short-circuit at constant current

L - unit Henry [H]

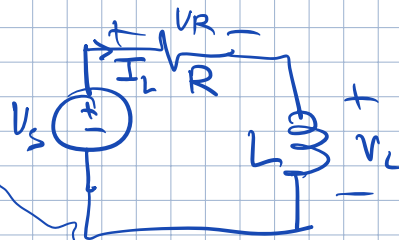

$\tau = ?$

Decaying exponentials

$e^{-\frac{t}{\tau}}$

$$V_s(t < 0) = 1V$$

$$V_s(t \geq 0) = 0V$$

Solve for $I_L(t)$.

First, find $I_L(0)$.

for $t < 0$

$$I_L(t) = \frac{V_s(t) - V_L(t)}{R} = \frac{1V - 0}{R} = \frac{1V}{R}$$

$$\rightarrow I_L(0) = \frac{1V}{R}$$

$$V_L(t) = L \frac{dI_L(t)}{dt}$$

$$I_L(t) = \frac{V_s(t) - V_L(t)}{R} = \frac{V_s(t)}{R} - \frac{L}{R} \frac{dI_L(t)}{dt}$$

For $V_s(t \geq 0) = 0V$

$$I_L(t) = -\frac{L}{R} \frac{dI_L(t)}{dt}$$

$$\frac{d}{dt} I_L(t) = -\frac{R}{L} I_L(t), \quad t \geq 0$$

compare this to




$$I_L(t) = I_L(0) \cdot e^{-\frac{R}{L}t}$$


$$\frac{d}{dt} V_C(t) = -\frac{1}{RC} V_C(t)$$

$$= I_L(0) e^{-\frac{t}{\tau}}, \quad \tau = \frac{L}{R} \text{ - time constant}$$

$$V_R(t) = R \cdot I_L(t) = R \cdot I_L(0) e^{-\frac{t}{\tau}}$$
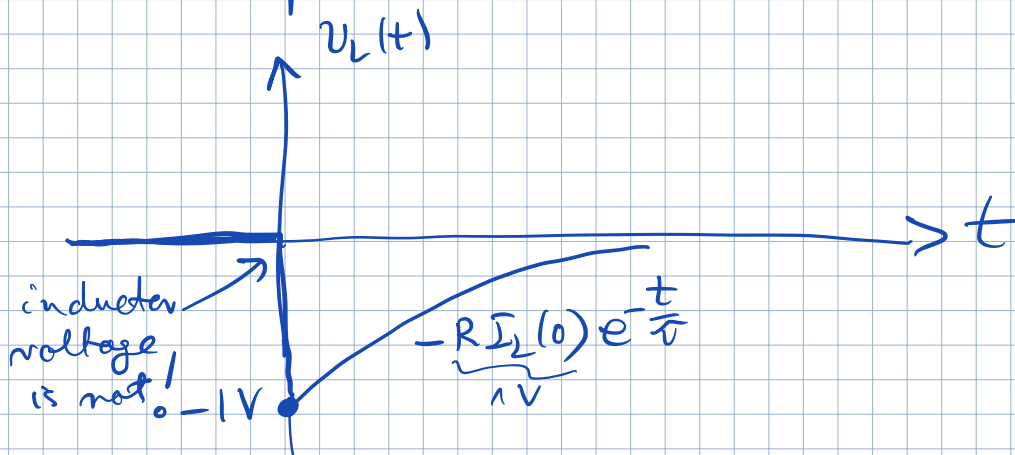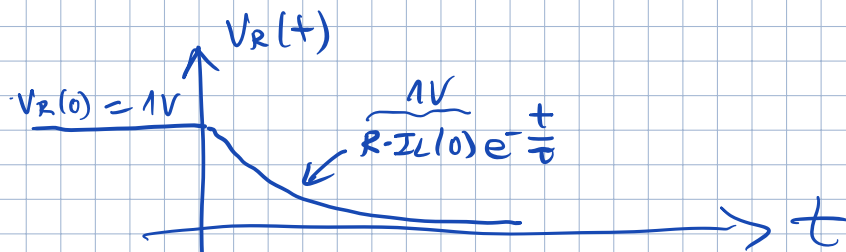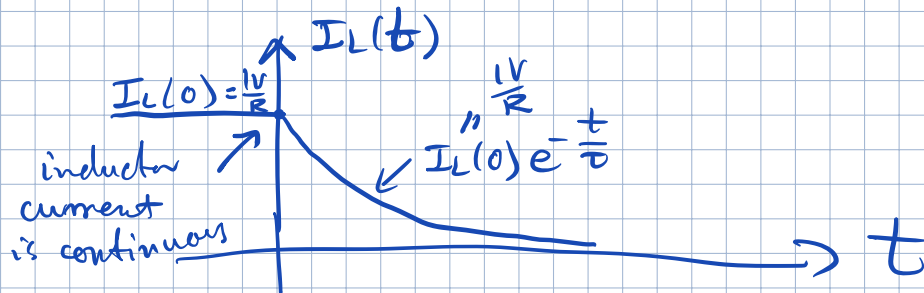
$$\begin{aligned}
 V_L(t) &= V_S(t) - V_R(t) = -V_R(t) \\
 &= -R I_L(t) e^{-\frac{t}{\tau}}
 \end{aligned}$$



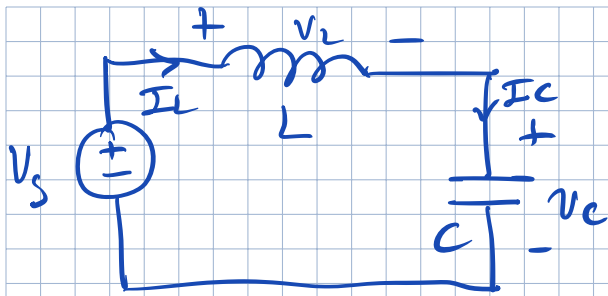

$$I_C(t) = C \frac{dV_C(t)}{dt}$$

$$V_L(t) = L \frac{dI_L(t)}{dt}$$

$$I_L(t) = I_C(t) \quad (KCL)$$

$$V_s(t < 0) = 1V$$

$$V_L(t) = V_s(t) - V_C(t)$$

$$V_s(t \geq 0) = 0V$$

For $t \geq 0$, $V_s(t) = 0V \Rightarrow$

$$V_C(0) = 1V$$

$$V_L(t) = -V_C(t)$$

$$I_L(0) = 0A$$

Use $v_C(t)$ & $I_L(t)$
as state-variables.

$$\left[\begin{array}{l} L \frac{dI_L(t)}{dt} = -V_C(t) \quad (1) \\ I_L(t) = C \frac{dV_C(t)}{dt} \quad (2) \end{array} \right.$$

$$(1) \quad \frac{d}{dt} I_L(t) = -\frac{1}{L} v_C(t)$$

$$(2) \quad \frac{d}{dt} v_C(t) = \frac{1}{C} I_L(t)$$

$$\underbrace{\frac{d}{dt} \begin{bmatrix} I_L(t) \\ v_C(t) \end{bmatrix}}_{\frac{d}{dt} \vec{x}(t)} = \underbrace{\begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & 0 \end{bmatrix}}_A \underbrace{\begin{bmatrix} I_L(t) \\ v_C(t) \end{bmatrix}}_{\vec{x}(t)}$$

↓
diagonalize A to solve.

Compute eigenvalues of A :

$$\det(\lambda I - A) = \det \begin{pmatrix} \lambda & \frac{1}{L} \\ -\frac{1}{C} & \lambda \end{pmatrix} = \\ = \lambda^2 + \frac{1}{LC} = 0$$

$$\lambda_{1,2} = \pm j \sqrt{\frac{1}{LC}} \quad , \quad j = \sqrt{-1}$$

Assume: $L = 1 \text{ H}$, $C = 1 \text{ F}$ [large artificial values]

$$A = \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \Rightarrow \lambda_{1,2} = \pm j$$

want to find \vec{v}_1 & \vec{v}_2 s.t.

$$A \vec{v}_1 = \lambda_1 \vec{v}_1 \quad \& \quad A \vec{v}_2 = \lambda_2 \vec{v}_2$$

Nullspace style

$$\lambda_1 = j \\ (A - \lambda_1 I) \cdot \vec{v}_1 = \vec{0}$$

$$\begin{bmatrix} -j & -1 \\ 1 & -j \end{bmatrix} \cdot \begin{bmatrix} 1 \\ -j \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\vec{v}_1 = \begin{bmatrix} 1 \\ -j \end{bmatrix}$$

$$\lambda_2 = -j \\ \vec{v}_2 = \begin{bmatrix} 1 \\ ? \end{bmatrix}$$

Any multiple of eigenvector is also an eigenvector from eigenspace

$$A k \vec{v}_2 = \lambda_2 k \vec{v}_2$$

so can normalize one element of \vec{v}_2 .

$$\begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} 1 \\ x \end{bmatrix} = -j \begin{bmatrix} 1 \\ x \end{bmatrix} \\ A \vec{v}_2 = \lambda_2 \vec{v}_2$$

$$V = \begin{bmatrix} 1 & 1 \\ -j & j \end{bmatrix}$$

← eigenbasis

$$-x = -j \Rightarrow x = j$$

$$v_2 = \begin{bmatrix} 1 \\ j \end{bmatrix}$$

$$V^{-1} = \begin{bmatrix} \frac{1}{2} & \frac{j}{2} \\ \frac{1}{2} & -\frac{j}{2} \end{bmatrix}$$

$$\vec{x}(t) = V \vec{\tilde{x}}$$

$$= [\vec{v}_1 \dots \vec{v}_n] \begin{bmatrix} \tilde{x}_1(t) \\ \vdots \\ \tilde{x}_n(t) \end{bmatrix}$$

$$= \tilde{x}_1(t) \vec{v}_1 + \dots + \tilde{x}_n \vec{v}_n$$

\uparrow coordinate \uparrow basis



$$\frac{d}{dt} \vec{x}$$

$$\frac{d}{dt} \vec{\tilde{x}}$$

Found a way
to express
 \vec{x} in V -eigen
basis
with $\vec{\tilde{x}}$ coordinates.

$$\frac{d}{dt} \vec{x}(t) = \underbrace{\begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix}}_A \vec{x}(t)$$

$$\frac{d}{dt} \vec{\tilde{x}}(t) = \underbrace{\begin{bmatrix} j & 0 \\ 0 & -j \end{bmatrix}}_{V^{-1}AV} \vec{\tilde{x}}(t)$$

$$\vec{\tilde{x}}(t) = \begin{bmatrix} \tilde{x}_1(0) e^{jt} \\ \tilde{x}_2(0) e^{-jt} \end{bmatrix}$$

need $\vec{\tilde{x}}(0)$

$$I_L(0) = 0A$$

$$\vec{\tilde{x}}(0) = V^{-1} \vec{x}(0) = \begin{bmatrix} \frac{1}{2} & \frac{j}{2} \\ \frac{1}{2} & -\frac{j}{2} \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} \frac{j}{2} \\ -\frac{j}{2} \end{bmatrix}$$

$$\vec{\tilde{x}}(t) = \begin{bmatrix} \frac{j}{2} e^{jt} \\ -\frac{j}{2} e^{-jt} \end{bmatrix}$$

$$v_c(0) = 1V$$

$$\vec{x}(t) = V \vec{\tilde{x}}(t) = \begin{bmatrix} 1 & 1 \\ j & -j \end{bmatrix} \begin{bmatrix} \frac{j}{2} e^{jt} \\ -\frac{j}{2} e^{-jt} \end{bmatrix}$$

$$\begin{bmatrix} I_1(t) \\ v_c(t) \end{bmatrix} = \vec{x}(t) = \begin{bmatrix} \frac{j}{2} e^{jt} - \frac{j}{2} e^{-jt} \\ \frac{e^{jt} + e^{-jt}}{2} \end{bmatrix}$$

Enter formula (or Taylor expansion)

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$x_1(t) = \frac{j}{2} e^{jt} - \frac{j}{2} e^{-jt} =$$

$$= \frac{j}{2} (e^{jt} - e^{-jt}) = \frac{j}{2} (\cos t + j \sin t - (\cos(-t) + j \sin(-t)))$$


$$= \frac{j}{2} (\cos t + j \sin t - (\cos t - j \sin t))$$

$$= \frac{j}{2} \cdot 2j \sin t = -\sin t$$

$$x_2(t) = \frac{e^{jt} + e^{-jt}}{2} = \cos t$$


$$\Rightarrow \vec{x}(t) = \begin{bmatrix} I_L(t) \\ v_C(t) \end{bmatrix} = \begin{bmatrix} -\sin t \\ \cos t \end{bmatrix}$$

↑ real functions

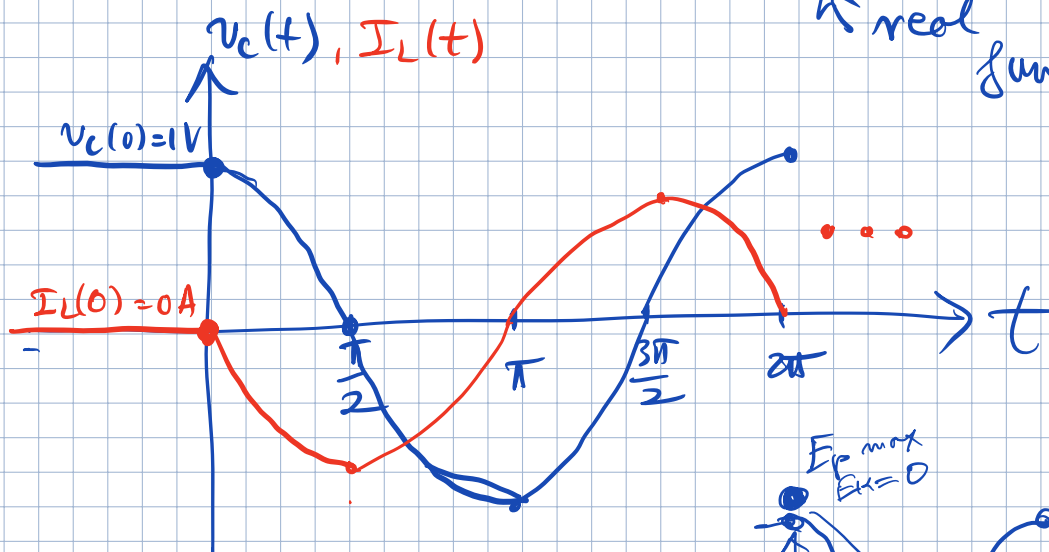

Note: $\lambda_{1,2} = \pm j \sqrt{\frac{1}{LC}}$
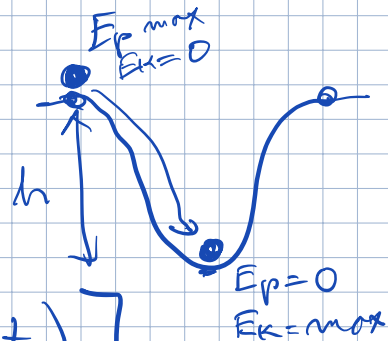
$$\vec{x}(t) = \begin{bmatrix} I_L(t) \\ v_C(t) \end{bmatrix} = \begin{bmatrix} -\sin\left(\frac{1}{\sqrt{LC}}t\right) \\ \cos\left(\frac{1}{\sqrt{LC}}t\right) \end{bmatrix}$$



Refresher:

For $\frac{d}{dt}x(t) = \lambda x(t) + u(t)$, when $u(t) = k \cdot e^{st}$

$$x(t) = \underbrace{\left(x(0) - \frac{k}{s-\lambda}\right) e^{\lambda t}}_{\text{Annoying}} + \underbrace{\frac{k}{s-\lambda} e^{st}}_{\text{Nice - same form as input}}$$

- transient solution
b/c of initial conditions

(steady-state soln)

Want the first part to disappear for $t \rightarrow \infty$.

If $\lambda < 0$, $e^{\lambda t} \xrightarrow{t \rightarrow \infty} 0$ and

$x(t) \rightarrow \text{steady-state } \left(\frac{k}{s-\lambda} e^{st}\right)$

What about λ complex?

$$\begin{aligned} e^{\lambda t} &= e^{(\lambda_r + j\lambda_i)t} = e^{\lambda_r t} \cdot e^{j\lambda_i t} = \\ &= e^{\lambda_r t} (\cos(\lambda_i t) + j \sin(\lambda_i t)) \end{aligned}$$

If $\lambda_r < 0$ $e^{\lambda_r t} \xrightarrow{t \rightarrow \infty} 0$

$x(t) \rightarrow \text{steady-state}$