

Lecture 9

* Filters

* Low-pass & high-pass examples

* Transfer functions

* Bode plot approximations

* Cascading filters

Objective: To find a steady-state solution of the system in response to sinusoidal inputs. ($\lambda_r < 0$)

Sinusoidal inputs allow us to transform the system of diff. eqns into a system of lin. eqns. (Phasor domain)

Phasor analysis:

Step 1) Write sources (inputs) as exponentials:

$$V_{si}(t) = \tilde{V}_{si} e^{j\omega t} + \bar{\tilde{V}}_{si} e^{-j\omega t}$$

$$I_{si}(t) = \tilde{I}_{si} e^{j\omega t} + \bar{\tilde{I}}_{si} e^{-j\omega t}$$

\tilde{V}_{si} & \tilde{I}_{si}
are phasors

Step 2) Transform the circuit into the phasor domain:

(s-impedances $s = j\omega$) $\frac{\tilde{V}_{el}}{\tilde{I}_{el}} = Z_{el}$

$$\frac{\hat{V}_R}{\hat{I}_R} = Z_R = R, \quad \frac{\hat{V}_C}{\hat{I}_C} = Z_C(j\omega) = \frac{1}{j\omega C}, \quad \frac{\hat{V}_L}{\hat{I}_L} = Z_L(j\omega) = j\omega L$$

Generalized Ohm's Law.

Step 3) Cast branch & element equations in phasor domain:

$$\text{KCL: } \sum_{\substack{i \text{ into} \\ \text{the node}}} \hat{I}_i = 0 \quad \text{Ohm's law: } \hat{V}_i = Z_i \hat{I}_i$$

$$\text{NVA: } \sum_i \frac{\hat{V}_j - \hat{V}_k}{Z_{jk}} = 0, \quad \text{KVL holds as well.}$$

Step 4) Solve for unknown variables:

$$\hat{V}_R, \hat{I}_R, \hat{V}_L, \hat{I}_L, \hat{V}_C, \hat{I}_C$$

(in general $\hat{V}_{el_i}, \hat{I}_{el_i}$)

Step 5) Transform the phasor solutions from step 4 into the time domain


$$v_{el}(t) = \hat{V}_{el} e^{j\omega t} + \overline{\hat{V}_{el}} e^{-j\omega t}$$

$$i_{el}(t) = \hat{I}_{el} e^{j\omega t} + \overline{\hat{I}_{el}} e^{-j\omega t}$$

$$v_{el}(t) = 2|\hat{V}_{el}| \cos(\omega t + \angle \hat{V}_{el})$$

$$i_{el}(t) = 2|\hat{I}_{el}| \cos(\omega t + \angle \hat{I}_{el})$$

Example 1 continued (Low-pass filter):

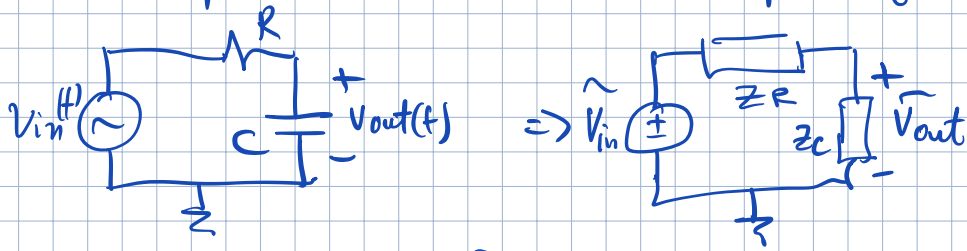

$$\hat{V}_{out} = \frac{Z_C}{Z_C + Z_R} \hat{V}_{in}$$

$$\underbrace{\frac{\hat{V}_{out}}{\hat{V}_{in}}}_{\text{transfer function}} = H_{LP}(j\omega) = \frac{Z_C}{Z_C + Z_R} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC}$$


$\omega_0 = \frac{1}{RC}$ we call ω_0 "cut-off freq"


$$H_{LP}(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_0}}$$

$$|H_{LP}(j\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}} \quad \begin{array}{l} \xrightarrow{\omega \gg \omega_0} 0 \\ \xrightarrow{\omega \ll \omega_0} 1 \end{array}$$

$$\angle H_{LP}(j\omega) = -\arctan\left(\frac{\omega}{\omega_0}, 1\right)$$

ω	$H(j\omega)$	$ H(j\omega) $	$\angle H(j\omega)$
$\omega \ll \omega_0$	≈ 1	1	$\approx 0^\circ$
$0.1\omega_0$	$\frac{1}{1+j0.1}$	0.995	-6°
ω_0	$\frac{1}{1+j}$	$\frac{1}{\sqrt{2}} \approx 0.71$	-45°
$10\omega_0$	$\frac{1}{1+j10}$	0.1	-84°
$\omega \gg \omega_0$	$-j \frac{\omega_0}{\omega}$	$\frac{\omega_0}{\omega}$	-90°

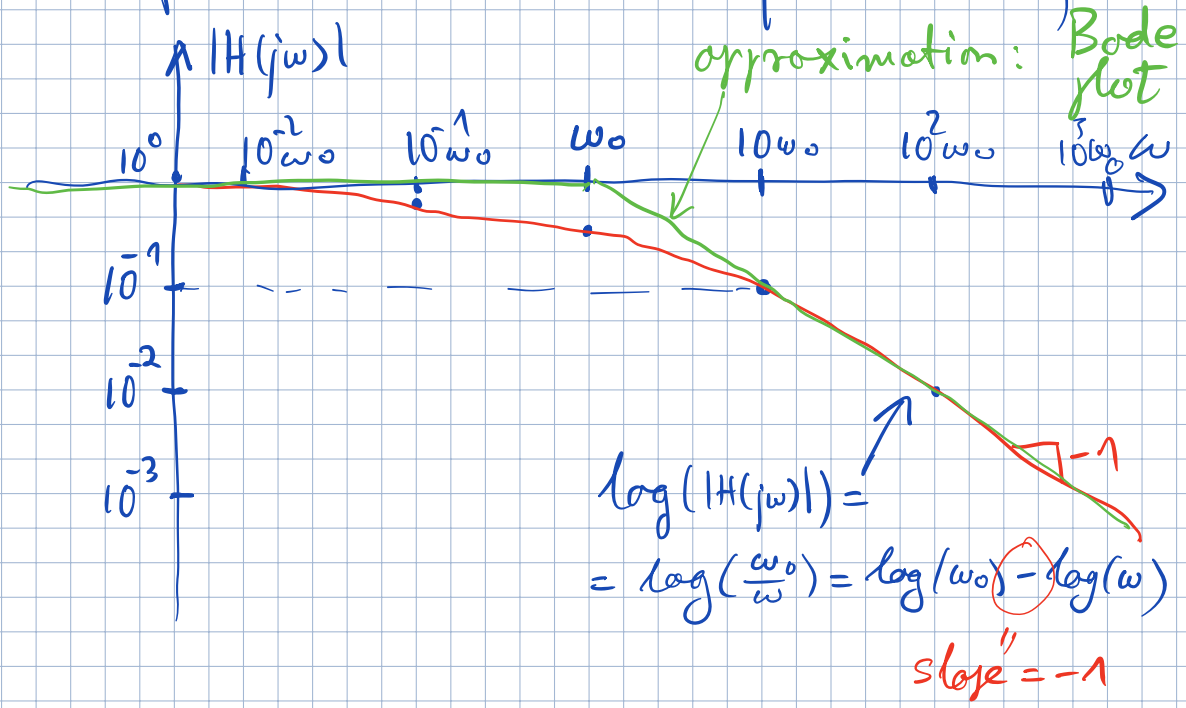

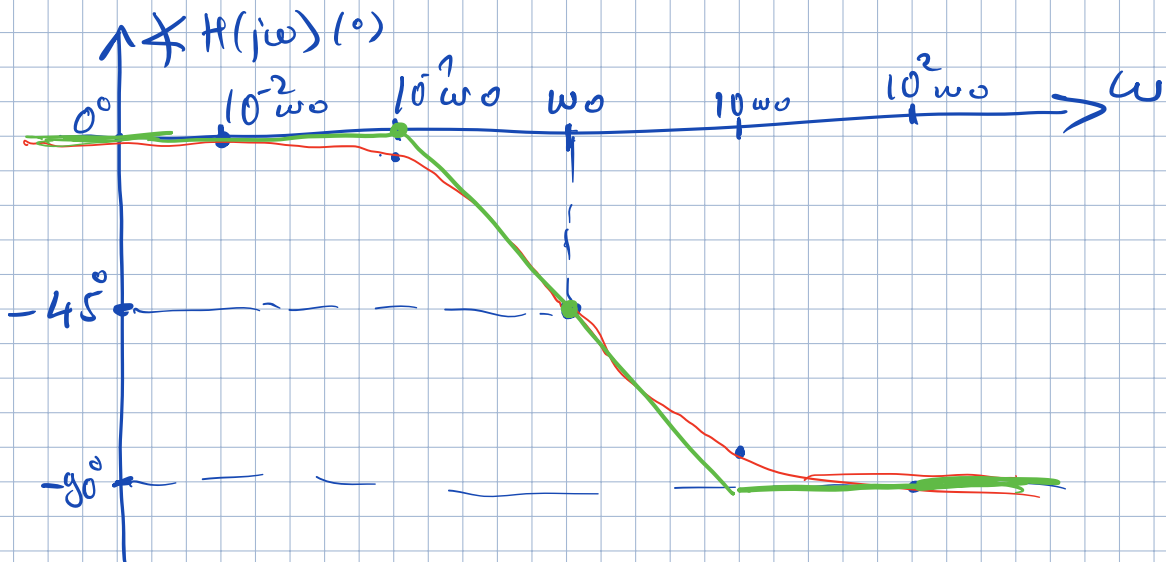

$$\begin{aligned}
 v_{out}(t) &= \hat{v}_{out} e^{j\omega t} + \overline{\hat{v}_{out}} e^{-j\omega t} \\
 &= |\hat{v}_{out}| e^{j\hat{\phi}_{out}} \cdot e^{j\omega t} + |\hat{v}_{out}| e^{-j\hat{\phi}_{out}} \cdot e^{-j\omega t} \\
 &= |\hat{v}_{out}| \left(e^{j(\omega t + \hat{\phi}_{out})} + e^{-j(\omega t + \hat{\phi}_{out})} \right) \\
 &\quad \text{Euler: } 2 \cos(\omega t + \hat{\phi}_{out}) \\
 &= 2 |\hat{v}_{out}| \cos(\omega t + \hat{\phi}_{out})
 \end{aligned}$$

$$\hat{v}_{out} = H_{LP}(j\omega) \cdot \tilde{v}_{in}$$

$$|\hat{v}_{out}| \cdot e^{j\hat{\phi}_{out}} = |H_{LP}(j\omega)| \cdot e^{j\hat{\phi}_{HLP}(j\omega)} \cdot |\tilde{v}_{in}| e^{j\hat{\phi}_{in}}$$

$$|\hat{v}_{out}| e^{j\hat{\phi}_{out}} = |H_{LP}(j\omega)| \cdot |\tilde{v}_{in}| \cdot e^{j(\hat{\phi}_{in} + \hat{\phi}_{HLP}(j\omega))}$$


$$\begin{aligned}
 |\hat{v}_{out}| &= |H_{LP}(j\omega)| |\tilde{v}_{in}| \\
 \hat{\phi}_{out} &= \hat{\phi}_{in} + \hat{\phi}_{HLP}(j\omega)
 \end{aligned}$$

$$V_{out}(t) = 2 \cdot |H_{LP}(j\omega)| \cdot |\hat{V}_{in}| \cos(\omega t + \phi_{\hat{V}_{in}} + \phi_{H_{LP}(j\omega)})$$

our input $v_{in}(t) = V_{in} \cos(\omega t + \phi)$

$$V_{out}(t) = |H_{LP}(j\omega)| \cdot V_{in} \cos(\omega t + \phi + \phi_{H_{LP}(j\omega)})$$

Example 2: (High-pass filter)

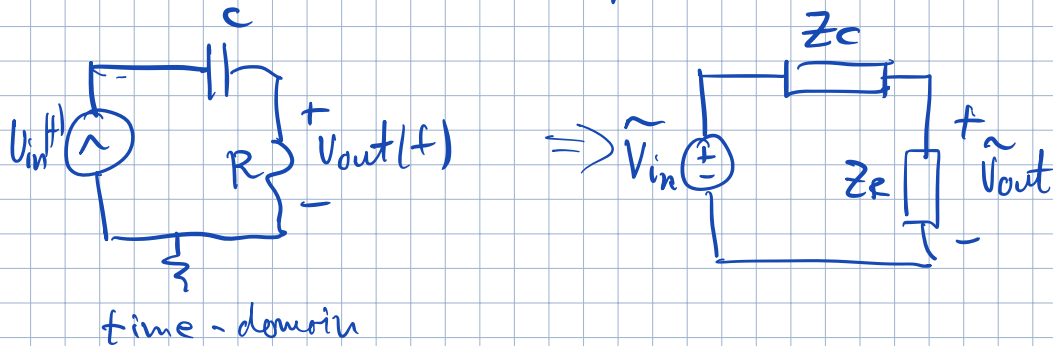

$$\tilde{V}_{out} = \frac{Z_R}{Z_R + Z_C} \tilde{V}_{in}$$

$$H_{HP}(j\omega) = \frac{\tilde{V}_{out}}{\tilde{V}_{in}} = \frac{Z_R}{Z_R + Z_C} = \frac{R}{R + \frac{1}{j\omega C}}$$


$$H_{HP}(j\omega) = \frac{j\omega RC}{1 + j\omega RC} \quad , \quad \omega_0 = \frac{1}{RC}$$

$$H_{HP}(j\omega) = \frac{j\frac{\omega}{\omega_0}}{1 + j\frac{\omega}{\omega_0}} = \frac{1}{1 - j\frac{\omega_0}{\omega}}$$


"cut-off freq"

$$|H_{HP}(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega_0}{\omega}\right)^2}}$$

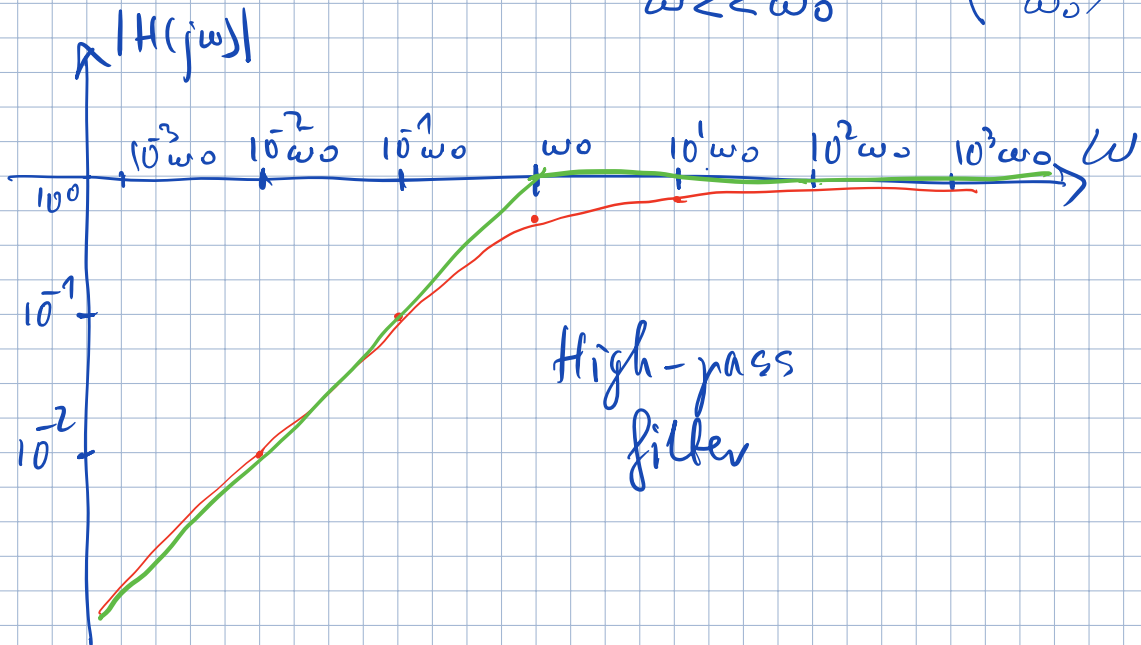$\omega \gg \omega_0 \rightarrow 1$
 $\omega \ll \omega_0 \rightarrow 0 \left(\frac{\omega}{\omega_0}\right)$



In 16 A :

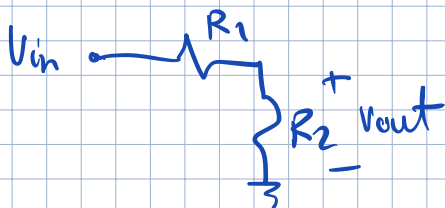


$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$


"Operatas"

Transfer functions

In 16 B :




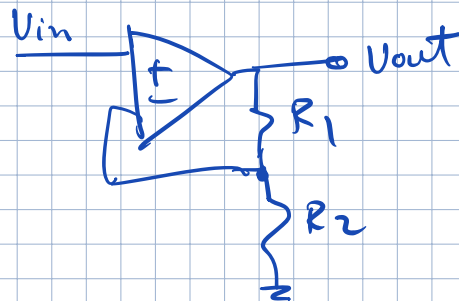

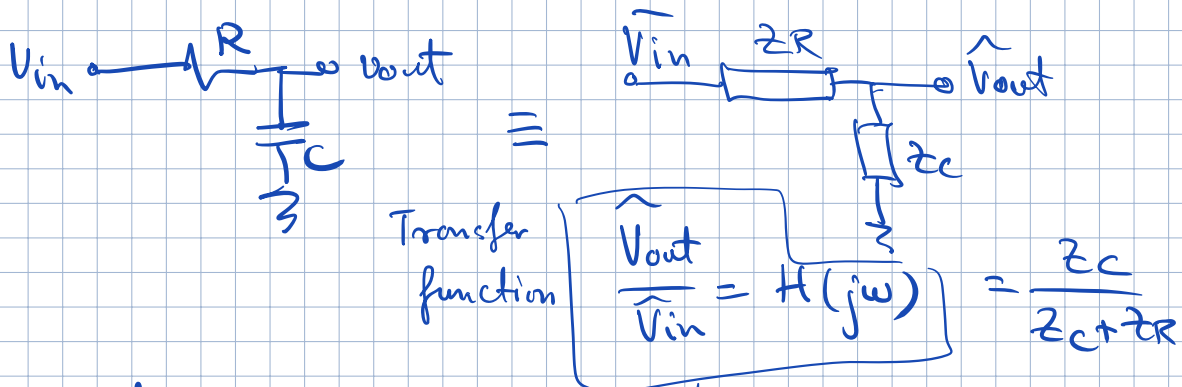
$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2}$$



How do we cascade circuits in a tractable way to build more complex functions?

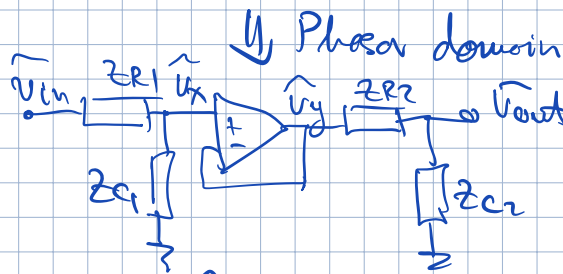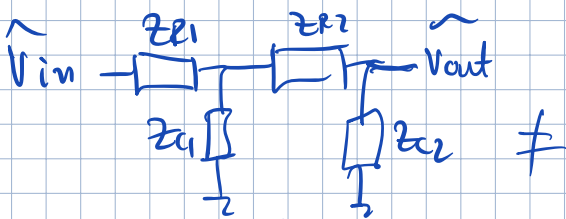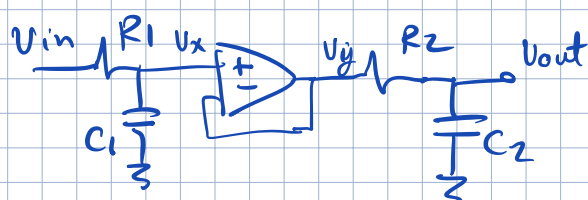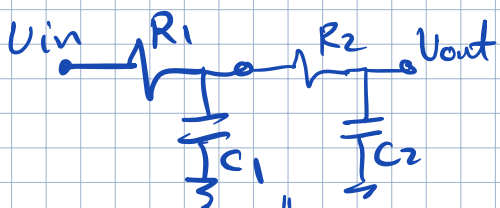Circuit blocks should not "load" (i.e. take current from) each other in order to preserve the transfer function.



Solve $H(j\omega) = \frac{\widehat{V}_{out}}{\widehat{V}_{in}}$

Need to calculate the soln.

$$H_1(j\omega) = \frac{\widehat{V}_x}{\widehat{V}_{in}}, \quad H_{buf}(j\omega) = \frac{\widehat{V}_y}{\widehat{V}_x}$$

$$H_2(j\omega) = \frac{\widehat{V}_{out}}{\widehat{V}_y}$$

$$H(j\omega) = \frac{\widehat{V}_{out}}{\widehat{V}_{in}} = \frac{\widehat{V}_{out}}{\widehat{V}_y} \cdot \frac{\widehat{V}_y}{\widehat{V}_x} \cdot \frac{\widehat{V}_x}{\widehat{V}_{in}}$$

$$= H_2(j\omega) \cdot H_{buf}(j\omega) \cdot H_1(j\omega)$$

$$H_1(j\omega) = \frac{z_{C1}}{z_{C1} + z_{R1}}$$

voltage div.

$$H_{buf}(j\omega) = 1$$

$\hat{V}_y = \hat{V}_x$

$$H_2(j\omega) = \frac{z_{C2}}{z_{C2} + z_{R2}}$$


voltage-div.

$$H_1(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_{01}}}, \quad H_2(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_{02}}}$$

$$\omega_{01} = \frac{1}{R_1 C_1}, \quad \omega_{02} = \frac{1}{R_2 C_2}$$

$$H(j\omega) = H_1(j\omega) \cdot \overset{1}{\cancel{H_{buf}(j\omega)}} \cdot \overset{1}{H_2(j\omega)}$$
$$= \frac{1}{1 + j\frac{\omega}{\omega_{01}}} \cdot \frac{1}{1 + j\frac{\omega}{\omega_{02}}}$$

In general:

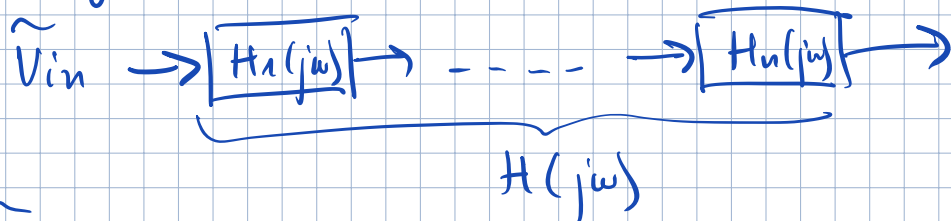

$$\frac{\widehat{v}_{out}}{\tilde{v}_{in}} = H_1(j\omega) \cdot \dots \cdot H_n(j\omega)$$

$$H_i(j\omega) = |H_i(j\omega)| \cdot e^{j\phi_{H_i}(j\omega)}$$

$$\frac{\widehat{v}_{out}}{\tilde{v}_{in}} = H(j\omega) = \underbrace{|H_1(j\omega)| \dots |H_n(j\omega)|}_{|H(j\omega)|} e^{j(\underbrace{\phi_{H_1}(j\omega) + \dots + \phi_{H_n}(j\omega)}_{\phi_{H(j\omega)}})}$$

Time domain:

$$v_{out}(t) = |H(j\omega)| \cdot |\tilde{v}_{in}| \cos(\omega t + \phi_{H(j\omega)} + \phi_{\tilde{v}_{in}})$$

for $v_{in}(t) = v_{in} \cos(\omega t + \phi)$

$$v_{out}(t) = |H(j\omega)| v_{in} \cos(\omega t + \phi + \phi_{H(j\omega)})$$