

The following sections from the textbook are useful for this discussion: Sections 4.1, 4.3, 4.4

### 1. RL Transient Analysis (Hambley Example 4.2)

Consider the circuit shown in Figure 1.

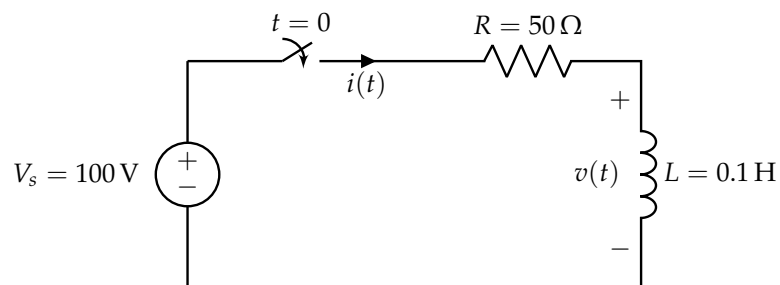


Figure 1

(a) Set up a differential equation for the current  $i(t)$  in the form:

$$\frac{di(t)}{dt} + ai(t) = b(t) \quad (1)$$

and determine the initial condition  $i(0)$ .

(b) Solve for the current  $i(t)$  using the integrating factor method.

(c) Find the voltage  $v(t)$ .

## 2. Analyzing an RC Circuit with a Sinusoidal Source (Hambley Example 4.4)

Assume you are given the following circuit, where the capacitor is initially charged so that  $v_C(t) = 1V$ .

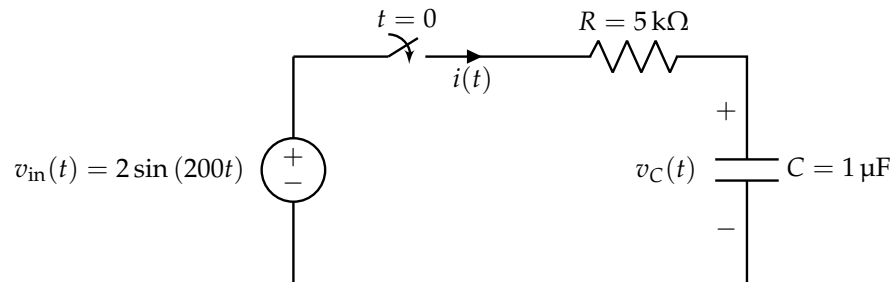


Figure 2

(a) Set up a differential equation for the current  $i(t)$  through the circuit in the form:

$$\frac{di(t)}{dt} + ai(t) = b(t) \quad (2)$$

(b) Determine the initial condition of  $i(t)$ . In other words, solve for  $i(0)$ .

- (c) **Solve for the current  $i(t)$  through the circuit. Also, identify the transient response and the forced response of  $i(t)$ .** You may directly use the fact that the solution to a differential equation in the same form as Equation 2 is:

$$i(t) = Ae^{-at} + e^{-at} \int e^{at'} b(t') dt' \quad (3)$$

(HINT: The following integral might be useful:

$$\int e^{at} \cos(bt) = \frac{1}{b^2 + a^2} e^{at} (b \sin(bt) + a \cos(bt)) \quad (4)$$

)

- (d) **(OPTIONAL) Solve for the voltage  $v_C(t)$  across the capacitor.**