

The following sections from the textbook are useful for this discussion: Sections 4.1, 4.3, 4.4

1. RL Transient Analysis (Hambley Example 4.2)

Consider the circuit shown in Figure 1.

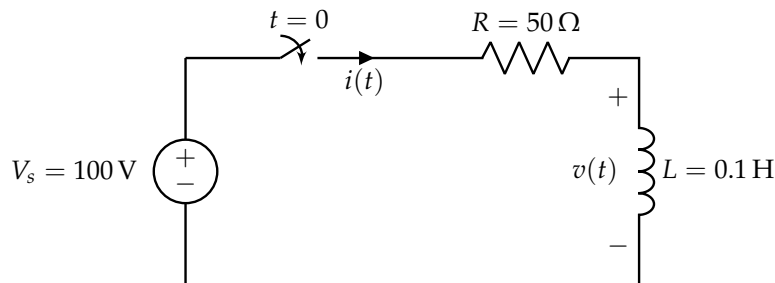


Figure 1

(a) **Set up a differential equation for the current $i(t)$ in the form:**

$$\frac{di(t)}{dt} + ai(t) = b(t) \tag{1}$$

and determine the initial condition $i(0)$.

Solution: Before the switch closes ($t < 0$), we have that the switch is open and thus current is zero.

$$i(t) = 0 \quad \text{for } t < 0 \tag{2}$$

Furthermore, since inductor current cannot change instantaneous/must be continuous, we know that immediately after the switch is closed, $i(0) = 0$. We will use this initial condition when solving our differential equation later on.

To begin solving for current $i(t)$, we will write out the KVL equation for the loop, which states that the sum of the voltages around a loop is 0:

$$V_s - V_R - V_L = 0 \tag{3}$$

$$V_R + V_L = V_s \tag{4}$$

$$Ri(t) + L \frac{di(t)}{dt} = V_s \tag{5}$$

Rearranging our differential equation to be in the desired form, we get:

$$Ri(t) + L \frac{di(t)}{dt} = V_s \tag{6}$$

$$L \frac{di(t)}{dt} + Ri(t) = V_s \tag{7}$$

$$\frac{di(t)}{dt} + \frac{R}{L}i(t) = \frac{V_s}{L} \tag{8}$$

where $a = \frac{R}{L}$ and $b(t) = \frac{V_s}{L}$.

(b) Solve for the current $i(t)$ using the integrating factor method.

Solution: Approach 1: Integrating Factor Method

Starting from the equation we derived above:

$$\frac{di(t)}{dt} + \frac{R}{L}i(t) = \frac{V_s}{L} \quad (9)$$

where $a = \frac{R}{L}$ and $b(t) = \frac{V_s}{L}$. From here, we know that the integrating factor $f(t)$ is

$$f(t) = e^{\int a dt} \quad (10)$$

$$= e^{\int \frac{R}{L} dt} \quad (11)$$

$$= e^{\frac{R}{L}t} \quad (12)$$

Multiplying both sides of our differential equation by this factor, we get:

$$e^{\frac{R}{L}t} \frac{di(t)}{dt} + e^{\frac{R}{L}t} \frac{R}{L}i(t) = e^{\frac{R}{L}t} \frac{V_s}{L} \quad (13)$$

$$\frac{d}{dt} \left(i(t)e^{\frac{R}{L}t} \right) = \frac{V_s}{L} e^{\frac{R}{L}t} \quad (14)$$

$$i(t)e^{\frac{R}{L}t} = \int \frac{V_s}{L} e^{\frac{R}{L}t'} dt' \quad (15)$$

$$i(t)e^{\frac{R}{L}t} = \frac{V_s}{L} \int e^{\frac{R}{L}t'} dt' \quad (16)$$

$$i(t)e^{\frac{R}{L}t} = \frac{V_s}{L} \left(\frac{L}{R} e^{\frac{R}{L}t} \right) + c \quad (17)$$

$$i(t)e^{\frac{R}{L}t} = \frac{V_s}{R} \left(e^{\frac{R}{L}t} \right) + c \quad (18)$$

$$i(t) = \frac{V_s}{R} + ce^{-\frac{R}{L}t} \quad (19)$$

Now, we will use our initial conditions to solve for the constant c .

$$i(0) = \frac{V_s}{R} + ce^{-\frac{R}{L}0} \quad (20)$$

$$0 = \frac{V_s}{R} + c \quad (21)$$

$$c = -\frac{V_s}{R} \quad (22)$$

Putting this all together, we get that our final equation for current is:

$$i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-\frac{R}{L}t} \quad (23)$$

$$i(t) = 2 - 2e^{-500t} \quad (24)$$

Approach 2: Pattern-Matching

Recall that the general form of the solution of a differential equation in the form:

$$\frac{dy}{dt} + ay(t) = b(t) \quad (25)$$

is

$$y(t) = Ae^{-at} + e^{-at} \int e^{at} b(t) dt \quad (26)$$

Plugging this into the general form and solving gives us:

$$i(t) = Ae^{-\frac{R}{L}t} + e^{-\frac{R}{L}t} \int e^{\frac{R}{L}t} \frac{V_s}{L} dt \quad (27)$$

$$i(t) = Ae^{-\frac{R}{L}t} + \frac{V_s}{L} e^{-\frac{R}{L}t} \int e^{\frac{R}{L}t} dt \quad (28)$$

$$i(t) = Ae^{-\frac{R}{L}t} + \frac{V_s}{L} e^{-\frac{R}{L}t} \left(\frac{L}{R} e^{-\frac{R}{L}t} \right) t \quad (29)$$

$$i(t) = Ae^{-\frac{R}{L}t} + \frac{V_s}{R} \quad (30)$$

Lastly, we will use the initial condition $i(t) = 0$ to solve for A :

$$i(0) = Ae^{-\frac{R}{L}0} + \frac{V_s}{R} \quad (31)$$

$$0 = A + \frac{V_s}{R} \quad (32)$$

$$A = -\frac{V_s}{R} \quad (33)$$

Therefore, our final equation is also:

$$i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-\frac{R}{L}t} \quad (34)$$

$$i(t) = 2 - 2e^{-500t} \quad (35)$$

Approach 3: Textbook, "Ad hoc" Method

This form of a differential leads us to want to try a solution in the form of:

$$i(t) = K_1 + K_2 e^{st} \quad (36)$$

where we need to determine the values of the constants K_1 , K_2 , and s . We will first proceed by plugging in our trial solution into the differential equation which results in:

$$R(K_1 + K_2 e^{st}) + L \frac{d}{dt} (K_1 + K_2 e^{st}) = V_s \quad (37)$$

$$RK_1 + RK_2 e^{st} + L(sK_2 e^{st}) = V_s \quad (38)$$

$$RK_1 + (RK_2 + sLK_2) e^{st} = V_s \quad (39)$$

By pattern matching the two sides of the equation: we have that:

$$K_1 = \frac{V_s}{R} = \frac{100}{50} = 2 \quad (40)$$

$$s = -\frac{R}{L} \quad (41)$$

If we plug this into our trial solution for current, we have:

$$i(t) = 2 + K_2 e^{-\frac{R}{L}t} \quad (42)$$

Lastly, we can solve for the value of K_2 using the initial conditions. Using the initial condition that $i(0) = 0$ in, we get:

$$i(0) = 2 + K_2 e^{-\frac{R}{L}0} \quad (43)$$

$$0 = 2 + K_2 \quad (44)$$

$$K_2 = -2 \quad (45)$$

Hence, putting this all together, we have that the final solution for current is:

$$i(t) = 2 - 2e^{-\frac{R}{L}t} \quad \text{for } t > 0 \quad (46)$$

or if we replace $\tau = \frac{L}{R}$ where τ is the time constant, we get:

$$i(t) = 2 - 2e^{-\frac{t}{\tau}} \quad \text{for } t > 0 \quad (47)$$

(c) **Find the voltage $v(t)$.**

Solution: There are two approaches we can use to solve for $v(t)$. The first one is using the I-V relationship of an inductor and the second is using the fact that $v(t)$ is also the difference between the source voltage and the resistor voltage.

Approach 1: We can use the equation:

$$v_L(t) = L \frac{di_L(t)}{dt} \quad (48)$$

which requires us to take the derivative of our derived current equation.

$$v(t) = L \frac{d}{dt} \left(-\frac{V_s}{R} e^{-\frac{R}{L}t} \right) \quad (49)$$

$$v(t) = L \frac{V_s}{R} \frac{R}{L} e^{-\frac{R}{L}t} \quad (50)$$

$$v(t) = L \frac{V_s}{R} \frac{R}{L} e^{-\frac{R}{L}t} \quad (51)$$

$$v(t) = V_s e^{-\frac{R}{L}t} \quad (52)$$

$$v(t) = 100e^{-500t} \quad (53)$$

Approach 2: The second approach involves recognizing that by KVL:

$$v(t) = V_s - V_R(t) \quad (54)$$

Leveraging Ohm's Law which states $V_R(t) = Ri(t)$, we can solve for $v(t)$:

$$v(t) = V_s - R \left(\frac{V_s}{R} - \frac{V_s}{R} e^{-\frac{R}{L}t} \right) \quad (55)$$

$$v(t) = V_s - V_s + V_s e^{-\frac{R}{L}t} \quad (56)$$

$$v(t) = V_s e^{-\frac{R}{L}t} \quad (57)$$

$$v(t) = 100e^{-500t} \quad (58)$$

which is the same solution as we got from Approach 1.

2. Analyzing an RC Circuit with a Sinusoidal Source (Hambley Example 4.4)

Assume you are given the following circuit, where the capacitor is initially charged so that $v_C(t) = 1V$.

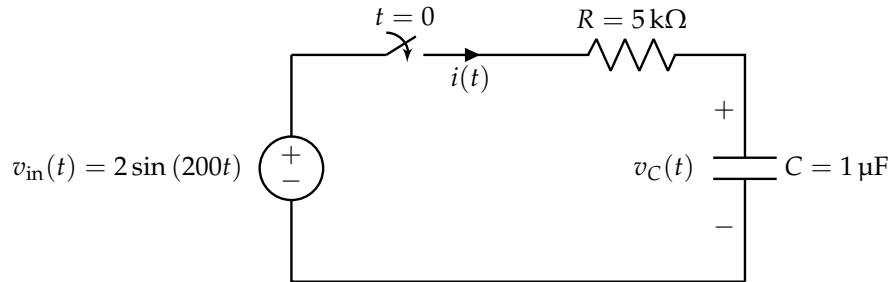


Figure 2

- (a) Set up a differential equation for the current $i(t)$ through the circuit in the form:

$$\frac{di(t)}{dt} + ai(t) = b(t) \quad (59)$$

Solution: Let's start by writing the voltage equation for $t > 0$ using KVL:

$$v_R(t) + v_C(t) - v_{in}(t) = 0 \quad (60)$$

$$Ri(t) + \frac{1}{C} \int_0^t i(t') dt' + v_C(0) - 2 \sin(200t) = 0 \quad (61)$$

We wish to convert this to a differential equation, so let's take the derivative of the whole equation and then rearrange so that it is in the general form for a first-order differential equation:

$$\frac{d}{dt} \left(Ri(t) + \frac{1}{C} \int_0^t i(t') dt' + v_C(0) - 2 \sin(200t) \right) = 0 \quad (62)$$

$$R \frac{di(t)}{dt} + \frac{1}{C} i(t) + 0 - 400 \cos(200t) = 0 \quad (63)$$

$$\frac{di(t)}{dt} + \frac{1}{RC} i(t) = \frac{400}{R} \cos(200t) \quad (64)$$

where $a = \frac{1}{RC} = \frac{1}{5 \times 10^{-3}} = 200$ and $b(t) = \frac{400}{R} \cos(200t) = 80 \times 10^{-3} \cos(200t)$.

- (b) Determine the initial condition of $i(t)$. In order words, solve for $i(0)$.

Solution: Initially we have that $v_C(0) = 1V$. We know that at $t = 0$, $V_{in}(0) = 2 \sin(200 \times 0) = 0V$. We can solve for the current using Ohm's Law:

$$i(0) = \frac{V_R(0)}{R} \quad (65)$$

$$i(0) = \frac{v_{in}(0) - v_C(t)}{R} \quad (66)$$

$$i(0) = \frac{0 - 1}{5 \times 10^3} \quad (67)$$

$$i(0) = -2 \times 10^{-4} A \quad (68)$$

- (c) Solve for the current $i(t)$ through the circuit. Also, identify the transient response and the forced response of $i(t)$. You may directly use the fact that the solution to a differential equation in the same form as Equation 59 is:

$$i(t) = Ae^{-at} + e^{-at} \int e^{at'} b(t') dt' \quad (69)$$

(HINT: The following integral might be useful:

$$\int e^{at} \cos(bt) = \frac{1}{b^2 + a^2} e^{at} (b \sin(bt) + a \cos(bt)) \quad (70)$$

)

Solution: Now that we have our differential equation in the standard form, we can use the general form of the solution to a first-order differential equation to solve for $i(t)$. Recall that the solution is:

$$y(t) = Ae^{-at} + e^{-at} \int e^{at'} b(t') dt' \quad (71)$$

so using our differential equation and plugging in a and $b(t)$, we get:

$$i(t) = Ae^{-\frac{1}{RC}t} + e^{-\frac{1}{RC}t} \int e^{\frac{1}{RC}t'} \frac{400}{R} \cos(200t') dt' \quad (72)$$

$$i(t) = Ae^{-\frac{1}{RC}t} + \frac{400}{R} e^{-\frac{1}{RC}t} \int e^{\frac{1}{RC}t'} \cos(200t') dt' \quad (73)$$

From here, we can apply Equation 70 from the hint:

$$i(t) = Ae^{-\frac{1}{RC}t} + \frac{400}{R} e^{-\frac{1}{RC}t} \frac{1}{\frac{1}{RC}^2 + 200^2} e^{\frac{1}{RC}t} (200 \sin(200t) - \frac{1}{RC} \cos(200t)) \quad (74)$$

$$i(t) = Ae^{-\frac{1}{RC}t} + \frac{400}{R \left(\frac{1}{RC}^2 + 200^2 \right)} (200 \sin(200t) - \frac{1}{RC} \cos(200t)) \quad (75)$$

Substituting values for $R = 5 \text{ k}\Omega$ and $C = 1 \text{ }\mu\text{F}$:

$$i(t) = Ae^{-\frac{1}{5 \times 10^{-3}}t} + \frac{400}{5 \times 10^3 \left(\frac{1}{5 \times 10^{-3}}^2 + 200^2 \right)} (200 \sin(200t) + \frac{1}{5 \times 10^{-3}} \cos(200t)) \quad (76)$$

$$i(t) = Ae^{-200t} + \frac{80 \times 10^{-3}}{8 \times 10^4} (200 \sin(200t) + 200 \cos(200t)) \quad (77)$$

$$i(t) = Ae^{-200t} + 10^{-6} (200 \sin(200t) + 200 \cos(200t)) \text{ A} \quad (78)$$

$$i(t) = Ae^{-200t} + 2 \times 10^{-4} (\sin(200t) + \cos(200t)) \text{ A} \quad (79)$$

Lastly, we need to solve for the value of the constant A which we will use the initial condition for.

$$i(0) = Ae^{-200 \times 0} + 2 \times 10^{-4} (\sin(200 \times 0) + \cos(200 \times 0)) \quad (80)$$

$$-2 \times 10^{-4} = A + 2 \times 10^{-4} \quad (81)$$

$$A = -4 \times 10^{-4} \quad (82)$$

Putting this all together, we get that our final solution for current $i(t)$ is:

$$i(t) = -4 \times 10^{-4} e^{-200t} + 2 \times 10^{-4} (\sin(200t) + \cos(200t)) \text{ A} \quad (83)$$

$$i(t) = -400e^{-200t} + 200 \sin(200t) + 200 \cos(200t) \mu\text{A} \quad (84)$$

where the transient response is $-400e^{-200t}$ (goes to 0 over time) and the forced response is $200 \sin(200t) + 200 \cos(200t)$.

(d) **(OPTIONAL) Solve for the voltage $v_C(t)$ across the capacitor.**

Solution: There are two ways to go about solving for $v_C(t)$:

(1) You can solve for the voltage by either setting up a differential equation for $v_C(t)$ and solving the differential equation or

(2) use the solution from part (a) and the IV relationship for a capacitor. For this problem, we are simply going to use our solution from part (a) and plug it into the voltage of a capacitor in terms of current:

$$v_C(t) = \frac{1}{C} \int_0^t i(t') dt' + v_C(0) \quad (85)$$

$$v_C(t) = \frac{1}{10^{-6}} \int_0^t \left(-4 \times 10^{-4} e^{-200t'} + 2 \times 10^{-4} \sin(200t') + 2 \times 10^{-4} \cos(200t') \right) dt' + 1 \quad (86)$$

$$v_C(t) = \frac{1}{10^{-6}} \left(\int_0^t -4 \times 10^{-4} e^{-200t'} dt' + \int_0^t 2 \times 10^{-4} \sin(200t') dt' + \int_0^t 2 \times 10^{-4} \cos(200t') dt' \right) + 1 \quad (87)$$

$$v_C(t) = -400 \left[\frac{e^{-200t'}}{200} \right]_0^t - 200 \left[\frac{\cos(200t')}{200} \right]_0^t + 200 \left[\frac{\sin(200t')}{200} \right]_0^t + 1 \quad (88)$$

$$v_C(t) = -2e^{-200t} + 2 - (\cos(200t) - 1) + (\sin(200t) - 0) + 1 \quad (89)$$

$$v_C(t) = -2e^{-200t} - \cos(200t) + \sin(200t) + 4 \text{ V} \quad (90)$$