

Discussion 3A

The following notes and sections are useful for this discussion: [Note j](#), Sections 4.5, 5.1, 5.2.

1. Analyzing a Second-Order Circuit (Hambley Example 4.5)

A DC source is connected to a series RLC circuit by a switch that closes at $t = 0$ as shown in Figure 1. The initial conditions are $i(0) = 0$ and $v_C(0) = 0$.


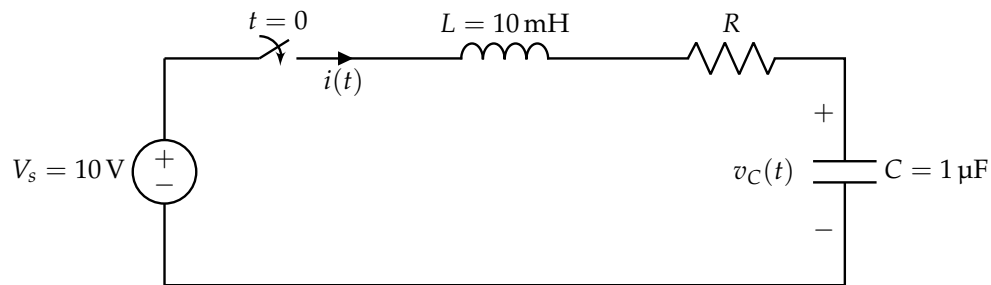


Figure 1: RLC Circuit

(a) Write the differential equation for $v_C(t)$

(b) **Solve for $v_C(t)$ if $R = 300\ \Omega$.**

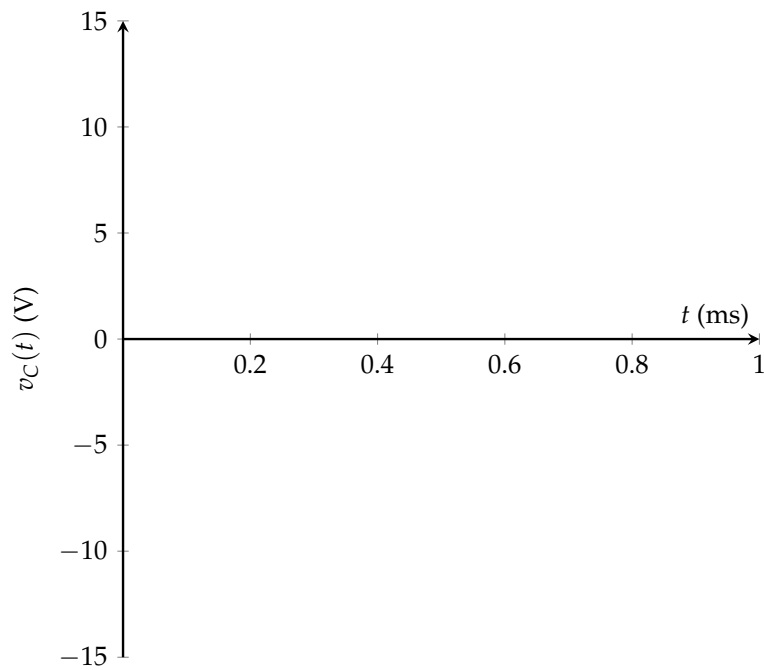
(c) **Plot the equation you calculated for $v_C(t)$.** It may be helpful to draw out each term in your general solution and then add them together.



2. Power Delivered by a Sinusoidal Source (Hambley Example 5.1)


Suppose that a voltage given by $v(t) = 100 \cos(100\pi t)$ V is applied to a $50\text{-}\Omega$ resistance.

(a) Sketch $v(t)$ to scale versus time.

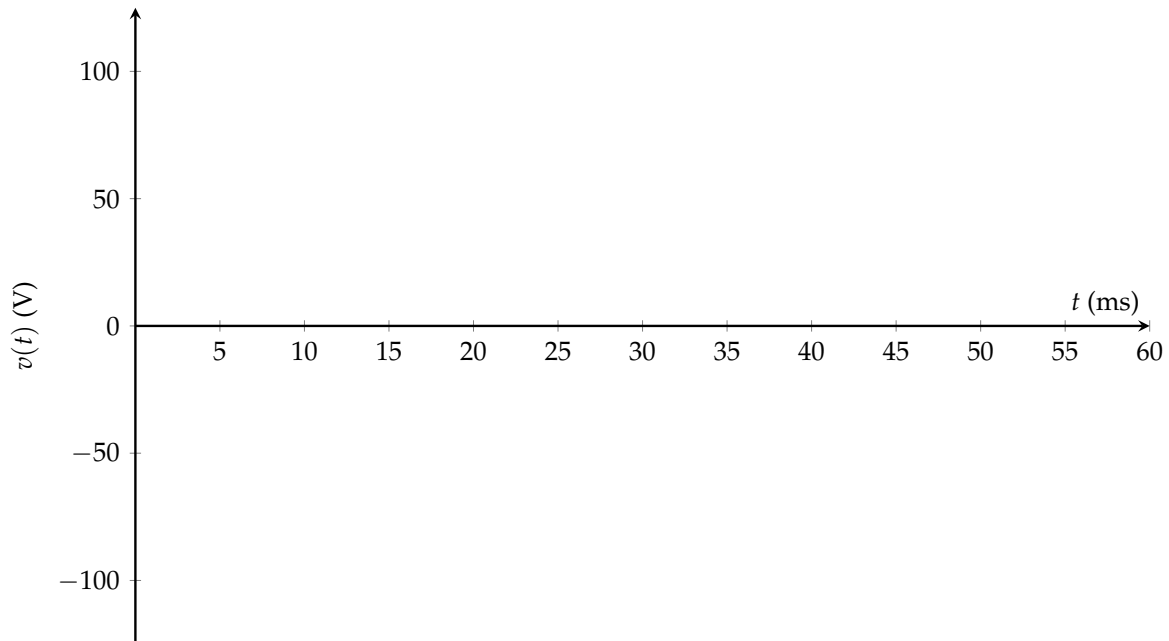

(b) Find the rms value of the voltage and the average power delivered to the resistance.

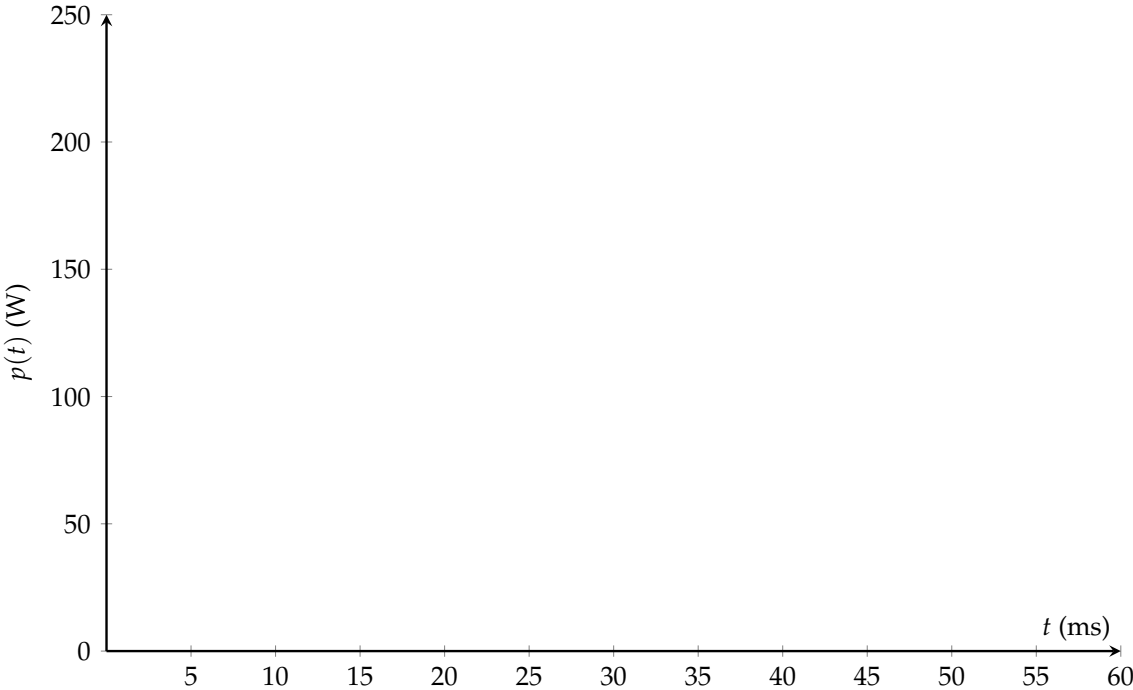(c) Find the power as a function of time and sketch to scale.



3. Complex Number Review

Recall Euler's Formula:

$$e^{j\theta} = \cos(\theta) + j \sin(\theta) \quad (1)$$

$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t) \quad (2)$$

Complex exponentials will also be seen written in a magnitude + phase notation as seen in the textbook. The following expressions are equivalent:

$$Re^{j\theta} = R\angle\theta \quad (3)$$

(a) Convert the following complex numbers from polar form to Cartesian form.

$$\mathbf{X}_1 = 2\sqrt{2}e^{j225^\circ} = 2\sqrt{2}\angle 225^\circ \quad (4)$$

$$\mathbf{X}_2 = e^{-j90^\circ} = 1\angle -90^\circ \quad (5)$$

(b) Convert the following complex numbers from Cartesian form to polar form.

$$\mathbf{X}_3 = 3 + j4 \quad (6)$$

$$\mathbf{X}_4 = -\sqrt{3} + j \quad (7)$$

(c) Plot the vectors from parts (a) and (b) on the complex plane.

