

Discussion 3B**1. Adding Sinusoids with Phasors (Hambley Example 5.3)**

Suppose you are given two sinusoidal inputs:

$$v_1(t) = 20 \cos(\omega t - 45^\circ) \quad (1)$$

$$v_2(t) = 10 \sin(\omega t + 60^\circ) \quad (2)$$

Add together the inputs $v_s(t) = v_1(t) + v_2(t)$ such that $v_s(t)$ is composed of a single cosine term.

2. Inductor Impedance (Hambley Exercise 5.6)

(a) A sample inductor circuit is given in Figure 1.

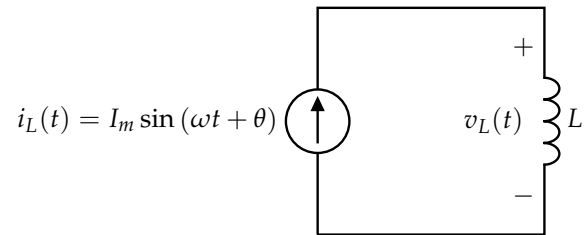



Figure 1: Sample inductor circuit

Derive the impedance of the inductor Z_L given that $\mathbf{V}_L = Z_L \mathbf{I}_L$.

(b) Assume that now you are told that a voltage of $v_L(t) = 10 \cos(20t)$ is applied to a 0.25-H inductance.

Calculate the impedance of the inductor, the phasor current, and the phasor voltage.

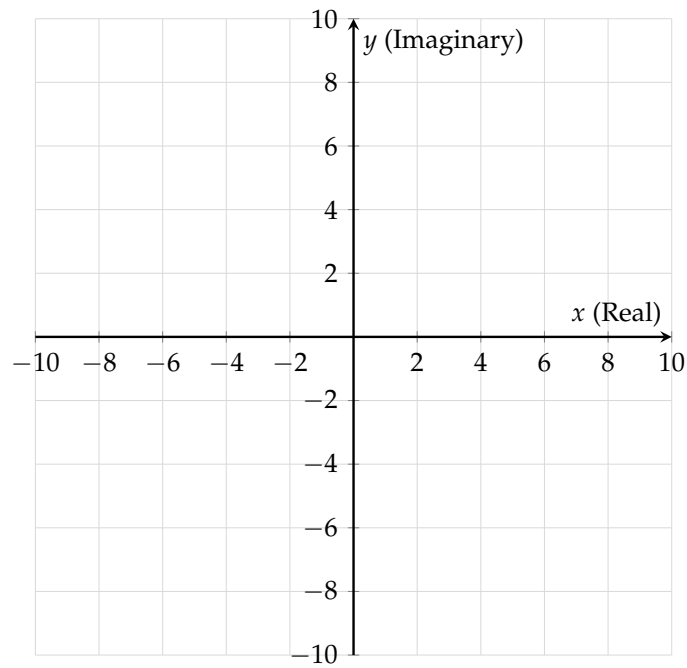- (c) Sketch the phasors V_L and I_L on the complex plane and state the phase relationship of the current and voltage of a pure inductance.



3. Series and Parallel Combinations of Complex Impedances

Consider the circuit shown in Figure 2.

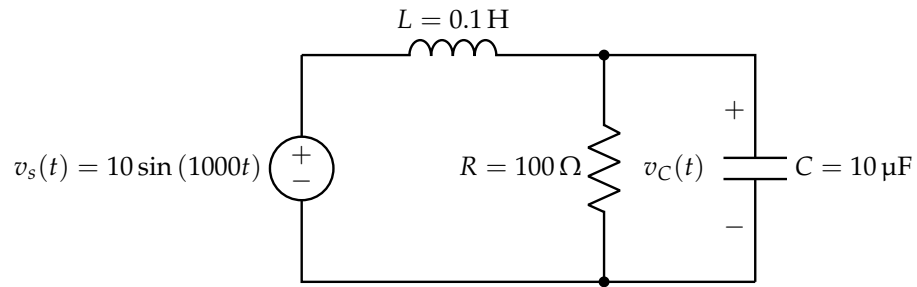


Figure 2: RLC Circuit

- Find the voltage $v_C(t)$ in steady state.
- Find the phasor current through each element.
- Sketch a phasor diagram showing the currents and the source voltage.