

1. Using the Transfer Function to Determine the Output (Hambley Example 6.1)

The transfer function $H(f)$ of a filter is shown in Figure 1.

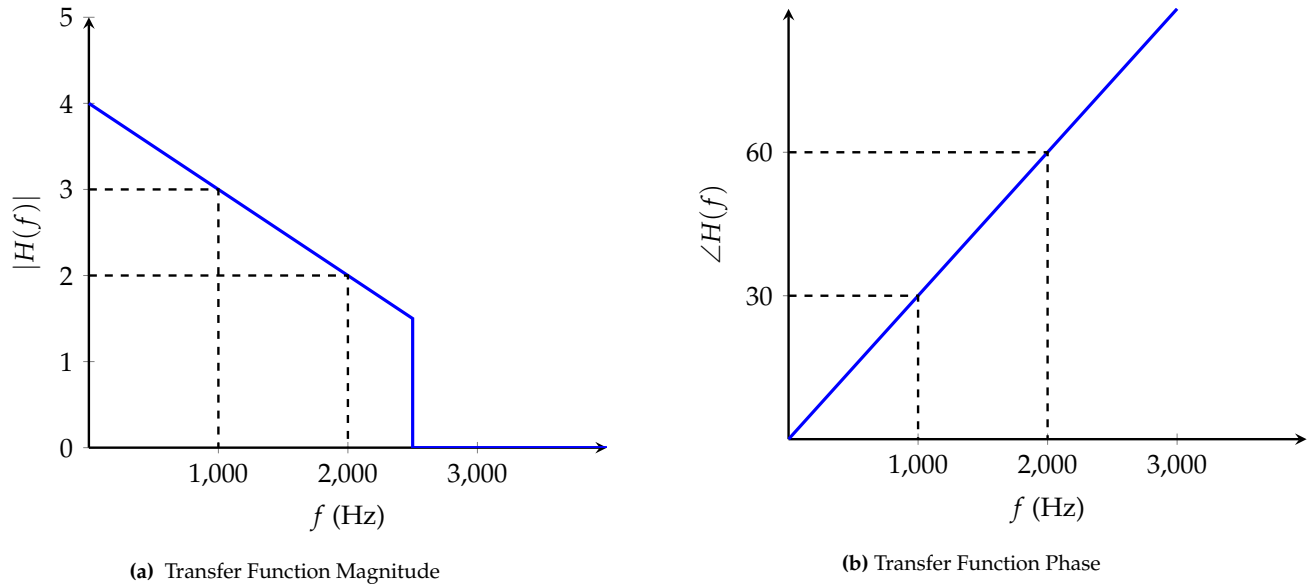


Figure 1: Transfer Function $H(f)$

If the input signal is given by

$$v_{in}(t) = 2 \cos(2000\pi t + 40^\circ) + 2 \cos(4000\pi t) \tag{1}$$

find an expression for the output of the filter $v_{out}(t)$.

Solution: Since our input is composed on two sinusoids with different frequencies we need to analyze them separately. Let's call:

$$v_{in,1} = 2 \cos(2000\pi t + 40^\circ) \tag{2}$$

$$v_{in,2} = 2 \cos(4000\pi t) \tag{3}$$

Let's first analyze the output of $v_{in,1}$. By inspection, we see that $\omega = 2000\pi$ and therefore $f = \frac{\omega}{2\pi} = 1000$ Hz. Using the provided graphs of the magnitude and phase, we can determine $|H(1000)| = 3$ and $\angle H(1000) = 30^\circ$. Putting this together we have:

$$H(1000) = 3\angle 30^\circ = \frac{V_{out,1}}{V_{in,1}} \tag{4}$$

The phasor for the input signal is $V_{in,1} = 2\angle 40^\circ$, so solving for the output phasor we have:

$$V_{out,1} = H(1000)V_{in,1} \tag{5}$$

$$= 3\angle 30^\circ \times 2\angle 40^\circ \tag{6}$$

$$= 6\angle 70^\circ \quad (7)$$

Converting the output phasor back into a time function, we have:

$$v_{\text{out},1}(t) = 6 \cos(2000\pi t + 70^\circ) \quad (8)$$

Now, we will apply the same process for $v_{\text{in},2}$. We observe that $\omega = 4000\pi$ and therefore, $f = 2000$ Hz. Then using the graphs we know that $|H(2000)| = 2$ and $\angle H(2000) = 60$. We also can represent $v_{\text{in},2}(t)$ as a phasor which would be $2\angle 0^\circ$. Putting this together and solving for the output phasor,

$$\mathbf{V}_{\text{out},2} = H(2000)\mathbf{V}_{\text{in},2} \quad (9)$$

$$= 2\angle 60^\circ \times 2\angle 0^\circ \quad (10)$$

$$= 4\angle 60^\circ \quad (11)$$

Converting this into a time function, we get:

$$v_{\text{out},2}(t) = 4 \cos(4000\pi t + 60^\circ) \quad (12)$$

Now combining the two output sinusoids we get:

$$v_{\text{out}}(t) = 6 \cos(2000\pi t + 70^\circ) + 4 \cos(4000\pi t + 60^\circ) \quad (13)$$

2. RC Filter (Hambley Example 6.3)

Suppose you have the RC circuit shown in Figure 2.

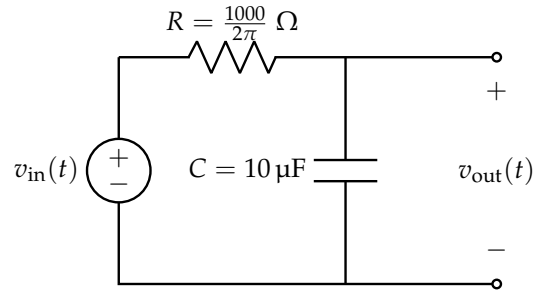


Figure 2: RC Lowpass Circuit

- (a) **Determine the transfer function $H(f)$ of the given circuit. Then, classify what type of filter this circuit is.** Recall that the transfer function $H(f)$ is defined as the ratio of the output phasor to the input phasor.

$$H(f) = \frac{\mathbf{V}_{\text{out}}}{\mathbf{V}_{\text{in}}} \quad (14)$$

Solution: To determine the transfer function, we can apply a sinusoidal input signal with phasor \mathbf{V}_{in} and then analyze the behavior of the circuit as a function of the source frequency f . The phasor current is given by dividing the input voltage phasor by the complex impedance of the circuit.

$$\mathbf{I} = \frac{\mathbf{V}_{\text{in}}}{R + \frac{1}{j2\pi fC}} \quad (15)$$

The phasor for the output voltage would be the product of the phasor current and the impedance of the capacitor:

$$\mathbf{V}_{\text{out}} = \frac{1}{j2\pi fC} \mathbf{I} \quad (16)$$

Then, substituting in our expression for \mathbf{I} , we have:

$$\mathbf{V}_{\text{out}} = \frac{1}{j2\pi fC} \times \frac{\mathbf{V}_{\text{in}}}{R + \frac{1}{j2\pi fC}} \quad (17)$$

$$\frac{\mathbf{V}_{\text{out}}}{\mathbf{V}_{\text{in}}} = \frac{1}{j2\pi fC \left(R + \frac{1}{j2\pi fC} \right)} \quad (18)$$

$$H(f) = \frac{1}{1 + j2\pi fRC} \quad (19)$$

An alternate solution involves applying the voltage divider principle with the complex impedances of the circuit.

$$\mathbf{V}_{\text{out}} = \frac{Z_C}{Z_R + Z_C} \mathbf{V}_{\text{in}} \quad (20)$$

$$\frac{\mathbf{V}_{\text{out}}}{\mathbf{V}_{\text{in}}} = \frac{\frac{1}{j2\pi fC}}{R + \frac{1}{j2\pi fC}} \quad (21)$$

$$H(f) = \frac{1}{1 + j2\pi fRC} \quad (22)$$

Plugging in the values for R and C , we get that our transfer function is:

$$H(f) = \frac{1}{1 + j \frac{f}{2\pi \times \frac{1000}{2\pi} \times 10 \times 10^{-6}}} = \frac{1}{1 + j \frac{f}{100}} \quad (23)$$

Now, to determine what type of filter this is, we can analyze the behavior for low and high ω . As $\omega \rightarrow 0$, notice that the magnitude of the transfer function $H(f)$ will get closer and closer to 1. On the other hand as $\omega \rightarrow \infty$, we see that the magnitude of the transfer function goes to 0. Therefore, we have that our circuit will attenuate/reduce high frequency and maintain low frequency signals, which leads us to conclude that we have a lowpass RC filter.

(b) Suppose, that you are given:

$$v_{in}(t) = 5 \cos(20\pi t) + 5 \cos(200\pi t) + 5 \cos(2000\pi t) \quad (24)$$

Find an expression for the output signal $v_{out}(t)$.

Solution: Let's call $v_{in,1} = 5 \cos(20\pi t)$, $v_{in,2} = 5 \cos(200\pi t)$, and $v_{in,3} = 5 \cos(2000\pi t)$ and their phasors $\mathbf{V}_{in,1}$, $\mathbf{V}_{in,2}$, and $\mathbf{V}_{in,3}$, respectively.

We have that:

$$\mathbf{V}_{in,1} = 5 \angle 0^\circ \quad (25)$$

$$\mathbf{V}_{in,2} = 5 \angle 0^\circ \quad (26)$$

$$\mathbf{V}_{in,3} = 5 \angle 0^\circ \quad (27)$$

Now, we must analyze the value of the transfer function at each of the different input frequency values. Recall that $f = \frac{\omega}{2\pi}$, therefore $f_1 = 10$ Hz, $f_2 = 100$ Hz, and $f_3 = 1000$ Hz.

$$H(f_1) = H(10) = \frac{1}{1 + j \frac{10}{100}} = 0.9950 \angle -5.71^\circ \quad (28)$$

$$H(f_2) = H(100) = \frac{1}{1 + j \frac{100}{100}} = 0.7071 \angle -45^\circ \quad (29)$$

$$H(f_3) = H(1000) = \frac{1}{1 + j \frac{1000}{100}} = 0.0995 \angle -84.29^\circ \quad (30)$$

Recall, that to simplify a fraction of complex numbers we can convert them into their polar form, then divide the magnitudes and subtract their phases. Taking $H(f_1)$ as an example:

$$H(f_1) = \frac{1}{1 + j0.1} \quad (31)$$

$$= \frac{1 \angle 0^\circ}{\sqrt{1^2 + 0.1^2} \angle \arctan\left(\frac{0.1}{1}\right)} \quad (32)$$

$$= \frac{1 \angle 0^\circ}{1.005 \angle 5.71^\circ} \quad (33)$$

$$= \frac{1}{1.005} \angle 0^\circ - 5.71^\circ \quad (34)$$

$$= 0.9950 \angle -5.71^\circ \quad (35)$$

The output phasor for each input phasor is simply the product of the input phasor with the transfer function evaluated at the given frequency $\mathbf{V}_{\text{out},1} = H(f_1)\mathbf{V}_{\text{in},1}$. Thus we have:

$$\mathbf{V}_{\text{out},1} = H(f_1)\mathbf{V}_{\text{in},1} = (0.9950\angle-5.71^\circ) \times (5\angle 0^\circ) \quad (36)$$

$$= 4.975\angle-5.71^\circ \quad (37)$$

$$\mathbf{V}_{\text{out},2} = H(f_2)\mathbf{V}_{\text{in},2} = 0.7071\angle-45^\circ \times (5\angle 0^\circ) \quad (38)$$

$$= 3.535\angle-45^\circ \quad (39)$$

$$\mathbf{V}_{\text{out},3} = H(f_3)\mathbf{V}_{\text{in},3} = 0.0995\angle-84.29^\circ \times (5\angle 0^\circ) \quad (40)$$

$$= 0.4975\angle-84.29^\circ \quad (41)$$

Converting the output phasors into their sinusoidal representations, we get:

$$v_{\text{out},1}(t) = 4.975 \cos(20\pi t - 5.71^\circ) \quad (42)$$

$$v_{\text{out},2}(t) = 3.535 \cos(200\pi t - 45^\circ) \quad (43)$$

$$v_{\text{out},3}(t) = 0.4975 \cos(2000\pi t - 84.29^\circ) \quad (44)$$

Lastly, we we sum together the output components to get:

$$v_{\text{out}} = 4.975 \cos(20\pi t - 5.71^\circ) + 3.535 \cos(200\pi t - 45^\circ) + 0.4975 \cos(2000\pi t - 84.29^\circ) \quad (45)$$

The important concept to understand here is that each input signal is impacted differently by the filter due to their varying frequencies. You can see that the $f = 10$ Hz input signal did not change much in amplitude and phase. On the other hand $f = 100$ Hz had its amplitude reduced by a factor of 0.7071 and phase shifted by -45° . Lastly the $f = 1000$ Hz signal is reduced by a whole order of magnitude (10^{-1}), demonstrating the lowpass behavior of the filter.

3. LR Filter (Hambley Exercise 6.5)

Suppose you are given the following circuit:

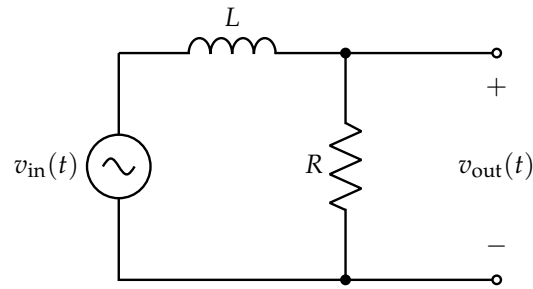


Figure 3: LR Circuit

Derive the transfer function of this filter, classify what type of filter it is, and determine an expression for the half-power frequency f_B .

Solution: Let's first convert our circuit into the phasor domain.

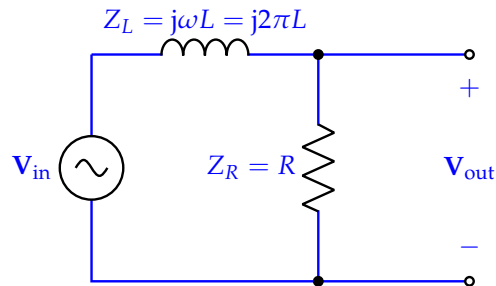


Figure 4: LR Circuit

Now, we can apply the voltage divider principle to write V_{out} in terms of V_{in} . You can also apply node-voltage analysis to solve for the transfer function as well.

$$V_{\text{out}} = \frac{Z_R}{Z_R + Z_L} V_{\text{in}} \quad (46)$$

$$V_{\text{out}} = \frac{R}{R + j2\pi f L} V_{\text{in}} \quad (47)$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R}{R + j2\pi f L} \quad (48)$$

$$H(f) = \frac{R}{R + j2\pi f L} \quad (49)$$

$$H(f) = \frac{1}{1 + j2\pi f \frac{L}{R}} \quad (50)$$

Notice that we can rewrite our transfer function to take on the same form as the low pass filter:

$$H(f) = \frac{1}{1 + j\frac{f}{f_B}} = \frac{1}{1 + j\frac{f}{\frac{R}{2\pi L}}} \quad (51)$$

Another way to determine that this is a lowpass filter is to analyze the magnitude of the transfer function as $f \rightarrow 0$ and $f \rightarrow \infty$. As $f \rightarrow 0$, we notice that the magnitude of the filter approaches 1, whereas when $f \rightarrow \infty$, the magnitude of the denominator will go to ∞ , which indicates that the magnitude of the overall transfer function will go to 0. This behavior of maintaining low frequency signals but reducing high frequency signals makes it a lowpass filter.

For this LR filter, we have that the half-power frequency is:

$$f_B = \frac{R}{2\pi L} \quad (52)$$