
Homework 1



This homework is due on Friday, September 2, 2022, at 11:59PM. Self-grades and HW Resubmissions are due on the following Friday, September 9, 2022, at 11:59PM.

1. Hambley P3.7

A constant (dc) current $i(t) = 3 \text{ mA}$ flows into a $50 \mu\text{F}$ capacitor. The voltage at $t = 0$ is $v(0) = -20 \text{ V}$. The references for $v(t)$ and $i(t)$ have the passive configuration. Find the power at $t = 0$ and state whether the power flow is into or out of the capacitor. Repeat for $t = 1$.

2. Hambley P3.16

A capacitance and the current through it are shown in Figure 1 and Figure 2 respectively. At $t = 0$, the voltage is $v_C(0) = 10$ V. Sketch the voltage, power, and stored energy to scale versus time.

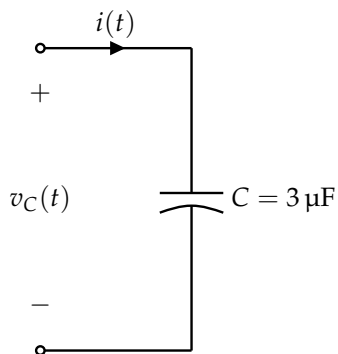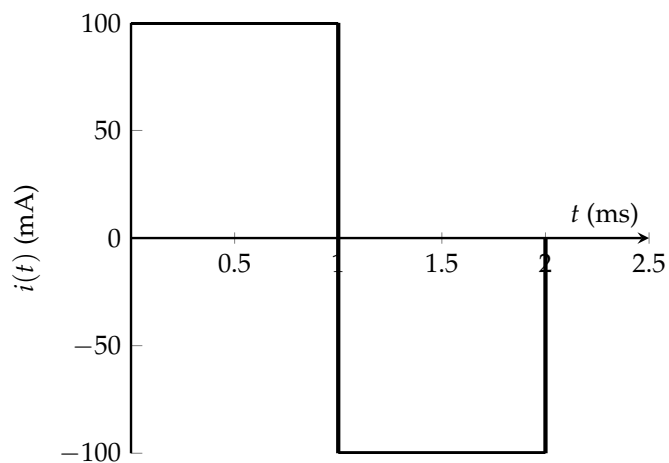**Figure 1:** Circuit for P3.16**Figure 2:** Current vs Time for P3.16

3. Hambley P3.34

We have a parallel-plate capacitor, with each plate having a width w and a length ℓ . The plates are separated by air with a distance d . Assume that ℓ and w are both much larger than d . The maximum voltage that can be applied is limited to $V_{\max} = Kd$, in which K is called the breakdown strength of the dielectric. Derive an expression for the maximum energy that can be stored in the capacitor in terms of K and the volume of the dielectric. If we want to store the maximum energy per unit volume, does it matter what values are chosen for ℓ , w , and d ? What parameters are important?

4. Hambley P3.43

The current flowing through a 2 H inductance is shown in Figure 3. Sketch the voltage, power, and stored energy vs time.

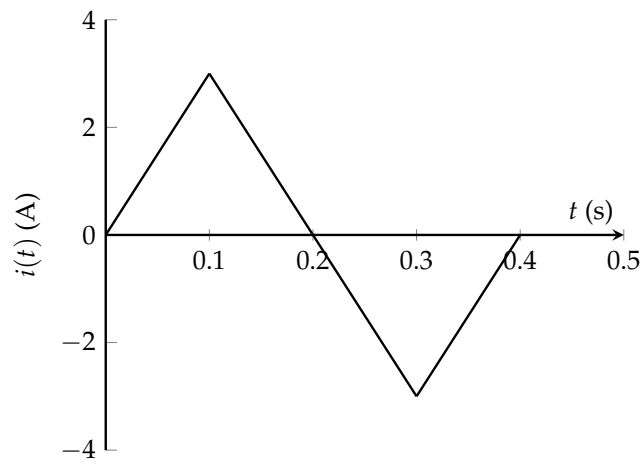


Figure 3: Current vs Time for P3.43

5. Hambley P3.7

The current in a 100 mH inductance is given by $0.5 \sin(1000t)$ A. Find expressions and sketch the waveforms to scale for the voltage, power, and stored energy, allowing t to range from 0 to 3π ms. The argument of the sine function is in radians.

6. Hambley P3.55

What value of inductance corresponds to an open circuit, assuming zero initial current? Explain your answer. Repeat for a short circuit.

7. Hambley P3.74

A pair of mutually coupled inductances has $L_1 = 2\text{ H}$, $L_2 = 1\text{ H}$, $i_1 = 2\cos(1000t)\text{ A}$, $i_2 = 0$, and $v_2 = 2000\sin(1000t)\text{ V}$. (The arguments of the sine and cosine functions are in radians.) Find $v_1(t)$ and the magnitude of the mutual inductance.