


Lab 2: Analog to Digital Circuit Interfaces

EECS 16B Fall 2022

Slides: links.eecs16b.org/lab2-slides



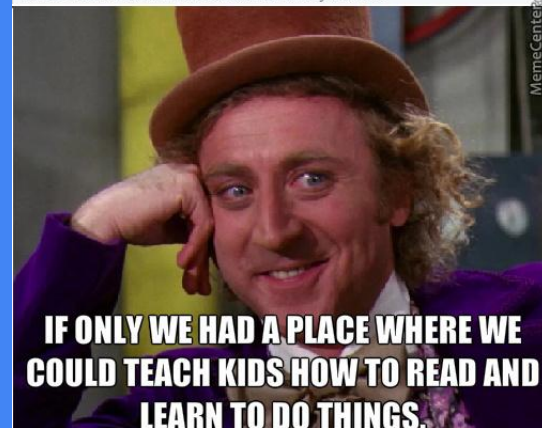Schools Are Removing Analogue Clocks Because Kids Can't Read Them
As our age becomes more technological, we've become more dependant on the our screens. And this has had a very drama...



**IF ONLY WE HAD A PLACE WHERE WE
COULD TEACH KIDS HOW TO READ AND
LEARN TO DO THINGS.**

Logistics: Makeups/Extensions

- **Makeup:** you need to attend a different lab section to finish the lab on time
 - Sign up at <https://makeup.eecs16b.org>
 - Only one group member needs to sign up
 - Labs are due by the end of your next section
- **Extension:** you need additional time to complete the lab
 - Same form as HW Extensions: <https://eecs16b.org/extensions>
 - Without an extension, late labs are 50% credit


Lab 2 Overview: DAC and ADC

- DAC = Digital to Analog Converter
- ADC = Analog to Digital Converter
- Real world is continuous, but computers need to store data digitally
 - Need to find a way to convert between analog and digital for signals
 - ~~• EE 123 discusses consequences of digitally sampling analog signals, EE 140 discusses the design of DACs/ADCs~~
- DAC/ADC in your life:
 - DAC for MP3 players, analog TVs, video on cell phones
 - ADC for sound/video recording
 - VoIP (voice over IP) uses both!


~~Can you think of a few more examples?~~

Review: Superposition

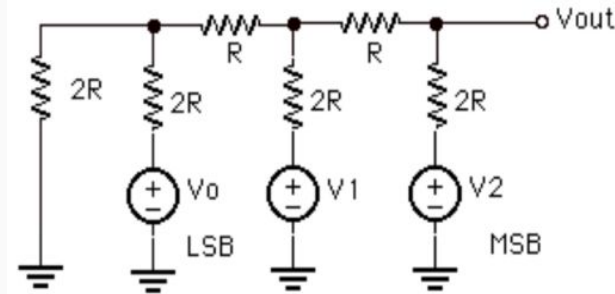
- Since resistive circuits are linear, we can apply the principle of superposition:
 - Treat each source independently – zero out all but one
 - The total effect is the sum of the effects of each source
- Example:


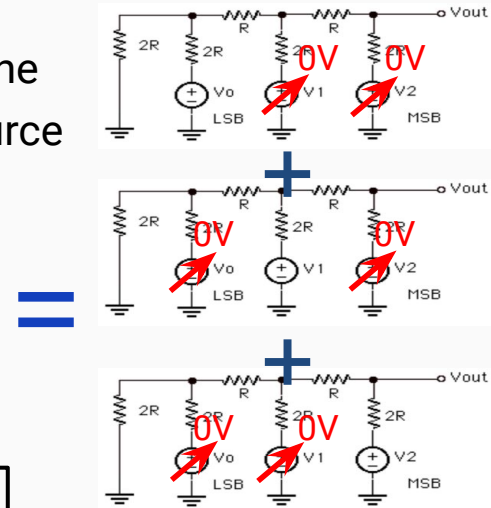
$$V_{out} = V_{out_1} + V_{out_2} + V_{out_3}$$




Review: Superposition Example

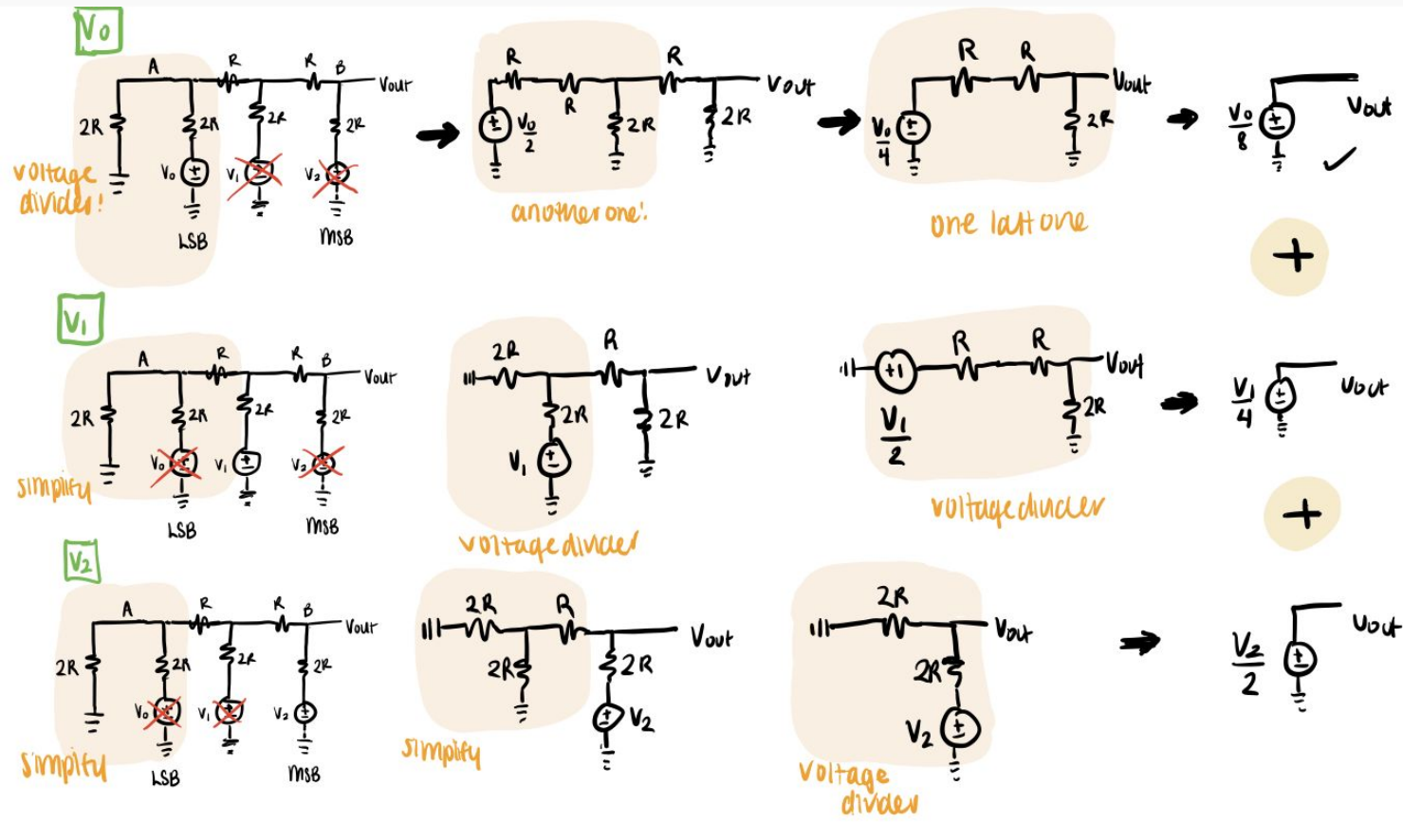

Review: Superposition Example

$$V_{out} = \frac{V_0}{8} + \frac{V_1}{4} + \frac{V_2}{2}$$

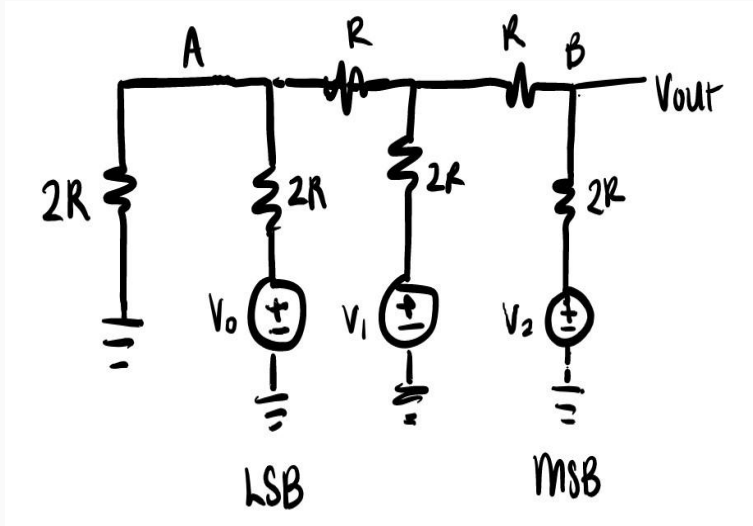least significant bit most significant bit



Treat each input as a bit. 3 bits represents 0 to $2^3 - 1 = 7$, [0, 7]

You can set $V_0 = V_1 = V_2 = 8V$ and it'll give you $\rightarrow 0b111$

$$V_{out} = \frac{V_0}{8} + \frac{V_1}{4} + \frac{V_2}{2} = 1 + 2 + 4 = 7$$

'turn off' $V_0 = 0V \rightarrow 0b110$

$$V_{out} = \frac{V_0^0}{8} + \frac{V_1}{4} + \frac{V_2}{2} = 0 + 2 + 4 = 6$$

'turn on' $V_0 = 8V$, 'turn off' $V_1 = 0V \rightarrow 0b101$


$$V_{out} = \frac{V_0}{8} + \frac{V_1^0}{4} + \frac{V_2}{2} = 1 + 0 + 4 = 5$$

we can keep going, counting down to 0.

$0b100 = 4_{10}$, $0b011 = 3_{10}$, $0b010 = 2_{10}$, $0b001 = 1_{10}$, $0b000 = 0_{10}$


Review: Comparators

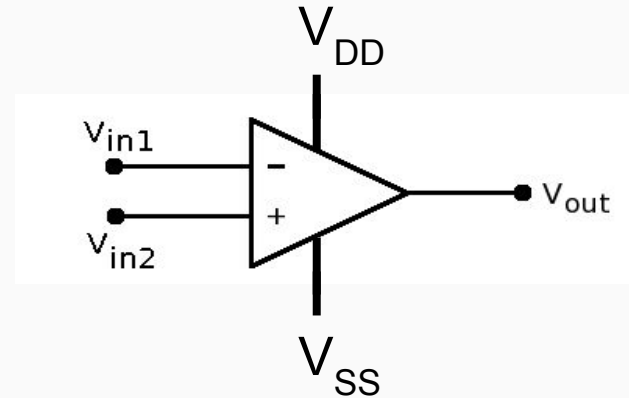- A device that compares two voltages (or currents) and outputs a digital signal to indicate which is larger
- Op-amp Implementation:
 - If $V_{in2} > V_{in1}$, V_{out} goes to VDD
 - If $V_{in1} > V_{in2}$, V_{out} goes to VSS
 - (think: if V_{out} is connected to V^- , its value will bring V^- closer to V^+)
- NOTE: Arduinos use 5V pin logic
 - VDD = 5 V
 - VSS = 0 V




Review: ADC

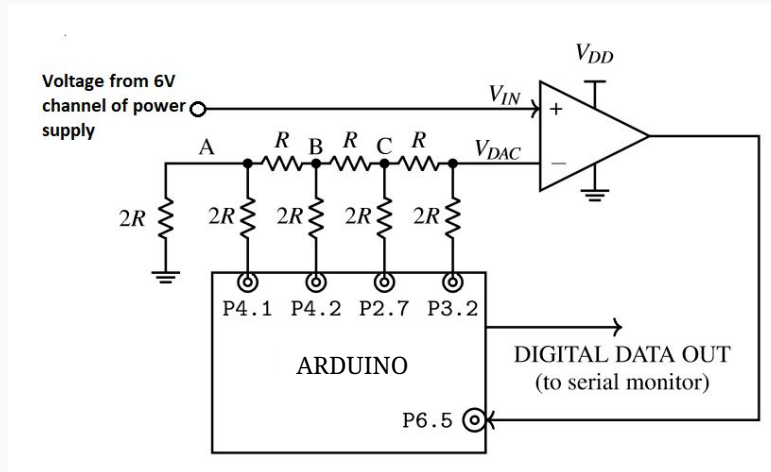- ADC - The Arduino uses binary search when turning on MSB (most significant bit) to LSB (least significant bit) and comparing the resulting V_{DAC} with V_{in}





Successive Approx. Register ADC

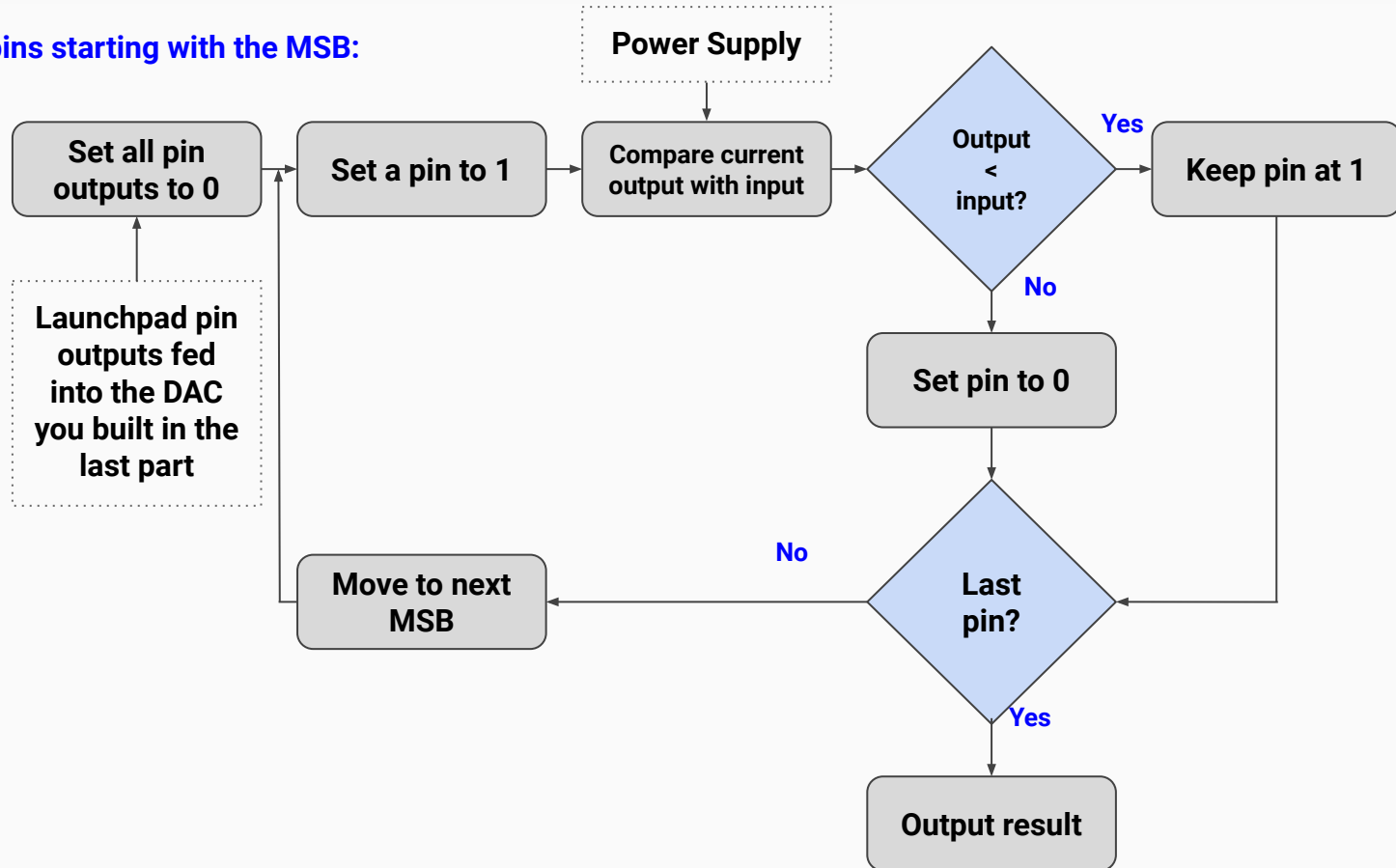Loop over all pins starting with the MSB:




Successive Approx. Register ADC

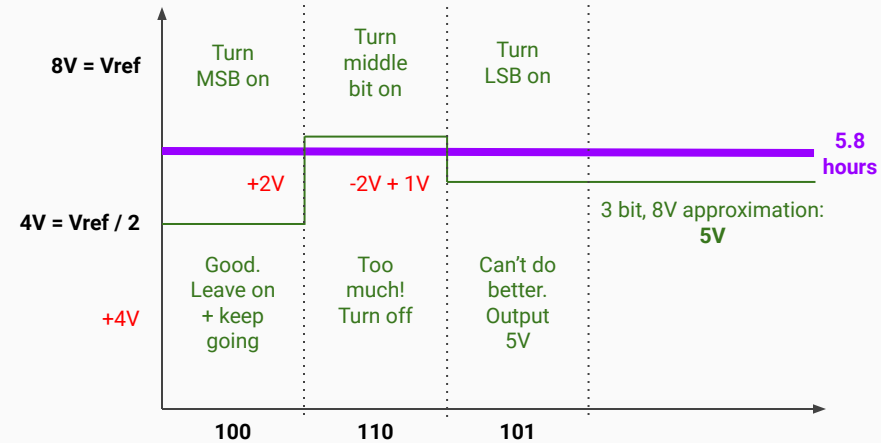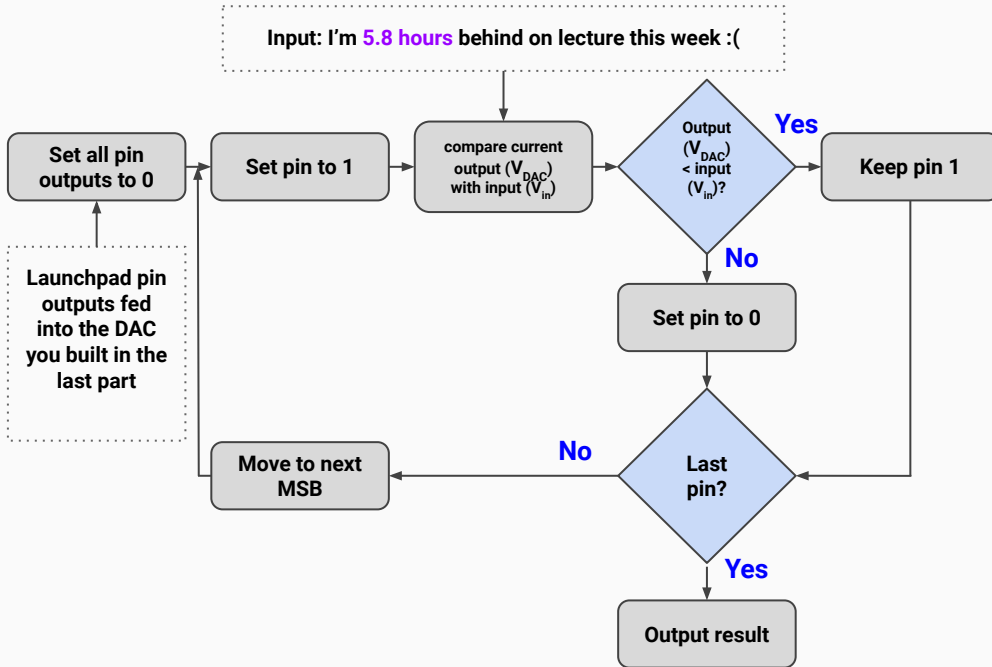Input: I'm 5.8 hours behind on lecture this week :(



Result: We forget to account for the last 0.8 hour of lecture because our 3 bits cannot represent it. :(

Successive Approx. Register ADC

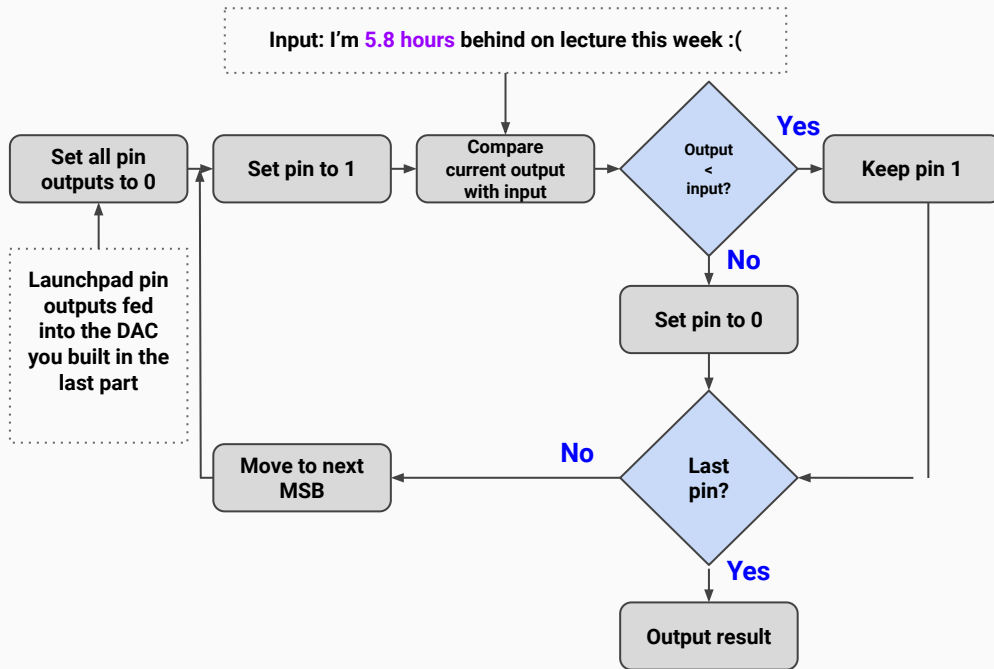


We're trying to match our 5.8V input:

- $V_{ref} = 8V$, we have 3 bits
- 1. Turn on MSB: **1 0 0**
 $4V < 5.8V$, keep going, keep bit on
- 1. We can do better: **1 1 0**
 $(4V + 2V) > 5.8V$, too much, turn off
- 1. Try the next pin (LSB): **1 0 1**
 $(4V + 1V) < 5.8V$
- 1. That's all folks, we're out of bits
Output: 5V


Result: We forget to account for the last 0.8 hour of lecture because our 3 bits cannot represent it. :(

Introduction to Arduinos

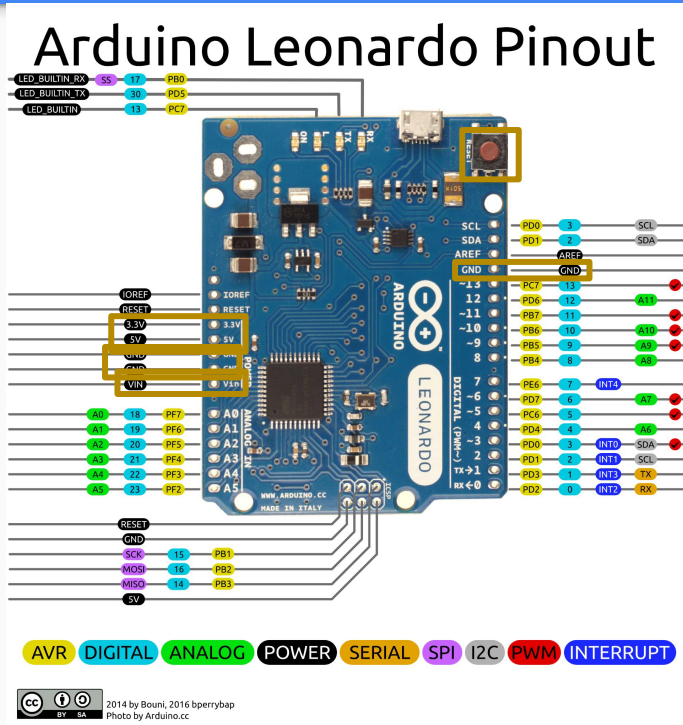

- There are 4 main “Pin Modes”
- Digital: High (5V) or Low (0V)
 1. Digital Output
 2. Digital Input
- Analog: range from 0-5V
 3. Analog Output: mapped from 0 - 255
 4. Analog Input: mapped to 0 - 1023

Introduction to Arduinos

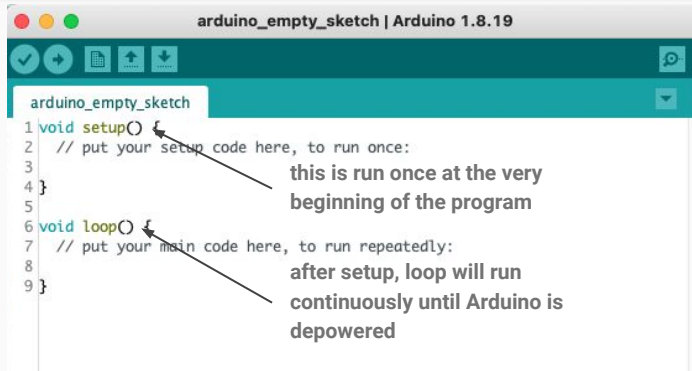

```
arduino_empty_sketch | Arduino 1.8.19
arduino_empty_sketch
1 void setup() {
2   // put your setup code here, to run once:
3
4 }
5
6 void loop() {
7   // put your main code here, to run repeatedly:
8
9 }
```

Annotations:

- Arrow pointing to line 1: **this is run once at the very beginning of the program**
- Arrow pointing to line 6: **after setup, loop will run continuously until Arduino is depowered**

Note: Arduino is programmed in **C** via the [Arduino IDE](#) (pre-installed on lab computers)


- Code is uploaded from computer to Arduino via microUSB port
- If powered, code is ALWAYS running
 - RST -> restart
 - Unpowering and powering Arduino -> begin re-running whatever was last uploaded
- If you find this to be an issue, the easiest solution is to upload a blank program

Quick Rundown: Arduino vs Launchpads

- Launchpads operate on 3.3V logic while Arduinos operate on 5V logic
 - However, for most labs other than this one, we will be keeping our circuits operating at 3.3V for stability reasons.
- External Power: the Launchpad can take 5V as an input to its 5V pin, while Arduino requires 7-12V as an input to its V_{in} pin.
 - safe to power the Arduino via both the micro-USB and V_{in} at the same time
 - Launchpads... however... go bakoom
- You actually see the word Arduino outside of 16B, when did you ever see the word “Launchpad” other than complaints about 16B




Uploading Code to Arduino

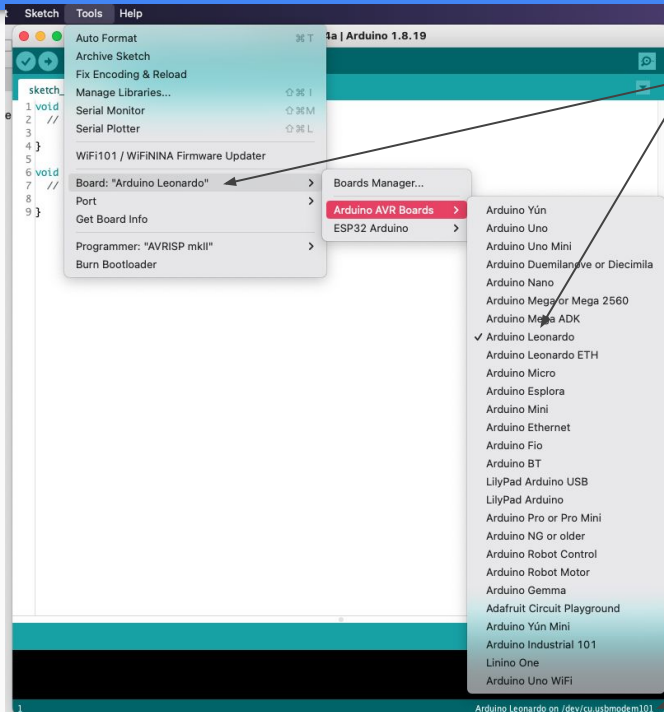

Ensure this says *Arduino Leonardo*, otherwise select it

- PORT selection
- Upload button

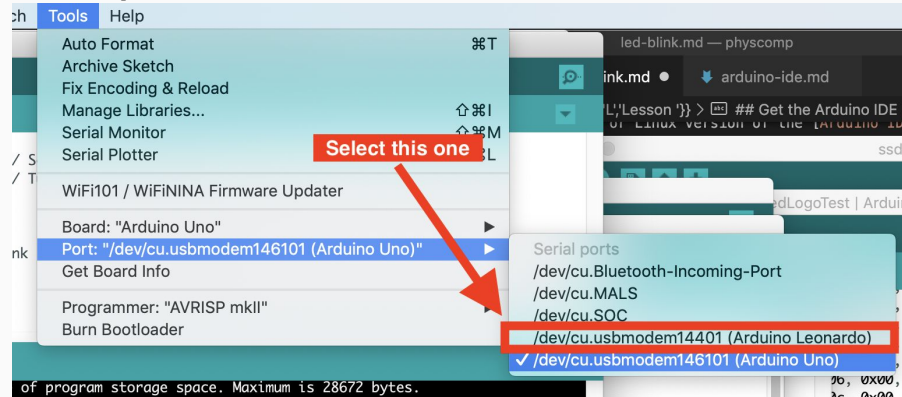

Arduino *should* auto-detect your port

(works 100% of the time 25% of the time)

Arduino Logistics

- Arduinos will be passed out during lab today
- **Arduinos are property of 16B and have to be returned to us by the end of the semester**
- Each Arduino will have a unique ID
 - Fill out <https://eecs16b.org/lab-groups> once you've received your Arduino

General Reminders/Habits

- connect all grounds together, including the Arduino GND pin (any works)
- In general, avoid having voltage/currents going into your Arduino if your Arduino isn't already powered
- Check that your probes are working by probing a known voltage value
 - I.e. 5V/3.3V/GND from power supply
- PLEASE CLEAN UP AFTER YOURSELF!! Put probes back, pack up kits, etc.
- Don't unplug computers

Let's get into it!

Important Forms/Links

- Help request form: <https://eecs16b.org/lab-help>
- Checkoff request form: <https://eecs16b.org/lab-checkoff>
- Extension Requests: <https://eecs16b.org/extensions>
- Slides: <links.eecs16b.org/lab2-slides>
- Anon Feedback: <https://eecs16b.org/lab-anon-feedback>
- <https://eecs16c.org>