

EECS 16B

Designing Information Devices and Systems II
Lecture 2

Prof. Sayeef Salahuddin

Department of Electrical Engineering and Computer Sciences, UC Berkeley,
sayeef@eecs.berkeley.edu

Recap: Current flow in a Capacitor

Current flow through a capacitor is proportional to the rate of change in potential difference of the plates

$$i = C \frac{dv}{dt}$$

Time Varying Voltage


$$v(t) = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$$

Also, from the definition of current

$$i = \frac{dq}{dt}$$

Time Varying Charge

$$q(t) = \int_{t_0}^t i dt + q(t_0)$$

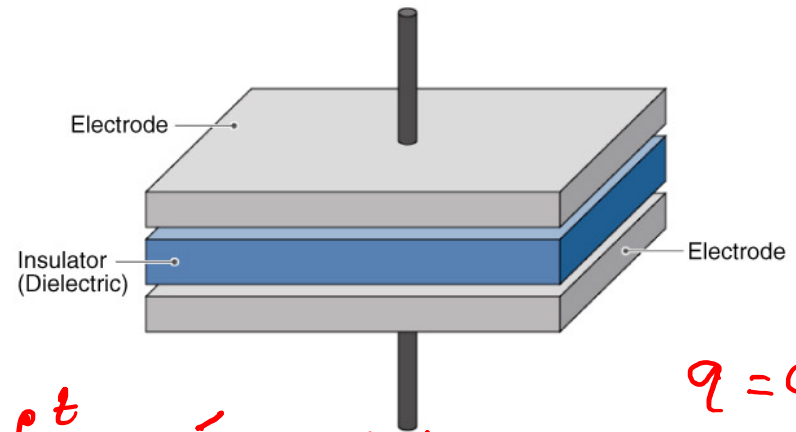


$$v(t) = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$$

$$q = cv$$

$$\frac{dq}{dt} = c \frac{dv}{dt}$$

$$i = c \frac{dv}{dt}$$

Recap: Current in an Inductor

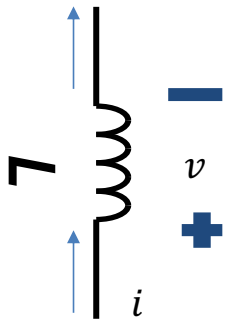

$$v(t) = L \frac{di}{dt}$$
$$i(t) = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$$

Remember the capacitors

$$i = C \frac{dv}{dt}$$
$$v(t) = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$$


Outline

- Outline
 - Mutual Inductance
 - DAC and ADC
 - R-C circuits
 - R-L circuits
 - Steady State

- Reading: Section 3.6, 4.1-4.4, Slides

Mutual Inductance

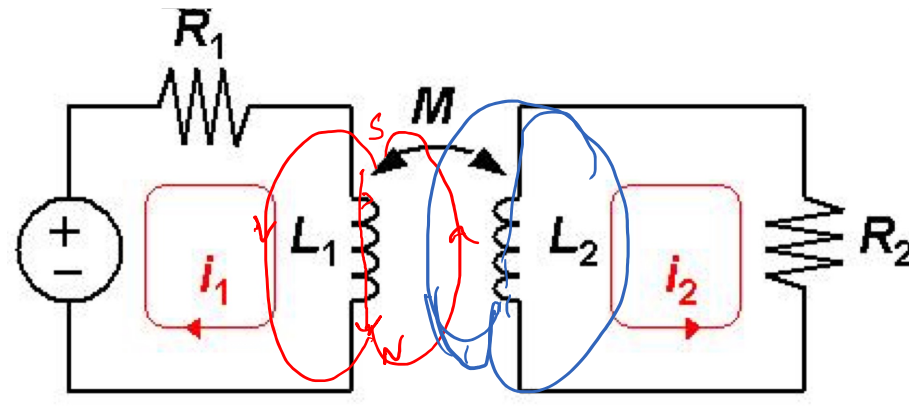
- Mutual inductance occurs when two windings are arranged so that they have a mutual flux linkage
- The change in current in one winding causes a voltage drop to be induced in the other



Transformers (adapters), motors, generators (electric cars)

The Dot Convention

- If a current enters the dotted terminal of a coil, the reference polarity of the voltage induced in the other coil is positive at its dotted terminal.
- If a current leaves the dotted terminal of a coil, the reference polarity of the voltage induced in the other coil is negative at its dotted terminal.
- Total voltage induced in a coil is a summation of its own induced voltage and the mutually induced voltage

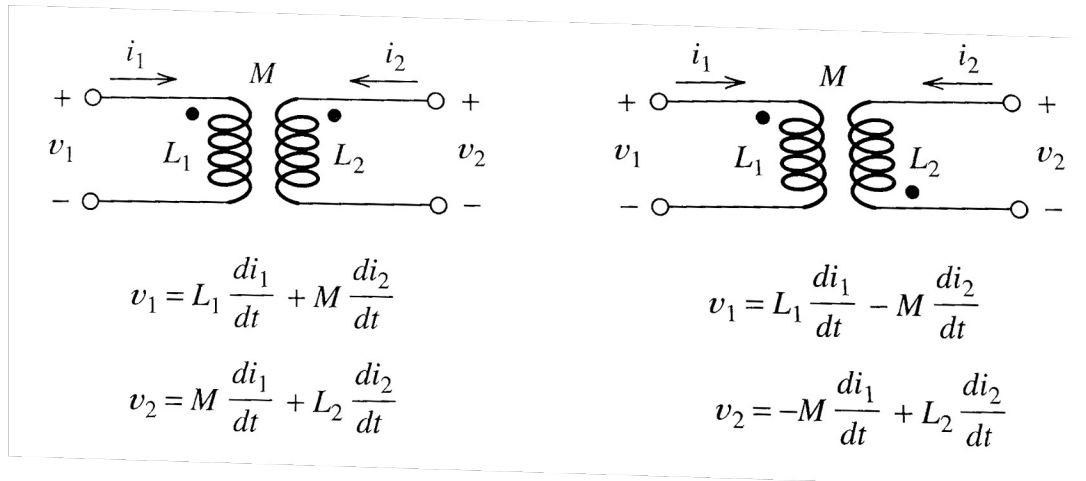

Summary

Capacitors:

$$i = C \frac{dv}{dt}$$
$$w = \frac{1}{2} C v^2$$

- v cannot change instantaneously
- i **can** change instantaneously (do not short circuit a charged capacitor)

- N capacitors in series $\frac{1}{C_{eq}} = \sum_{i=1}^N \frac{1}{C_i}$

- N capacitors in parallel $C_{eq} = \sum_{i=1}^N C_i$

Inductors:


$$v = L \frac{di}{dt}$$
$$w = \frac{1}{2} L i^2$$

- i cannot change instantaneously
- v **can** change instantaneously (do not open an inductor with current)


- N inductors in series $L_{eq} = \sum_{i=1}^N L_i$

- N inductors in parallel $\frac{1}{L_{eq}} = \sum_{i=1}^N \frac{1}{L_i}$

R-2R Ladder Digital-to-Analog Converter

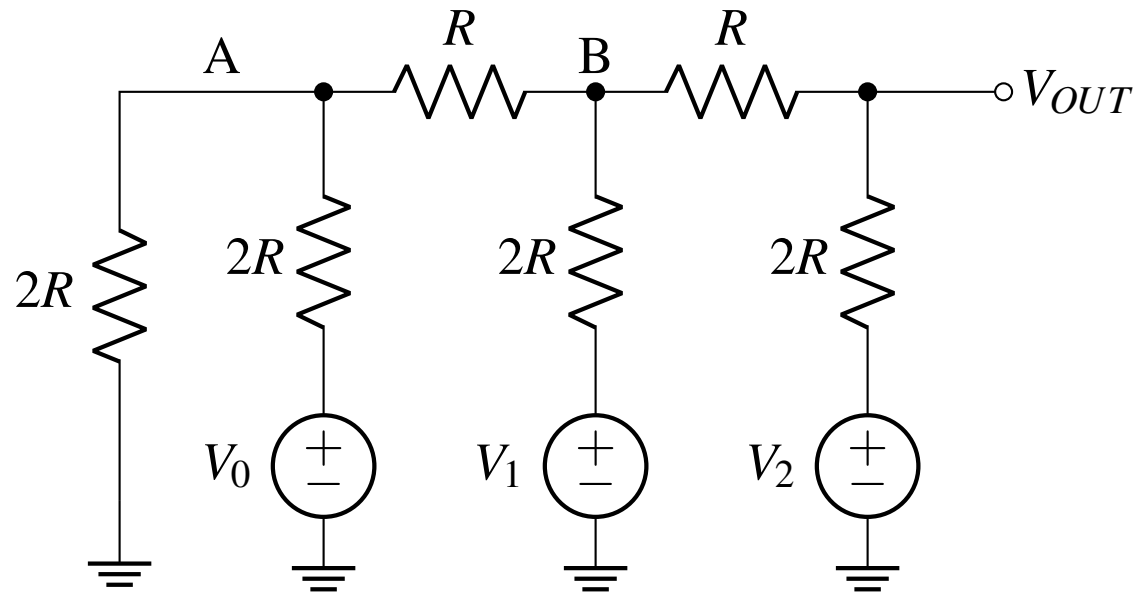


Remember Superposition and Equivalence?

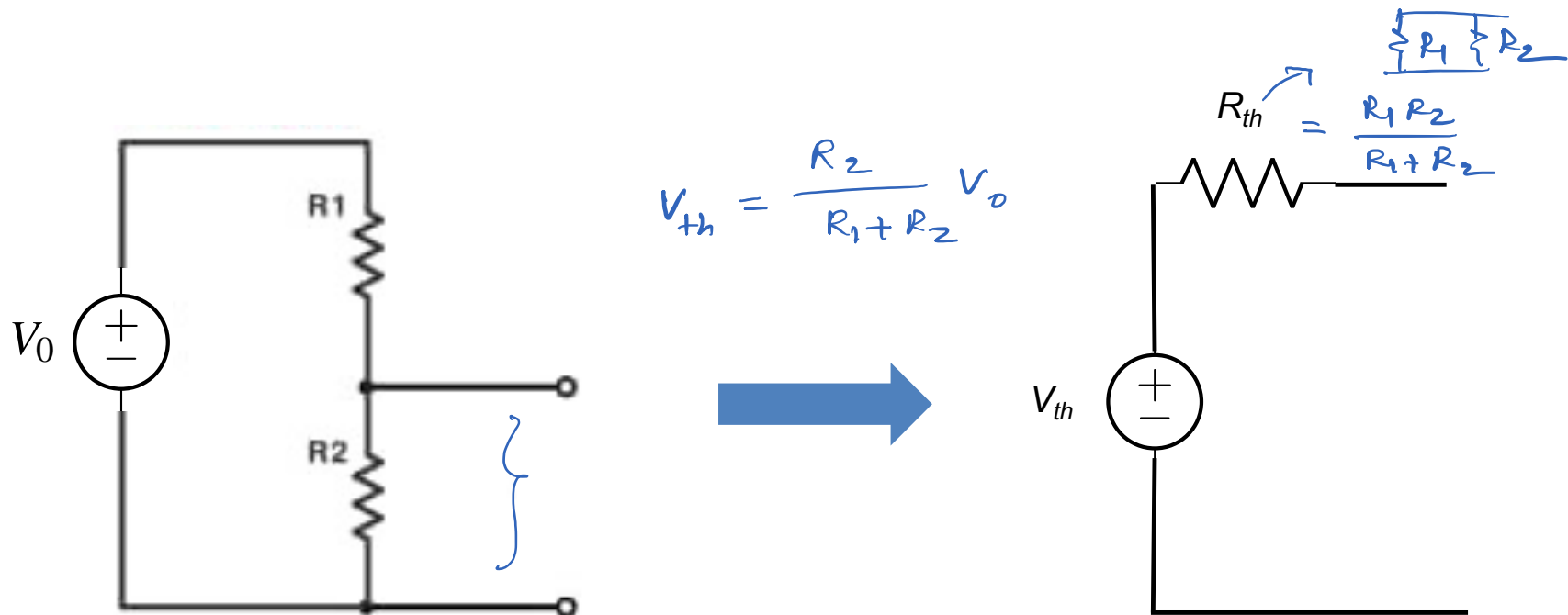

Thevenin Equivalent


R-2R Ladder Digital-to-Analog Converter

Use superposition: Start with V_0

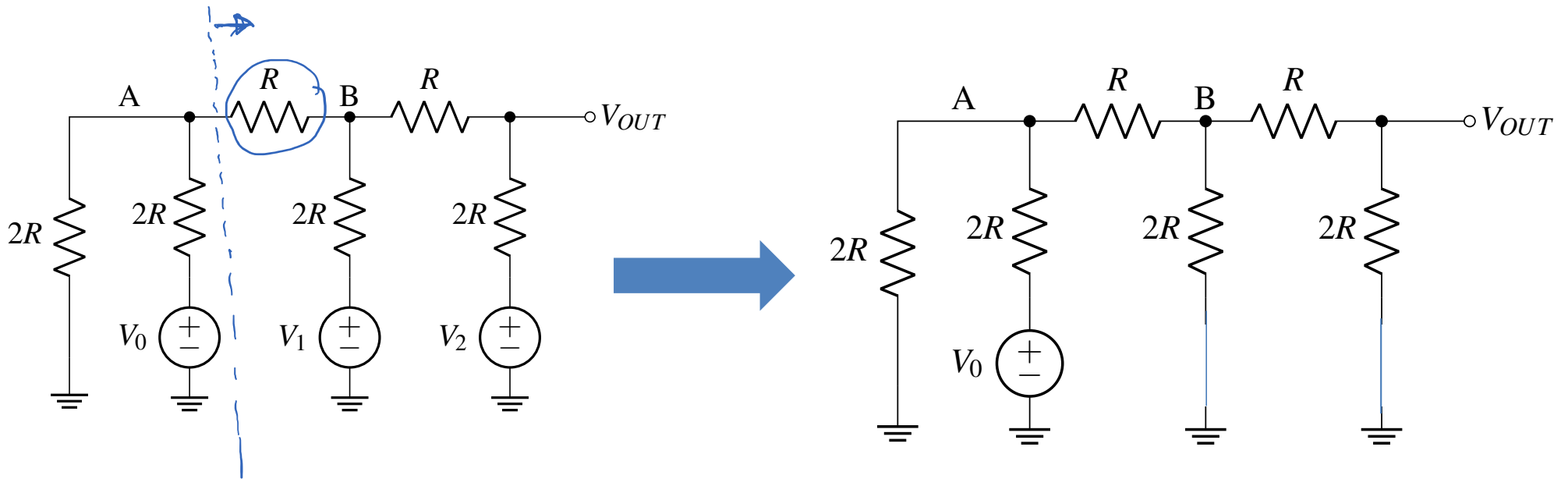


R-2R Ladder Digital-to-Analog Converter

Use superposition: Start with V_0

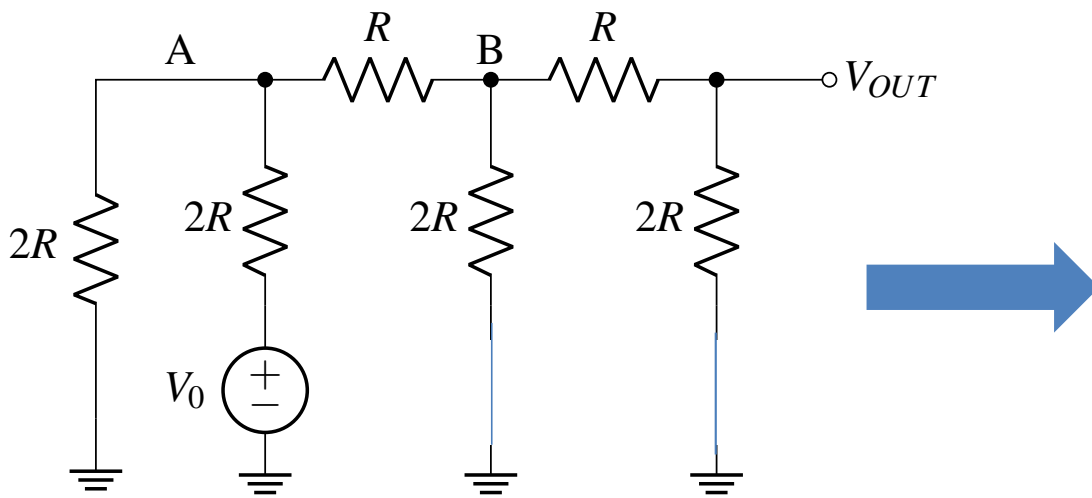


R-2R Ladder Digital-to-Analog Converter

Using Thevenin Equivalent

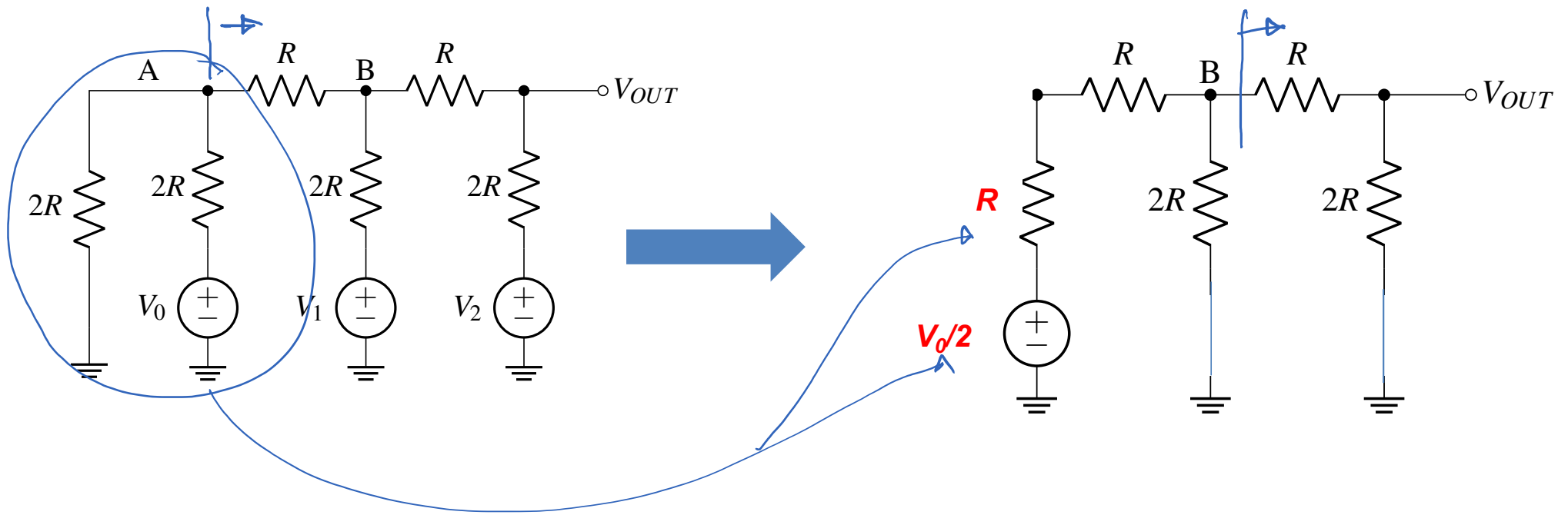


R-2R Ladder Digital-to-Analog Converter

Using Thevenin Equivalent

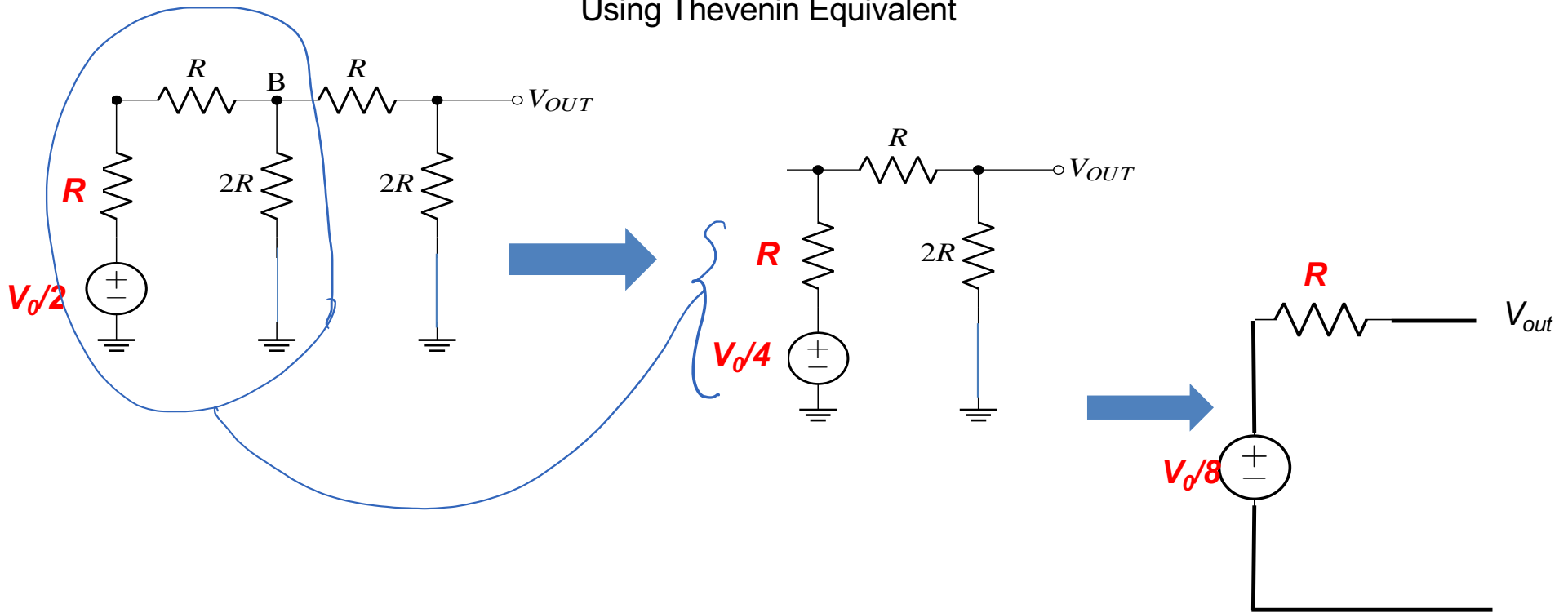


R-2R Ladder Digital-to-Analog Converter

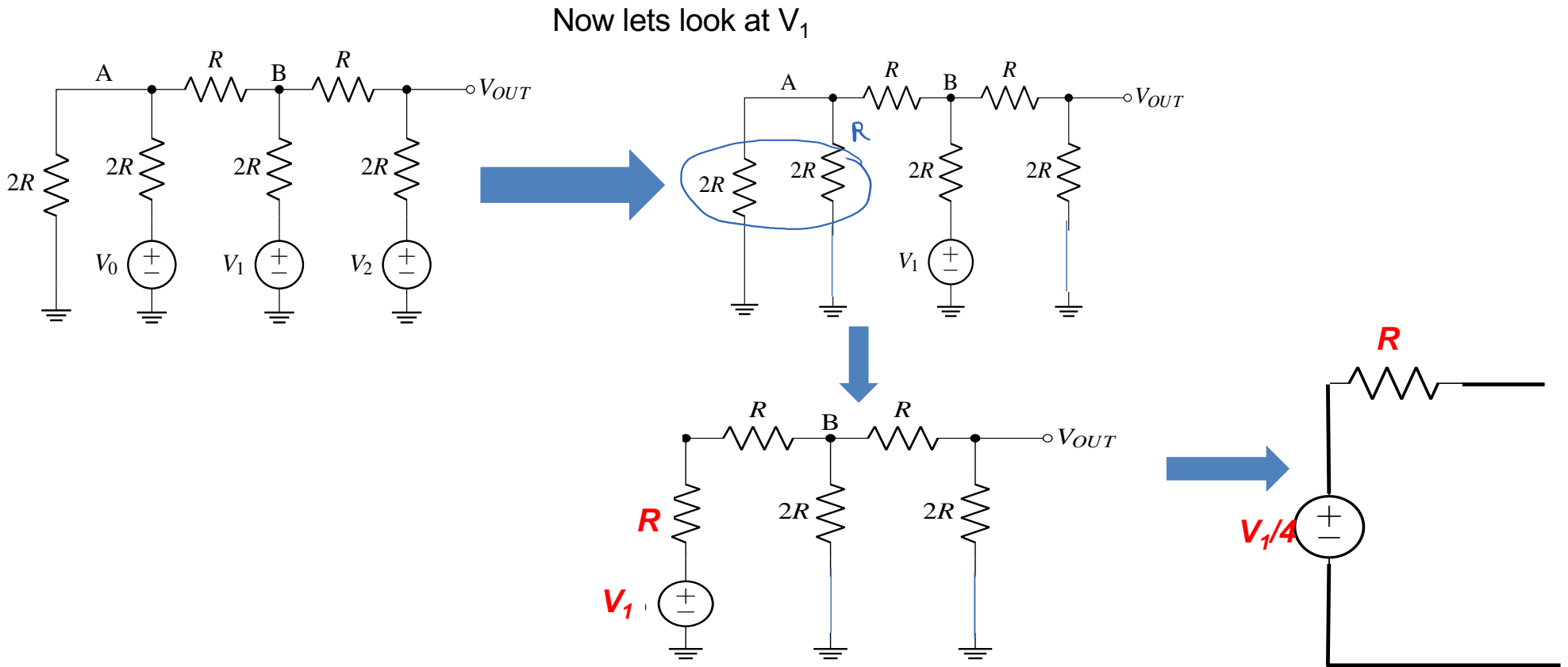

R-2R Ladder Digital-to-Analog Converter

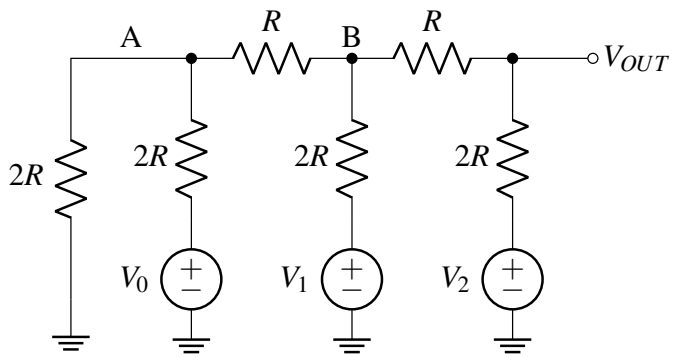
Adding all contributions from the sources




$$V_{out} = \frac{V_0}{8} + \frac{V_1}{4} + \frac{V_2}{2}$$

Analog to Digital Conversion

Say we want to convert an analog signal to a 2 bit digital signal \rightarrow 4 levels

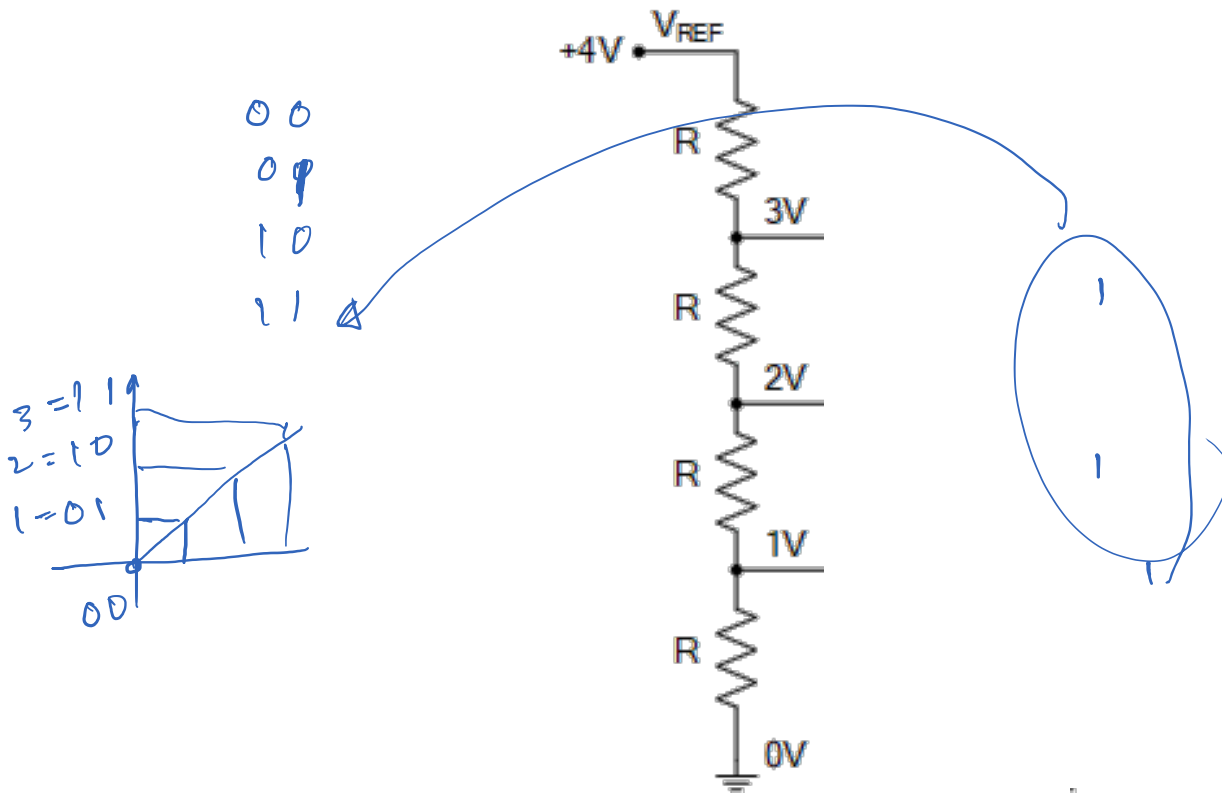

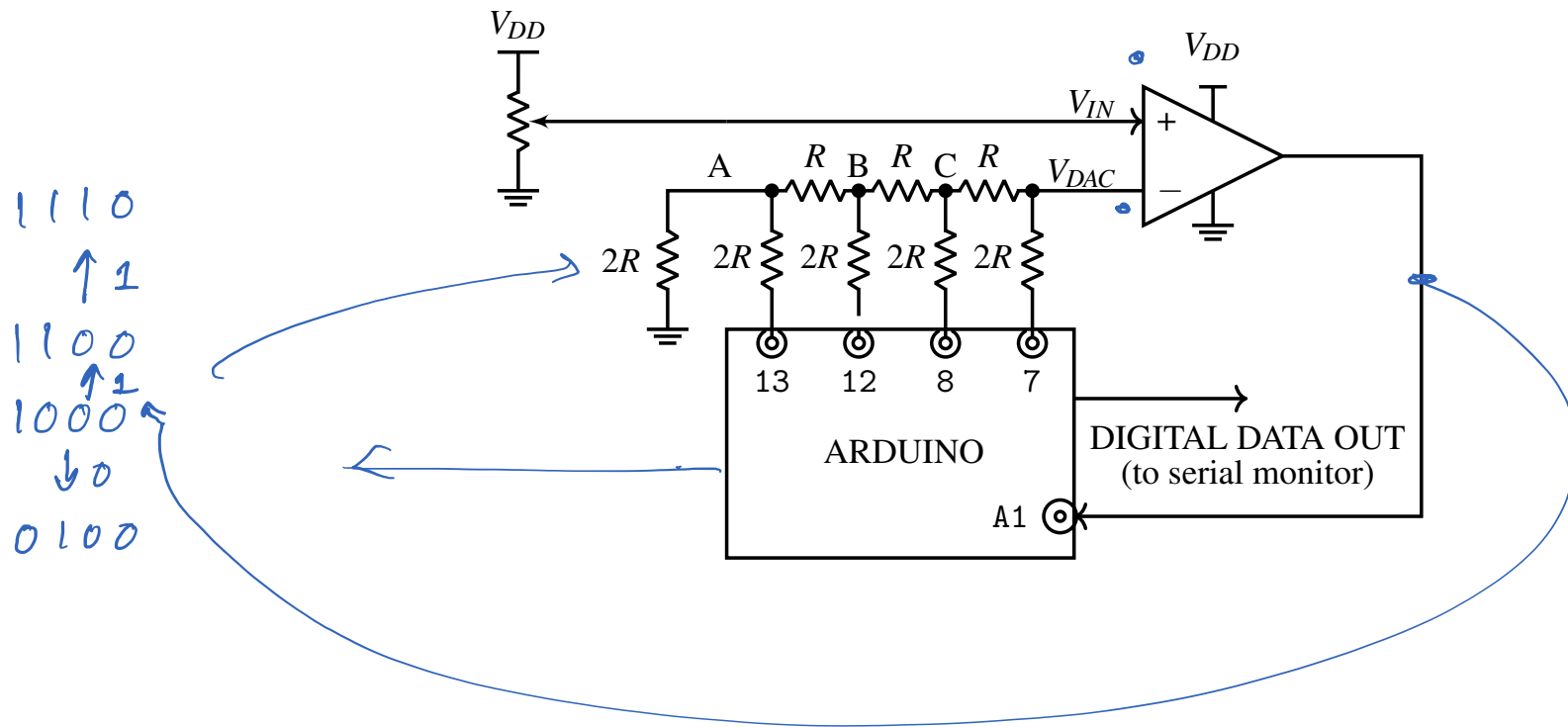Lab 2: SAR (Successive Approximation Resistor) ADC



Transience

R-C circuits: Response in time

$$\int \frac{dy}{y} = \log y$$

Say a capacitor C had a stored charge of Q so that it held a voltage of V_i across it. At $t=0$ a switch connects it to a resistor completing the circuit.

$$Q = C V_i$$

$$\tau = RC$$

$$v_c + v_R = 0$$

$$\Rightarrow v_c + iR = 0$$

$$\Rightarrow v_c + RC \frac{dv_c}{dt} = 0$$

divide by RC

$$\frac{dv_c}{dt} + \frac{v_c}{RC} = 0$$

$$\Rightarrow \frac{dv_c}{dt} = -\frac{v_c}{RC}$$

$$\frac{dv_c}{v_c} = -\frac{dt}{\tau}$$


$$\int \frac{dv_c}{v_c} = -\frac{1}{\tau} \int_0^t dt'$$

$$\log v_c = -\frac{1}{\tau} t' \Big|_0^t + c$$

$$\log v_c = -t/\tau + c$$


$$v_c = e^{(-t/\tau + c)}$$

$$v_c = e^c e^{-t/\tau}$$

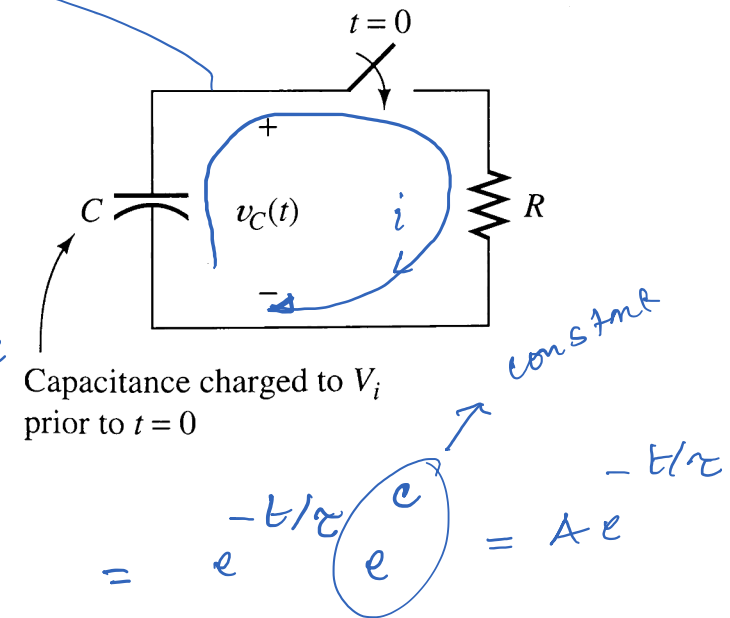


R-C circuits: Response in time

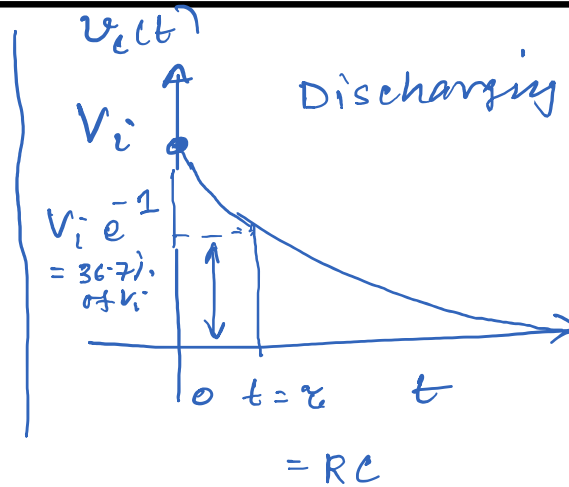$v_c(t) = A e^{-t/\tau}$
 given,
 at, $t = 0$, $v_c(0) = V_i$
 $v_c(0) = V_i = A e^0 = A$
 $v_c(t) = V_i e^{-t/\tau}$



$e^{-1} = 0.367$

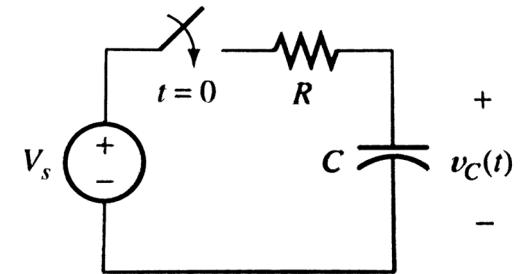

= characteristic time / time constant

R-C circuits: Response in time

We now ask a slightly different question. What happens if a capacitor that had initially no charge is connected to a constant voltage at $t=0$

$$v_R + v_C = V_S$$

$$iR + v_C = V_S$$

$$RC \frac{dv_C}{dt} + v_C = V_S$$

$$\Rightarrow \frac{dv_C}{dt} + \frac{v_C}{\tau} = \frac{V_S}{\tau} \quad \text{Divide by } RC$$

Put, $V_S = 0 \rightarrow$ find v_C

Put $V_S \rightarrow$ find v_C

add those two results

$$\tau = RC$$

$$V_S = 0$$

natural response

homogeneous solution

$$\frac{dv_C}{dt} + \frac{v_C}{\tau} = 0$$

$$v_C^h(t) = A e^{-t/\tau}$$

