

EECS 16B

Designing Information Devices and Systems II

Lecture 4

Prof. Sayeef Salahuddin

Department of Electrical Engineering and Computer Sciences, UC Berkeley,
sayeef@eecs.berkeley.edu

Transient Response

- Outline
 - R-L-C Circuits
 - Phasors
- Reading- Hambley text sections 4.5, 5.1, 5.2 slides

R-L-C circuits: Response in time

$$v_s = iR + v_c + v_L$$

$$v_s = RC \frac{dv_c}{dt} + v_c + L \frac{di}{dt}$$

$$\Rightarrow v_s = RC \frac{dv_c}{dt} + v_c + LC \frac{d}{dt} \left(\frac{dv_c}{dt} \right)$$

$$\Rightarrow v_s = RC \frac{dv_c}{dt} + v_c + LC \frac{d^2 v_c}{dt^2}$$

$$\Rightarrow \boxed{\frac{d^2 v_c}{dt^2} + \frac{d v_c / dt}{LC} + \frac{v_c}{LC} = \frac{v_s}{LC}}$$


$$i = C \frac{dv_c}{dt}$$

$$\frac{dv_s}{dt} = R \frac{di}{dt} + \frac{dv_c}{dt} + \frac{1}{dt} (L \frac{di}{dt})$$

$$\Rightarrow \frac{dv_s}{dt} = R \frac{di}{dt} + \frac{i}{C} + L \frac{d^2 i}{dt^2}$$

$$\boxed{\frac{d^2 i}{dt^2} + \frac{1}{LC} i + \frac{1}{LC} = \frac{1}{L} \frac{dv_s}{dt}}$$

Filters, antennas, resonances

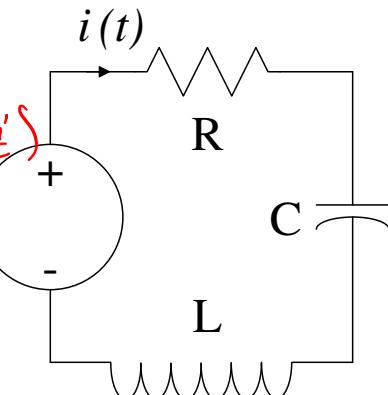

R-L-C circuits: Response in time

$$\frac{d^2v_c}{dt^2} + \frac{1}{(L/R)} \frac{dv_c}{dt} + \frac{1}{LC} v_c = \frac{v_s}{LC}$$

$$2\alpha = \frac{1}{L/R} \Rightarrow \alpha = \frac{R}{2L}$$

$$\frac{d^2v_c}{dt^2} + 2\alpha \frac{dv_c}{dt} + \omega_0^2 v_c = \frac{v_s}{LC}$$

$$\omega_0^2 = \frac{1}{LC}$$

Homogeneous solution


$$\frac{d^2v_c}{dt^2} + 2\alpha \frac{dv_c}{dt} + \omega_0^2 v_c = 0$$

From previous discussions we have seen that an exponential solution works

Lets try: $v_c(t) = Ae^{st}$

$$As^2 e^{st} + 2\alpha As e^{st} + \omega_0^2 A e^{st} = 0$$
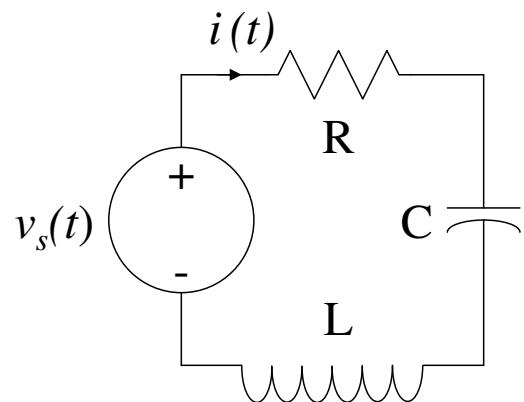
$$\Rightarrow [s^2 + 2\alpha s + \omega_0^2] = 0$$



R-L-C circuits: Response in time

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$s = \frac{-2\alpha \pm \sqrt{4\alpha^2 - 4\omega_0^2}}{2\alpha}$$

$$\Rightarrow s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$v_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$


$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$\alpha > \omega_0$ \Rightarrow both s_1 and s_2 are negative

$$v_c(t) = A_1 e^{-\alpha t} + A_2 e^{-bt}$$

over damped system
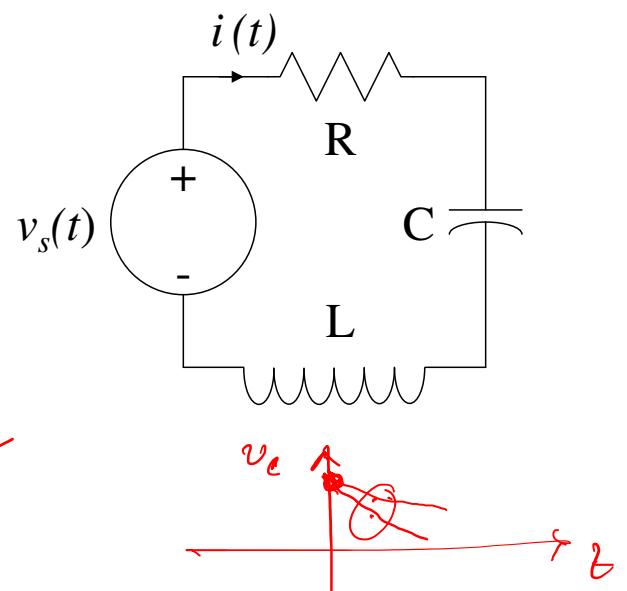
$$\alpha = b = -\alpha ; v_c(t) = \underbrace{(A_1 + A_2)}_{K} e^{-\alpha t} \rightarrow \text{critically damped}$$



R-L-C circuits: Response in time

$$\boxed{\alpha < \omega_0}$$

$$\begin{cases} S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \end{cases}$$

under damped



$$S_1 = -\alpha + \sqrt{-1(\omega_0^2 - \alpha^2)} \\ = -\alpha + j\beta$$

$$S_2 = -\alpha - j\beta$$

$$V_c(t) = A_1 e^{-\alpha t + j\beta t} + A_2 e^{-\alpha t - j\beta t}$$

$$= A_1 e^{-\alpha t} e^{j\beta t} + A_2 e^{-\alpha t} e^{-j\beta t}$$

$$\sqrt{-1} = j$$

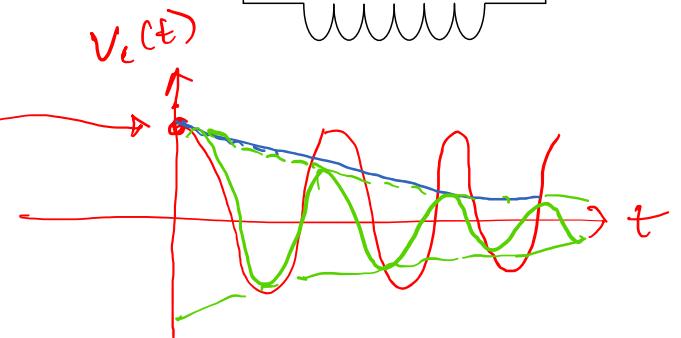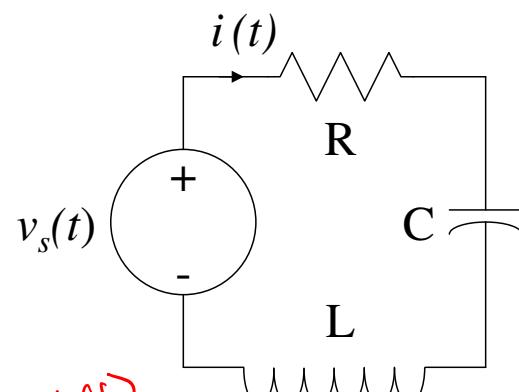


R-L-C circuits: Response in time

$$R=0 \quad \alpha = \frac{R}{2L} = 0$$



$$\zeta_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = j\beta \quad \omega_0 = \frac{j\omega_0}{\omega_0}$$

$$\zeta_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -j\beta = -j\omega_0$$
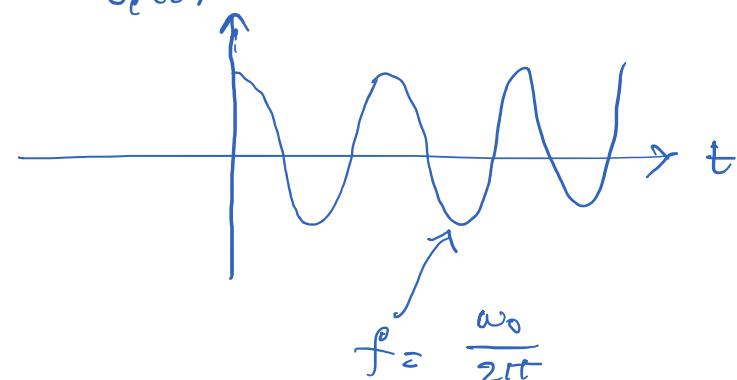
$$v_c(t) = A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t}$$



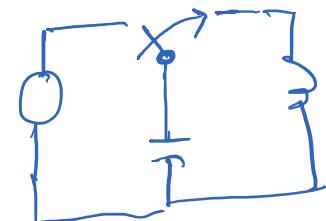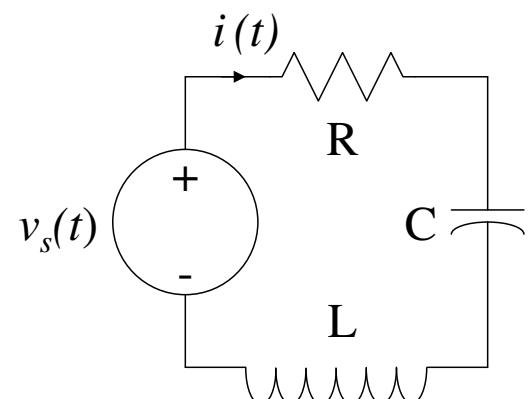$\omega_0 = \frac{1}{\sqrt{LC}}$
 ≡ resonance frequency



Summary

- Overdamped – real unequal roots
- Critically damped – Real Equal roots
- Underdamped – Complex roots


R-L-C circuits: Response in time

Particular solution:


$$\frac{d^2v_c}{dt^2} + \frac{1}{(L/R)} \frac{dv_c}{dt} + \frac{1}{LC} v_c = v_s$$

$$\frac{d^2i}{dt^2} + \frac{1}{(L/R)} \frac{di}{dt} + \frac{1}{LC} i = \frac{1}{L} \frac{dv_s}{dt}$$

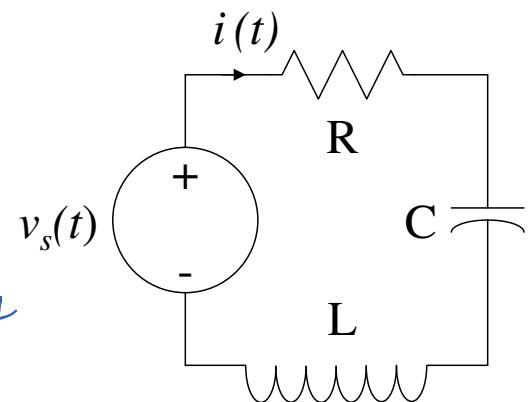Constant source: $v_s = V_0$ → particular solution is simply
the steady state solution




Sinusoidal voltages

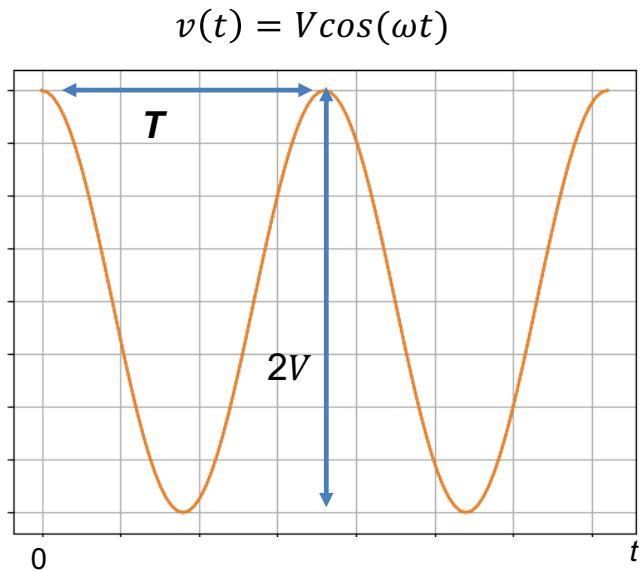

T : Period


$$\omega = \frac{2\pi}{T}$$

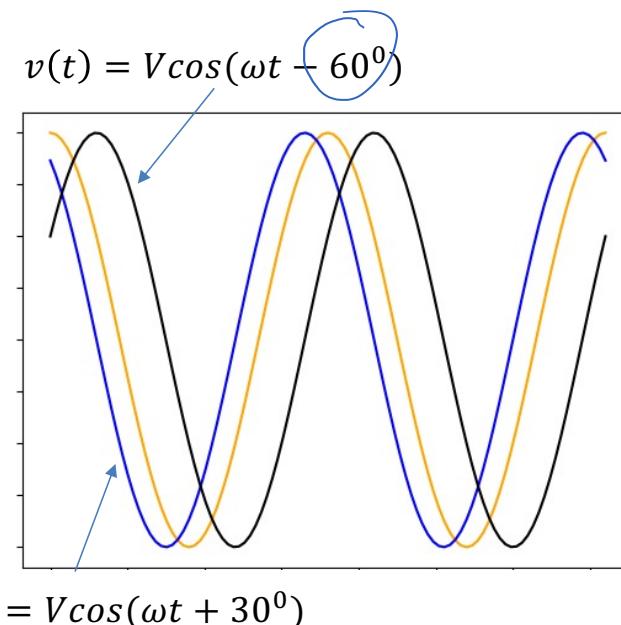

Degree $\rightarrow R : \text{Deg} \times \frac{\pi}{180}$

Root Mean Square Values

$$v(t) = V \cos(\omega t)$$

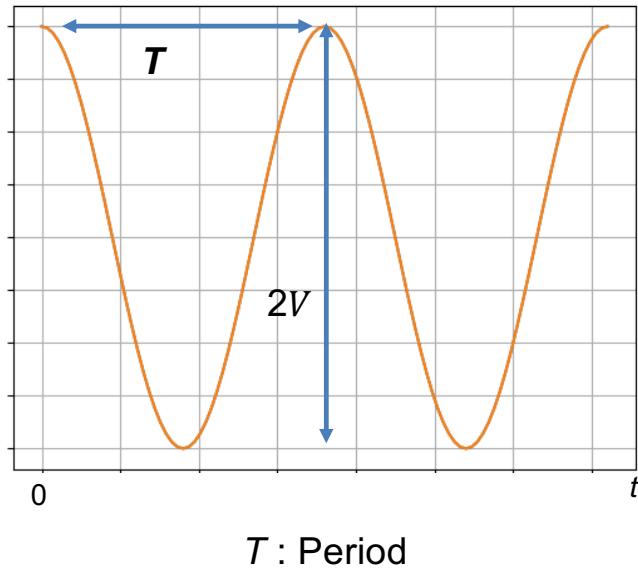

T : Period

$$\omega = \frac{2\pi}{T}$$

Average Power over one period:

$$P = \frac{1}{T} \int_0^T \frac{v^2}{R} dt$$

$$P = \frac{\left[\sqrt{\frac{1}{T} \int_0^T v^2 dt} \right]^2}{R}$$


Comparing with conventional equation: $P = \text{voltage}^2 / R$

A new quantity is defined for time-varying voltages known as the root-mean-square voltage

$$v_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

Root Mean Square Value for Sinusoidal Voltage

$$v(t) = V \cos(\omega t)$$

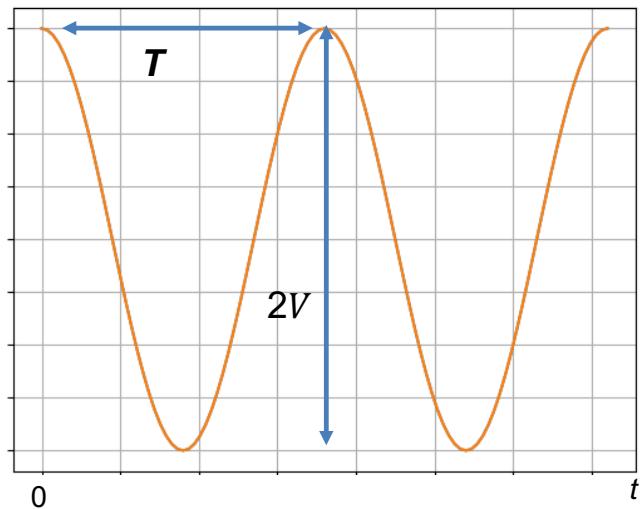

T : Period

$$\omega = \frac{2\pi}{T}$$

$$2 \cos^2 \omega t = 1 + \cos(2\omega t)$$

$$v_{rms}^2 = \frac{1}{T} \int_0^T v^2 dt = \frac{1}{T} \int_0^T V^2 \cos^2(\omega t) dt = \frac{1}{2} \frac{1}{T} V^2 \int_0^T (1 + \cos 2\omega t) dt$$

$$v_{rms}^2 = \frac{V^2}{2T} (t + 2 \sin 2\omega t)_0^T = \frac{V^2}{2T} [T - 0 + \sin 2\omega T - 0] = \frac{V^2}{2}$$

$$v_{rms} = \frac{V}{\sqrt{2}}$$

$$\begin{aligned} \sin 2\omega \cdot \frac{2\pi}{\omega} &= \sin 2\pi \\ &= 0 \end{aligned}$$

How do we add arbitrary sinusoids?

$$v(t) = 10\cos\omega t + 5\sin\omega t - 5\cos(\omega t - 30^\circ)$$

$$v(t) = 10\cos\omega t + 5\cos(\omega t - 90^\circ) - 5\cos(\omega t - 30^\circ)$$

Remember? $\cos(a + b) = \cos a \cos b - \sin a \sin b$

Lets do it differently $e^{j\theta} = \cos\theta + j\sin\theta$


$$e^{-j\theta} = \cos\theta - j\sin\theta$$

Then

$$\cos\theta = \frac{1}{2}(e^{j\theta} + e^{-j\theta})$$

$$\sin\theta = \frac{1}{2}(e^{j\theta} - e^{-j\theta})$$

$$v(t) = V\cos(\omega t - 60^\circ)$$

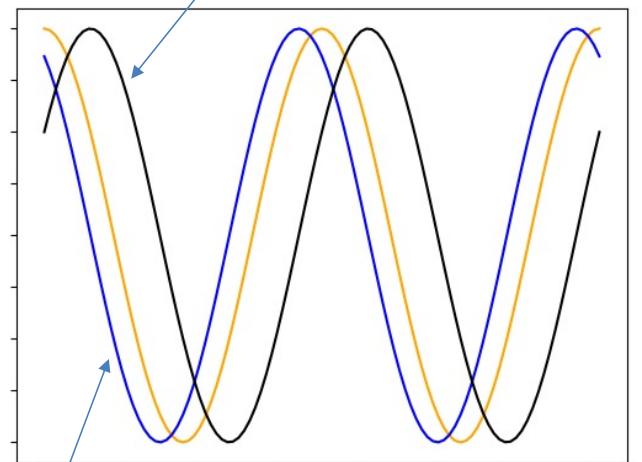

$$v(t) = V\cos(\omega t + 30^\circ)$$

How do we add arbitrary sinusoids?

$$\begin{aligned} v(t) &= 10\cos\omega t + 5\cos(\omega t - 90^\circ) - 5\cos(\omega t - 30^\circ) \\ &= \frac{1}{2}e^{j\omega t}[10] + \frac{1}{2}e^{j(\omega t - 90^\circ)}[5] - \frac{1}{2}e^{j(\omega t - 30^\circ)}[5] \\ &\quad + \frac{1}{2}e^{-j\omega t}[10] + \frac{1}{2}e^{-j(\omega t - 90^\circ)}[5] - \frac{1}{2}e^{-j(\omega t - 30^\circ)}[5] \end{aligned}$$

$$= \frac{1}{2}e^{j\omega t}[10 + 5e^{-j90^\circ} - 5e^{-j30^\circ}] + \frac{1}{2}e^{-j\omega t}[10 + 5e^{+j90^\circ} - 5e^{+j30^\circ}]$$

$$= \frac{1}{2}e^{j\omega t}[10 + 5\cos 90^\circ - j5\sin 90^\circ - 5\cos 30^\circ + j5\sin 30^\circ] + cc$$

$$= \frac{1}{2}e^{j\omega t}\left[10 + 0 - j5 - 5\frac{\sqrt{3}}{2} + \frac{j5}{2}\right] + cc$$

$$= \frac{1}{2}e^{j\omega t}[5.66 - j2.5] + cc$$

$$= \frac{1}{2}6.18e^{j(\omega t - 23^\circ)} + cc$$

$$= 6.18\cos(\omega t - 23^\circ)$$

$$\begin{aligned} \cos\theta &= \frac{1}{2}(e^{j\theta} + e^{-j\theta}) \\ \sin\theta &= \frac{1}{2}(e^{j\theta} - e^{-j\theta}) \end{aligned}$$

multiplying $\begin{cases} Ae^{-j\theta} = 5.66 - j2.5 \\ Ae^{j\theta} = 5.66 + j2.5 \end{cases}$

$$A^2 = 5.66^2 - j^2 2.5^2$$

$$A^2 = 5.66^2 + 2.5^2$$

$$A = \sqrt{5.66^2 + 2.5^2} = 6.18$$

$$\cos\theta = 5.66/6.18; \sin\theta = 2.5/6.18$$

$$\tan\theta = \frac{2.5}{5.66} = 0.44$$

$$\theta = 0.41 = 23^\circ$$

Some Observations

$$\begin{aligned}v(t) &= \frac{1}{2} e^{j\omega t} [5.66 - j2.5] + cc \\&= \frac{1}{2} 6.18 e^{j(\omega t - 23^\circ)} + \frac{1}{2} 6.18 e^{-j(\omega t - 23^\circ)} \\&= \frac{1}{2} 6.18 [\cos(\omega t - 23^\circ) + j\sin(\omega t - 23^\circ) + \cos(\omega t - 23^\circ) - j\sin(\omega t - 23^\circ)] = 6.18 \cos(\omega t - 23^\circ) \\&= \text{Real} [6.18 e^{j(\omega t - 23^\circ)}] \quad \text{Phasors}\end{aligned}$$

In short hand, it is represented as 6.18 ∠ -23°