

EECS 16B

Designing Information Devices and Systems II

Lecture 5

Prof. Sayeef Salahuddin


Department of Electrical Engineering and Computer Sciences, UC Berkeley,
sayeef@eecs.berkeley.edu

Transient Response

- Outline
 - Phasors
 - Complex Impedances
 - Solution of circuits using complex impedances
- Reading- Hambley text sections 5.2, 5.3, 5.4, 5.6, 5.5, slides

Recap: Sinusoidal voltages


$$v(t) = V \cos(\omega t)$$

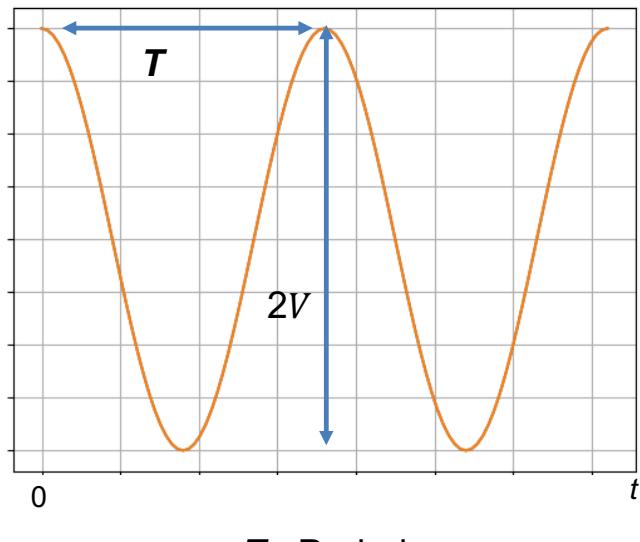

T : Period

$$\omega = \frac{2\pi}{T}$$

$$v(t) = V \cos(\omega t - 60^\circ)$$

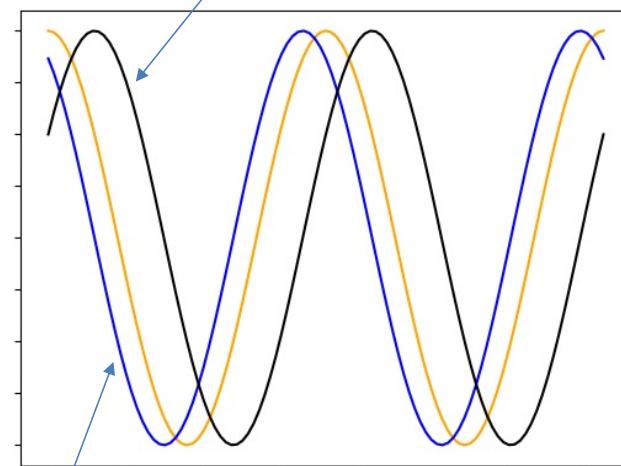

$$v(t) = V \cos(\omega t + 30^\circ)$$

Recap: How do we add arbitrary sinusoids?

$$v(t) = 10\cos\omega t + 5\sin\omega t - 5\cos(\omega t - 30^\circ)$$

$$v(t) = 10\cos\omega t + 5\cos(\omega t - 90^\circ) - 5\cos(\omega t - 30^\circ)$$

Remember? $\cos(a + b) = \cos a \cos b - \sin a \sin b$

Lets do it differently $e^{j\theta} = \cos\theta + j\sin\theta$


$$e^{-j\theta} = \cos\theta - j\sin\theta$$

Then

$$\cos\theta = \frac{1}{2}(e^{j\theta} + e^{-j\theta})$$

$$\sin\theta = \frac{1}{2}(e^{j\theta} - e^{-j\theta})$$

$$v(t) = V\cos(\omega t - 60^\circ)$$

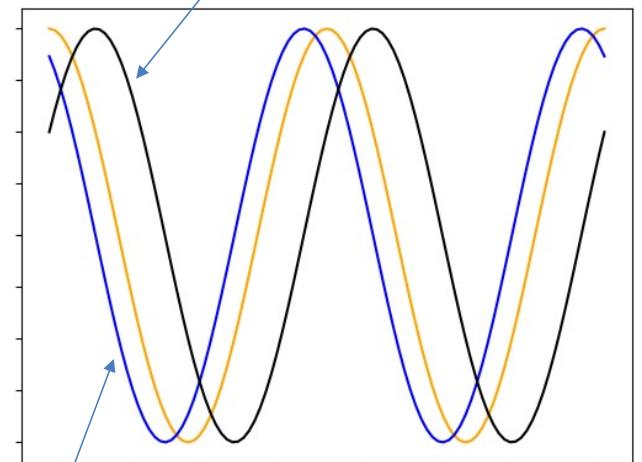

$$v(t) = V\cos(\omega t + 30^\circ)$$

Recap: How do we add arbitrary sinusoids?

$$\begin{aligned}v(t) &= 10\cos\omega t + 5\cos(\omega t - 90^\circ) - 5\cos(\omega t - 30^\circ) \\&= \frac{1}{2}e^{j\omega t}[10] + \frac{1}{2}e^{j(\omega t - 90^\circ)}[5] - \frac{1}{2}e^{j(\omega t - 30^\circ)}[5] \\&\quad + \frac{1}{2}e^{-j\omega t}[10] + \frac{1}{2}e^{-j(\omega t - 90^\circ)}[5] - \frac{1}{2}e^{-j(\omega t - 30^\circ)} \\&= \frac{1}{2}e^{j\omega t}[10 + 5e^{-j90^\circ} - 5e^{-j30^\circ}] + \frac{1}{2}e^{-j\omega t}[10 + 5e^{+j90^\circ} - 5e^{+j30^\circ}] \\&= \frac{1}{2}e^{j\omega t}[10 + 5\cos 90^\circ - j5\sin 90^\circ - 5\cos 30^\circ + j5\sin 30^\circ] + cc \\&= \frac{1}{2}e^{j\omega t}\left[10 + 0 - j5 - 5\frac{\sqrt{3}}{2} + \frac{j5}{2}\right] + cc \\&= \frac{1}{2}e^{j\omega t}[5.66 - j2.5] + cc \\&= \frac{1}{2}6.18e^{j(\omega t - 23^\circ)} + cc \\&= 6.18\cos(\omega t - 23^\circ)\end{aligned}$$

$$\begin{aligned}\cos\theta &= \frac{1}{2}(e^{j\theta} + e^{-j\theta}) \\ \sin\theta &= \frac{1}{2}(e^{j\theta} - e^{-j\theta})\end{aligned}$$

$$\begin{aligned}Ae^{-j\theta} &= 5.66 - j2.5 \\ Ae^{j\theta} &= 5.66 + j2.5 \\ A^2 &= 5.66^2 - j^2 2.5^2 \\ A^2 &= 5.66^2 + 2.5^2 \\ A &= \sqrt{5.66^2 + 2.5^2} = 6.18 \\ \cos\theta &= 5.66/6.18; \sin\theta = 2.5/6.18\end{aligned}$$

$$\begin{aligned}\tan\theta &= \frac{2.5}{5.66} = 0.44 \\ \theta &= 0.41 = 23^\circ\end{aligned}$$

Recap: Some Observations

$$\begin{aligned}v(t) &= \frac{1}{2} e^{j\omega t} [5.66 - j2.5] + cc \\&= \frac{1}{2} 6.18 e^{j(\omega t - 23^0)} + \frac{1}{2} 6.18 e^{-j(\omega t - 23^0)} \\&= \frac{1}{2} 6.18 [\cos(\omega t - 23^0) + j\sin(\omega t - 23^0) \cos(\omega t - 23^0) - j\sin(\omega t - 23^0)]\end{aligned}$$

$$= \text{Real} [6.18 e^{j(\omega t - 23^0)}]$$

Phasors

In short hand, it is represented as $6.18 \angle -23^0$

Some Observations

$$A(t) = 5\cos(\omega t) = \text{Real}[5e^{j(\omega t)}]$$

$$B(t) = 5\cos(\omega t - 90^\circ) = \text{Real}[5e^{j(\omega t - 90^\circ)}]$$

$$C(t) = 5\cos(\omega t + 90^\circ) = \text{Real}[5e^{j(\omega t + 90^\circ)}]$$

At any given time t , $B(t)$ is trailing or lagging behind $A(t)$ by 90° while $C(t)$ is leading $A(t)$ by the same amount


Let us now look at the phasors at $t=0$

$$5e^{j(\omega t - 90^\circ)} = 5$$

$$5e^{j(\omega t - 90^\circ)} = 5(\cos 90^\circ - j\sin 90^\circ) = -j5$$

$$5e^{j(\omega t + 90^\circ)} = 5(\cos 90^\circ + j\sin 90^\circ) = +j5$$

$$v(t) = V\cos(\omega t - 90^\circ)$$

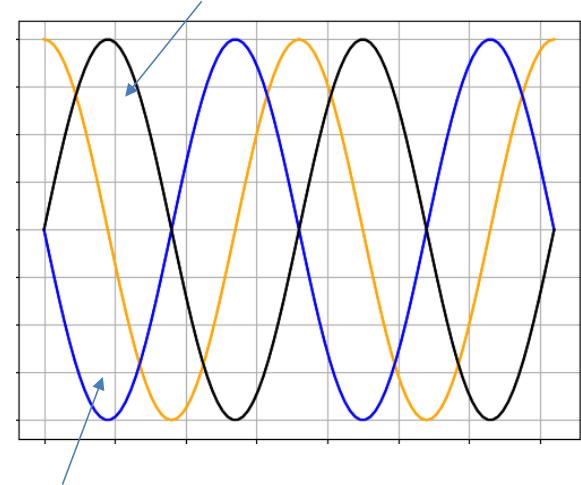


$$v(t) = V\cos(\omega t + 90^\circ)$$

Therefore $+j$ or $-j$ signifies signals having 90° phase lead or lag respectively.

Some Observations

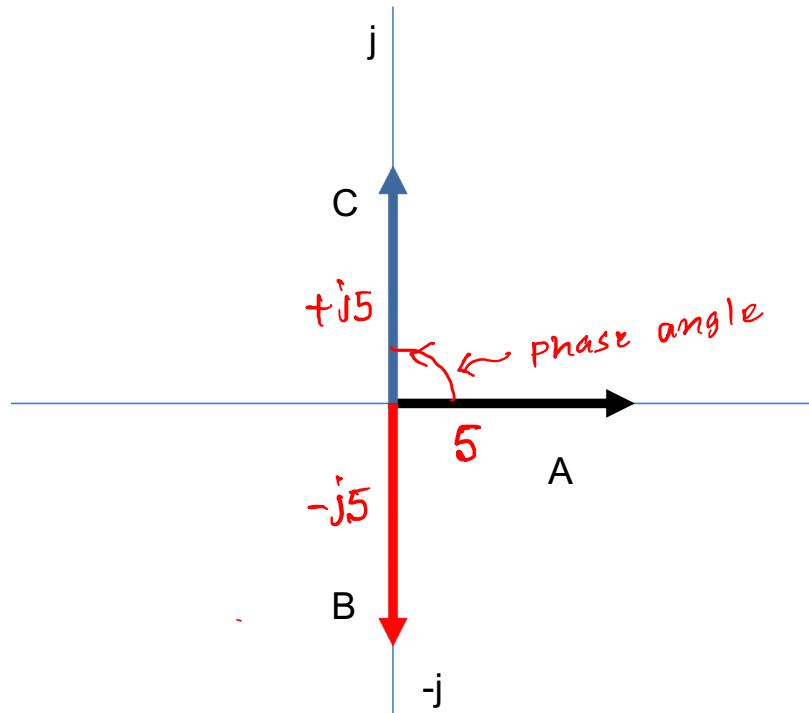$+j$ or $-j$ signifies signals having 90° phase lead or lag respectively.



$$5e^{j(\omega t - 90^\circ)} = 5$$


$$5e^{j(\omega t - 90^\circ)} = 5(\cos 90^\circ - j \sin 90^\circ) = -j5$$

$$5e^{j(\omega t + 90^\circ)} = 5(\cos 90^\circ + j \sin 90^\circ) = +j5$$

$$\sum = 5$$

Some Observations
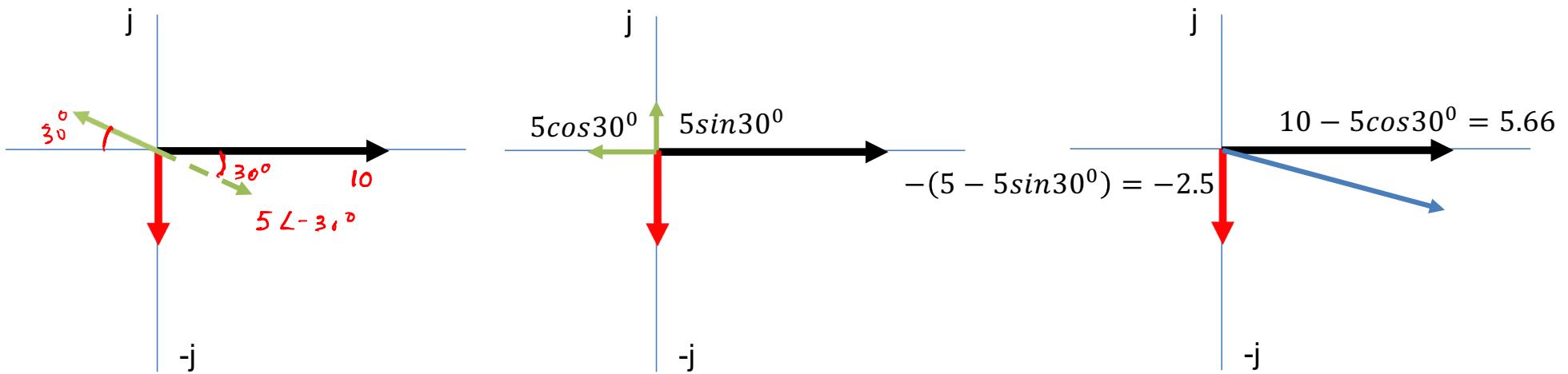
$$\begin{aligned}v(t) &= 10\cos\omega t + 5 \cos(\omega t - 90^\circ) - 5 \cos(\omega t - 30^\circ) \\&= 10 + 5\angle - 90^\circ - 5\angle - 30^\circ \quad \text{In phasor notation} \\&= 6.18\angle - 23^\circ\end{aligned}$$



Phasors are like vectors where the phase angle denotes the angle between coordinate axes with j representing 90°

Some Observations

What is $\frac{1}{e^{j\theta}}$?

$$j(\omega t + \theta)$$

$$|e^{j\theta}| = 1$$

$$-j(\omega t + \theta)$$

$$\frac{1}{e^{j\theta}} = \frac{1}{e^{-j(\omega t + \theta)}} = e^{-j(\omega t + \theta)}$$

$$= 1 e^{-j\theta}$$



$$= \frac{1}{\cos(\omega t + \theta) + j \sin(\omega t + \theta)}$$

$$\left. \begin{aligned} A e^{j\theta_1} \times B e^{j\theta_2} \\ = AB e^{j(\theta_1 + \theta_2)} \end{aligned} \right\}$$

Complex Impedances

Inductance:

Say a sinusoidal current is flowing in a circuit with inductance

$$i(t) = I_0 \sin(\omega t) = I_0 \cos(\omega t - 90^\circ)$$

$$v_L(t) = L \frac{di}{dt} = \omega L I_0 \cos \omega t$$

Therefore, the current in an inductor lags the voltage by 90°


In the phasor notation

$$\mathbf{V} = \omega L I_0 \angle -90^\circ$$

$$\mathbf{I} = I_0 \angle -90^\circ$$

Then, inductive impedance
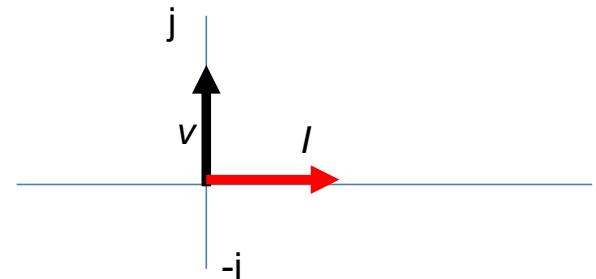
$$\mathbf{Z}_L = \frac{\mathbf{V}}{\mathbf{I}} = \frac{\omega L}{\angle -90^\circ} = \frac{\omega L}{-j} = j\omega L$$



We could have obtained the same result working directly with exponentials

$$\mathbf{V} = L \frac{d}{dt} [I_0 e^{j(\omega t - 90^\circ)}]$$

$$\mathbf{V} = L j \omega [I_0 e^{j(\omega t - 90^\circ)}]$$

$$\mathbf{V} = j \omega L I_0 \angle -90^\circ$$

$$\mathbf{V} = j \omega L \mathbf{I}$$

Complex Impedances

$$\hat{j} = \angle 90^\circ$$

Capacitance:

$$\hat{i} = C \frac{d\hat{v}}{dt}$$

$$\hat{I} = C \frac{d}{dt} V_0 e^{j\omega t}$$

$$= C j\omega V_0 e^{j\omega t}$$


$$\hat{I} = (j\omega C) \hat{V}$$

capacitive impedance:

$$\hat{V} = \left(-\frac{j}{\omega C} \right) \hat{I}$$

voltage lags the current by 90°
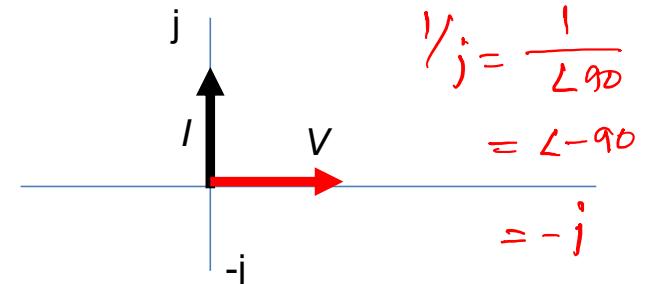
$$\frac{\hat{V}}{\hat{I}} = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$



$$\begin{aligned} Y_j &= \frac{1}{\omega C} \\ &= \angle -90^\circ \\ &= -j \end{aligned}$$



Complex Impedances

- AC steady-state analysis using phasors allows us to express the relationship between current and voltage using a formula that looks like Ohm's law:

$$V = IZ$$

- Impedance depends on the frequency ω .
- Impedance is a complex number.
- Impedance allows us to use the same solution techniques for AC steady state as

Circuit Solution with sinusoidal sources

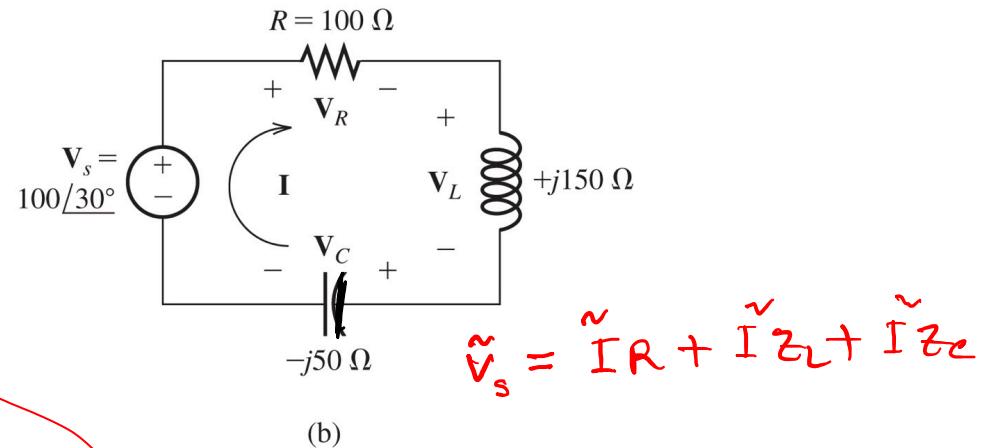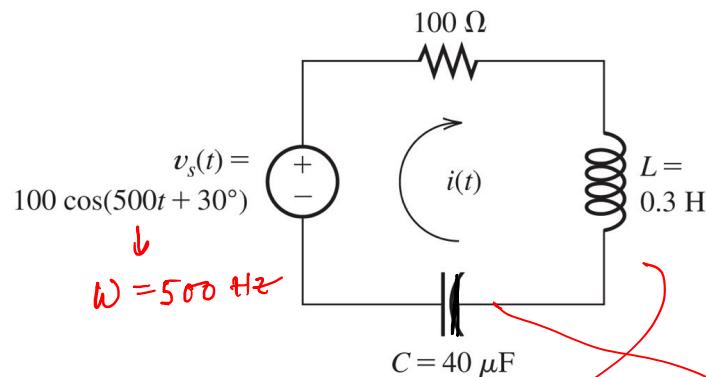

$$\tilde{V}_s = 100 \angle 30^\circ$$

$$z_L = j\omega L = j500 \times 0.3 = j150 \Omega$$

$$z_C = \frac{-j}{\omega C} = \frac{-j}{500 \times 40 \times 10^{-6}} = \frac{-j}{2 \times 10^0} = -j50 \Omega$$

Circuit Solution with sinusoidal sources

$$100 \angle 30^\circ = (100 + j150 - j50) \tilde{I}$$
$$= (100 + j100) \tilde{I}$$

$$\tilde{I} = \frac{100 \angle 30^\circ}{100 + j100}$$

$$= \frac{100 \angle 30^\circ}{\sqrt{100^2 + 100^2} \angle 45^\circ}$$

$$\tilde{I} = \frac{100}{100\sqrt{2}} \angle \frac{30^\circ - 45^\circ}{2} = \frac{100}{100\sqrt{2}} \angle -15^\circ$$

$$\tilde{I} = \frac{1}{\sqrt{2}} \angle -15^\circ$$

$$\tilde{V}_R = \tilde{I} R = \frac{1}{\sqrt{2}} \angle -15^\circ \times 100$$

$$\tilde{V}_R = 0.71 \times 100 \angle -15^\circ = 71 \angle -15^\circ$$

$$\tilde{V}_L = \tilde{Z}_L \tilde{I} = j\omega L \times \frac{1}{\sqrt{2}} \angle -15^\circ$$

$$= 150 \angle 90^\circ \times \frac{1}{\sqrt{2}} \angle -15^\circ$$

$$= A \angle 75^\circ$$

$$\tilde{V}_C = \tilde{Z}_C \tilde{I} = -j50 \times 0.71 \angle -15^\circ$$

$$\tilde{V}_C = 35 \angle -90^\circ \angle -15^\circ$$

$$\tilde{V}_C = 35 \angle -105^\circ$$

$$v_R = 71 \angle -15^\circ$$

$$v_L = 41 \angle 75^\circ$$

$$v_c = 35 \angle -105^\circ$$

$$v_s = 100 \angle 20^\circ$$

