

EECS 16B

Designing Information Devices and Systems II

Lecture 6


Prof. Sayeef Salahuddin

Department of Electrical Engineering and Computer Sciences, UC Berkeley,
sayeef@eecs.berkeley.edu

Transient Response


- Outline
 - Power in the AC circuits
 - Transfer Function and Filters
- Reading- Hambley text sections 5.6, 6.1, 6.2, slides

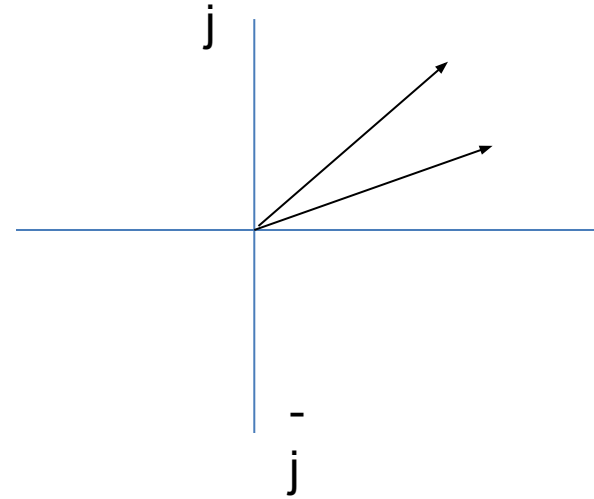Recap: Phasors and sinusoidal steady state




Phasors define phase relationships at an instant of time, i.e., with respect to ωt


Recap: Solving circuits with R, L and C

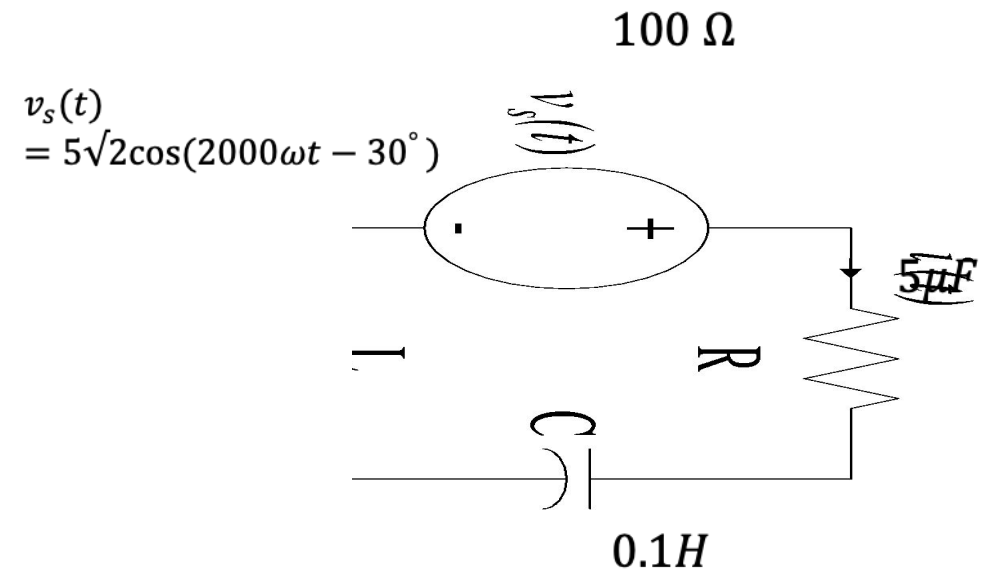

Recap: Solving circuits with R, L and C

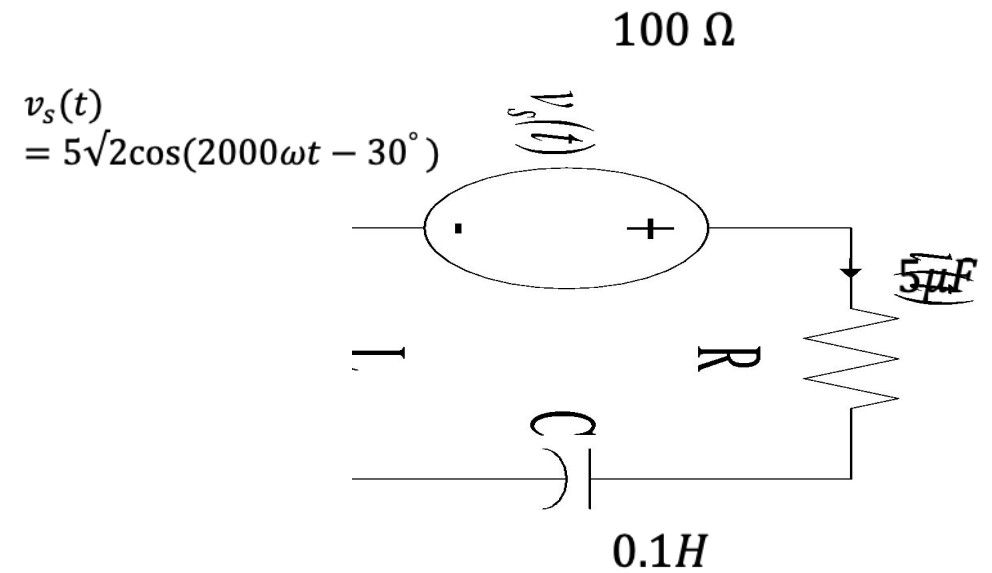

Recap: Solving circuits with R, L and C

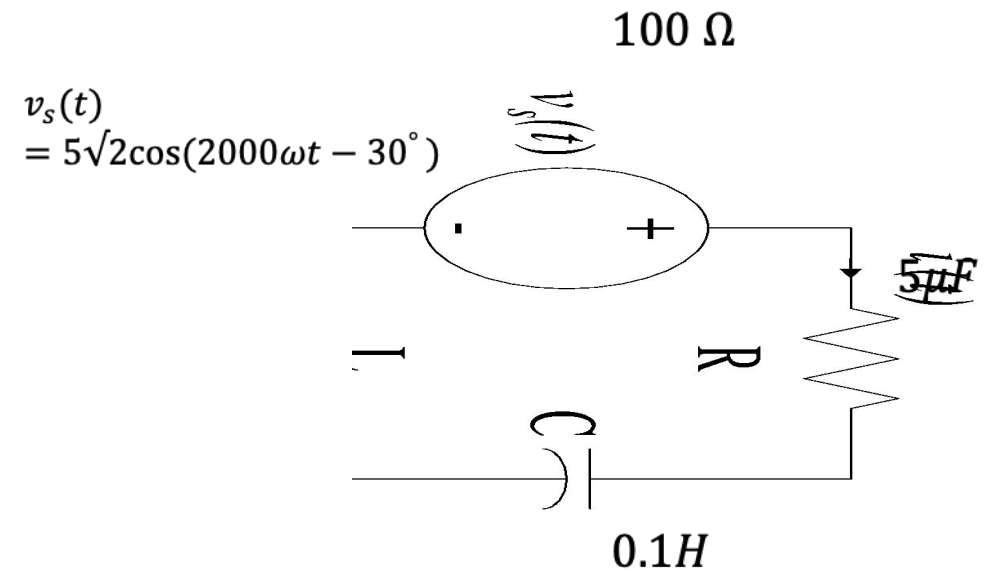

Recap: Power in AC Circuits

Purely resistive Circuit

$$v(t) = V_m \cos \omega t$$

$$i(t) = I_m \cos \omega t$$

$$P_{avg} = \frac{1}{T} \int_0^T dt v(t)i(t) = \frac{V_m I_m}{T} \int_0^T dt \cos^2 \omega t = \frac{V_m I_m}{T} \times \frac{T}{2}$$

$$P_{avg} = \frac{V_m I_m}{2}$$

Power in AC Circuits

Purely Inductive Circuit

$$v(t) = V_m \cos \omega t$$

$$i(t) = I_m \cos(\omega t - 90^\circ)$$

$$\begin{aligned} P_{avg} &= \frac{1}{T} \int_0^T dt v(t)i(t) = \frac{V_m I_m}{T} \int_0^T dt \cos \omega t \sin \omega t \\ &= \frac{V_m I_m}{2T} \int_0^T dt \sin 2\omega t \end{aligned}$$

Purely Capacitive Circuit

$$v(t) = V_m \cos(\omega t - 90^\circ)$$

$$i(t) = I_m \cos(\omega t)$$

$$\begin{aligned} P_{avg} &= \frac{1}{T} \int_0^T dt v(t)i(t) = \frac{V_m I_m}{T} \int_0^T dt \cos \omega t \sin \omega t \\ &= \frac{V_m I_m}{2T} \int_0^T dt \sin 2\omega t = 0 \end{aligned}$$

Power in AC Circuits

General case

Power in AC Circuits


General case

Power in AC Circuits: Power Triangle

Power in AC Circuits: Power Triangle

Power in AC Circuits: Maximum Power Transfer


Concept of Transfer Function

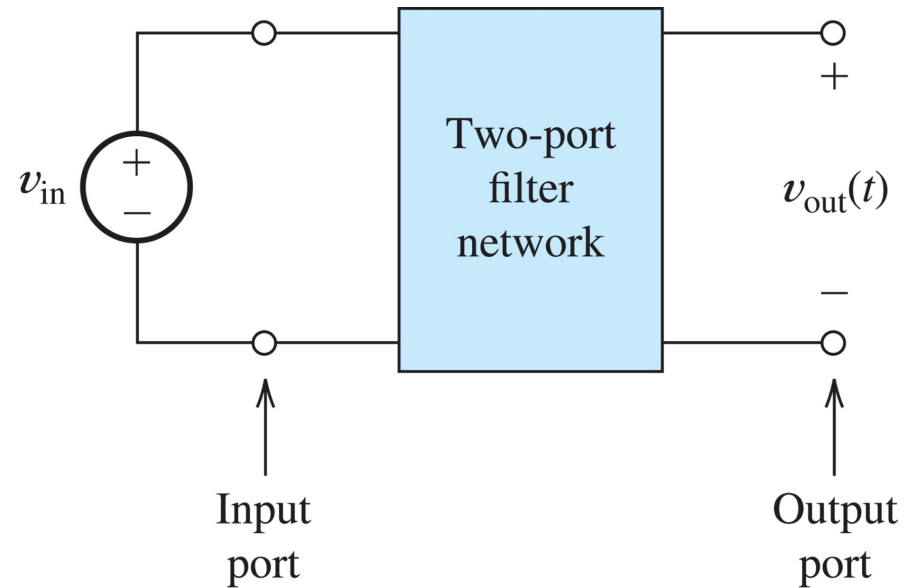

Copyright ©2018 Pearson Education, All Rights Reserved.

Two port Filter Network or more generally Two port network

Concept of Transfer Function

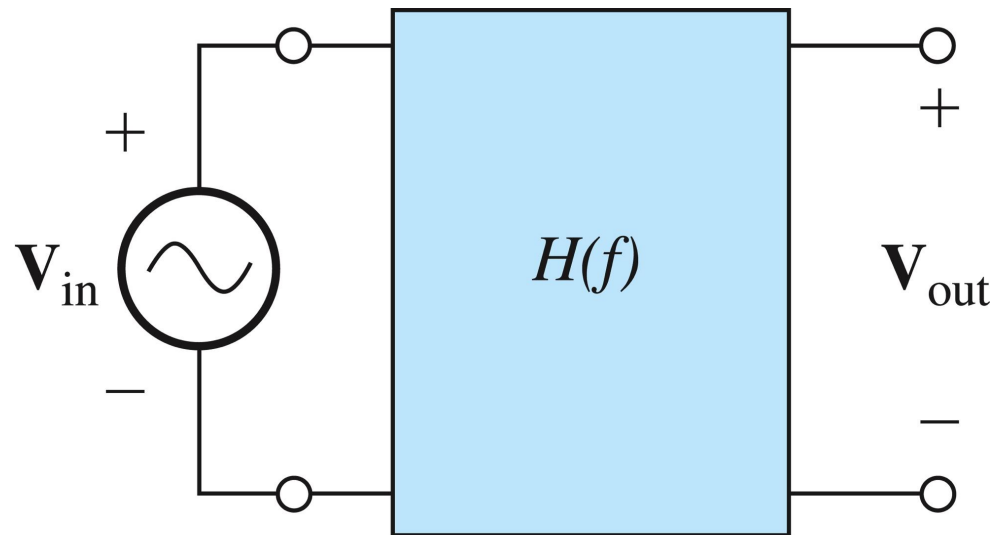


$$H(f) = \frac{V_{out}}{V_{in}}$$


Copyright ©2018 Pearson Education, All Rights Reserved.

$H(f)$ is a complex number


A simple RC Circuit

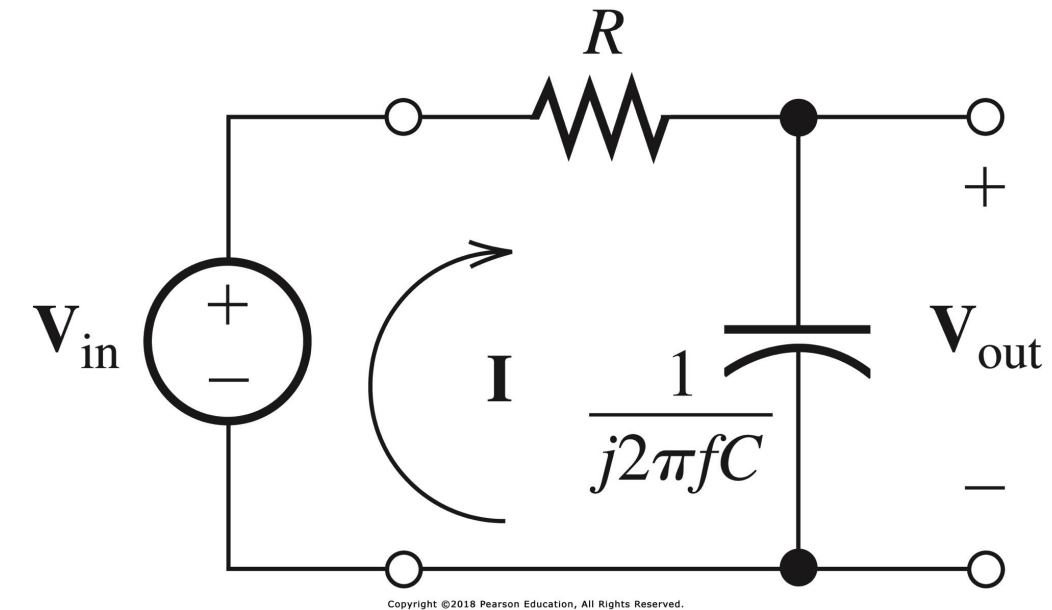

A simple RC Circuit

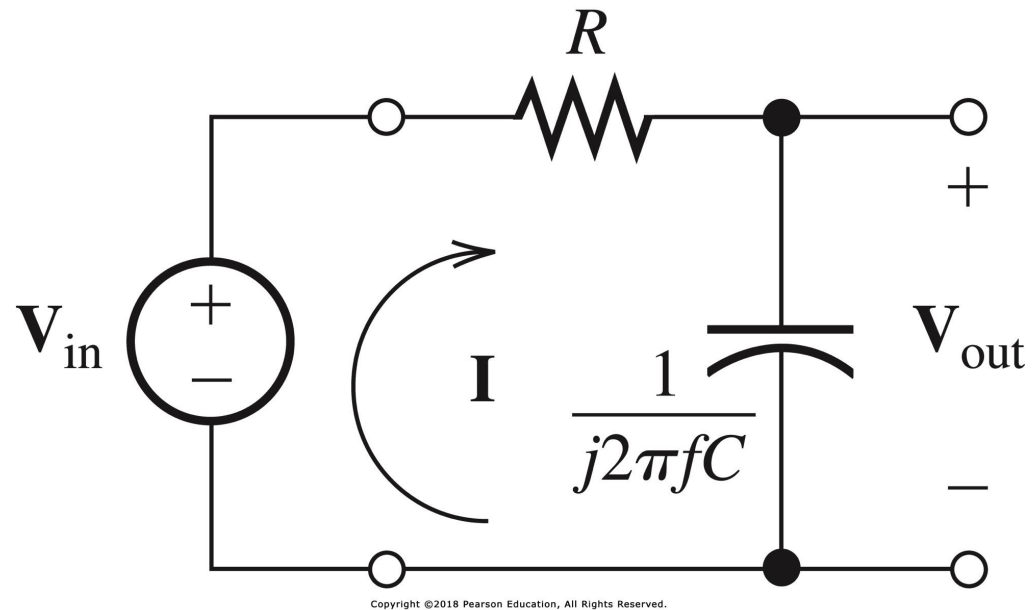

First Order low pass filter

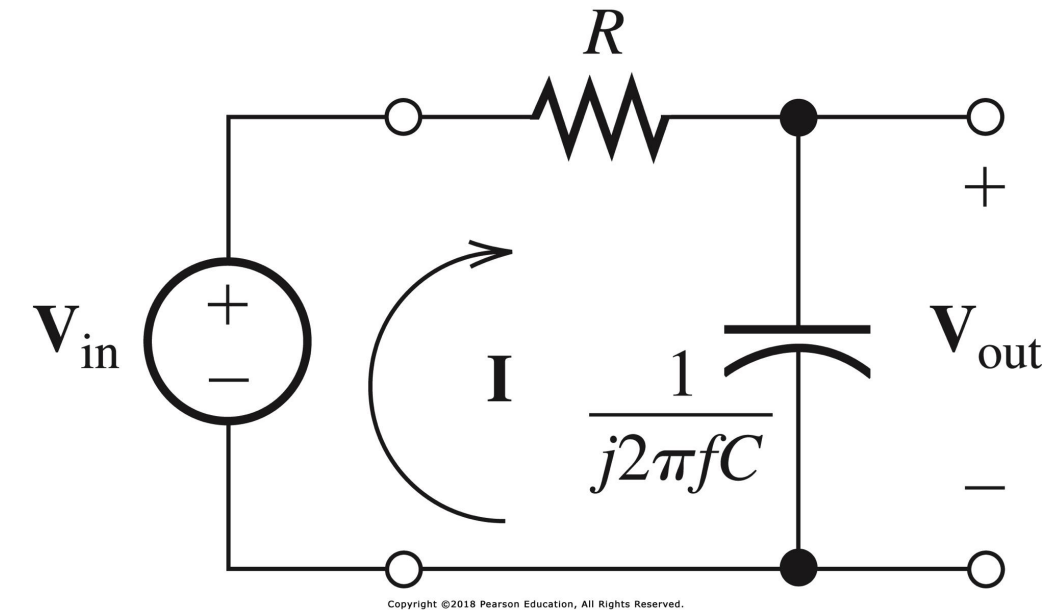

Decibels
