

EECS 16B

Designing Information Devices and Systems II

Lecture 6

Prof. Sayeef Salahuddin

Department of Electrical Engineering and Computer Sciences, UC Berkeley,
sayeef@eecs.berkeley.edu

Transient Response

- Outline
 - Power in the AC circuits
 - Transfer Function and Filters
- Reading- Hambley text sections 5.6, 6.1, 6.2, slides

Recap: Phasors and sinusoidal steady state

$$\tilde{V}_1 = A \angle \theta_1$$


$$\tilde{V}_2 = B \angle \theta_2$$

$$\frac{\tilde{V}_1}{\tilde{V}_2} = \frac{A e^{j\omega t_1}}{B e^{j\omega t_2}} = \frac{A}{B} e^{j\omega(\theta_1 - \theta_2)} = \frac{A}{B} \angle \theta_1 - \theta_2$$

$$\tilde{V}_1 \tilde{V}_2 = AB e^{j\omega(\theta_1 + \theta_2)} = AB \angle \theta_1 + \theta_2$$

↓
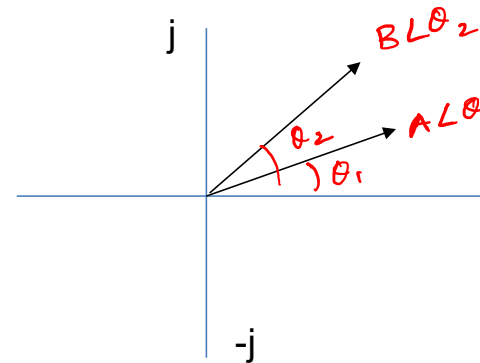
$$AB \cos \{ \omega t + (\theta_1 + \theta_2) \}$$



Phasors define phase relationships at an instant of time, i.e., with respect to ωt

Recap: Solving circuits with R, L and C

$$v_s(t) = iR + v_c + L \frac{di}{dt}$$

$$= R \frac{dv_c}{dt} + v_c + L \frac{d^2 v_c}{dt^2}$$

$$\Rightarrow \frac{d^2 v_c}{dt^2} + \frac{dv_c/dt}{L/R} + \frac{v_c}{Lc} = \frac{v_s}{Lc}$$

$$\Rightarrow \frac{d^2 v_c}{dt^2} + 2\alpha \frac{dv_c}{dt} + \omega_0^2 v_c = \omega_0^2 v_s$$

Homogeneous solⁿ:


$$\frac{d^2 v_c}{dt^2} + 2\alpha \frac{dv_c}{dt} + \omega_0^2 v_c = 0$$

$$\text{Try: } e^{st} \rightarrow s^2 + 2\alpha s + \omega_0^2 = 0 \Rightarrow s_1, s_2$$

$$v_c^h(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$Z = R + j\omega L + \frac{1}{j\omega c}$$

$$= 100 + j2000 - j100 = 100 + j100$$

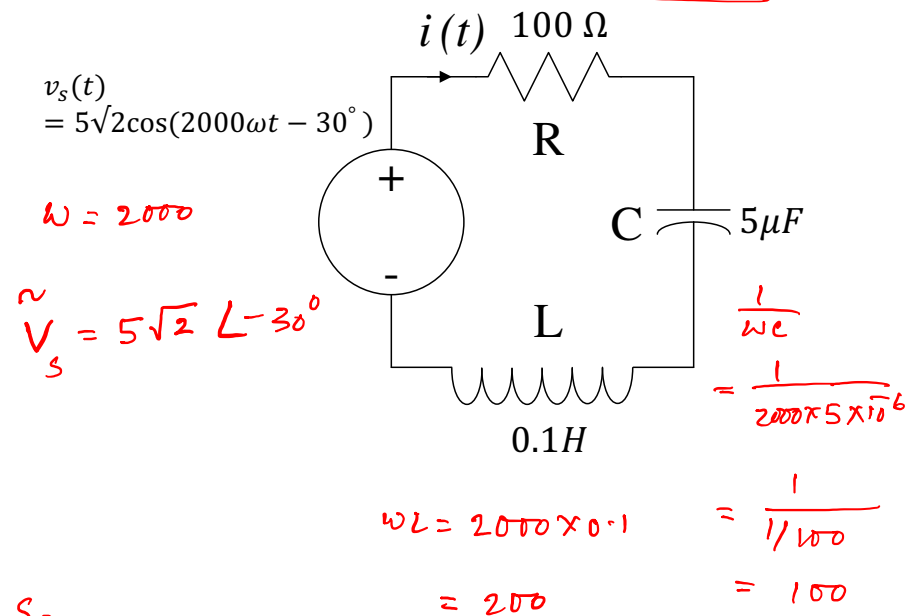


Recap: Solving circuits with R, L and C

$$\begin{aligned} \tilde{I} &= \frac{\tilde{V}}{Z} = \frac{5\sqrt{2} \angle -30^\circ}{100 + j100} \\ &= \frac{5\sqrt{2} \angle -30^\circ}{100\sqrt{2} \angle 45^\circ} \\ &= \frac{1}{20} \angle -75^\circ \end{aligned}$$


$$\begin{aligned} \tilde{V}_c &= I \left(\frac{1}{j\omega C} \right) = -j \frac{1}{20} \angle -75^\circ (100) \\ &= 5 \angle -90^\circ \angle -75^\circ \\ &= 5 \angle -165^\circ \end{aligned}$$

$$v_c(t) = 5 \cos(2000t - 165^\circ)$$

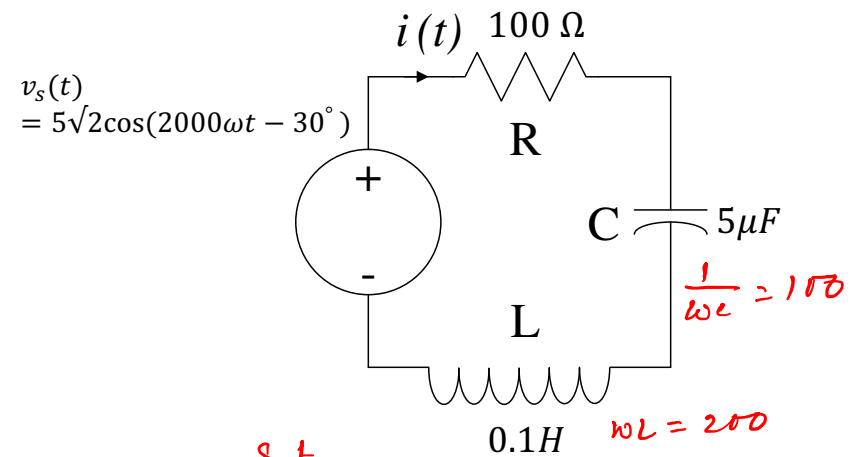

$$v_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + 5 \cos(2000t - 168^\circ)$$

Recap: Solving circuits with R, L and C

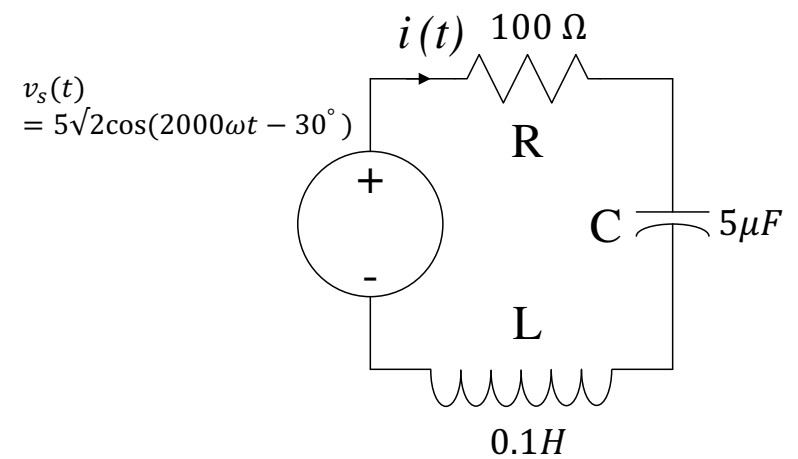

Recap: Power in AC Circuits

Purely resistive Circuit

$$v(t) = V_m \cos \omega t$$

$$i(t) = I_m \cos \omega t$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$P_{avg} = \frac{1}{T} \int_0^T dt v(t)i(t) = \frac{V_m I_m}{T} \int_0^T dt \cos^2 \omega t = \frac{V_m I_m}{T} \times \frac{T}{2}$$

$$P_{avg} = \frac{V_m I_m}{2}$$

$$= (V_{rms} I_{rms})$$

$$\frac{V_m I_m}{2T} \int_0^T 2 \cos^2 \omega t dt$$

$$= \frac{V_m I_m}{2T} \int_0^T (1 + \cos 2\omega t) dt$$

$$= \frac{V_m I_m}{2T} \left[T - 0 + \frac{1}{2\omega} (\sin 2\omega t) \Big|_0^T \right]$$

$$= \frac{V_m I_m}{2T} \left[T + \frac{1}{2\omega} (\sin 4\pi - \sin 0) \right] = \frac{V_m I_m}{2}$$

Power in AC Circuits

Purely Inductive Circuit

$$v(t) = V_m \cos \omega t$$

$$i(t) = I_m \cos(\omega t - 90^\circ)$$

$$P_{avg} = \frac{1}{T} \int_0^T dt v(t)i(t) = \frac{V_m I_m}{T} \int_0^T dt \cos \omega t \sin \omega t$$

$$= \frac{V_m I_m}{2T} \int_0^T dt \sin 2\omega t$$

$$= 0$$

Purely Capacitive Circuit

$$v(t) = V_m \cos(\omega t - 90^\circ)$$

$$i(t) = I_m \cos(\omega t)$$

$$P_{avg} = \frac{1}{T} \int_0^T dt v(t)i(t) = \frac{V_m I_m}{T} \int_0^T dt \cos \omega t \sin \omega t$$

$$= \frac{V_m I_m}{2T} \int_0^T dt \sin 2\omega t = 0$$

Power in AC Circuits

General case

$$v(t) = V_m \cos(\omega t + \theta_1)$$

$$i(t) = I_m \cos(\omega t + \theta_2)$$


$$P(t) = v(t) i(t)$$

$$= V_m \cos(\omega t + \theta_1) I_m \cos(\omega t + \theta_2)$$

$$= \operatorname{Re} \left\{ \underbrace{V_m e^{j(\omega t + \theta_1)}}_{\tilde{V}} \right\} \operatorname{Re} \left\{ \underbrace{I_m e^{j(\omega t + \theta_2)}}_{\tilde{I}} \right\}$$

$$= \frac{1}{2} (\tilde{V} + \text{c.c.}) \times \frac{1}{2} (\tilde{I} + \text{c.c.})$$
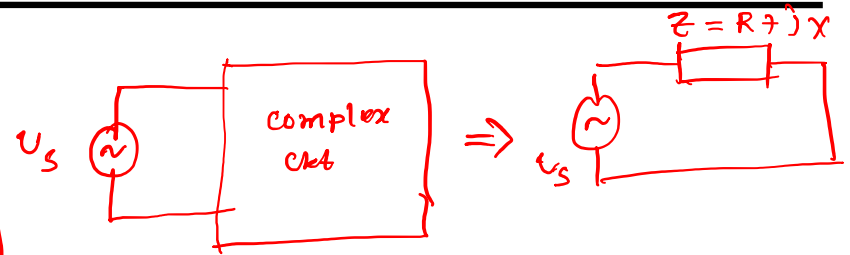
$$= \frac{1}{2} (\tilde{V} + \tilde{V}^*) \times \frac{1}{2} (\tilde{I} + \tilde{I}^*)$$



* \equiv complex conjugate

$$= \frac{1}{4} \left[(\tilde{V} \tilde{I} + \tilde{V}^* \tilde{I}^*) + (\tilde{V} \tilde{I}^* + \tilde{V}^* \tilde{I}) \right]$$

$$= \frac{1}{4} \left[(\tilde{V} \tilde{I}) + (\tilde{V} \tilde{I})^* \right] + \left[\tilde{V} \tilde{I}^* + (\tilde{V} \tilde{I}^*)^* \right]$$

$$= \frac{1}{2} \left[\operatorname{Re}(\tilde{V} \tilde{I}) + \operatorname{Re}(\tilde{V} \tilde{I}^*) \right]$$

$$= \frac{1}{2} \left[\operatorname{Re} \left\{ V_m I_m e^{j(\omega t + \theta_1 + \omega t + \theta_2)} \right\} + \operatorname{Re} \left\{ V_m I_m e^{j(\omega t + \theta_1 - \omega t - \theta_2)} \right\} \right]$$

$$p(t) = \frac{1}{2} \operatorname{Re} \left\{ V_m I_m e^{j(2\omega t + \theta_1 + \theta_2)} \right\} + \frac{1}{2} \operatorname{Re} \left\{ V_m I_m^* e^{j(\theta_1 - \theta_2)} \right\}$$

$$= \frac{V_m I_m}{2} \cos(2\omega t + \theta_1 + \theta_2) + \frac{V_m I_m}{2} \cos(\theta_1 - \theta_2)$$

$V_m I_m$
both
are real
numbers

$$P_{\text{avg}} = \frac{1}{T} \int_0^T dt p(t)$$

$$= \frac{V_m I_m}{2T} \int_0^T dt \cos(2\omega t + \theta_1 + \theta_2) + \frac{V_m I_m}{2T} \left[\int_0^T dt \right] \cos(\theta_1 - \theta_2)$$

$$= \frac{V_m I_m}{2} \cos \theta_d$$

$\theta_d = \theta_1 - \theta_2 =$ Difference in the phase angle
between v and i

$$P_{\text{avg}} = (V_{\text{rms}} I_{\text{rms}}) \cos \theta_d \rightarrow \text{power factor}$$

Power in AC Circuits

General case

$$A = a + jb$$

$$B = c + jd$$

$$\begin{aligned} AB &= (a + jb)(c + jd) \\ &= ac - bd + j(bc + da) \end{aligned}$$

$$\begin{aligned} A^* B^* &= (a^* - jb^*)(c^* - jd^*) \\ &= a^* c^* - b^* d^* - j(b^* c^* + d^* a^*) \end{aligned}$$

$$(AB)^* = a^* c^* - b^* d^* - j(b^* c^* + d^* a^*) = A^* B^*$$

Power in AC Circuits: Power Triangle

$$z = |z| \angle \theta$$

$$I = \frac{\tilde{V}_s}{z} = \frac{\tilde{V}_s}{|z|} \angle -\theta$$

$\underbrace{\tilde{V}_s}_{I_m}$

$$P_{avg} = \frac{V_m I_m}{2} \cos \theta_d$$

$$= \frac{V_m I_m}{2} \frac{R}{|z|}$$

$$= \frac{1}{2} I_m \left(\frac{V_m}{|z|} \right) R$$

$\underbrace{\left(\frac{V_m}{|z|} \right)}_{I_m}$

$$P_{avg} = \frac{1}{2} I_m^2 R \equiv P$$

$$\theta \equiv \theta_d$$

$$\tilde{V}_s = V_m \angle 0^\circ$$



$$\frac{V_m}{|z|} = \frac{|V_s|}{|z|} = I_m$$

$$Q = \frac{1}{2} I_m^2 X$$

$$= \frac{1}{2} I_m \frac{V_m}{|z|} X$$

$$Q = \frac{1}{2} V_m I_m \sin \theta$$

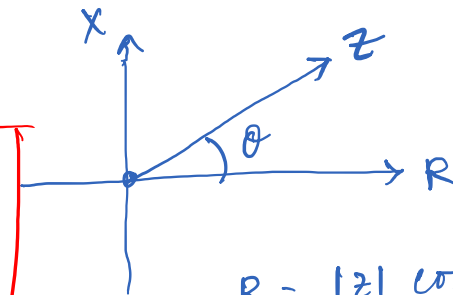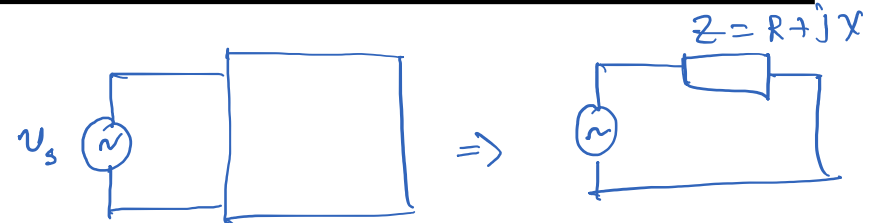
$$P^2 + Q^2 = \left(\frac{V_m I_m}{2} \right)^2$$



$$R = |z| \cos \theta$$

$$X = |z| \sin \theta$$

Power in AC Circuits: Power Triangle

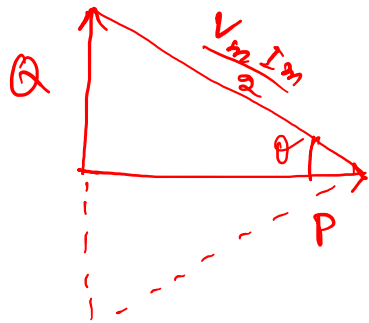

complex power:


$$\begin{aligned}\tilde{V} &= V_m e^{j\omega t} \\ \tilde{I} &= I_m e^{j(\omega t + \phi)}\end{aligned}$$

$$S = \frac{1}{2} \tilde{V} \tilde{I}^*$$

$$= \frac{1}{2} V_m I_m [\cos\phi + j \sin\phi]$$

$$S = P + jQ$$

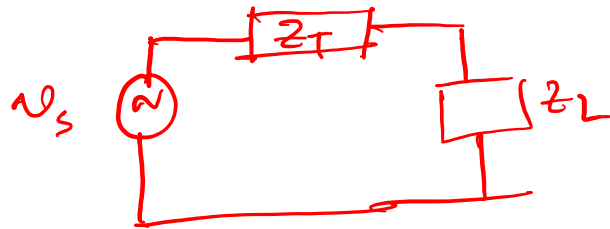Power in AC Circuits: Maximum Power Transfer



$$z = z_T + z_L$$

$$= R + jX$$

$$I = \frac{\tilde{V}_s}{R + jX}$$

$$\approx \frac{V_s}{\sqrt{R^2 + X^2}} \angle \tan^{-1} X/R$$

max power gets transferred
when $X = 0$

$$z_T = z_L^*$$

$$\text{if } z_T = a + jb$$

$$z_L = a - jb$$

$$z = 2a$$