

EECS 16B

Designing Information Devices and Systems II

Lecture 7


Prof. Sayeef Salahuddin

Department of Electrical Engineering and Computer Sciences, UC Berkeley,
sayeef@eecs.berkeley.edu


Transient Response

- Outline
 - Power in the AC circuits
 - Transfer Function and Filters
- Reading- Hambley text sections 5.6, 6.1, 6.2, 6.3 slides

Maximum Power Transfer

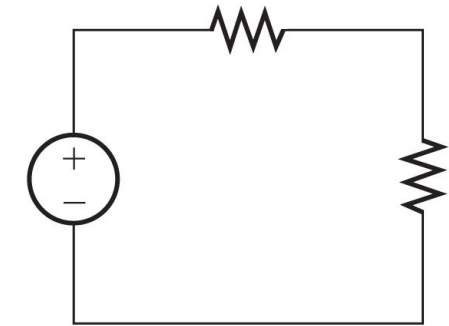


Concept of Transfer Function

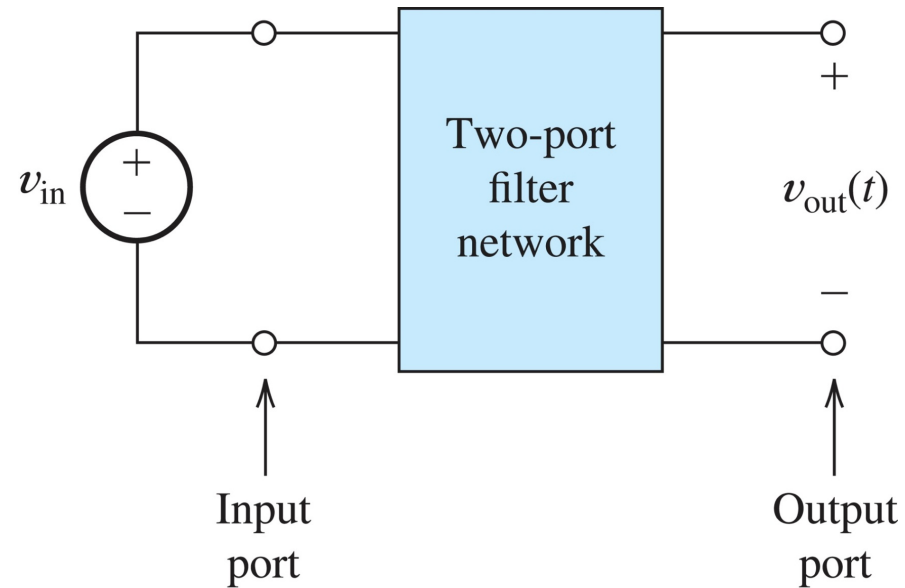

Copyright ©2018 Pearson Education, All Rights Reserved.

Two port Filter Network or more generally Two port network


Concept of Transfer Function

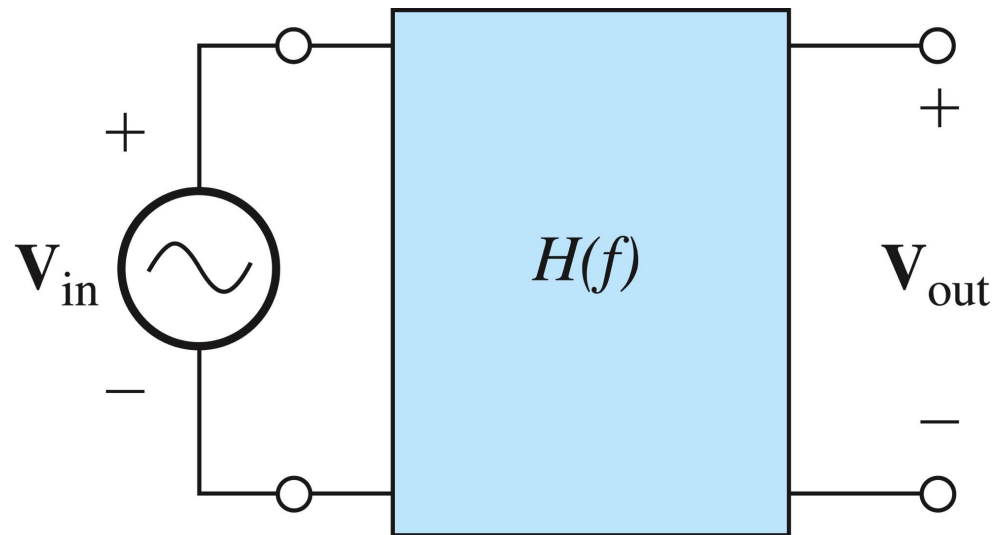


$$H(f) = \frac{V_{out}}{V_{in}}$$

$H(f)$ is a complex number




A simple RC Circuit

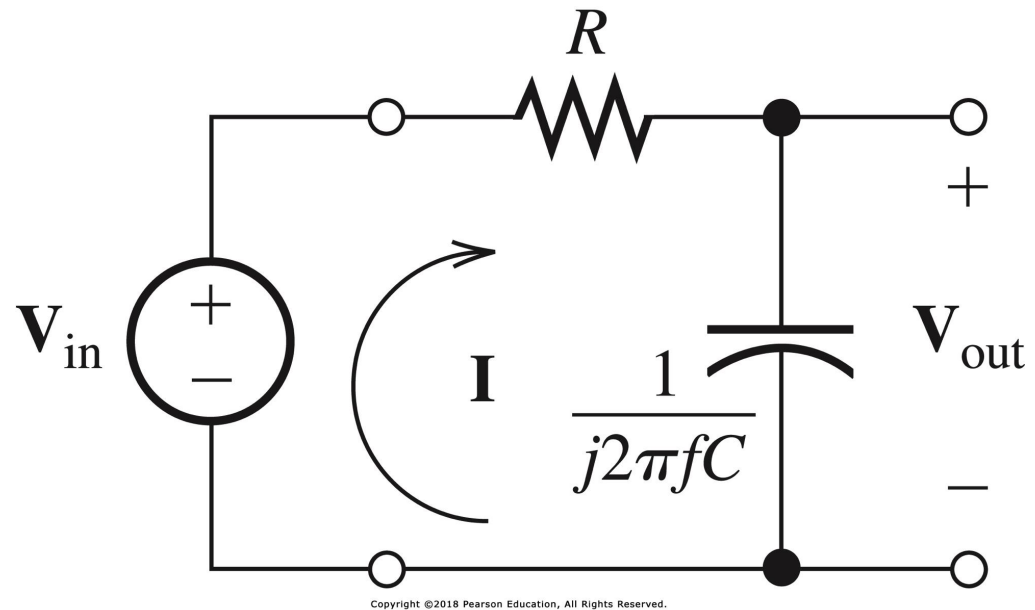

A simple RC Circuit

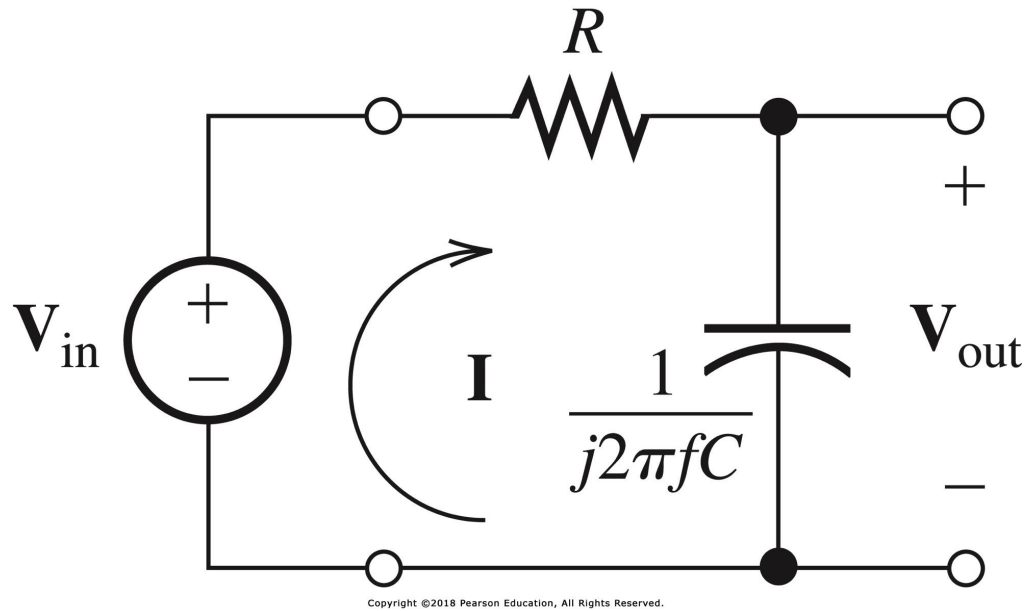

First Order low pass filter

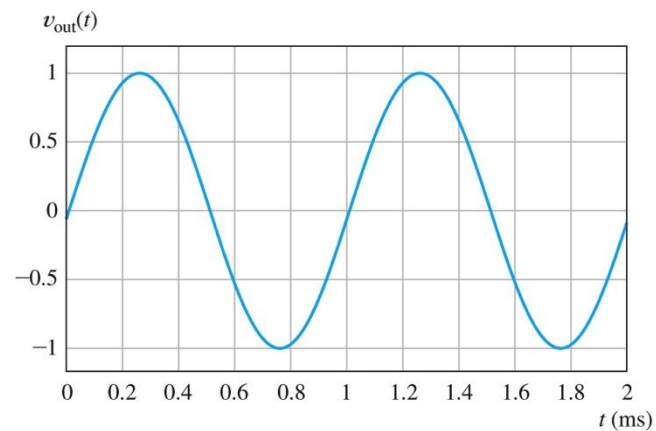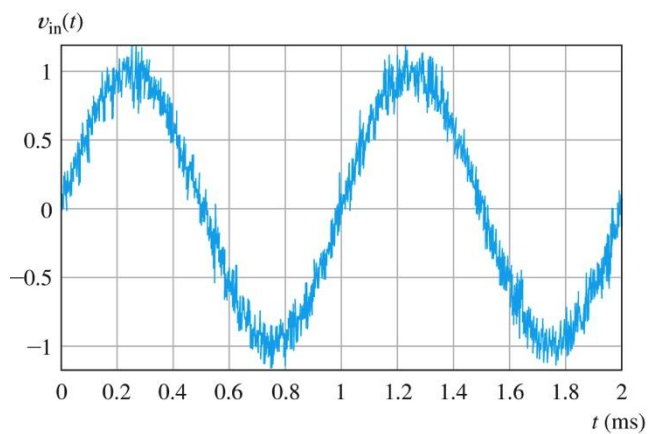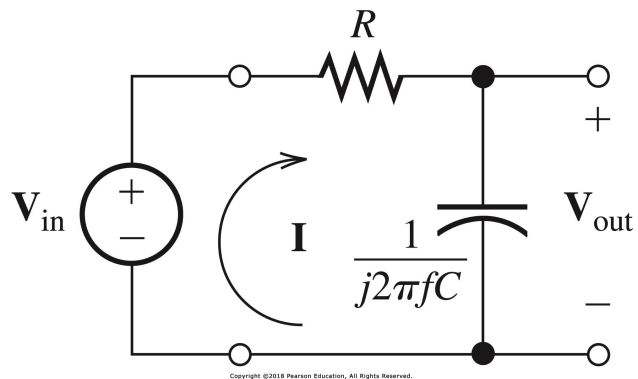

Decibels

Decibel:


$$|H(f)|_{\text{dB}} = 20 \log_{10} |H(f)|$$

Table 6.2 Transfer-Function Magnitudes and Their Decibel Equivalents

$ H(f) $	$ H(f) _{\text{dB}}$
100	40
10	20
2	6
$\sqrt{2}$	3
1	0
$1/\sqrt{2}$	-3
1/2	-6
0.1	-20
0.01	-40

Copyright ©2018 Pearson Education, All Rights Reserved.


Cascaded Networks

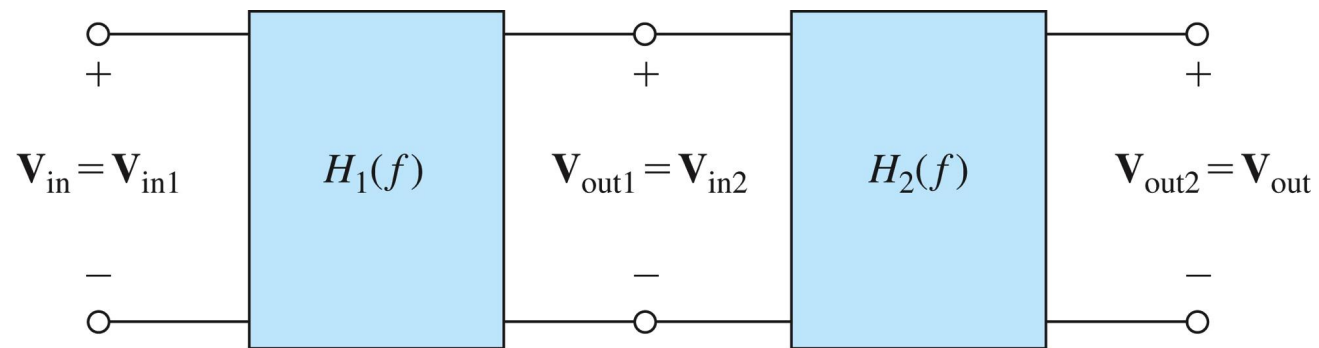

Copyright ©2018 Pearson Education, All Rights Reserved.

Logarithmic Frequency Scales

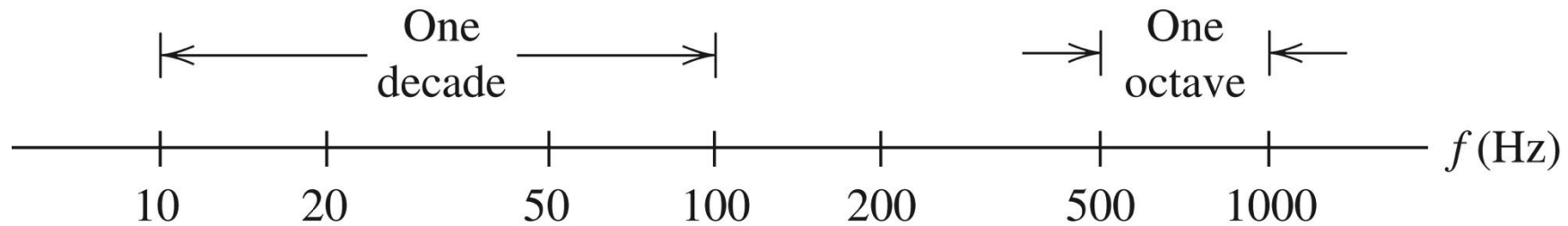- A **decade** is a range of frequencies for which the ratio of the highest frequency to the lowest is **10**
- An **Octave** is a range of frequencies for which the ratio of the highest frequency to the lowest is **2**




Copyright ©2018 Pearson Education, All Rights Reserved.

Logarithmic Frequency Scales

Bode Plots

A **Bode** plot is a plot of the decibel magnitude of a newtwork function versus log-scale frequency

Bode Plots

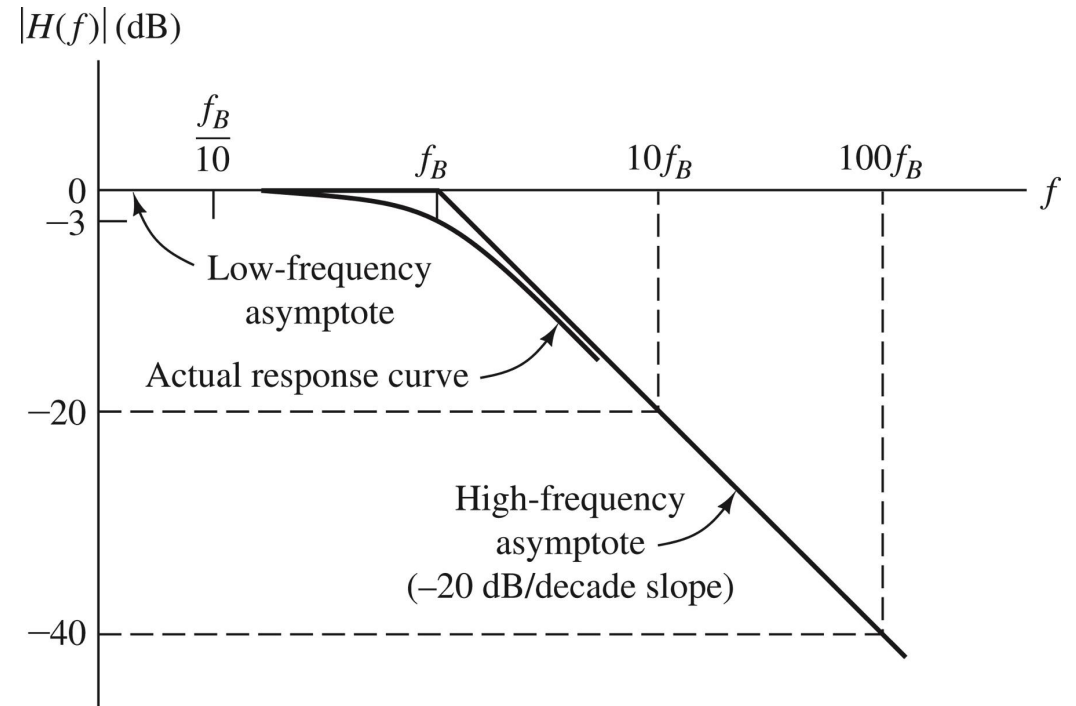

Copyright ©2018 Pearson Education, All Rights Reserved.

Phase Plot
