

EECS 16B

Designing Information Devices and Systems II
Lecture 7

Prof. Sayeef Salahuddin

Department of Electrical Engineering and Computer Sciences, UC Berkeley,
sayeef@eecs.berkeley.edu

Transient Response

- Outline
 - Power in the AC circuits
 - Transfer Function and Filters
- Reading- Hambley text sections 5.6, 6.1, 6.2, 6.3 slides

Maximum Power Transfer

$$P_{R_2} = I^2 R_2$$


$$= \frac{V^2}{(R_1 + R_2)^2} \cdot R_2$$

$$= \frac{V^2}{R_1} \cdot \frac{R_1 R_2}{(R_1 + R_2)^2}$$

$$= \frac{1}{4} \frac{V^2}{R_1} \frac{4 R_1 R_2}{(R_1 + R_2)^2}$$

$$= \frac{1}{4} \frac{V^2}{R_1} \frac{(R_1 + R_2)^2 - (R_1 - R_2)^2}{(R_1 + R_2)^2}$$

$$I = \frac{V}{R_1 + R_2}$$

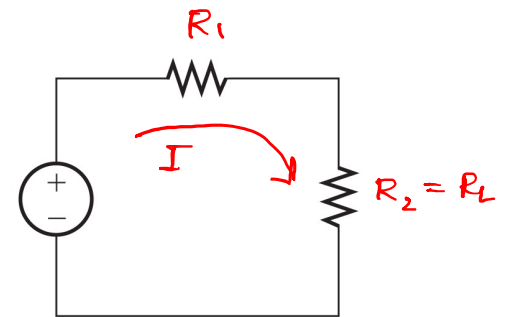


$$P_{R_2} = \frac{1}{4} \frac{V^2}{R_1} \left[1 - \left(\frac{R_1 - R_2}{R_1 + R_2} \right)^2 \right]$$

$P_{R_2}^{\text{max}}$ happens at $R_1 = R_2 = R$


$$P_{R_2}^{\text{max}} = \frac{1}{4} \frac{V^2}{R}$$

Concept of Transfer Function

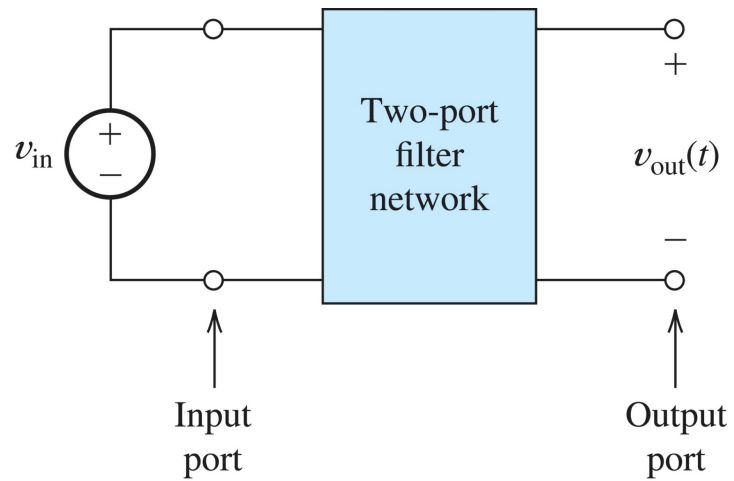

Two port Filter Network or more generally Two port network

Concept of Transfer Function

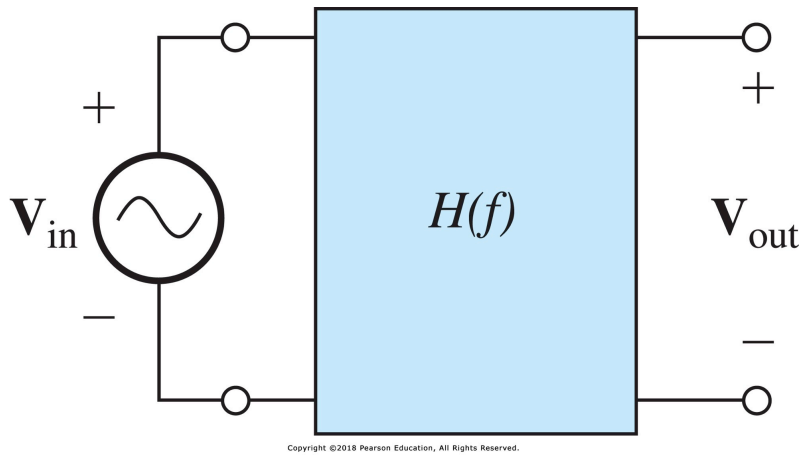


$$H(f) = \frac{\tilde{V}_{out}}{\tilde{V}_{in}}$$

Transfer function

$H(f)$ is a complex number

A simple RC Circuit

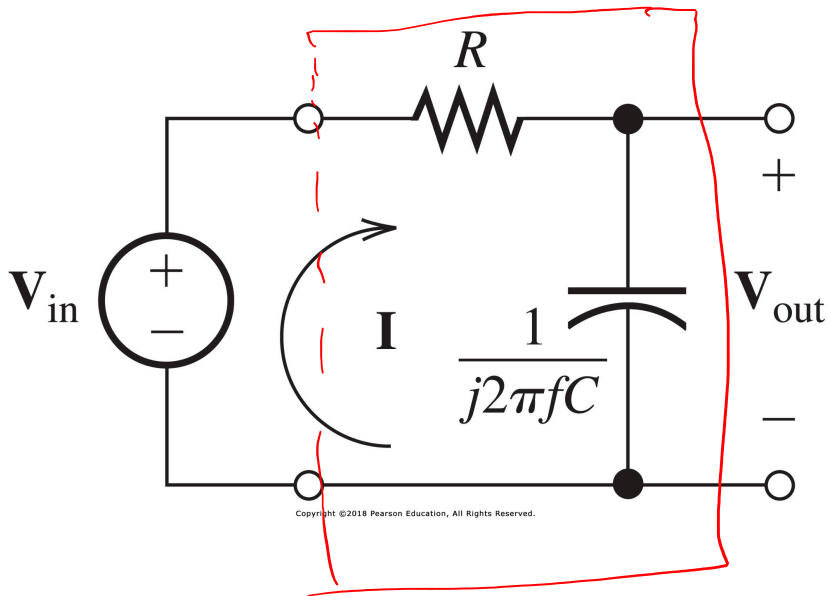

$$H(f) = \frac{V_{out}}{V_{in}}$$

$$V_{out} = I z_c = \frac{V_{in}}{R + z_c} z_c = \frac{V_{in}}{R + \frac{1}{j\omega C}} \cdot \frac{1}{j\omega C}$$


$$\frac{V_{out}}{V_{in}} = H(f) = \frac{1}{j\omega R C + 1}$$

$$= \frac{1}{\sqrt{1 + (\omega R C)^2}} \angle -\tan^{-1}(\omega R C)$$

$$= \frac{\angle -\tan^{-1}\left(\frac{\omega}{\omega_B}\right)}{\sqrt{1 + \left(\frac{\omega}{\omega_B}\right)^2}}$$

$$\boxed{\frac{1}{RC} = \omega_B}$$

A simple RC Circuit

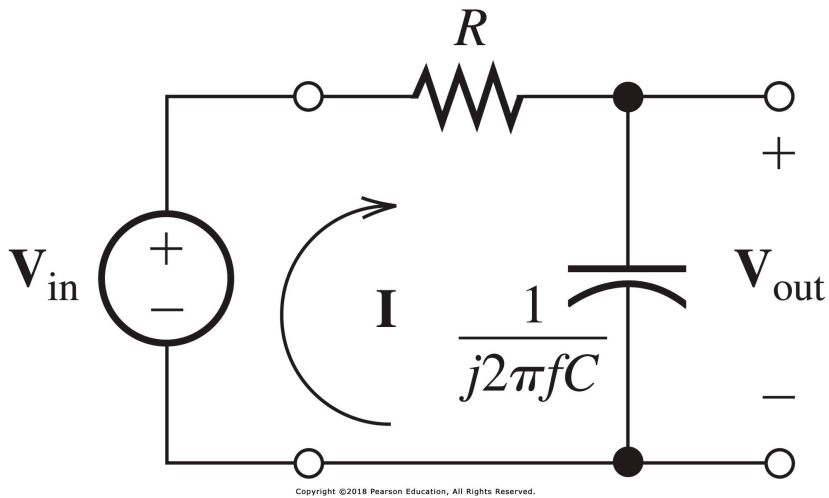


$$H(j\omega) = \frac{1}{\sqrt{1 + (\omega/\omega_B)^2}} \quad \angle = -\tan^{-1} \frac{\omega}{\omega_B}$$


$$\omega = 2\pi f$$

$$\omega_B = \frac{1}{RC} = 2\pi f_B$$



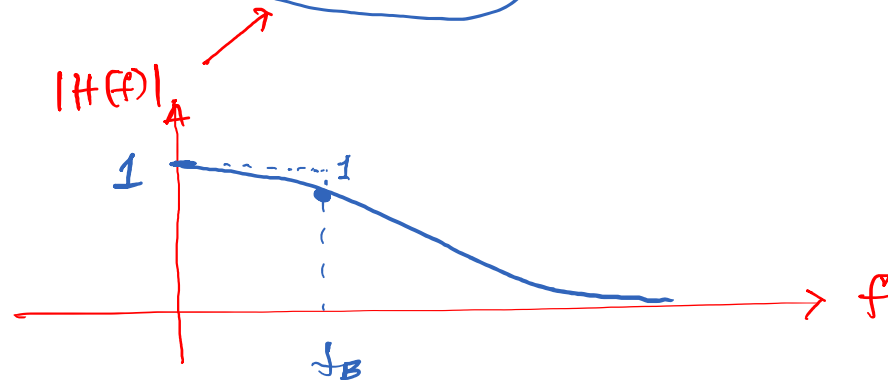
$$H(f) = \frac{1}{\sqrt{1 + (f/f_B)^2}} \quad \angle = -\tan^{-1} (f/f_B)$$



First Order low pass filter

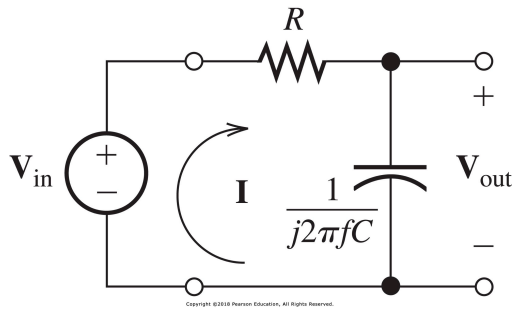

phase: $-\tan^{-1}(f/f_B)$

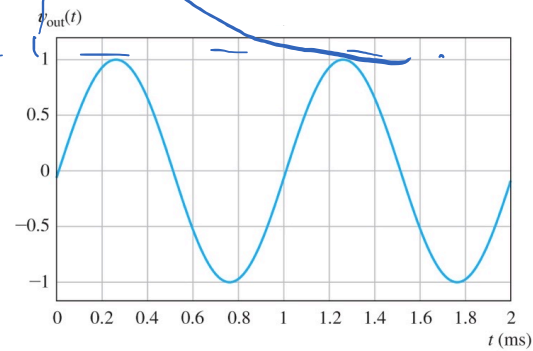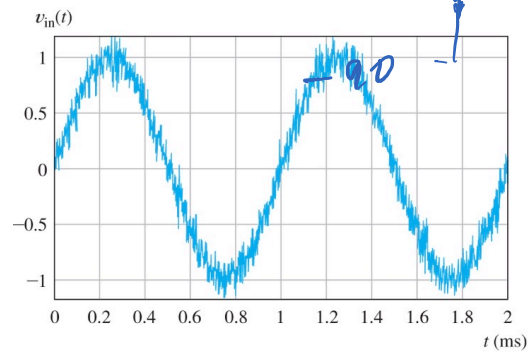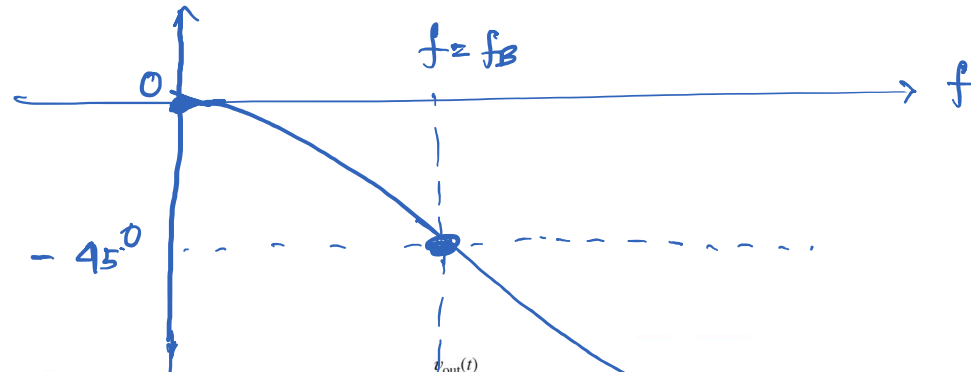

Decibels

Decibel:

$$|H(f)|_{\text{dB}} = 20 \log_{10} |H(f)|$$

$$\begin{aligned}
 & 20 \log_{10} 10^2 \\
 &= 40 \underbrace{\log_{10} 10}_1 \\
 &= 40 \text{ dB}
 \end{aligned}$$

$$\begin{aligned}
 20 \log_{10} \frac{1}{\sqrt{2}} &= 20 \log_{10} 2^{-\frac{1}{2}} \\
 &= -10 \underbrace{\log_{10} 2}_{0.3} \\
 &= -3 \text{ dB}
 \end{aligned}$$

Table 6.2 Transfer-Function Magnitudes and Their Decibel Equivalents

$ H(f) $	$ H(f) _{\text{dB}}$
100	40
10	20
2	6
$\sqrt{2}$	3
1	0
$1/\sqrt{2}$	-3
1/2	-6
0.1	-20
0.01	-40


Copyright ©2018 Pearson Education, All Rights Reserved.

Cascaded Networks

$$\begin{aligned} H(f) &= \frac{V_{out}}{V_{in}} \\ &= \frac{V_{out2}}{V_{in2}} \times \frac{V_{in2}}{V_{in}} \\ &= \frac{V_{out2}}{V_{in2}} \times \frac{V_{out1}}{V_{in1}} \end{aligned}$$

$$= H(f)_1 \times |H(f)|_2$$


$$|H(f)|_{dB} = 20 \log_{10} |H(f)|_1 + 20 \log_{10} |H(f)|_2$$

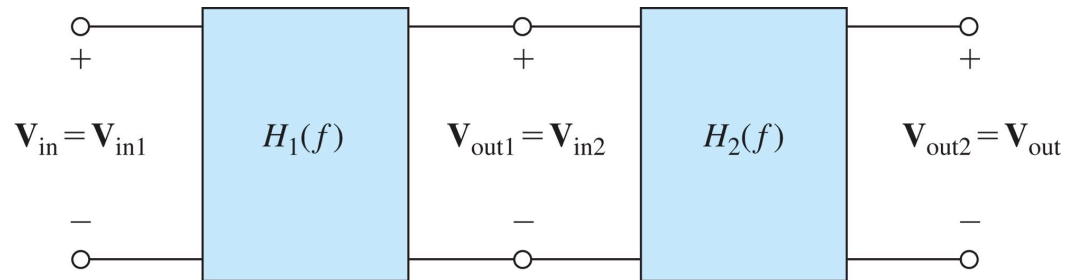

Copyright ©2018 Pearson Education, All Rights Reserved.

Logarithmic Frequency Scales

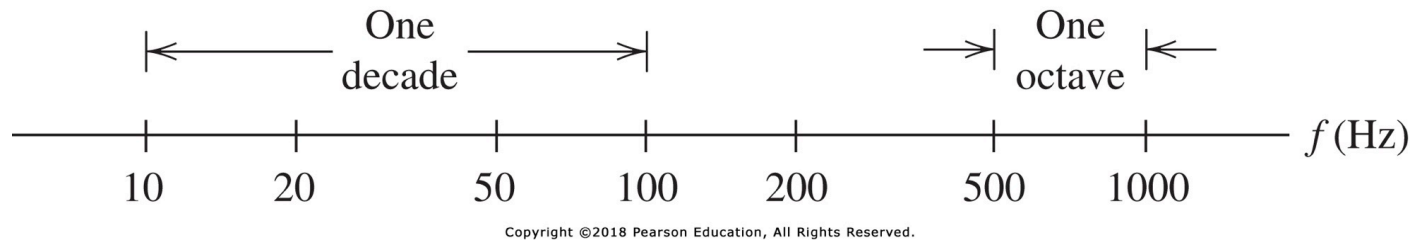- A **decade** is a range of frequencies for which the ratio of the highest frequency to the lowest is **10**
- An **Octave** is a range of frequencies for which the ratio of the highest frequency to the lowest is **2**




Logarithmic Frequency Scales


10 Hz \longleftrightarrow 1000 Hz \longrightarrow

Octaves:
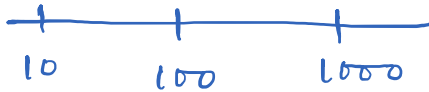
$$n = \log_2 \left(\frac{f_2}{f_1} \right) = \frac{\log_{10} f_2/f_1}{\log_{10} 2} = \frac{2}{0.3} \approx 6$$


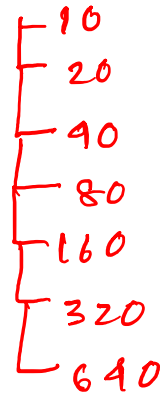
$$\begin{aligned} n &= \log_{10} \left(\frac{f_2}{f_1} \right) \\ &= \log_{10} \frac{10^3}{10^1} \\ &= \log_{10} 10^2 \\ &= 2 \end{aligned}$$



Bode Plots

A **Bode** plot is a plot of the decibel magnitude of a newtwork function versus log-scale frequency


$$f = 0, |H(f)|_{dB} = 0$$

$$f = f_B, |H(f)|_{dB} = -10 \log_{10} (1 + 1) = -3dB$$

$$f \gg f_B, |H(f)|_{dB} \approx -10 \log_{10} (f/f_B)^2$$
$$= -20 \log_{10} (f/f_B)$$

$$|H(f)|_{dB} = -20 \log_{10} f + 20 \log_{10} f_B \leftarrow y = mx + c$$

$$|H(f)|_{dB} = 20 \log_{10} |H(f)|$$
$$= 20 \log_{10} \frac{1}{\sqrt{1 + (f/f_B)^2}}^{-1/2}$$
$$= 20 \log_{10} [1 + (f/f_B)^2]$$
$$= -20 \log_{10} [1 + (f/f_B)^2]$$

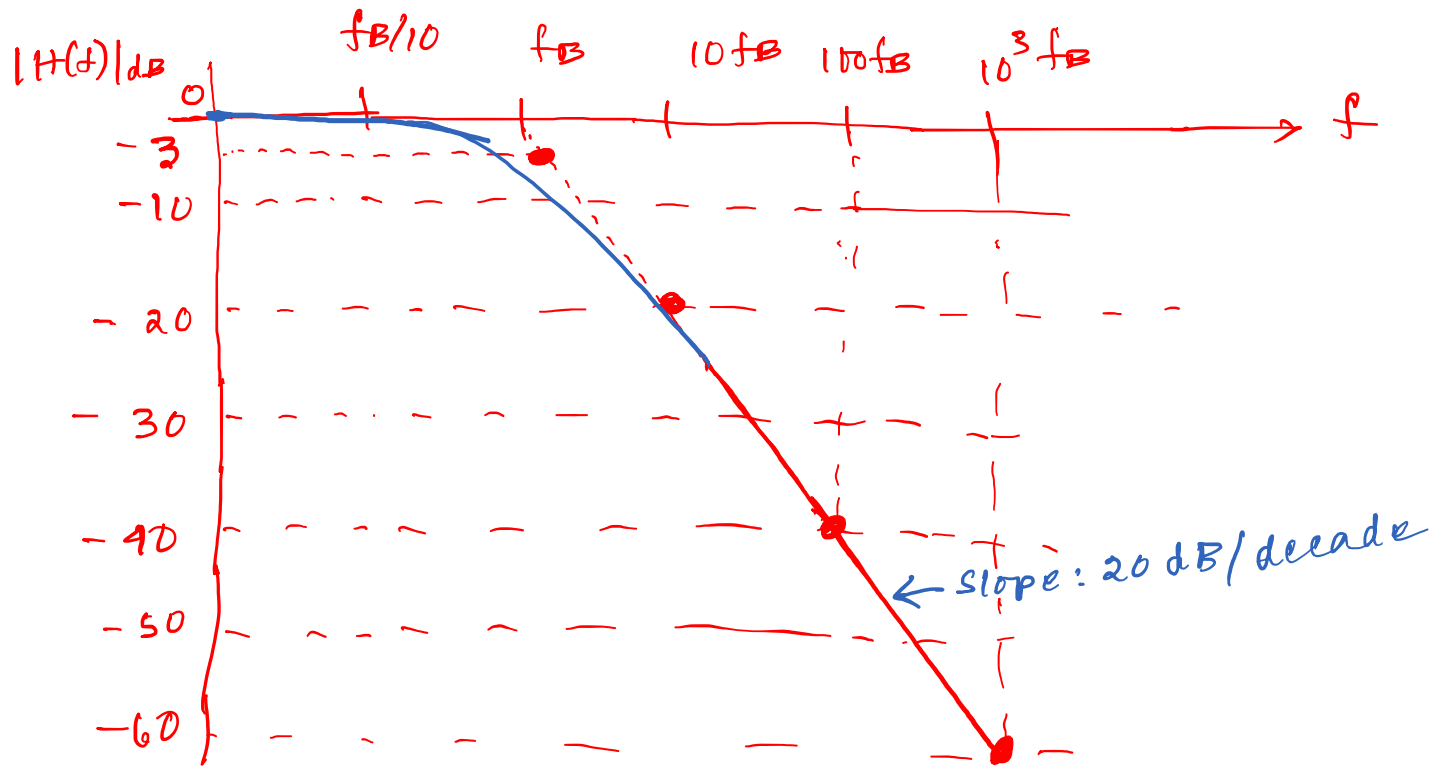



Bode Plots

Phase: $\angle -\tan^{-1} f/f_B$

$f=0 \rightarrow \text{phase} = 0$

$f=f_B \rightarrow \text{phase} = -45^\circ$

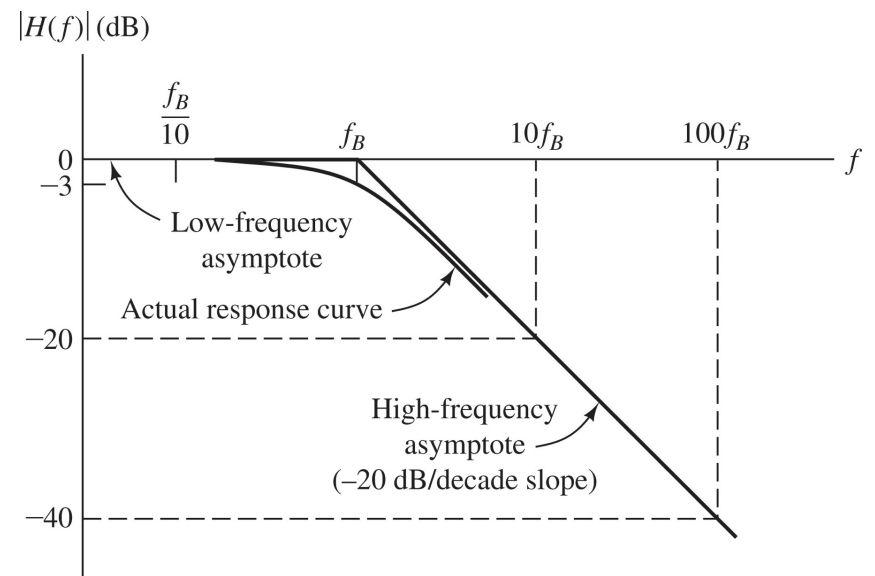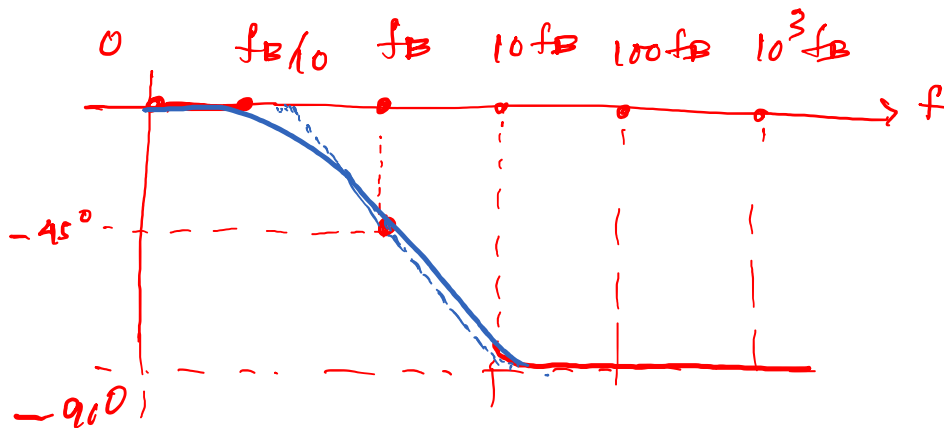$f \gg f_B \rightarrow \text{phase} = -90^\circ$



Copyright ©2018 Pearson Education, All Rights Reserved.

High Pass Filter

