

**EECS 16B**

# **Designing Information Devices and Systems II**

## **Lecture 10**

Prof. Sayeef Salahuddin


Department of Electrical Engineering and Computer Sciences, UC Berkeley,  
sayeef@eecs.berkeley.edu

# Devices

---

- Outline
  - Amplifiers and Devices
  - Vector Differential Equations
- Reading-slides

# Recap: Active Devices

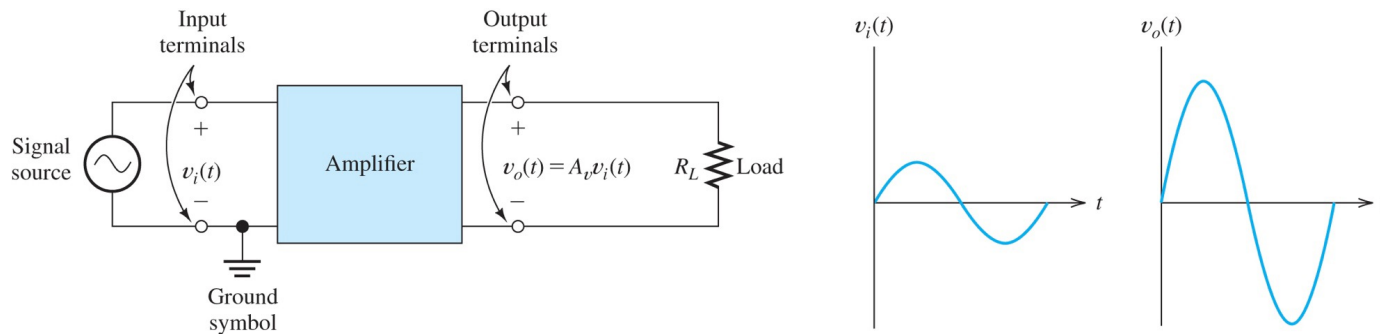




Copyright ©2018 Pearson Education, All Rights Reserved.

- Active devices are made of semiconductors
- Semi-conductors are materials whose resistance is in between a metal and insulator

## Half

- More interestingly, one is able to change the resistance of the semiconductor materials by using external control such as voltage or current

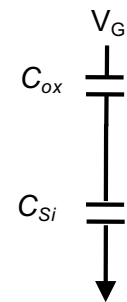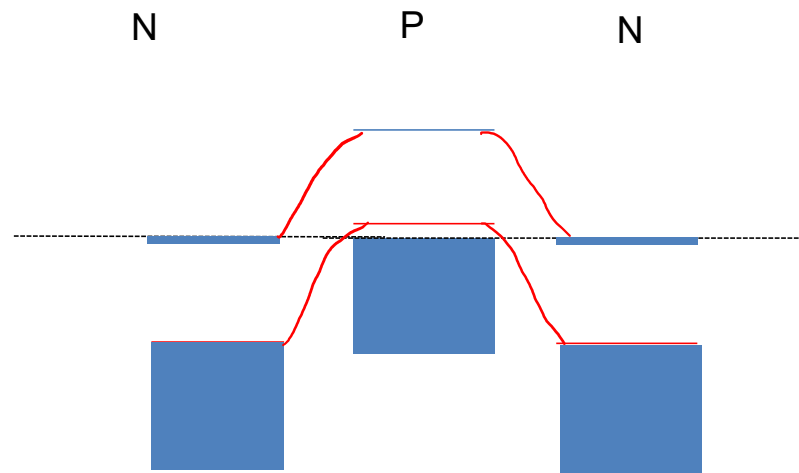
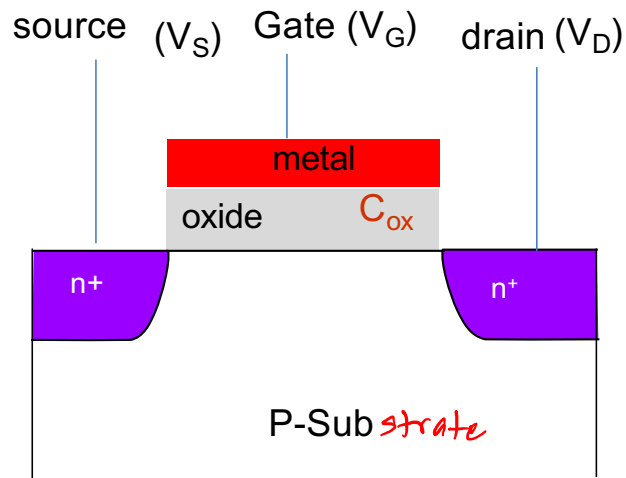
# Metal-Oxide-Semiconductor Field Effect Transistor (MOSFET)




- + or – in the name of n or p type material indicates extent of doping. N+ means doped **heavily** to n type.
- In common MOSFET source and drain voltages are interchangeable

P-type semiconductor in the middle with little to no electrons on the conduction band acts like an insulator




# Recap: Capacitors (Review)

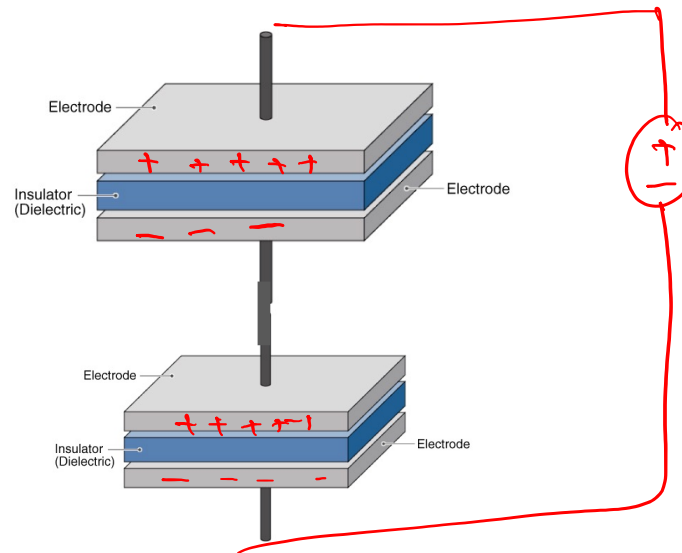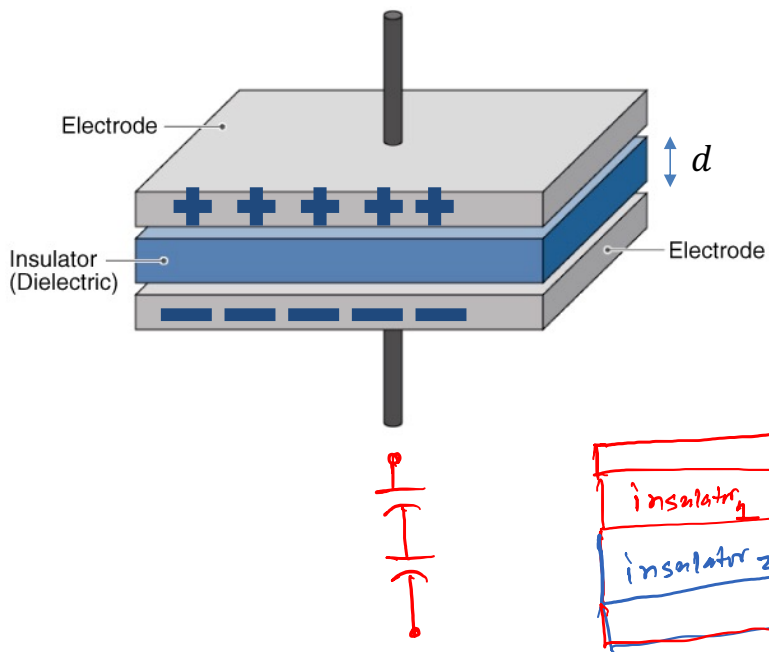

# MOSFET



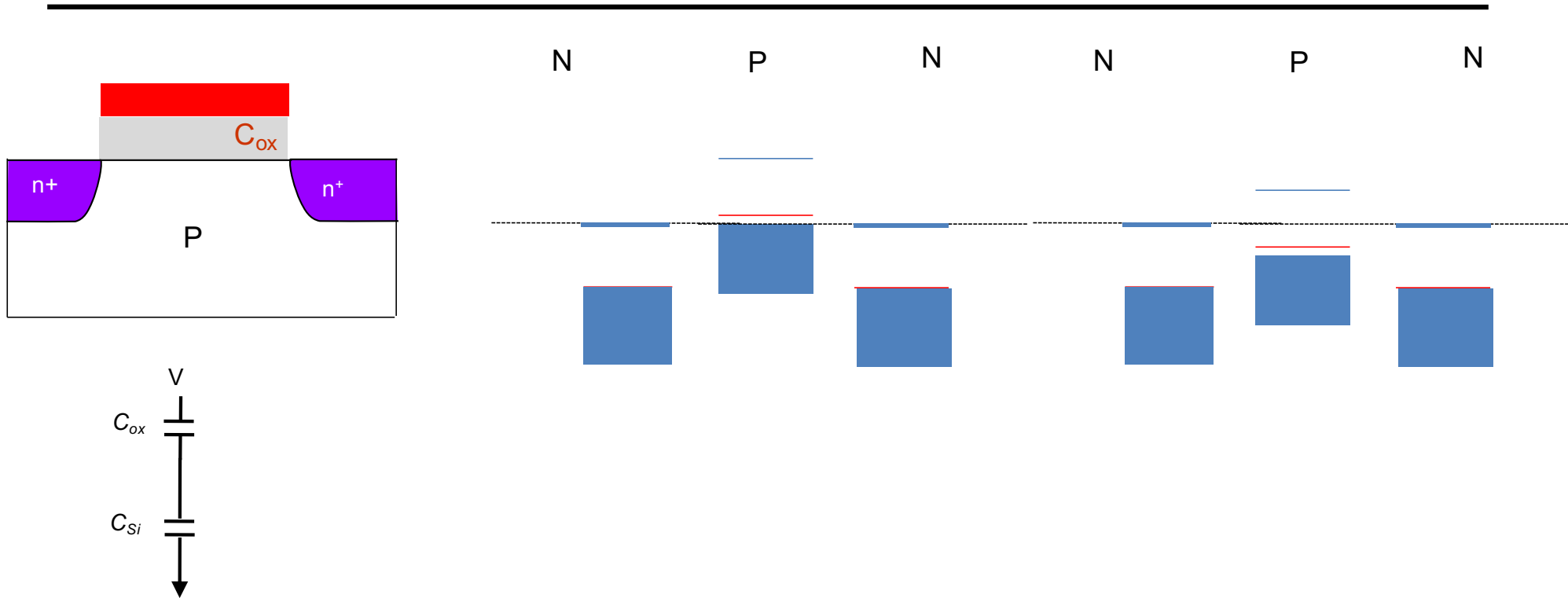


# MOSFET

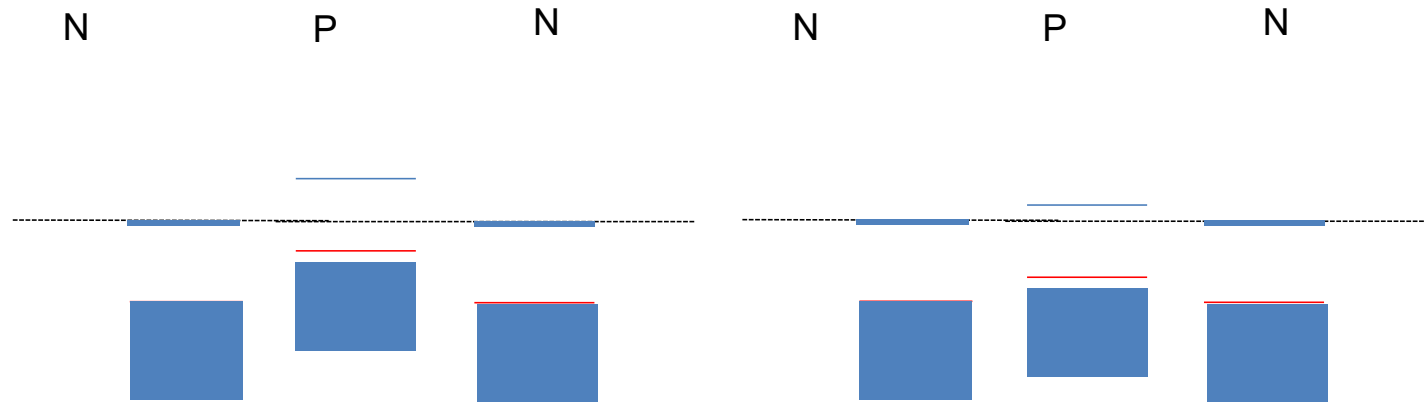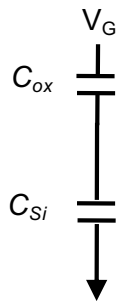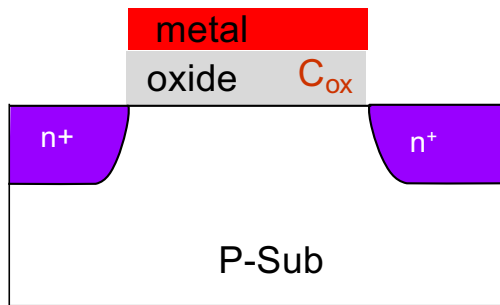


At large gate voltages, one reaches close to maximum charge density achievable in Si. So rate of change in increase in electron density with gate voltage slows down

# MOSFETs

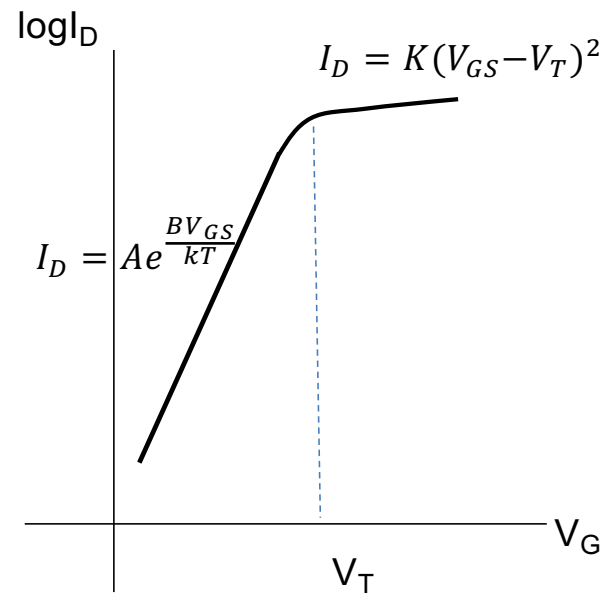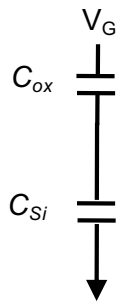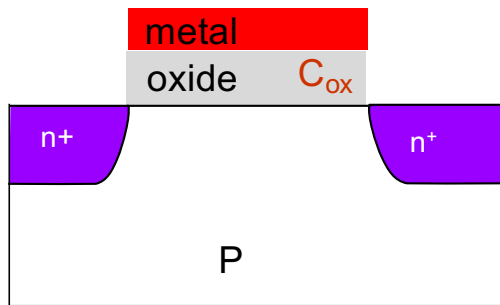

Assuming large  $V_{DS}$  is present


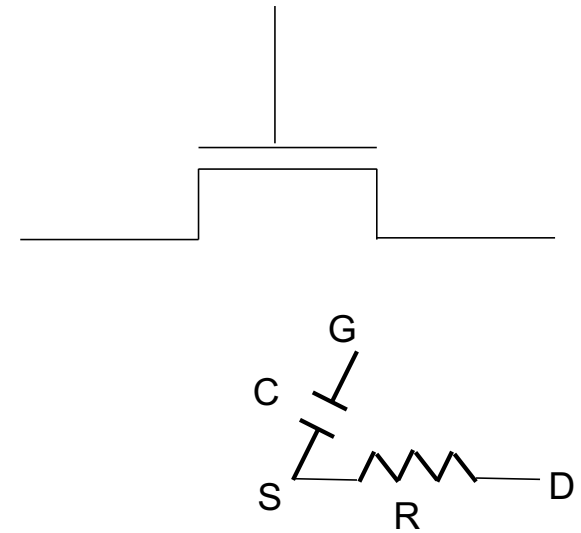


- C is the series combination of  $C_{ox}$  and  $C_{si}$
- $R = I_{DS}/V_{DS}$





# nFET vs pFET



---

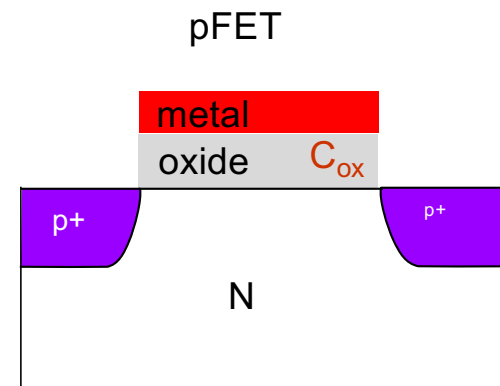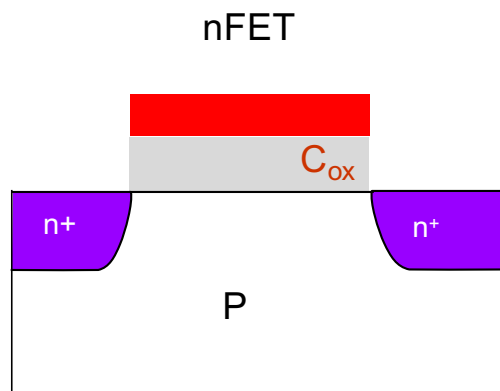

# nFET vs pFET

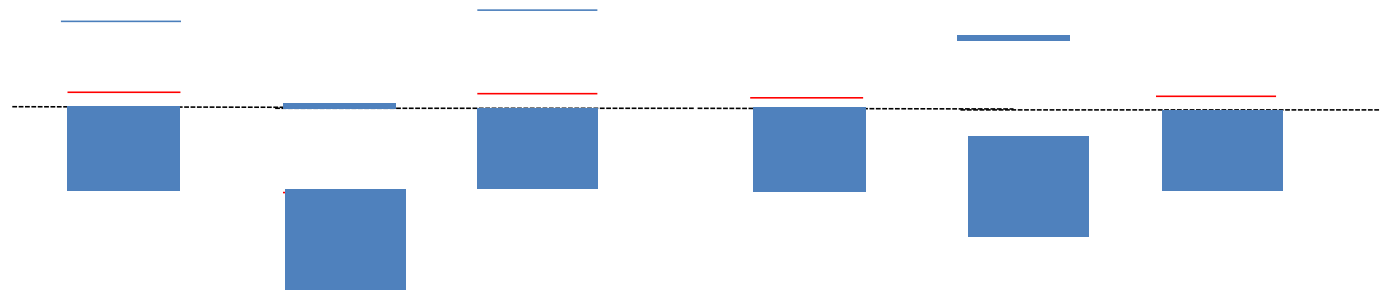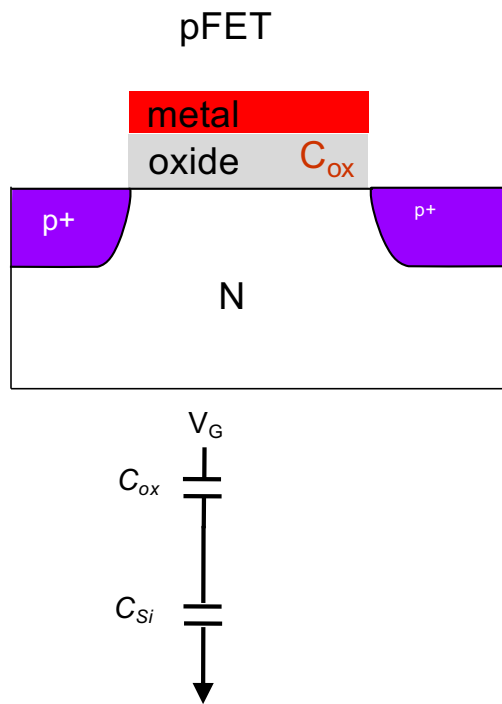


# nFET vs pFET

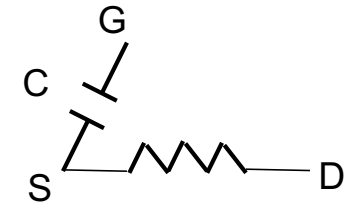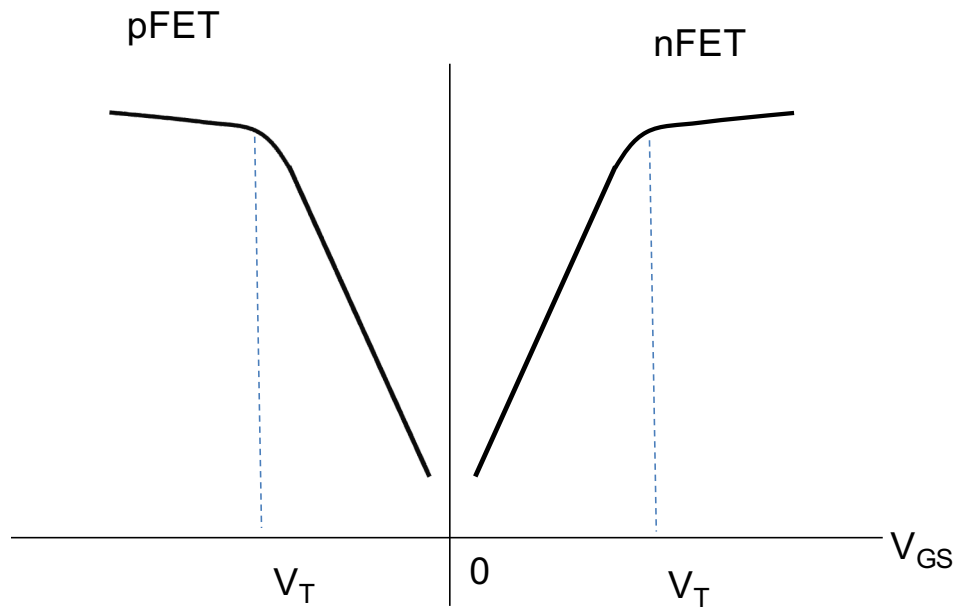

- nFET,  $V_{GS}$  and  $V_T$  are positive
- pFET,  $V_{GS}$  and  $V_T$  are negative

# FET as an analog amplifier

---

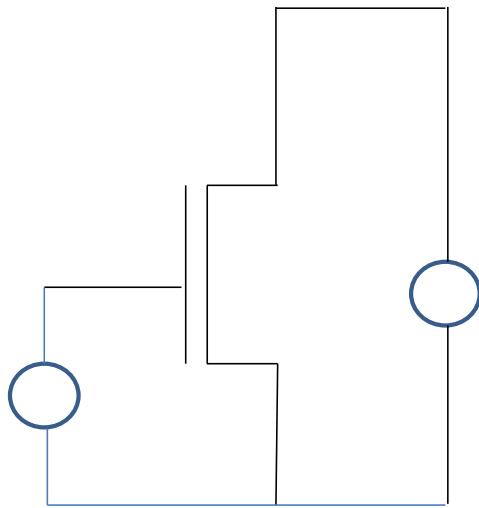

When  $V_{GS} < V_T$

$$I_D = A e^{\frac{BV_{GS}}{kT}}$$

Small change in  $V_{GS}$  changes  $I_D$  exponentially

When  $V_{GS} > V_T$




$$I_D = K(V_{GS} - V_T)^2$$

Small change in  $V_{GS}$  changes  $I_D$  quadratically

Overall, Large changes in the Drain current can be achieved by changing Gate Voltage



The parameter that is used to quantify the amplification is called **Transconductance**  $g_m = \frac{dI_D}{dV_{GS}}$

# FET in digital logic

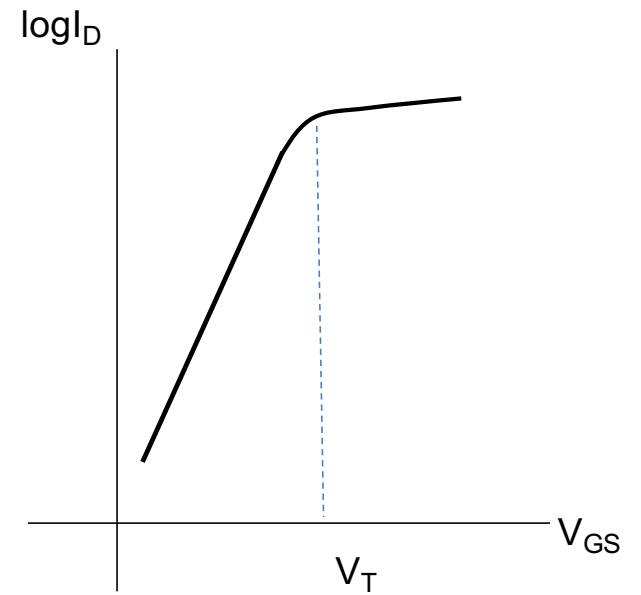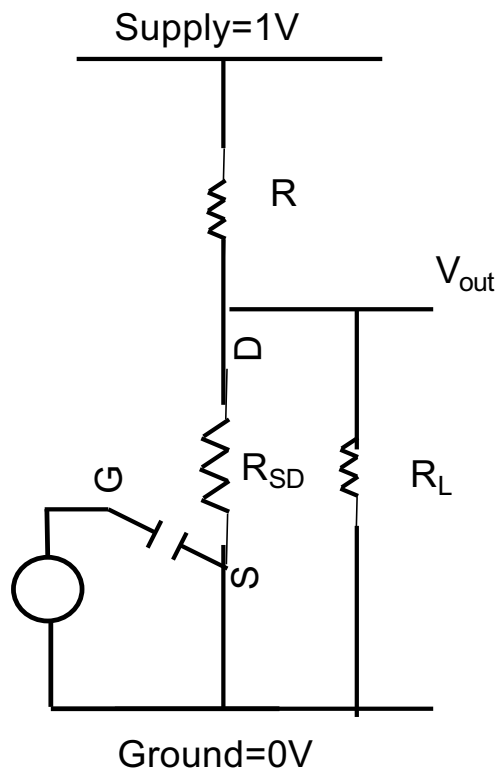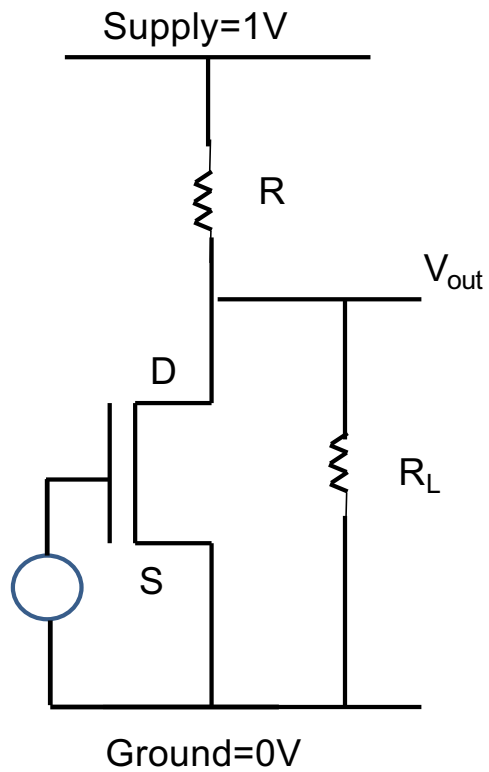

When  $V_{GS}$  is High,  $R_{SD}$  is low  
When  $V_{GS}$  is Low,  $R_{SD}$  is High



# FET in digital logic

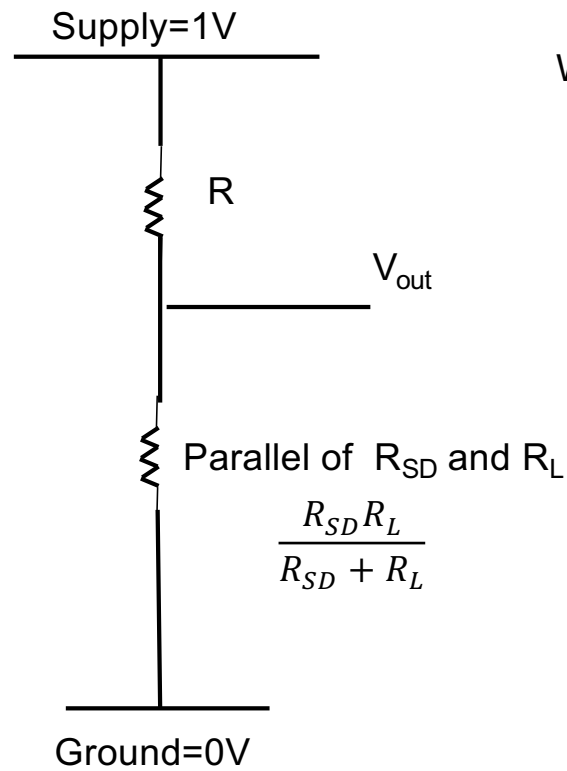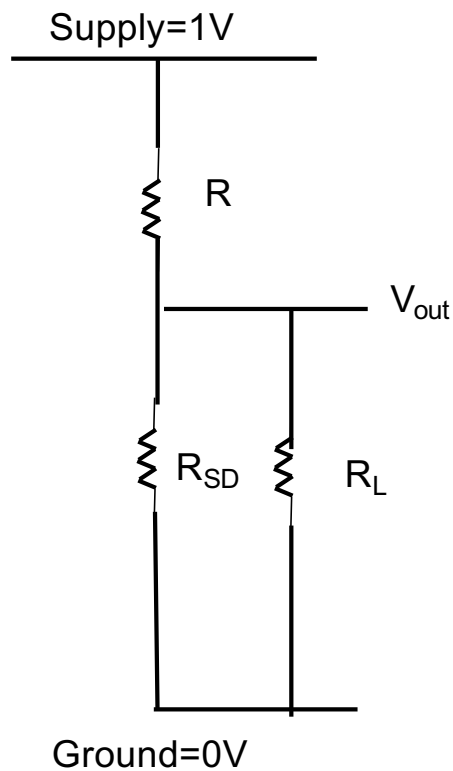

When  $R_{SD} \ll R_L$ ;  $\frac{R_{SD}R_L}{R_{SD} + R_L} \approx \frac{R_{SD}}{R_L} \approx 0$


When  $R_{SD} \gg R_L$ ;  $\frac{R_{SD}R_L}{R_{SD} + R_L} \approx R_L$

# FET in digital logic

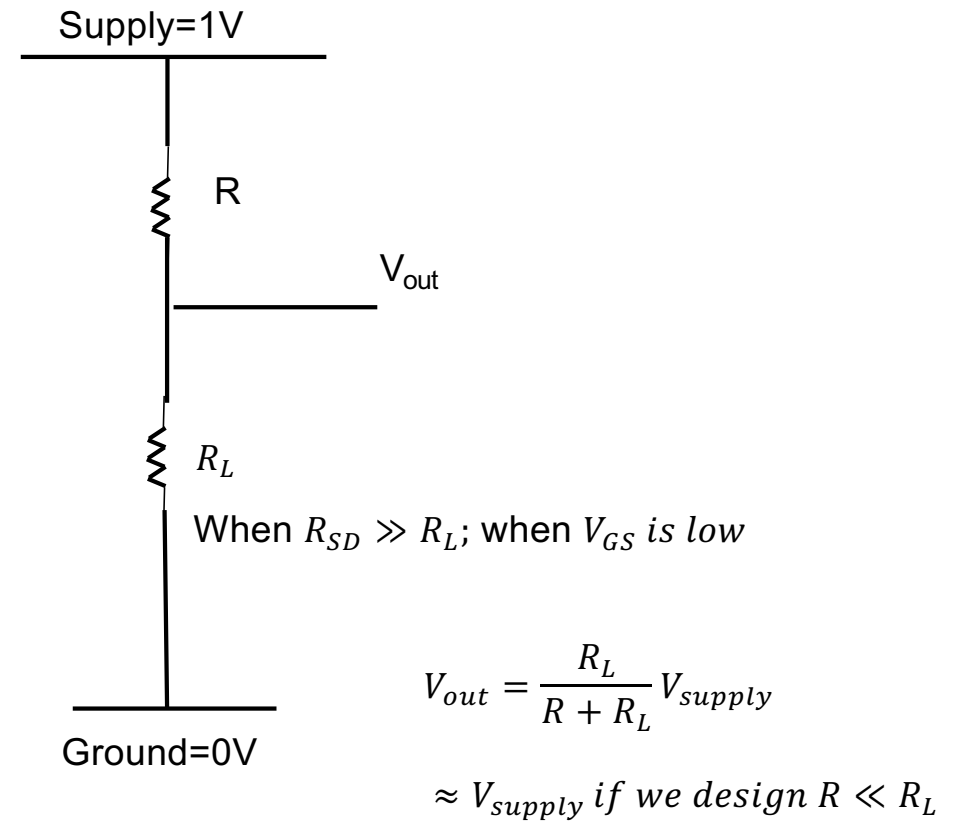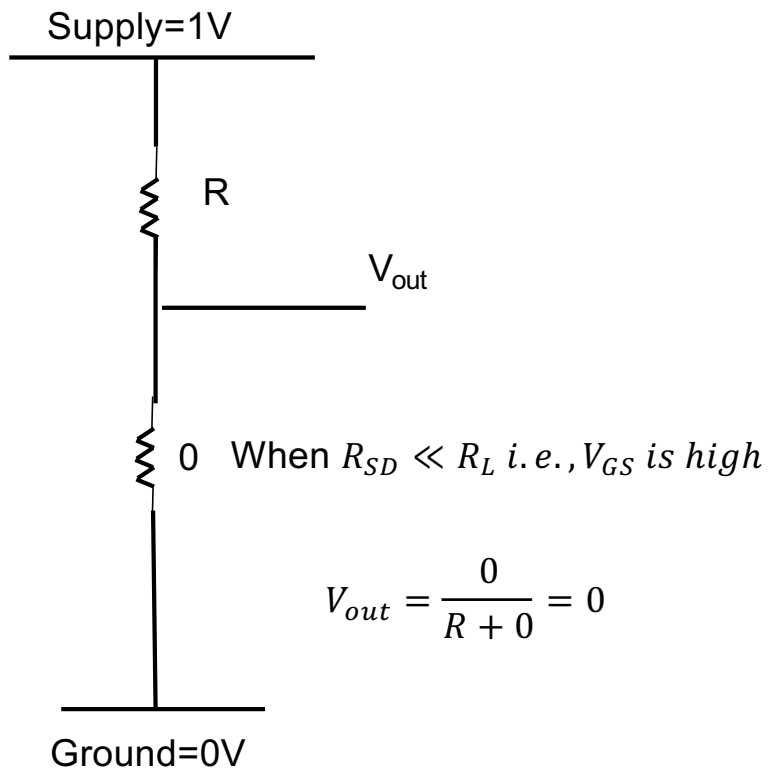





# FET in digital logic

---

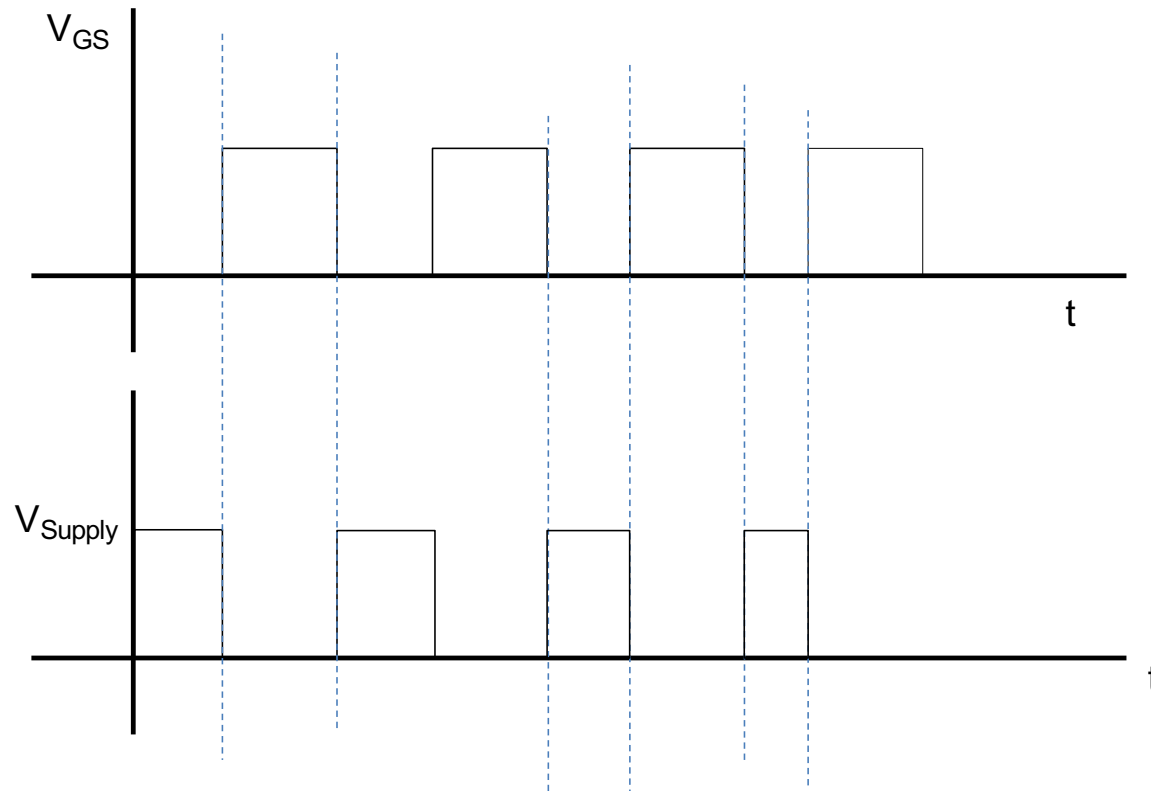



# CMOS

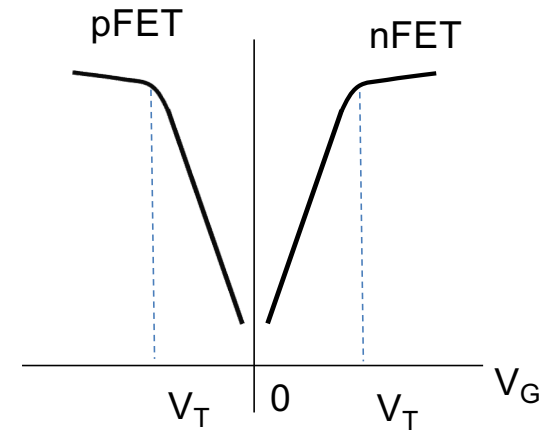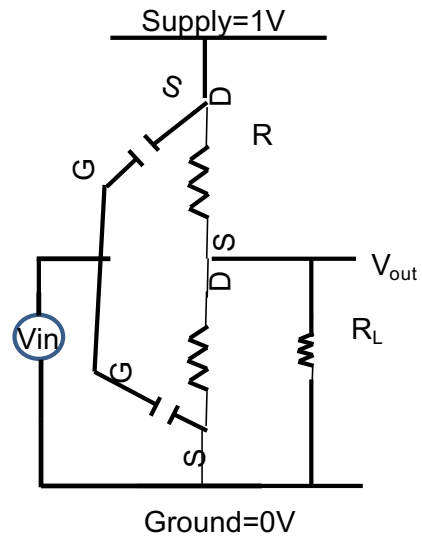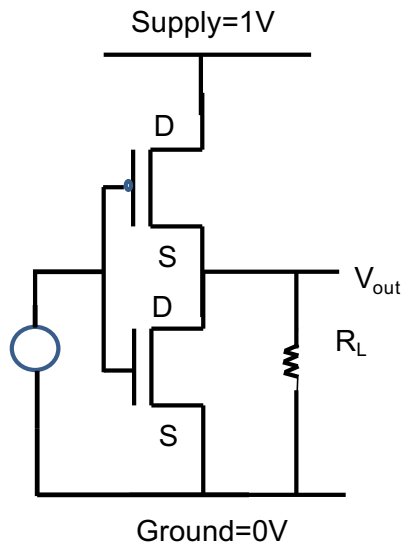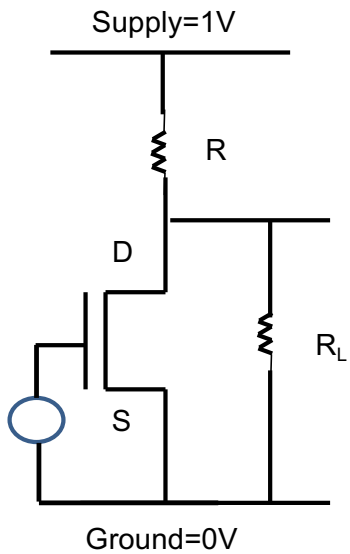

**$V_{in}=1V$**

$V_{GS}$  for nFET is HIGH  $\rightarrow R_{SD}$  is LOW


$V_{GS}$  for pFET is LOW  $\rightarrow R_{SD}$  is high

**$V_{in}=0V$**

$V_{GS}$  for nFET is LOW  $\rightarrow R_{SD}$  is HIGH

$V_{GS}$  for pFET is HIGH **NEGATIVE**  $\rightarrow R_{SD}$  is LOW

# Vector Differential Equations

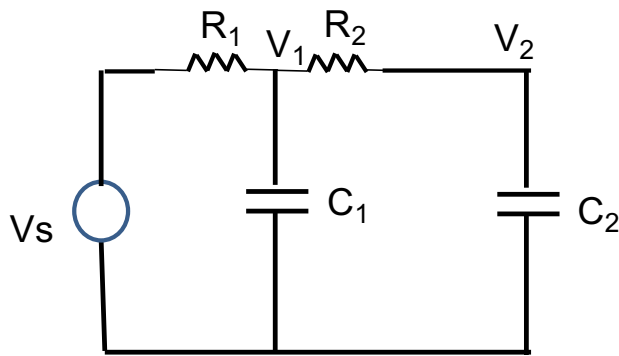

$$V_1 = I_2 R_2 + V_2 = R_2 C_2 \frac{dV_2}{dt} + V_2$$

$$\frac{dV_2}{dt} = \frac{1}{R_2 C_2} V_1 - \frac{1}{R_2 C_2} V_2$$

$$\frac{dV_1}{dt} = -\left(\frac{1}{R_2 C_1} + \frac{1}{R_1 C_1}\right) V_1 + \frac{1}{R_2 C_1} V_2 + \frac{1}{R_1 C_1} V_s$$

$$\frac{dV_2}{dt} = \frac{1}{R_2 C_2} V_2 - \frac{1}{R_2 C_2} V_2$$

$$V_s - V_1 = I R_1 \quad ; \quad I = I_1 + I_2 = C_1 \frac{dV_1}{dt} + C_2 \frac{dV_2}{dt}$$

$$V_s - V_1 = \left(C_1 \frac{dV_1}{dt} + C_2 \frac{dV_2}{dt}\right) R_1$$


$$R_2 (V_s - V_1) = \left(R_2 C_1 \frac{dV_1}{dt} + R_2 C_2 \frac{dV_2}{dt}\right) R_1$$

$$\frac{dV_1}{dt} = -\frac{1 + \frac{R_2}{R_1}}{R_2 C_1} V_1 + \frac{1}{R_2 C_1} V_2 + \frac{1}{R_1 C_1} V_s$$

$$\frac{dV_1}{dt} = -\left(\frac{1}{R_2 C_1} + \frac{1}{R_1 C_1}\right) V_1 + \frac{1}{R_2 C_1} V_2 + \frac{1}{R_1 C_1} V_s$$

# Vector Differential Equations

---

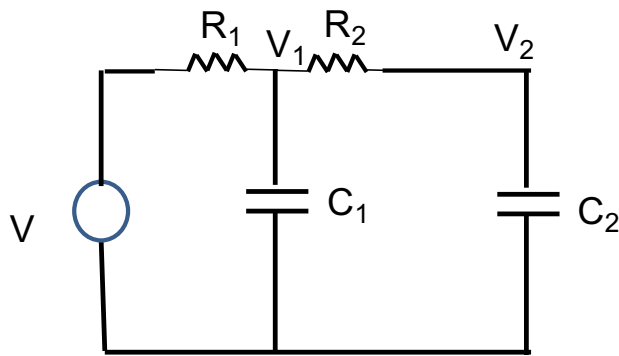

$$\frac{dV_1}{dt} = -\left(\frac{1}{R_2 C_1} + \frac{1}{R_1 C_1}\right) V_1 + \frac{1}{R_2 C_1} V_2 + \frac{1}{R_1 C_1} V_s$$

$$\frac{dV_2}{dt} = \frac{1}{R_2 C_2} V_1 - \frac{1}{R_2 C_2} V_2$$

$$\frac{d}{dt} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -\left(\frac{1}{R_2 C_1} + \frac{1}{R_1 C_1}\right) & \frac{1}{R_2 C_1} \\ \frac{1}{R_2 C_2} & -\frac{1}{R_2 C_2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} \frac{1}{R_1 C_1} V_s \\ 0 \end{bmatrix}$$