
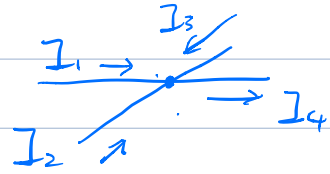


EECS 16B DLS 1 Crayne

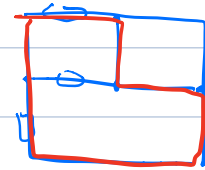


Review

- KCL: the sum of all currents entering a node must equal 0
- KVL: the sum of all voltages in a circuit loop must equal 0




- Op-amp (operational amplifier)

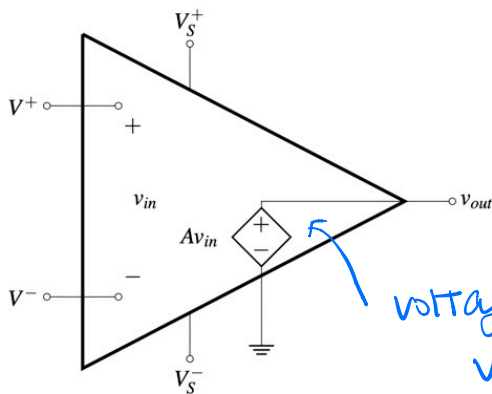

voltage-controlled voltage source

Figure 3: General Op-Amp Model

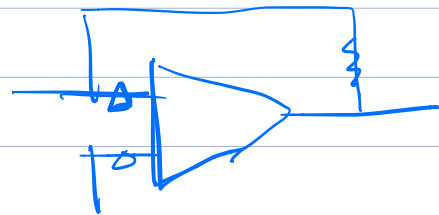

ideal op-amp:

a) $R_{in} \rightarrow \infty$

b) $R_{out} \rightarrow 0$

c) $A \rightarrow \infty$

gain

$$V_{out} = A(V_+ - V_-)$$

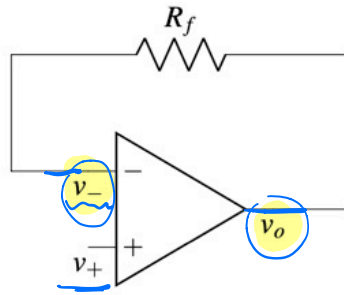


Figure 4: Ideal Op-Amp in Negative Feedback

Golden Rules of ideal op-amps in negative feedback:

- (a) No current can flow into the input terminals ($I_- = 0$ and $I_+ = 0$).
- (b) The (+) and (-) terminals are at the same voltage ($V_+ = V_-$).

regardless of
negative feedback

1. KVL/KCL Review

Use Kirchhoff's Laws on the circuit below to find V_x in terms of V_{in}, R_1, R_2, R_3 .

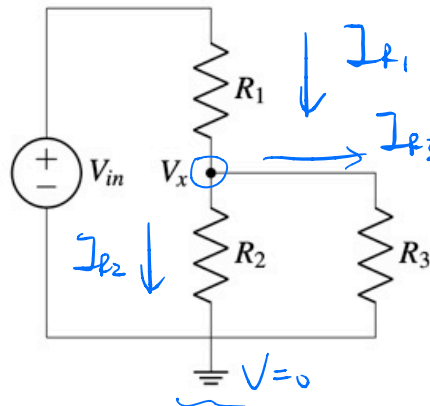


Figure 5: Example Circuit

(a) What is V_x ?

(b) As $R_3 \rightarrow \infty$, what is V_x ? What is the name we used for this type of circuit?

a) approach: use KCL at node V_x

$$I_{R_1} - I_{R_2} - I_{R_3} = 0$$

$$\frac{V_{in} - V_x}{R_1} - \frac{V_x - 0}{R_2} - \frac{V_x - 0}{R_3} = 0$$

$$\Rightarrow V_x = V_{in} \frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

b) $R_3 \rightarrow \infty$

may ignore

$$\Rightarrow V_x = V_{in} \frac{R_2}{R_1 + R_2}$$

Voltage divider

2. Op-Amp Summer

Consider the following circuit (assume the op-amp is ideal):

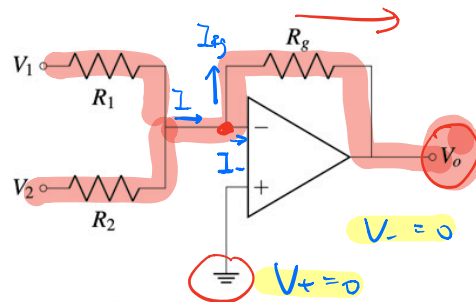


Figure 6: Op-amp Summer

What is the output V_o in terms of V_1 and V_2 ? You may assume that R_1 , R_2 , and R_g are known.

approach: KCL at V_-

$$I - I_{Pg} - I_- = 0$$

$$I = I_{Pg}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = I_{Pg}$$


$$I_{Pg} = -\frac{V_o}{R_g}$$

$$V_o = -\left(\frac{R_g}{R_1} V_1 + \frac{R_g}{R_2} V_2\right)$$

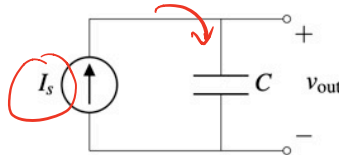3. **Current Sources And Capacitors** (The following problem has been adapted from EECS16A Fall 20 Disc 9A.)

Recall charge has units of Coulombs (C), and capacitance is measured in Farads (F) = $\frac{\text{Coulomb}}{\text{Volt}}$.
 It may also help to note metric prefix examples: $3\mu\text{F} = 3 \times 10^{-6}\text{F}$.

Given the circuit below, find an expression for $v_{\text{out}}(t)$ in terms of I_s , C , V_0 , and t , where V_0 is the initial voltage across the capacitor at $t = 0$.



Then plot the function $v_{\text{out}}(t)$ over time on the graph below for the following conditions detailed below. Use the values $I_s = 1\text{mA}$ and $C = 2\mu\text{F}$.

- (a) Capacitor is initially uncharged $V_0 = 0$ at $t = 0$.
- (b) Capacitor has been charged with $V_0 = +1.5\text{V}$ at $t = 0$.
- (c) **Practice:** Swap this capacitor for one with half the capacitance $C = 1\mu\text{F}$, which is initially uncharged $V_0 = 0$ at $t = 0$.


HINT: Recall the calculus identity $\int_a^b f'(x)dx = f(b) - f(a)$, where $f'(x) = \frac{df}{dx}$.

Capacitor: $Q = CV$

$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

this problem →
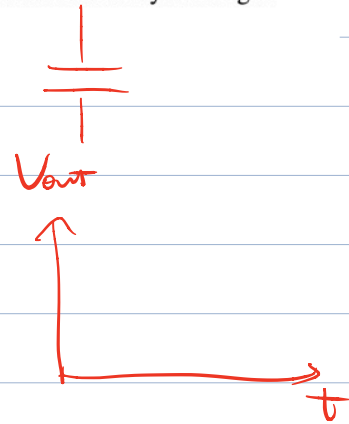
$$\frac{dV_{\text{out}}}{dt} = \frac{I_s}{C}$$



$$V_{\text{out}}(t) = V_0 + \left(\frac{I_s}{C}\right)t$$