

# EECS 16B D7S 2B Grayne

## 1. RC Circuits

In this problem, we will be using differential equations to find the voltage across a capacitor over time in an RC circuit. We set up our problem by first defining four functions over time:  $I(t)$  is the current at time  $t$ ,  $V(t)$  is the voltage across the circuit at time  $t$ ,  $V_R(t)$  is the voltage across the resistor at time  $t$ , and  $V_C(t)$  is the voltage across the capacitor at time  $t$ .

Recall from 16A that the voltage across a resistor is defined as  $V_R = RI_R$  where  $I_R$  is the current across the resistor. Also, recall that the voltage across a capacitor is defined as  $V_C = \frac{Q}{C}$  where  $Q$  is the charge across the capacitor.

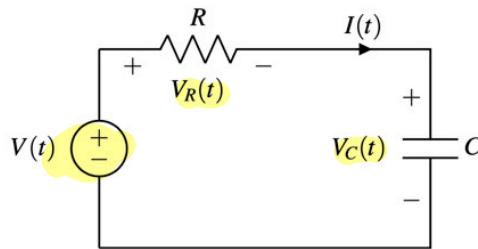


Figure 1: Example Circuit

- (a) First, find an equation that relates the current across the capacitor  $I(t)$  with the voltage across the capacitor  $V_C(t)$ .

$$Q(t) = C V_C(t)$$

$$V_C(t) = \frac{Q(t)}{C}$$

$$\frac{dV_C(t)}{dt} = \frac{1}{C} \frac{dQ(t)}{dt}$$

$$\rightarrow \frac{d}{dt} V_C(t) = \frac{1}{C} I(t)$$

- (b) Write a system of equations that relates the functions  $I(t)$ ,  $V_C(t)$ , and  $V(t)$ .

$$\text{From KVL, } V(t) - V_R(t) - V_C(t) = 0$$

$$V(t) - I(t)R - V_C(t) = 0$$

$$\rightarrow RI(t) + V_C(t) = V(t)$$


- (c) So far, we have three unknown functions and only one equation, but we can remove  $I(t)$  from the equation using what we found in part (a). Rewrite the previous equation in part (b) in the form of a differential equation.

From a),

$$I(t) = \frac{dV_C(t)}{dt} C$$

$$R C \frac{dV_C(t)}{dt} + V_C(t) = V(t)$$

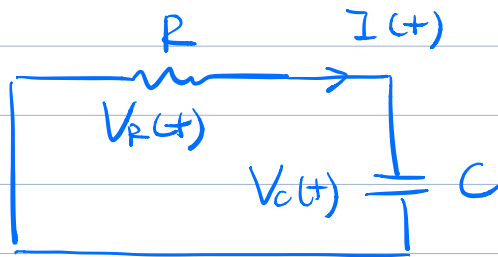- (d) Let's suppose that at  $t = 0$ , the capacitor is charged to a voltage  $V_{DD}$  ( $V_C(0) = V_{DD}$ ). Let's also assume that  $V(t) = 0$  for all  $t \geq 0$ . Solve the differential equation for  $V_C(t)$  for  $t \geq 0$ .



$$R C \frac{dV_C(t)}{dt} + V_C(t) = V(t)$$

$$\frac{dV_C(t)}{dt} = - \frac{1}{RC} V_C(t)$$

$$\frac{dV(t)}{dt} = aV(t)$$

$$\frac{d}{dt} (Ae^{bt})$$

Guess:  $V_C(t) = Ae^{bt}$  ←  $= Abe^{bt}$   
 $b = -\frac{1}{RC}$   $= b(Ae^{bt})$


Now solve A using initial condition.

$$\rightarrow V_C(0) = V_{DD}$$

$$V_C(0) = A e^{b \cdot 0} = A = V_{DD}$$

$$V_C(t) = V_{DD} e^{-\frac{t}{RC}}$$

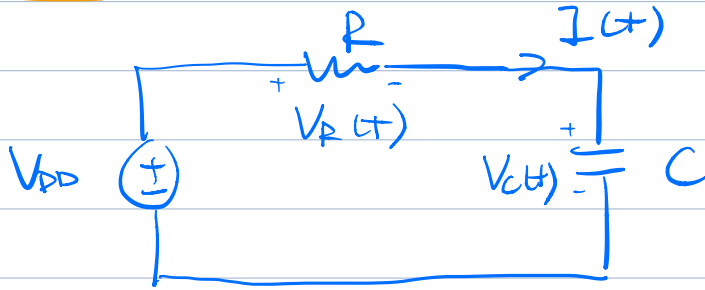(e) Now, let's suppose that we start with an uncharged capacitor  $V_C(0) = 0$ . We apply some constant voltage  $V(t) = V_{DD}$  across the circuit. Solve the differential equation for  $V_C(t)$  for  $t \geq 0$ .



$$\rightarrow RC \frac{dV_C(t)}{dt} + V_C(t) = V_{DD}$$

$$\frac{dV_C(t)}{dt} = \frac{V_{DD} - V_C(t)}{RC}$$

$$= -\frac{1}{RC} (V_C(t) - V_{DD})$$

$$\frac{dX(t)}{dt} = aX(t) + b$$

$$= a \left( X(t) + \frac{b}{a} \right)$$

$$V_C(t) = V_{DD} + \tilde{V}_C(t)$$

$$\frac{d}{dt} (V_C(t) - V_{DD}) = \frac{d}{dt} V_C(t) - \frac{d}{dt} V_{DD}$$

$$\frac{d}{dt} \tilde{V}_c(t) = \frac{d}{dt} V_c(t)$$

$$\rightarrow \frac{d\tilde{V}_c(t)}{dt} = -\frac{1}{RC} \tilde{V}_c(t)$$

$$\Rightarrow \tilde{V}_c(t) = B e^{-\frac{1}{RC}t}$$

Solve B.

$$\tilde{V}_c(0)$$

$$\text{I.C. } V_c(0) = 0$$

$$\tilde{V}_c(0) = 0 - V_{DD}$$

$$\tilde{V}_c(0) = -V_{DD}$$

$$\tilde{V}_c(0) = B e^0 = B = -V_{DD}$$

$$\tilde{V}_c(t) = -V_{DD} e^{-\frac{1}{RC}t}$$

$$V_c(t) = V_{DD} + \tilde{V}_c(t)$$
$$= V_{DD} (1 - e^{-\frac{1}{RC}t})$$