

EECS 16B

Review of 16A material

Topics:

* Eigenvalues / Eigenspaces ← 16 ←

• Voltage dividers ← 16

* Capacitors ← ~~40~~ 40

* Op-Amps / NFB. ← 40

* Least squares. ← 25-30.

Capacitors

$$V_c = \frac{1}{C} Q$$

$$Q = C V_c$$

Charge ↑ Capacitance. Voltage


$$I = \frac{dQ}{dt}$$

$$I = C \cdot \frac{dV}{dt}$$

Example 1:

$V_c(t)$, $V_c(T)$

Find $V_c(t)$ in terms of I_s, C .

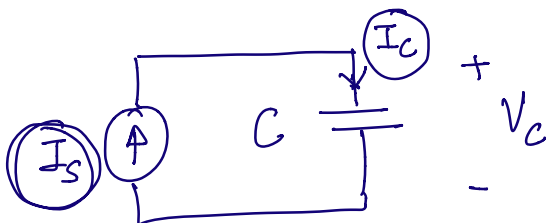


$$I_c(t) = C \cdot \frac{dV_c(t)}{dt}$$

$$I_c(t) = I_s$$


$$\int_0^T I_c(t) dt = \int_0^T I_s dt = \int_0^T C \cdot \frac{dV_c(t)}{dt} dt$$

$$I_s(T-0) = C \cdot [V_c(T) - V_c(0)]$$

$$V_c(T) = \frac{I_s \cdot T}{C} + V_c(0)$$

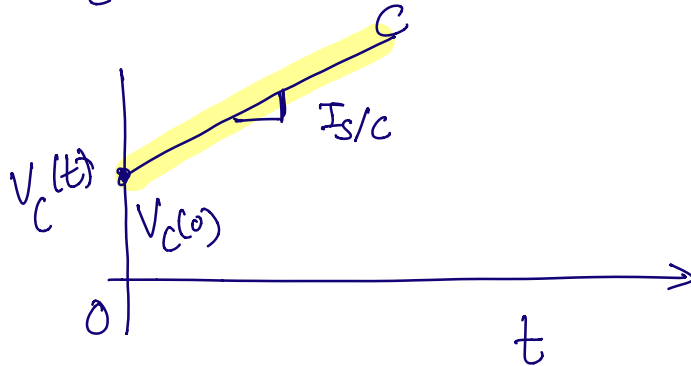

Example 2: Capacitors do not pass DC

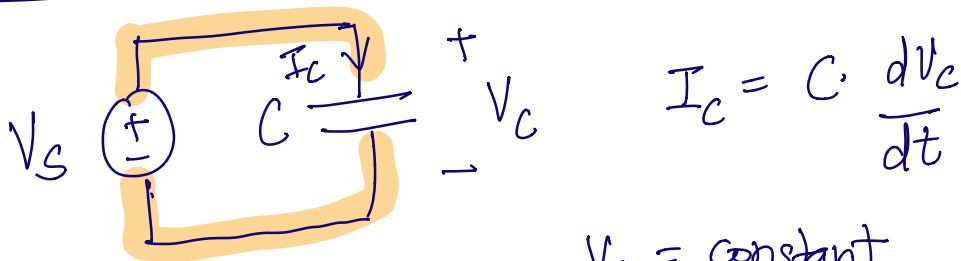


$$I_c = C \cdot \frac{dV_c}{dt}$$

$$\underline{V_c = \text{constant}}$$


$$I_c = C \cdot 0 = 0$$

$$\frac{dV_c}{dt} = 0$$

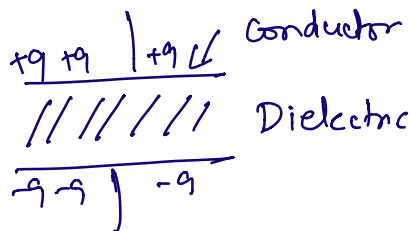

Example 3:

$$V_c(0) = V_0$$

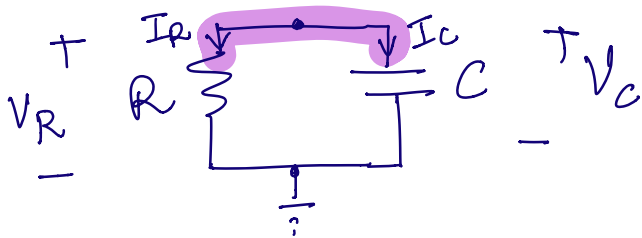

$$\text{KCL: } I_R + I_C = 0 \quad (1)$$

$$V_R = I_R \cdot R \quad \text{Ohme Law.}$$

$$I_C = C \cdot \frac{dV_c}{dt}$$

$$V_c = V_R$$

$$\frac{V_R}{R} + \frac{C dV_c}{dt} = 0.$$

$$\left(\begin{array}{l} f(x) = e^{ax} \\ \frac{df}{dx} = a \cdot e^{ax} \end{array} \right.$$


$$\frac{V_c}{R} + \frac{C \cdot dV_c}{dt} = 0.$$

$$\frac{dV_c(t)}{dt} + \frac{V_c(t)}{RC}$$

Differential equation.

$$V_c(t) = \underline{a} \cdot e^{\underline{bt}}$$

GUESS

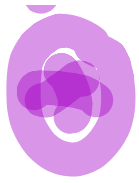

$$\frac{dV_c(t)}{dt} = a \cdot b \cdot e^{bt}$$

$$\text{LHS } a \cdot b \cdot e^{bt} = \frac{-a \cdot e^{bt}}{RC} \text{ RHS}$$


$$b = -\frac{1}{RC} \checkmark$$

$$V_c(0) = a \cdot e^{b \cdot 0} = a \cdot 1 = a$$

$$V_c(0) = V_0$$

$$\Rightarrow a = V_0$$

$$V_c(t) = V_0 \cdot e^{-t/RC}$$

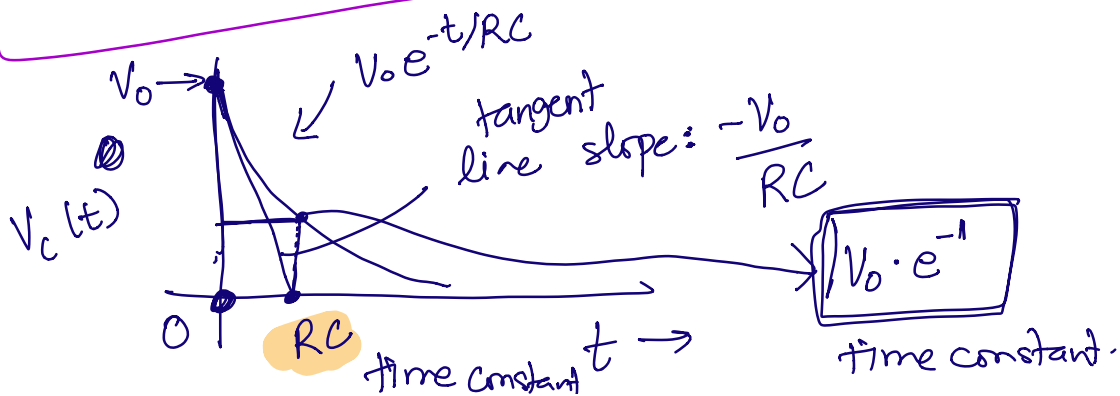

$$mx + c = y.$$

$$\frac{-V_0}{RC} \cdot x + c = y \quad \text{if } x=0, mx+c=V_0.$$


$$\Rightarrow c = V_0$$

$$\text{Eq}^n \text{ of tangent: } y = \frac{-V_0}{RC} \cdot x + V_0$$


$$\text{at } y=0, \Rightarrow x=RC$$

Op-Amps Operational Amplifier.

Negative Feedback.

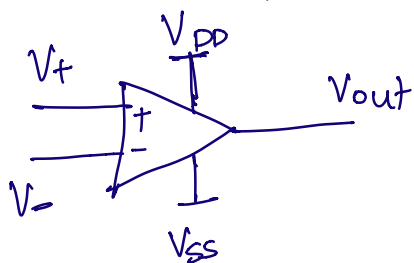

Innards of an Op-Amp.

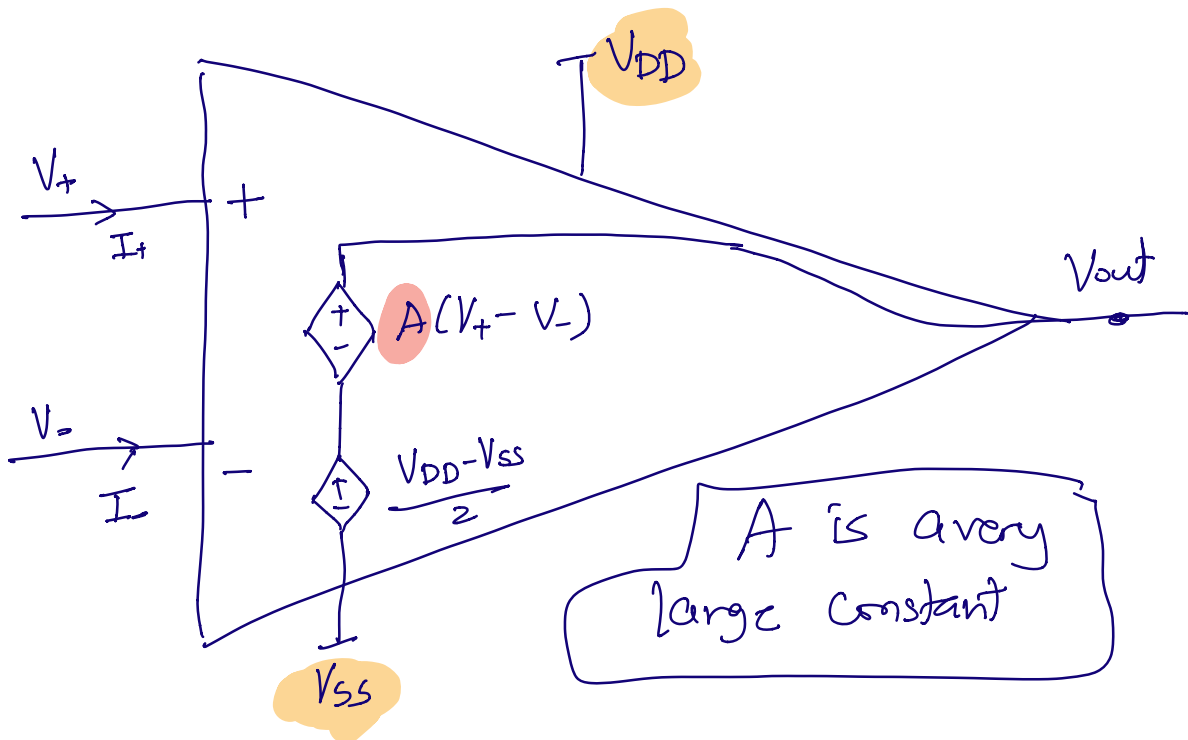

Golden Rule #1: $I_+ = I_- = 0$

$$V_{out} = V_{SS} + \frac{V_{DD} - V_{SS}}{2} + A(V_+ - V_-)$$


Subject to:

Max. value of $V_{out} = V_{DD}$

Min. value of $V_{out} = V_{SS}$.

$$V_{out} = \frac{V_{DD} + V_{SS}}{2} + A(V_+ - V_-)$$

Connect an op-amp in negative feedback.

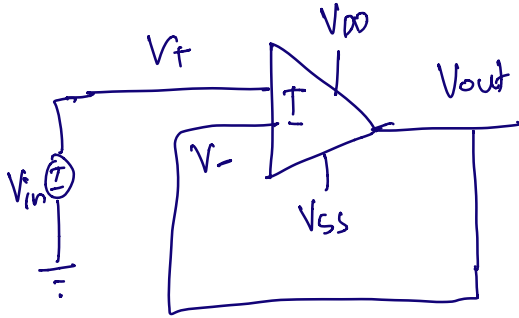

"Buffer circuit"

$$\underline{\underline{V_{out} = V_{in}}}$$

$$V_{out} = \frac{V_{DD} + V_{SS}}{2} + A(V_+ - V_-)$$

$$V_{out} = V_-$$

$$V_{in} = V_+$$

$$V_{out} = \frac{V_{DD} + V_{SS}}{2} + A(V_{in} - V_{out})$$

$$V_{out}(1 + A) = \frac{V_{DD} + V_{SS}}{2} + A \cdot V_{in}$$

$$V_{out} = \left(\frac{1}{1+A} \right) \cdot \frac{V_{DD} + V_{SS}}{2} + \frac{A}{1+A} \cdot V_{in}$$

$A \rightarrow \infty$.


$$V_{out} = 0 + 1 \cdot V_{in}.$$

$$V_{out} = V_{in}$$

$$V_+ = V_-$$

Golden Rule #2: For op-amp in
negative feedback: $V_+ = V_-$

Non-inverting amplifier

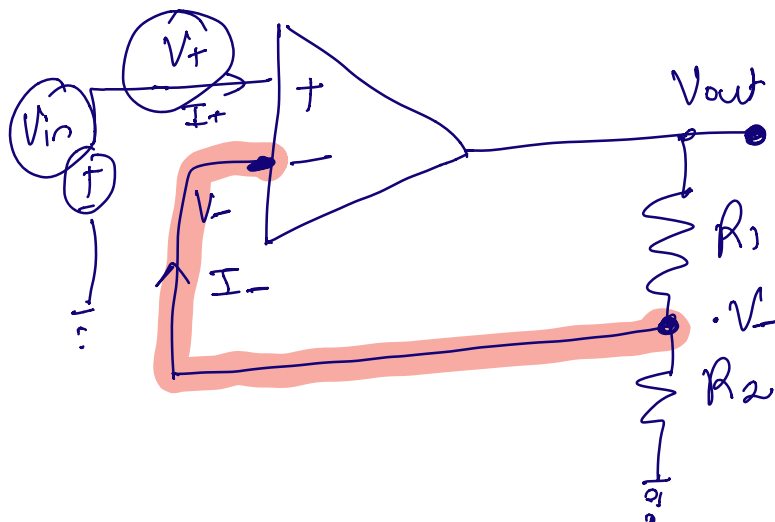


NFB:

$$\underline{V_+ = V_-}$$
$$I_+ = I_- = 0$$

$$V_- = \frac{R_2 \cdot V_{out}}{R_1 + R_2}$$

How is V_- connected to V_{out} ?

Voltage dividers

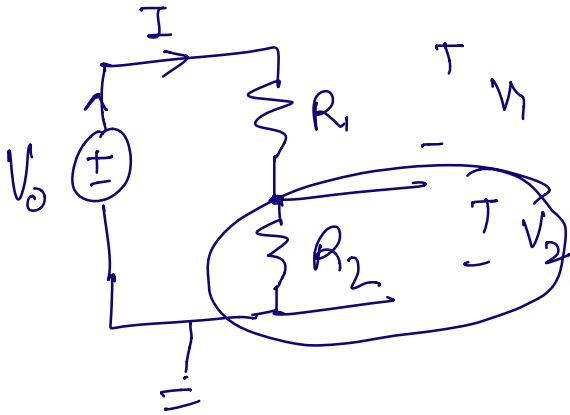

$$V_1 = IR_1$$

$$V_2 = IR_2$$

$$V_1 + V_2 = V_0$$

$$I(R_1 + R_2) = V_0$$

$$I = \frac{V_0}{R_1 + R_2}$$

$$V_2 = \frac{V_0 \cdot R_2}{R_1 + R_2}$$

$$V_+ = V_-$$

$$V_+ = V_{in}$$

$$V_- = \frac{R_2 \cdot V_{out}}{R_1 + R_2}$$




$$V_{in} = \frac{R_2 V_{out}}{R_1 + R_2}$$

$$\underline{\underline{V_{out}}} = \frac{R_1 + R_2}{R_2} \cdot V_{in} = \underbrace{\left(1 + \frac{R_1}{R_2}\right)}_{\text{"Gain"}} V_{in}$$

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2}$$

Back to RC circuits.

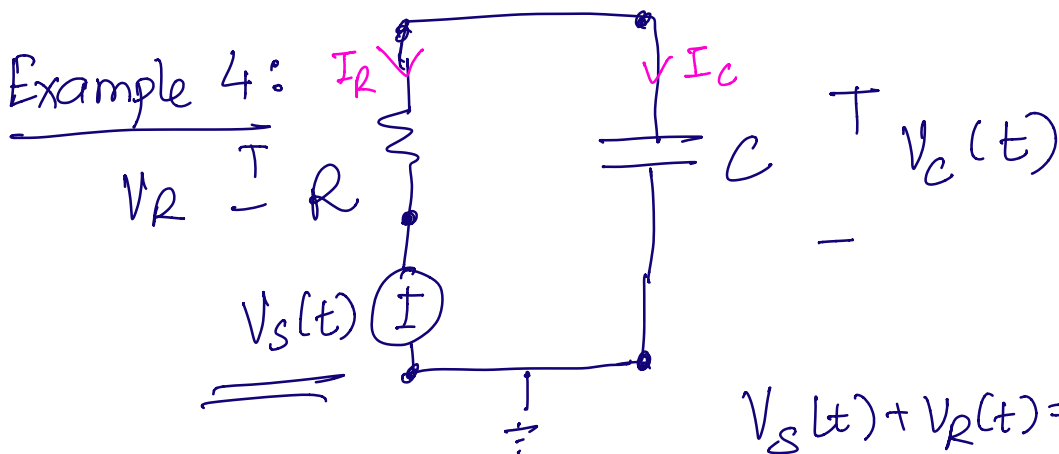

$$V_S(t) + V_R(t) = V_C(t)$$

KCL

$$I_R + I_C = 0$$

$$I_C(t) = C \cdot \frac{dV_C(t)}{dt}$$

KVL

$$V_R(t) = I_R(t) \cdot R$$

$$\frac{V_R(t)}{R} + C \cdot \frac{dV_C(t)}{dt} = 0$$

$$\Rightarrow \frac{V_C(t) - V_S(t)}{R} + \frac{C \cdot dV_C(t)}{dt} = 0$$

$$\Rightarrow \frac{C \cdot dV_C(t)}{dt} = -\frac{V_C(t)}{R} + \frac{V_S(t)}{R}$$

$$= \frac{dV_C(t)}{dt} = -\frac{V_C(t)}{RC} + \frac{V_S(t)}{RC}$$

$$\frac{d\alpha(t)}{dt} = \lambda \cdot \alpha(t) + u(t)$$

Eigenvalues / Eigenspaces.

$$A \in \mathbb{R}^{n \times n}$$

$$A \vec{x} = \lambda \vec{x}$$

\vec{x} = eigenvector

λ = eigenvalue.

Direction unchanged by the operation
of the matrix.

$$A \vec{x} = \lambda \vec{x}$$

$$\lambda \in \mathbb{R}$$

$$A \vec{x} - \lambda \vec{x} = 0$$

$$A = \begin{bmatrix} 1 & 2 \\ 4 & 3 \end{bmatrix}$$

$$\underbrace{(A - \lambda I)}_{\in \mathbb{R}^{n \times n}} \vec{x} = \vec{0} \quad \Rightarrow$$

$\vec{x} \in \text{Nullspace}(A - \lambda I)$

Find λ such that determinant

$$\det(A - \lambda I) = 0.$$

$$A = \begin{bmatrix} 1 & 2 \\ 4 & 3 \end{bmatrix}$$

$$A - \lambda I = \begin{bmatrix} 1-\lambda & 2 \\ 4 & 3-\lambda \end{bmatrix}$$

$$\det(A - \lambda I)$$

$$= (1-\lambda)(3-\lambda) - 8$$

$$= \lambda^2 - 4\lambda - 5$$

$$= (\lambda + 1)(\lambda - 5)$$

$\lambda_1 = -1, \lambda_2 = 5$ are our eigenvalues

$$\text{Null}(A - 5I)$$

$$(A - 5I) = \begin{bmatrix} -4 & 2 \\ 4 & -2 \end{bmatrix}$$

Null:

GE: $\left[\begin{array}{cc|c} -4 & 2 & 0 \\ 4 & -2 & 0 \end{array} \right]$

\downarrow

$\left[\begin{array}{cc|c} 1 & -1/2 & 0 \\ 0 & 0 & 0 \end{array} \right]$

\uparrow basic \uparrow free

$x_1 - \frac{1}{2}x_2 = 0$

$\vec{x} = \begin{bmatrix} 1/2x_2 \\ x_2 \end{bmatrix}$

eigenspace: $\text{span} \left\{ \begin{bmatrix} 1/2 \\ 1 \end{bmatrix} \right\}$

Least - Squares:


$A\vec{x} \approx \vec{b}$

$\left[\begin{array}{c} \\ \\ \end{array} \right] \cdot \left[\begin{array}{c} \\ \end{array} \right] = \left[\begin{array}{c} \\ \\ \end{array} \right]$

More eqⁿ
than
unknowns

$$\underline{A\vec{x}} \quad A = \begin{bmatrix} 1 & 2 \\ 3 & 4 \\ 5 & 6 \end{bmatrix}$$

Columnspace (A)

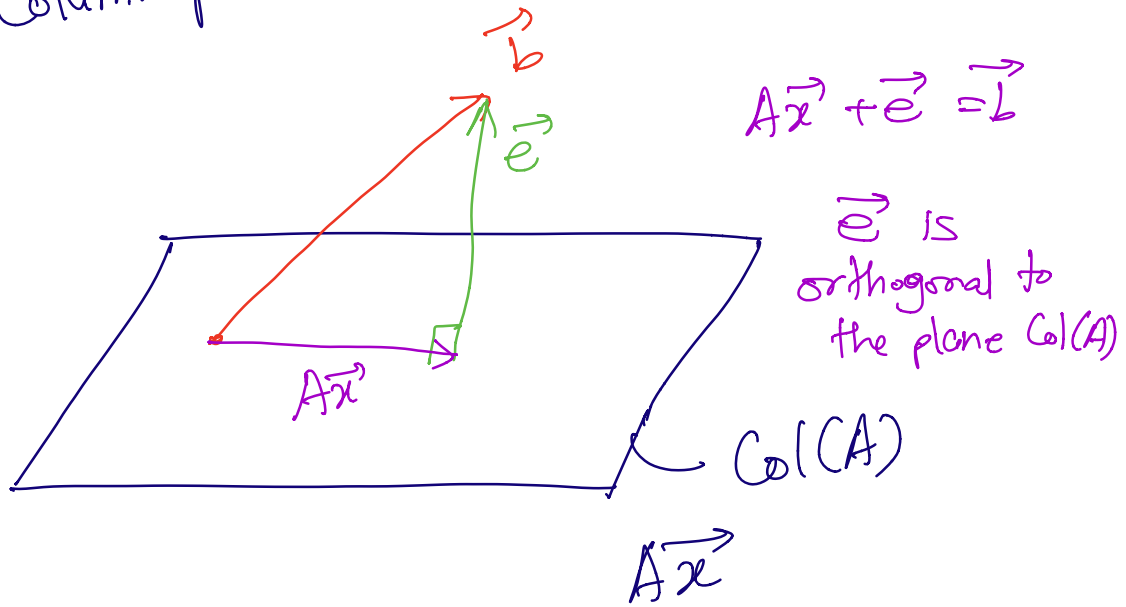

$\vec{e} \perp$ Columns of A

$$\text{Minimize}_{\vec{x}} \|A\vec{x} - \vec{b}\|^2 = \min_{\vec{x}} \|\vec{e}\|^2$$

$$A = \begin{bmatrix} \vec{a}_1 & \vec{a}_2 & \dots & \vec{a}_n \\ | & | & & | \\ 1 & 1 & & 1 \end{bmatrix} \Rightarrow$$

$$\vec{a}_i^T \cdot \vec{e} = 0$$

$$\left. \begin{array}{l} \langle \vec{q}_1, \vec{e} \rangle = 0 \\ \vdots \\ \langle \vec{q}_n, \vec{e} \rangle = 0 \end{array} \right\}$$

$$\underline{\underline{A^T \cdot \vec{e} = 0}}$$

$$A^T (\vec{b} - A\vec{x}) = 0$$

$$A^T \vec{b} = A^T A \vec{x}$$

$$\Rightarrow \vec{x} = (A^T A)^{-1} A^T \vec{b}$$

if invertible

$A^T A$
Square