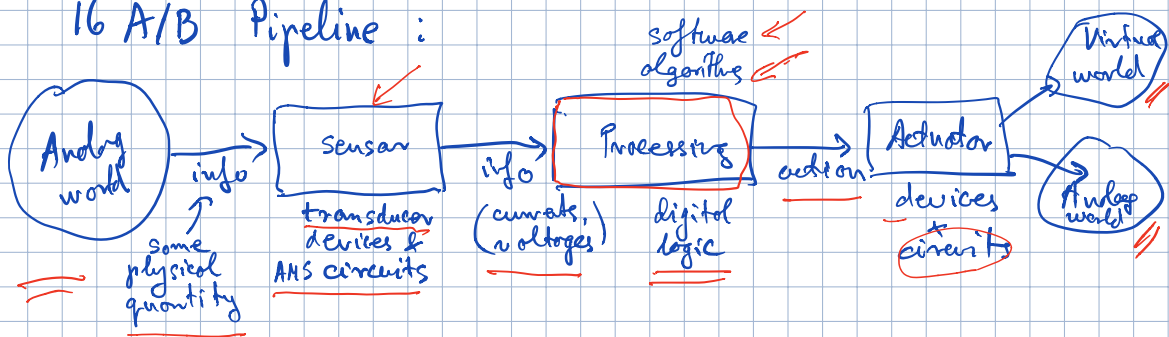


Lecture 2



- * Computing : Transistors & logic
- * R-C models
- * Solving R-C circuits

16 A/B Pipeline :




How do we implement computation ?


16A : Switch

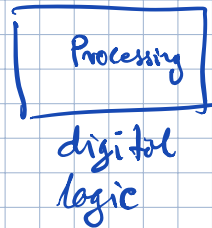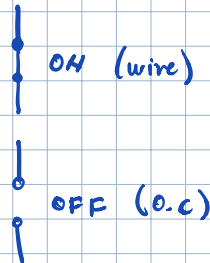

16B : Transistor

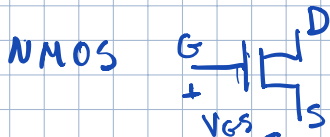


Simple model

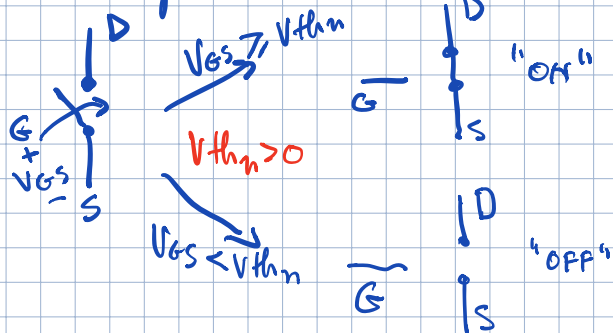

$V_{gs} < V_{thn}$

with





is

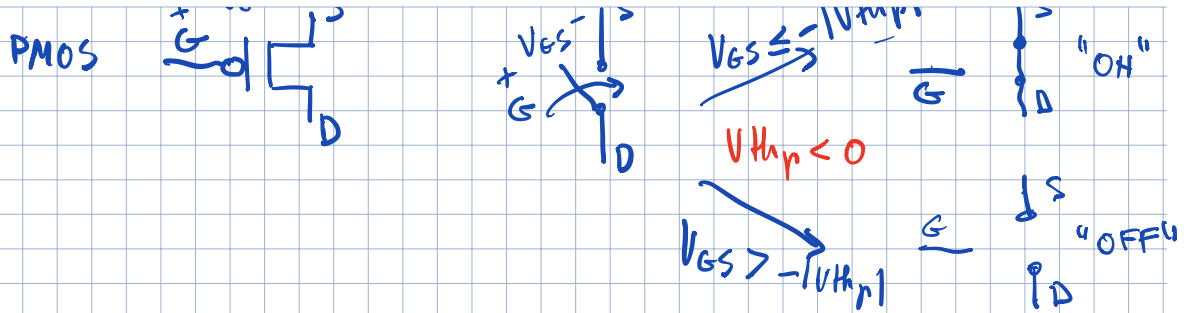

Simplest logic gate: an inverter "logic symbol"

$0 \leq V_{thn}, |V_{thp}| \leq V_{dd}$

Schematic:

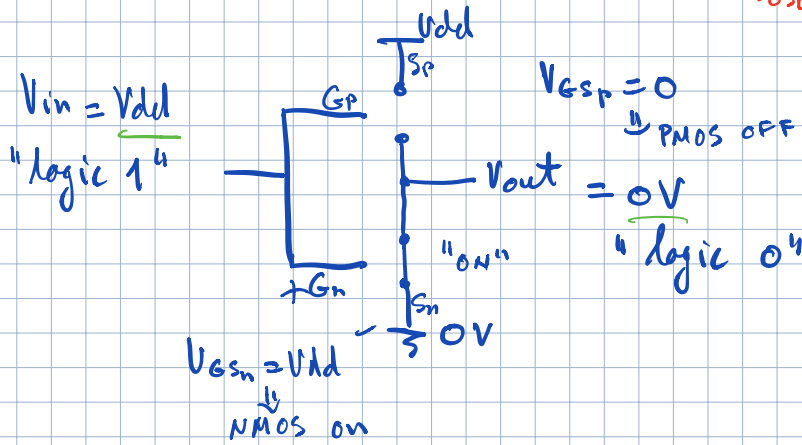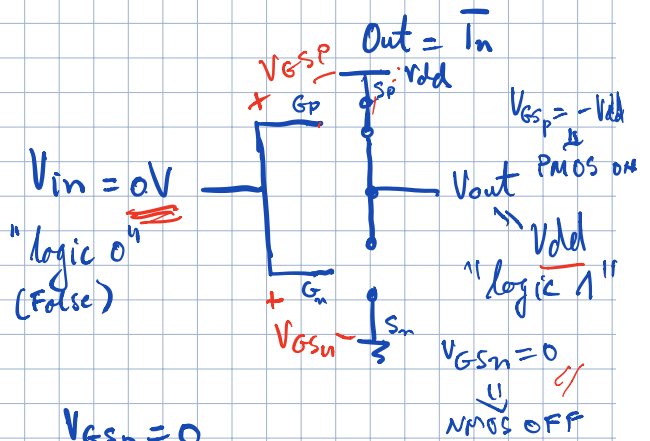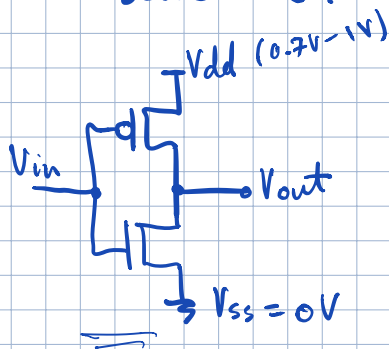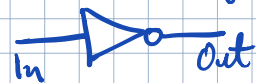

Truth table:

V_{in}	V_{out}
0V	Vdd
Vdd	0V


boolean: $Out = \bar{In}$

In	Out
0	1
1	0

Inverter!

Let's make a processor: Cascading logic

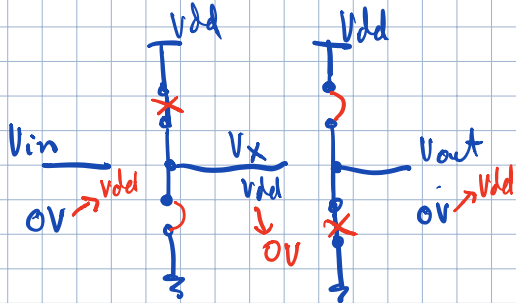Simple model: $In \rightarrow \text{NOT} \rightarrow x \rightarrow \text{NOT} \rightarrow Out = In$



State:

- ① $V_{in} = 0V \Rightarrow V_x = V_{dd} \Rightarrow V_{out} = 0V = V_{in}$
- ② $V_{in} = V_{dd} \Rightarrow V_x = 0V \Rightarrow V_{out} = V_{dd} = V_{in}$




It looks like this process is instantaneous.

Would make a super-fast processor!

Not real! 😞


Need to look at how a device is made.

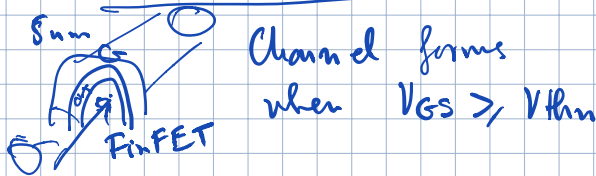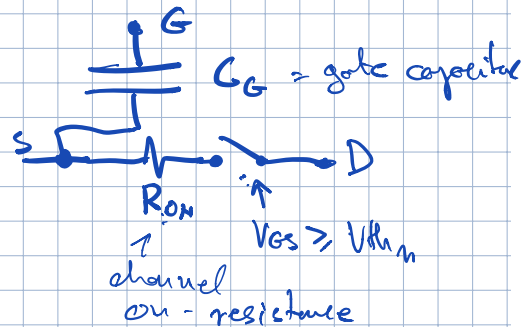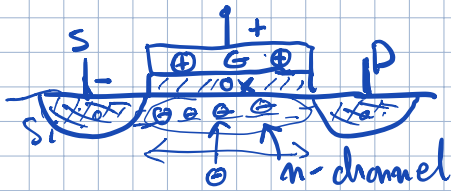NMOS (n-channel metal-oxide semiconductor)
field effect transistor n-MOSFET



Better model

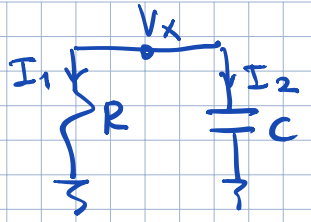To analyze this model need to understand RC circuits.



Elements:

$$I_2 = C \cdot \frac{dV_x}{dt}$$

$$V_x = I_1 \cdot R$$

$$I_1 + I_2 = 0 \quad \text{: KCL}$$

$$\frac{V_x}{R} + C \frac{dV_x}{dt} = 0$$

$t \geq 0$

$$\frac{dV_x}{dt} = -\frac{V_x}{RC}$$

: Differential equation


Guess: $V_x(t) = a \cdot e^{bt}$

$V_x(0) = a$
initial state

$$\frac{dV_x(t)}{dt} = a \cdot b \cdot e^{bt} = b \cdot V_x(t)$$

$$b = -\frac{1}{RC}$$
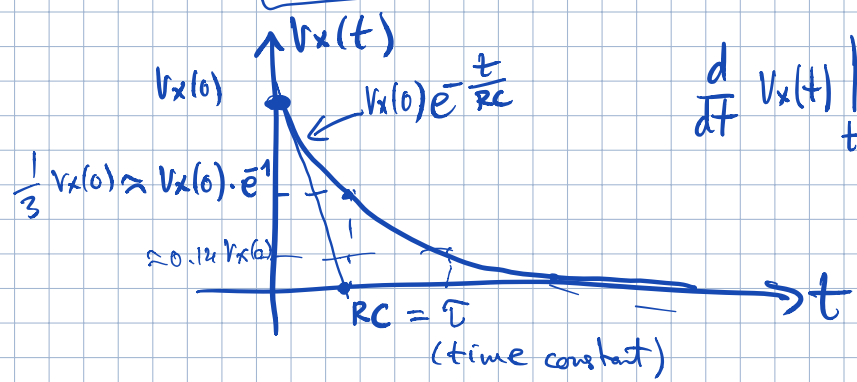
$$V_x(t) = V_x(0) \cdot e^{-\frac{t}{RC}}$$



check for uniqueness:

Suppose $y(t)$ which also solves. //

charac notation: $x(0) = X_0 \quad (1)$

$$\frac{d}{dt} x(t) = \lambda \cdot x(t) \quad (2) \quad \neq$$

Guessed and checked that $x_d(t) = \underline{X_0 \cdot e^{\lambda t}}$, $t \geq 0$ satisfies (1) & (2)

Need to show that $y(t) = x_d(t)$.

Either prove that $\frac{y(t)}{x_d(t)} = 1$ or $y(t) - x_d(t) = 0$

$$\frac{y(t)}{x_d(t)} = \frac{y(t)}{x_0 \cdot e^{\lambda t}}$$

$$(2) \frac{d}{dt} y(t) = \lambda y(t)$$

$$\frac{d}{dt} \left(\frac{y(t)}{x_d(t)} \right) = \frac{d}{dt} \left(\frac{y(t)}{x_0 e^{\lambda t}} \right) = \frac{1}{x_0} \frac{d}{dt} (y(t) \cdot e^{-\lambda t}) =$$

$$= \frac{1}{x_0} \cdot \left(\underbrace{\frac{d}{dt} y(t)}_{(2) \lambda \cdot y(t)} \cdot e^{-\lambda t} - y(t) \lambda \cdot e^{-\lambda t} \right) =$$




$$= \frac{1}{x_0} \cdot \left(\lambda \cdot y(t) \cdot e^{-\lambda t} - \lambda \cdot y(t) \cdot e^{-\lambda t} \right) = 0$$

$$\frac{y(t)}{x_d(t)} = \underline{a} \text{ (constant)}$$

$$y(0) = x_0$$

$$\frac{y(0)}{x_d(0)} = \frac{x_0}{x_0} = 1 = a \Rightarrow \frac{y(t)}{x_d(t)} = 1$$

unique

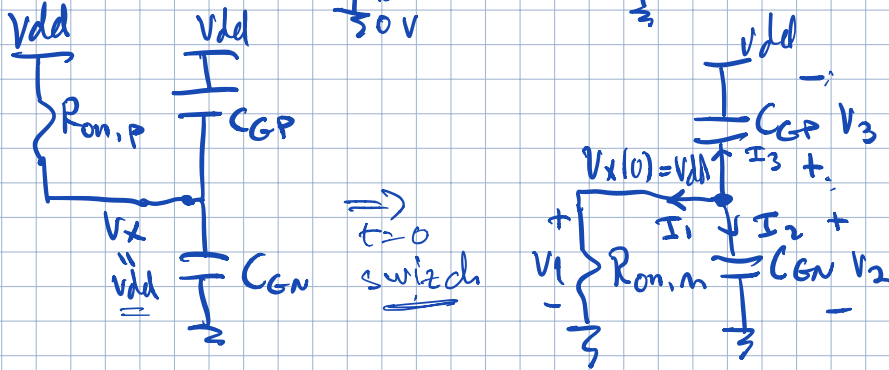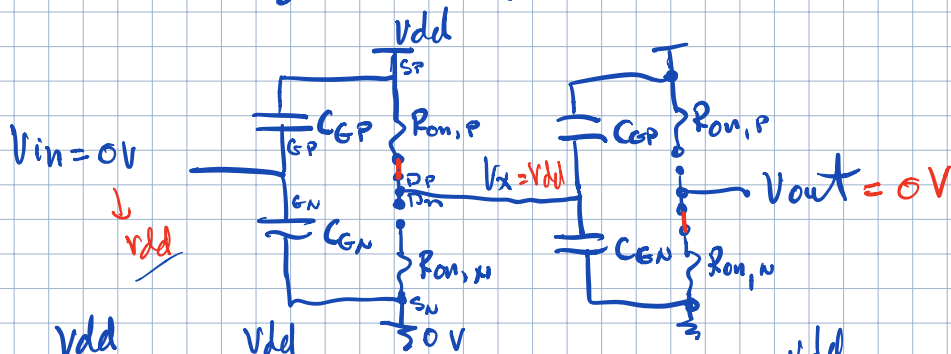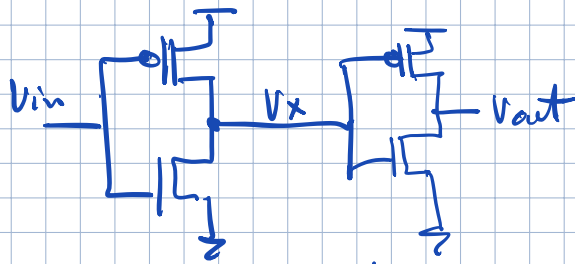

$$\text{KCL: } I_1 + I_2 + I_3 = 0$$

$$V_1 = V_x = I_1 \cdot R_{on,n}$$

$$\frac{V_x}{R_{on,n}} + C_{Gn} \cdot \frac{dV_x}{dt} + C_{Gp} \cdot \frac{dV_x}{dt} = 0$$

$$I_2 = C_{Gn} \cdot \frac{dV_2}{dt} = C_{Gn} \cdot \frac{dV_x}{dt}$$

$$\frac{V_x}{R_{on,n}} + (C_{Gn} + C_{Gp}) \cdot \frac{dV_x}{dt} = 0$$

$$I_3 = C_{Gp} \cdot \frac{dV_3}{dt}$$

$$= C_{Gp} \cdot \frac{d(V_x - V_{dd})}{dt}$$

$$\frac{dV_x}{dt} = - \frac{V_x}{R_{on,n} \cdot (C_{Gn} + C_{Gp})}$$

$$= C_{Gp} \cdot \frac{dV_x}{dt}$$

$$V_x(t) = V_x(0) \cdot e^{-\frac{t}{\tau}}, \quad \tau = R_{on,n} \cdot (C_{int} + C_x)$$

$$\boxed{V_x(t) = V_{dd} \cdot e^{-\frac{t}{\tau}}}$$