

Lecture 3


EECS 16B

* RC Transients


- nonhomogeneous diff eqns (with piecewise & const. input)

* Intro to filters

①
Lecture 2

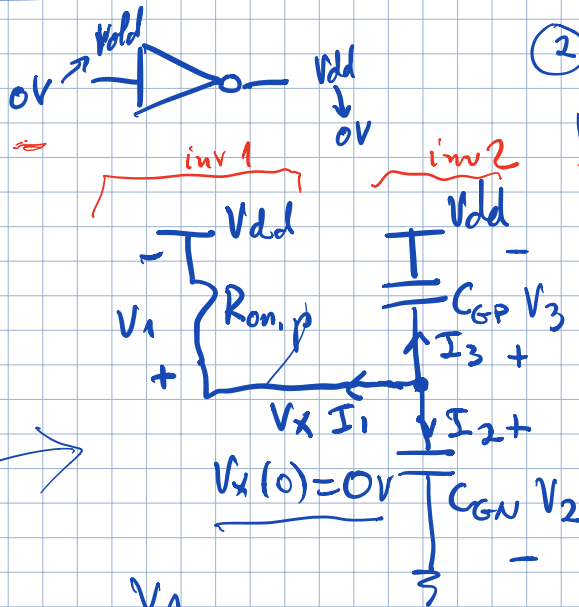

② Today:

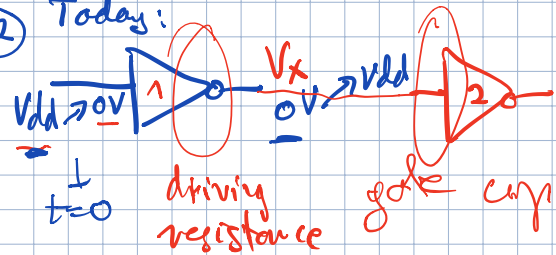

$$\text{KCL: } I_1 + I_2 + I_3 = 0$$

↓

$$\frac{V_x - V_{dd}}{R_{on,p}} + C_{gn} \frac{dV_x}{dt} + C_{gp} \frac{d(V_x - V_{dd})}{dt} = 0$$

$$\frac{V_x - V_{dd}}{R_{on,p}} + (C_{gn} + C_{gp}) \frac{dV_x}{dt} = 0 \quad (1)$$

$$\frac{dV_x}{dt} = - \frac{V_x}{R_{on,p} (C_{gn} + C_{gp})} + \frac{V_{dd}}{R_{on,p} (C_{gn} + C_{gp})}$$

homogeneous diff. eq. non-homogeneous.

Form:

$$\frac{d}{dt} x(t) = \lambda x(t) + u //$$

Non-homogeneous

$$\frac{d}{dt} x(t) = \lambda x(t) \quad (\text{homogeneous})$$

From (1)

$$\rightarrow \frac{V_x - V_{dd}}{R_{on,p}} + (C_{in} + C_{gp}) \cdot \frac{d}{dt} (V_x - V_{dd}) = 0$$

$$\hat{V}_x = V_x - V_{dd}$$

$$\frac{\hat{V}_x}{R_{on,p}} + (C_{in} + C_{gp}) \cdot \frac{d\hat{V}_x}{dt} = 0$$

$$\frac{d\hat{V}_x}{dt} = - \frac{\hat{V}_x}{R_{on,p} (C_{in} + C_{gp})} \quad (\text{homogeneous diff. eq. from lecture 2})$$

$$\frac{d\hat{V}_x}{dt} = - \frac{\hat{V}_x}{\tau}$$

$$\tau = R_{on,p} \cdot (C_{in} + C_{gp})$$


$$\hat{V}_x(t) = \hat{V}_x(0) \cdot e^{-\frac{t}{\tau}}$$

$$V_x(t) - V_{dd} = (V_x(0) - V_{dd}) \cdot e^{-\frac{t}{\tau}}$$


$$U_x(0) = 0V$$



$$U_x(t) - V_{dd} = -V_{dd} e^{-\frac{t}{\tau}}$$
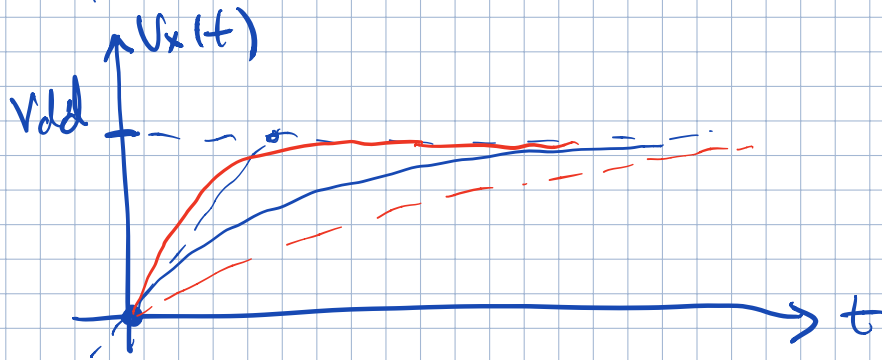
$$\boxed{U_x(t) = V_{dd} (1 - e^{-\frac{t}{\tau}})}, \quad t \geq 0$$



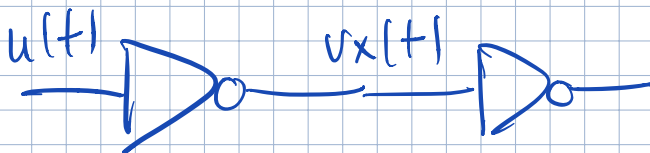
$$\begin{aligned} \frac{d}{dt} (U_x(t) - V_{dd}) &= \frac{d}{dt} (U_x(t)) - \frac{d}{dt} (V_{dd}) = \\ &= \frac{d}{dt} (U_x(t)) \end{aligned}$$



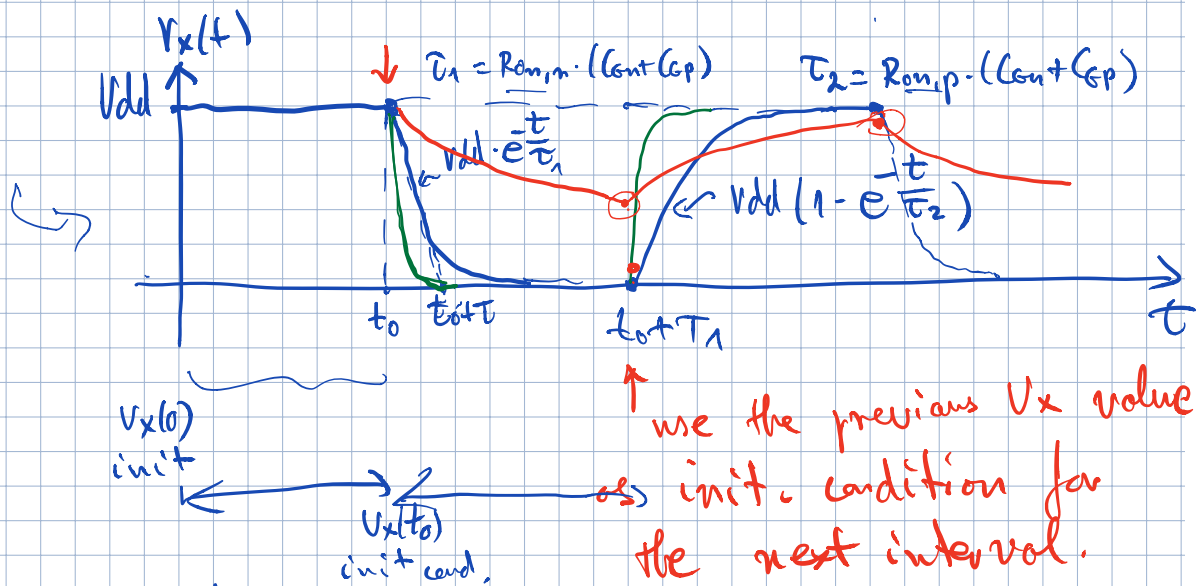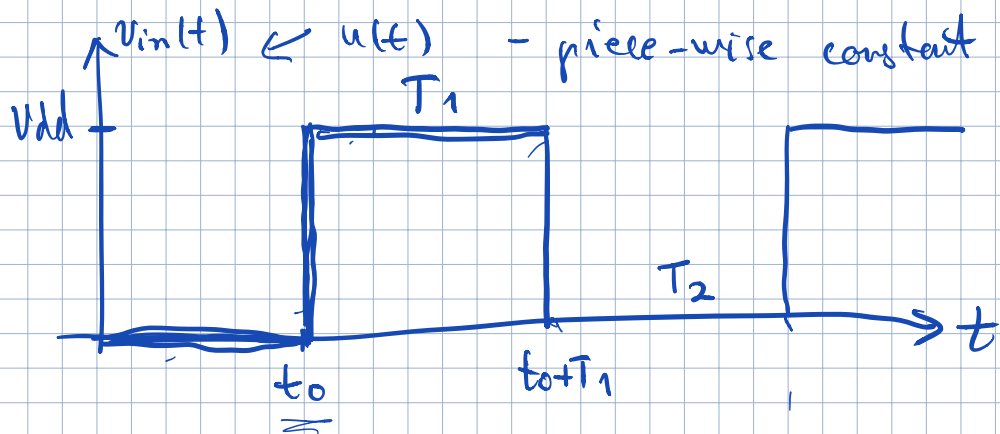


$$\frac{d}{dt} x(t) = \lambda x(t) + u(t) \leftarrow \text{piece wise constant}$$

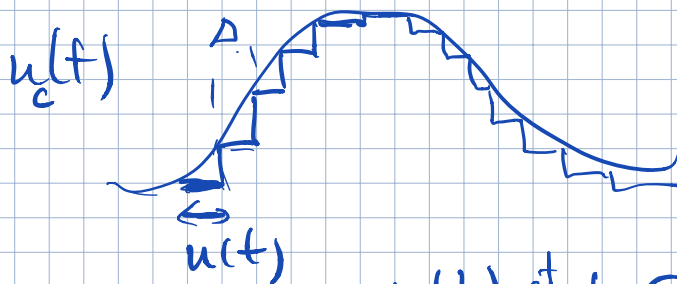then use the solution to solve for continuous $u(t)$ \rightarrow will use limits





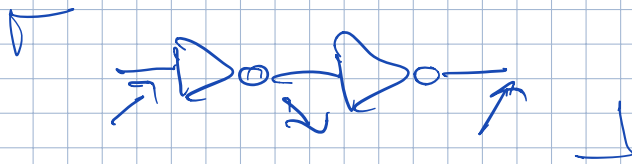
$$u(t) = c_i \cdot t \in [t_0, t_0 + \Delta]$$



$$\tau_1 < \tau_1 < \tau_1$$

16A/B Pipeline

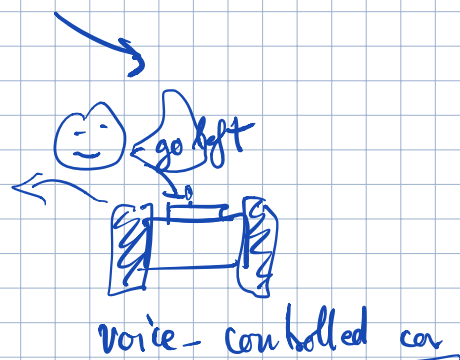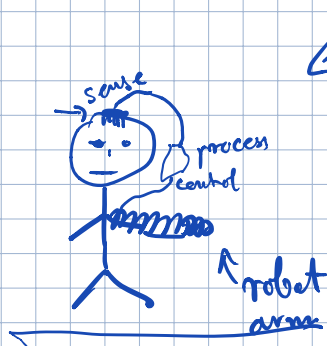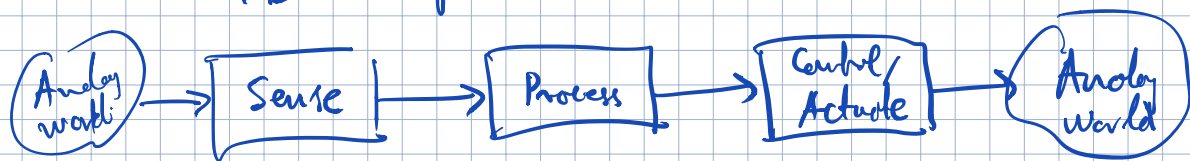


Module 1: Get signals from the brain (sensing)

Module 2: Controlling the arm (control/actuate)

Module 3: Figure out the intention from brain (processing)


Sensor electrodes pick up the

brain signal + other unwanted signals

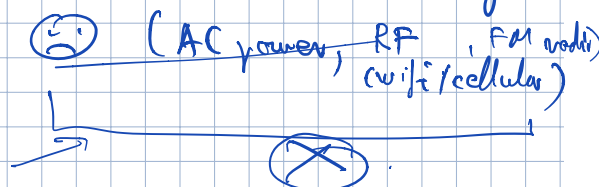

Goal: Filter the electrical signals
(with circuits)

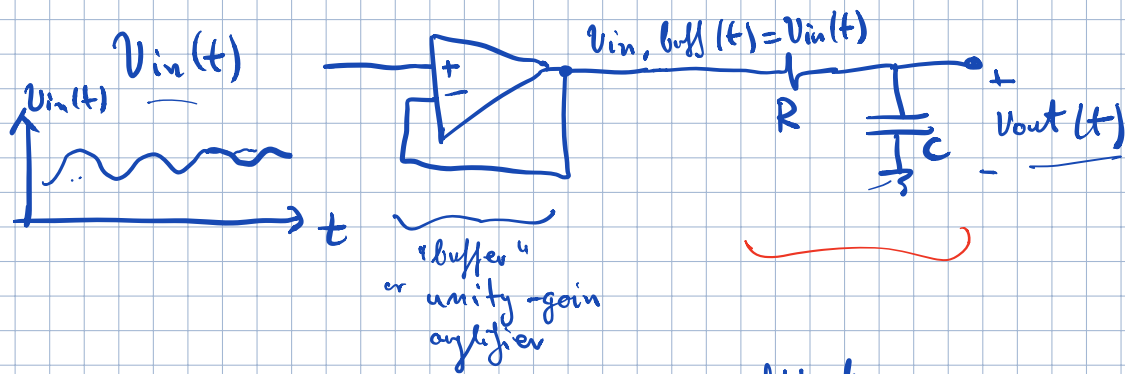How can a circuit process/filter the signal?



$$V_{in}(t) = V_{out}(t) + RC \frac{dV_{out}(t)}{dt}$$

$$\frac{dV_{out}(t)}{dt} = \left(-\frac{V_{out}(t)}{RC} \right) + \frac{V_{in}(t)}{RC}$$

$$\left[\frac{d}{dt} x(t) = \lambda x(t) + u(t) \right]$$

will see in discussion:

$$V_{out}(t) = V_{in}(0) e^{-\frac{t}{RC}} + \frac{1}{RC} \int_0^t V_{in}(\theta) e^{-\frac{1}{RC}(t-\theta)} d\theta$$

The circuit "computes" this

homogeneous solution

response to input in time

Try different examples for $V_{in}(t)$ to see what the circuit does.

Example 1: $u_{in}(t) = e^{st}$

$$(1) \quad \frac{d}{dt} x(t) = \lambda x + u(t) \quad \boxed{u(t) = e^{st}} \quad \begin{matrix} t \geq 0 \\ s \neq \lambda \end{matrix}$$

can solve: $x(t) = x_0 e^{\lambda t} + \int_0^t e^{s\theta} e^{\lambda(t-\theta)} d\theta \quad \leftarrow$

Guess: $x(t) = k e^{st}$

From (1) $k s e^{st} = \lambda k e^{st} + e^{st}$

$$k s = \lambda k + 1$$

$$\boxed{k = \frac{1}{s - \lambda}}$$

$$\Rightarrow x(t) = \frac{e^{st}}{s - \lambda}$$

$$x(t) = \frac{e^{st}}{s - \lambda} + k_2 \cdot e^{\lambda t}$$

homogenous
solution

(or solution
to no input)

Example 2:

$$u(t) = \cos(\omega t)$$

- mimics AC
power interference