


Lecture 5

EECS 16B

* RC filter review

* Solving systems of diff eqs.
(e.g. 2nd order diff. eqs with
2-capacitor RC filter)

Color organ led

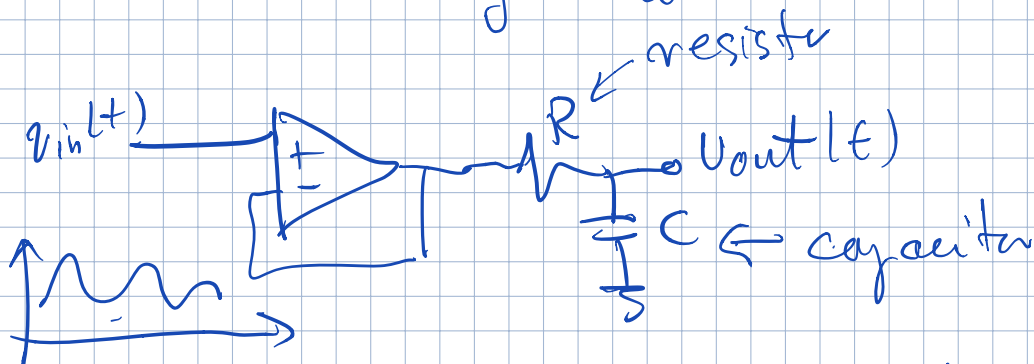

$$\frac{d}{dt} V_{out}(t) = -\frac{V_{out}(t)}{RC} + \frac{V_{in}(t)}{RC} = \tau$$

interested in $V_{out}(t)$ for $V_{in}(t) = V_{in} \cos(\omega t)$

guess: $V_{out}(t) = A \cdot \cos(\omega t + \theta)$


$$-A\omega \sin(\omega t + \theta) = -\frac{A}{RC} \cos(\omega t + \theta) + \frac{V_{in}}{RC} \cdot \cos(\omega t)$$

$$-A\omega RC \sin(\omega t + \theta) = -A \cos(\omega t + \theta) + V_{in} \cos(\omega t)$$

$$A \cos(\omega t + \theta) - A\omega RC \sin(\omega t + \theta) = V_{in} \cos(\omega t)$$

$$A \sqrt{1 + (\omega RC)^2} \left(\underbrace{\frac{1}{\sqrt{1 + (\omega RC)^2}}}_{\cos(\alpha)} \cos(\omega t + \theta) - \underbrace{\frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}}_{\sin(\alpha)} \sin(\omega t + \theta) \right)$$

$\tan(\alpha) = \frac{\omega RC}{1} = \omega RC$



$\cos(\alpha + \beta) = \cos(\alpha)\cos(\beta) - \sin(\alpha)\sin(\beta)$

$$A \sqrt{1 + (\omega RC)^2} \cdot \cos(\alpha + \omega t + \theta) =$$

$$\theta = -\alpha \quad V_{in} \cos(\omega t)$$

$$\theta = -\tan^{-1}(\omega RC)$$

$$A \sqrt{1 + (\omega RC)^2} = V_{in} \Rightarrow A = \frac{V_{in}}{\sqrt{1 + (\omega RC)^2}}$$

$$V_{out}(t) = \frac{V_{in}}{\sqrt{1 + (\omega RC)^2}} \cdot \cos(\omega t - \tan^{-1}(\omega RC))$$

$$V_{out}(t) = \frac{V_{in}}{\sqrt{1+(\omega RC)^2}} \cdot \cos(\omega t - \tan^{-1}(\omega RC))$$

$$\text{If } \omega \gg \frac{1}{RC}$$

$$V_{out}(t) \xrightarrow{V_{in}} 0$$

$$\text{If } \omega \ll \frac{1}{RC}$$

$$V_{out}(t) \approx V_{in} \cos(\omega t + \theta)$$


Attenuated signal has a decreased amplitude.

"RC filter" \Rightarrow "low-pass"

$$\omega \gg \frac{1}{RC} \Rightarrow \omega RC \gg 1$$

$$\omega \ll \frac{1}{RC} \Rightarrow \omega RC \ll 1$$

* Solving systems of diff. eqns.

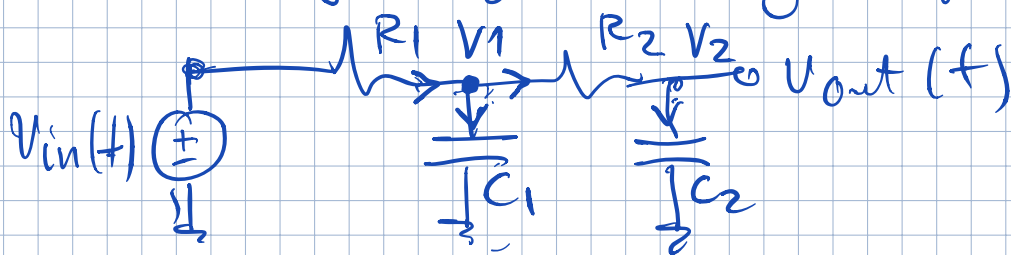

NVA:

$$\frac{V_{in} - V_1}{R_1} = C_1 \frac{dV_1}{dt} + \frac{V_1 - V_2}{R_2}$$

$$\frac{V_1 - V_2}{R_2} = C_2 \frac{dV_2}{dt}$$

$$\frac{dV_1}{dt} = -\left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1}\right) V_1 + \frac{V_2}{R_2 C_1} + \frac{V_{in}}{R_1 C_1}$$

$$\frac{dV_2}{dt} = \frac{1}{R_2 C_2} V_1 - \frac{1}{R_2 C_2} V_2$$

$$\frac{d}{dt} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -\left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1}\right) & \frac{1}{R_2 C_1} \\ \frac{1}{R_2 C_2} & -\frac{1}{R_2 C_2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} +$$

know how to solve:

$$\frac{d}{dt} x = \lambda x + u$$

$$\begin{bmatrix} \frac{1}{R_1 C_1} \\ 0 \end{bmatrix} V_{in}$$

$$R_1 = \frac{1}{3} \text{ M}\Omega, \quad R_2 = \frac{1}{2} \text{ M}\Omega, \quad C_1 = C_2 = 1 \mu\text{F}$$

$$\frac{d}{dt} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} 3 \\ 0 \end{bmatrix} v_{in}$$

How about "magic"?

Assumption:

$$v_{in} = 1 \text{ V } t < 0$$

or $t > 0$

$$v_1(0) = 1 \text{ V}$$

$$v_2(0) = 1 \text{ V}$$

Solving for $t > 0$

$$u_1 = v_2$$

$$u_2 = v_1 + 2v_2$$

$$\frac{d}{dt} u_1 = \frac{d}{dt} v_2 = 2v_1 - 2v_2 =$$

$$= 2u_2 - 4v_2 - 2v_2 =$$

$$= 2u_2 - 6v_2 = 2u_2 - 6u_1$$

$$\frac{d}{dt} u_2 = \frac{dv_1}{dt} + 2 \frac{dv_2}{dt} =$$

$$= -5v_1 + 2v_2 + 4v_1 - 4v_2$$

$$= -v_1 - 2v_2 = -u_2 \quad \text{Whoa!}$$

$$\frac{d}{dt} u_2 = -u_2 \quad \text{know how to solve!}$$

$$\frac{d}{dt} u_2 = -u_2 \Rightarrow u_2(t) = u_2(0) \cdot e^{-t} \quad t \geq 0$$

$$u_2(0) = v_1(0) + 2v_2(0) = 3 \text{ V}$$

$$\Rightarrow \boxed{u_2(t) = 3 \cdot e^{-t}} \quad t \geq 0 \quad \left(\begin{array}{l} \text{assuming} \\ v_{in}(t < 0) = 1 \text{ V} \end{array} \right)$$

$$\frac{d}{dt} u_1(t) = 2u_2 - 6u_1 \quad \text{"s}$$

$$\frac{d}{dt} u_1(t) = -6u_1 + 6 \cdot e^{-t}, \quad t \geq 0$$

Remember:

$$\frac{d}{dt} x(t) = \lambda x(t) + u(t)$$

where $u(t) = e^{st}, t \geq 0$

$$x(t) = k_2 e^{\lambda t} + \frac{e^{st}}{s - \lambda}$$

$$k_2 + \frac{1}{s - \lambda} = x(0)$$

$\lambda = -6$

$$u_1(t) = k_2 \cdot e^{-6t} + 6 \cdot \frac{e^{-t}}{-1 + 6}$$

$$u_1(t) = k_2 \cdot e^{-6t} + \frac{6}{5} e^{-t}$$

$$u_1(0) = k_2 + \frac{6}{5}$$

$$u_1(0) = v_2(0) = 1V \Rightarrow k_2 = -\frac{1}{5}$$

$$u_1(t) = -\frac{1}{5} e^{-6t} + \frac{6}{5} e^{-t}$$

have $u_1(t), u_2(t) \Rightarrow$ back solve
for $v_1(t), v_2(t)$

$$v_1(t) = u_2(t) - 2u_1(t)$$

$$= 3 \cdot e^{-t} - 2 \left(-\frac{1}{5} e^{-6t} + \frac{6}{5} e^{-t} \right)$$

$$v_1(t) = 3 \cdot e^{-t} + \frac{2}{5} e^{-6t} - \frac{12}{5} e^{-t}$$

$$v_1(t) = \frac{2}{5} e^{-6t} + \frac{3}{5} e^{-t}$$

$$v_2(t) = u_1(t) = -\frac{1}{5} e^{-6t} + \frac{6}{5} e^{-t}$$

$$\frac{d}{dt} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \underbrace{\begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix}}_A \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} 3 \\ 0 \end{bmatrix} v_{in}$$

$$\begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 2 \end{bmatrix}}_B \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Leftrightarrow \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \underbrace{\begin{bmatrix} -2 & 1 \\ 1 & 0 \end{bmatrix}}_{B^{-1}} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix}$$

$$\frac{d}{dt} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 2 \end{bmatrix}}_B \frac{d}{dt} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} =$$

$$= \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 2 \end{bmatrix}}_B \left(\underbrace{\begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix}}_A \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} 3 \\ 0 \end{bmatrix} v_{in} \right)$$

$$\frac{d}{dt} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 2 \end{bmatrix}}_B \left(\underbrace{\begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix}}_A \underbrace{\begin{bmatrix} -2 & 1 \\ 1 & 0 \end{bmatrix}}_{B^{-1}} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} + \begin{bmatrix} 3 \\ 0 \end{bmatrix} v_{in} \right)$$

$$\frac{d}{dt} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \underbrace{\begin{bmatrix} -6 & 2 \\ 0 & -1 \end{bmatrix}}_{BAB^{-1}} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 3 \end{bmatrix} v_{in}$$

BAB^{-1} is upper-triangular
 \Rightarrow so can read back
 we saw this in GE

Summary:


$$\frac{d}{dt} \vec{x}(t) = A \vec{x}(t) \quad \vec{x}(0)$$

Native \vec{x} coordinates:

"Nice" $\hat{\vec{x}}$ coordinates:

$$\vec{x}(t) = V \hat{\vec{x}}(t)$$

$$\hat{\vec{x}}(t) = V^{-1} \vec{x}(t)$$

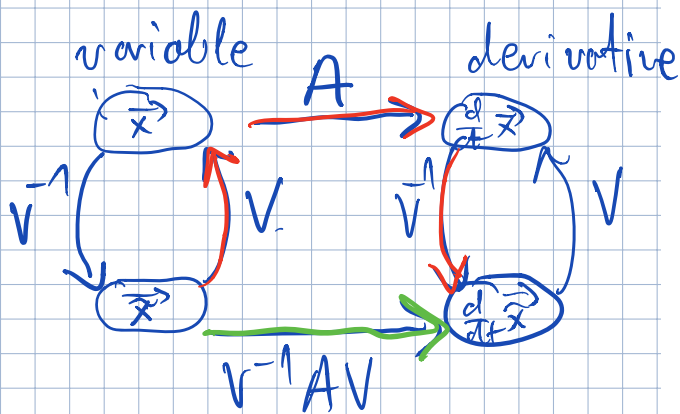

$$\frac{d}{dt} \vec{x} = \frac{d}{dt} V^{-1} \vec{x}(t) = V^{-1} \frac{d}{dt} \vec{x}(t)$$

$$= V^{-1} A \vec{x}(t) = V^{-1} A V \hat{\vec{x}}(t)$$

want this matrix
to be "nice"

upper-triangular or even
better - diagonal.