

Lecture 9

EECS16B

- * Phasor circuit analysis
- * Filter examples
- * Transfer functions

Phasor analysis steps:

1) Write sources as exponentials:

$$v_s(t) = \hat{V}_s e^{j\omega t} + \bar{\hat{V}}_s e^{-j\omega t} \quad : \quad \hat{V}_s \text{ \& \ } \hat{I}_s$$

$$i_s(t) = \hat{I}_s e^{j\omega t} + \bar{\hat{I}}_s e^{-j\omega t} \quad \text{are source phasors}$$

2) Transform the circuit to the phasor domain: s-impedances to impedances

$$Z_R = R, \quad Z_C = \frac{1}{j\omega C}, \quad Z_L = j\omega L \quad (s = j\omega)$$

3) Cast the branch & element equations in phasor domain:

$$\text{KVL: } \sum_i \hat{V}_i = 0 \quad \text{KCL: } \sum_i \hat{I}_i = 0$$

i around the loop
i into the node

$$\text{Ohm's law: } \hat{V}_i = Z_i \cdot \hat{I}_i \quad \text{NVA: } \sum \frac{\hat{V}_j - \hat{V}_k}{Z_{jk}} = 0$$

4) Solve for unknown variables:


$$\hat{V}_R, \hat{I}_R, \hat{V}_C, \hat{I}_C, \hat{V}_L, \hat{I}_L \quad (\text{in general } \hat{V}_\ell, \hat{I}_\ell)$$

5) Transform solutions (4) from phasor domain to time domain:

$$v(t) = \hat{V} e^{j\omega t} + \bar{\hat{V}} e^{-j\omega t}$$


$$i(t) = \hat{I} e^{j\omega t} + \bar{\hat{I}} e^{-j\omega t}$$

Example 1:

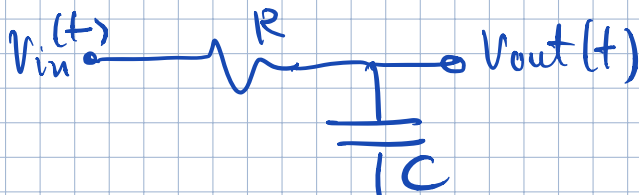

$$v_{in}(t) = V_{in} \cos(\omega t + \phi)$$

$$v_{out}(t) = ? \quad \neq V_{in}$$

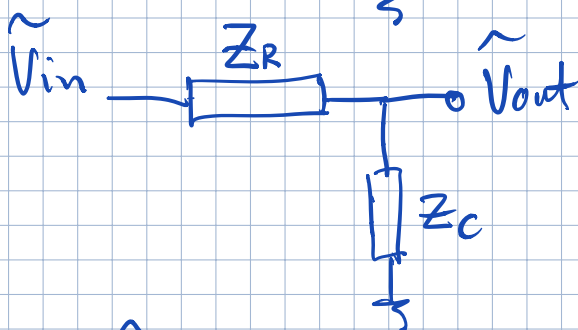

$$Z_R = R, \quad Z_C = \frac{1}{j\omega C}$$


$$v_{in}(t) = \hat{V}_{in} e^{j\omega t} + \bar{\hat{V}_{in}} e^{-j\omega t}$$

$$v_{out}(t) = \hat{V}_{out} e^{j\omega t} + \bar{\hat{V}_{out}} e^{-j\omega t}$$

$$\hat{V}_{out} = \frac{Z_C}{Z_C + Z_R} \hat{V}_{in} = \frac{1}{j\omega C + R} \hat{V}_{in}$$

$$\hat{V}_{out} = \frac{1}{1 + j\omega RC} \hat{V}_{in}$$
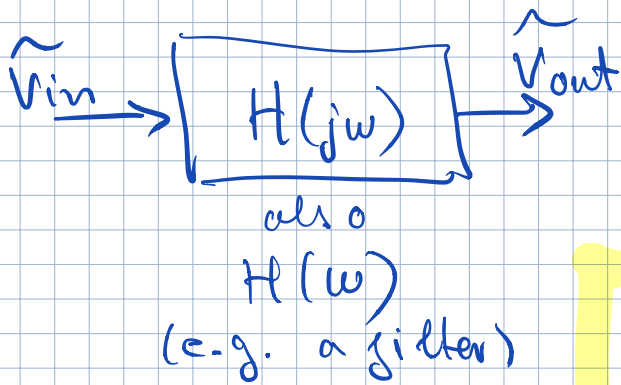
$$\hat{V}_{out}(\omega) = \frac{1}{1 + j\omega RC} \hat{V}_{in}(\omega)$$



$$H(j\omega) = \frac{\hat{V}_{out}}{\hat{V}_{in}}$$

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$H(j\omega) = \frac{1}{1 + j\omega RC} = \frac{1 - j\omega RC}{1 + (\omega RC)^2}$$

$$\text{Magnitude: } |H(j\omega)| = \frac{1}{|1 + j\omega RC|} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\hat{V}_{out} = H(j\omega) \cdot \hat{V}_{in}$$

$$\hat{V}_{in} = |\hat{V}_{in}| \cdot e^{j\phi_{in}}$$

$$\hat{V}_{out} = |\hat{V}_{out}| \cdot e^{j\phi_{out}}$$

$$|\hat{V}_{out}| \cdot e^{j\phi_{out}} = |H(j\omega)| \cdot e^{j\phi_{H(j\omega)}} \cdot |\hat{V}_{in}| \cdot e^{j\phi_{in}}$$

$$|\hat{V}_{out}| \cdot e^{j\phi_{out}} = |H(j\omega)| \cdot |\hat{V}_{in}| \cdot e^{j(\phi_{H(j\omega)} + \phi_{in})}$$

$$|\hat{V}_{out}| = |H(j\omega)| \cdot |\hat{V}_{in}|$$

$$\phi_{out} = \phi_{H(j\omega)} + \phi_{in}$$

$$\omega \cdot t_d = \phi_{H(j\omega)}$$

$$t_d = \frac{\phi_{H(j\omega)}}{\omega}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1+(\omega RC)^2}} \quad \begin{array}{l} \rightarrow 1 \text{ as } \omega \rightarrow 0 \\ \rightarrow 0 \text{ as } \omega \rightarrow \infty \\ \text{as } \omega \gg \frac{1}{RC} \end{array}$$

i.e. this is a low-pass filter (first-order)

$$V_{in}(t) = \tilde{V}_{in} e^{j\omega t} + \tilde{V}_{in} e^{-j\omega t} = 2|\tilde{V}_{in}| \cos(\omega t + \phi_{\tilde{V}_{in}})$$

$$V_{out}(t) = \tilde{V}_{out} e^{j\omega t} + \tilde{V}_{out} e^{-j\omega t} = 2|\tilde{V}_{out}| \cos(\omega t + \phi_{\tilde{V}_{out}})$$

$$\tilde{V}_{out} = H(j\omega) \tilde{V}_{in} = \underbrace{|H(j\omega)| \cdot |\tilde{V}_{in}|}_{|\tilde{V}_{out}|} \cdot e^{j(\phi_{H(j\omega)} + \phi_{\tilde{V}_{in}})} = \underbrace{\phi_{\tilde{V}_{out}}}$$

$$V_{out}(t) = |H(j\omega)| \cdot 2|\tilde{V}_{in}| \cdot \cos(\omega t + \phi_{\tilde{V}_{in}} + \phi_{H(j\omega)})$$

Recall: $V_{in}(t) = V_{in} \cos(\omega t) \Rightarrow 2|\tilde{V}_{in}| = V_{in}$
 $\phi_{\tilde{V}_{in}} = 0$

$$= V_{in} \left(\frac{e^{j\omega t} + e^{-j\omega t}}{2} \right) = \underbrace{\frac{V_{in}}{2}}_{|\tilde{V}_{in}|} e^{j\omega t} + \underbrace{\frac{V_{in}}{2}}_{|\tilde{V}_{in}|} e^{-j\omega t}$$

$$V_{out}(t) = |H(j\omega)| \cdot V_{in} \cdot \cos(\omega t + \phi_{H(j\omega)})$$

RC filter:

$$\frac{1}{\sqrt{1+(\omega RC)^2}}$$

$$-\tan^{-1}(\omega RC)$$



with some as derived with diff. equations.

Remember:

$$\hat{V} = a + jb$$

$$|\hat{V}| = \sqrt{a^2 + b^2}$$
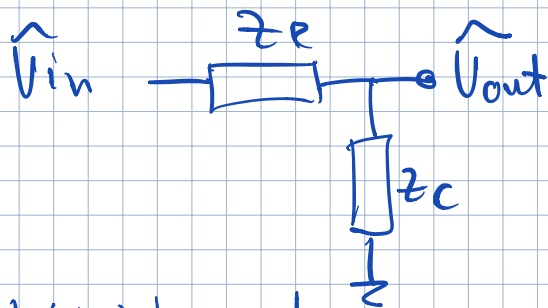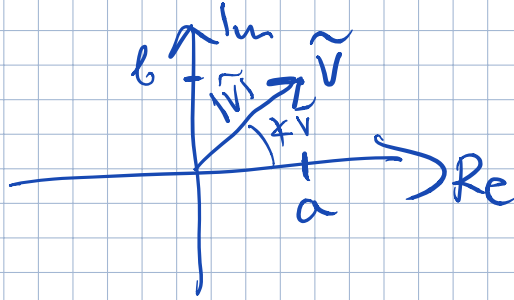
$$\angle \hat{V} = \tan^{-1}\left(\frac{b}{a}\right) = \text{atan2}(b, a)$$



$$H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{z_C}{z_C + z_R} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\frac{\omega}{\omega_0}}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}}$$

where $\omega_0 = \frac{1}{RC}$

$$\angle H(j\omega) = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

call ω_0 - a "cut-off" frequency

ω	$H(j\omega)$	$ H(j\omega) $	$\angle H(j\omega)$
$\omega \ll \omega_0$	≈ 1	1	$\approx 0^\circ$
$0.1\omega_0$	$\frac{1}{1 + j0.1}$	0.995	-6°
ω_0	$\frac{1}{1 + j}$	$\frac{1}{\sqrt{2}} = 0.71$	-45°
$10\omega_0$	$\frac{1}{1 + j10}$	0.1	-84°
$\omega \gg \omega_0$	$-j\frac{\omega_0}{\omega}$	$\frac{\omega_0}{\omega}$	-90°

