
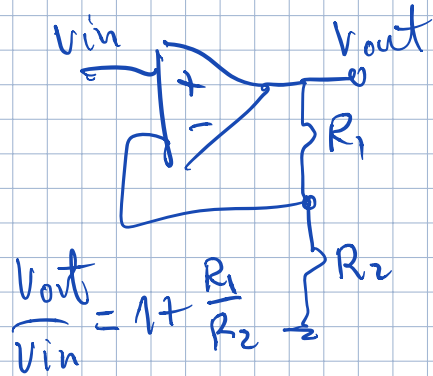





Lecture 10

EECS 16B

- * Cascading ckt blocks transfer function
- * Filter design example

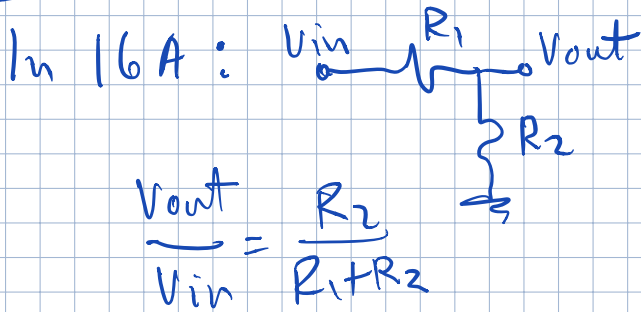

In 16B:

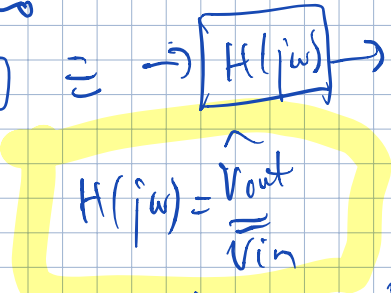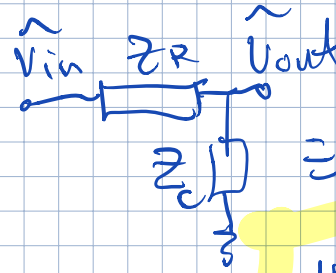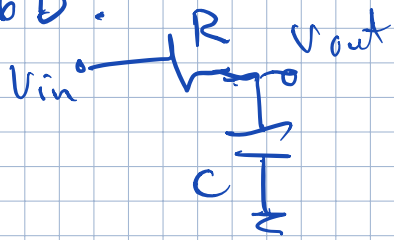


How do we cascade these circuits?

Circuit blocks should not

"load" each other in order to preserve the transfer function.
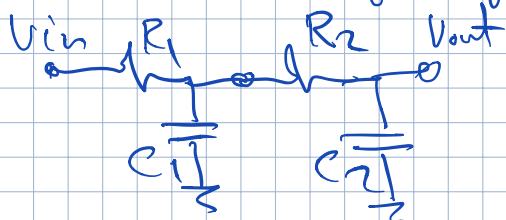
$$= \frac{1}{1 + j\frac{\omega}{\omega_0}} \quad \omega_0 = \frac{1}{RC}$$



$$H(j\omega) = H_1(j\omega) H_{buf}(j\omega) H_2(j\omega)$$

Ex 1

$$H_1(j\omega) = \frac{\widehat{V}_{out1}}{\widehat{V}_{in1}} ; H_{buf}(j\omega) = \frac{\widehat{V}_{in2}}{\widehat{V}_{out1}} ; H_2(j\omega) = \frac{\widehat{V}_{out2}}{\widehat{V}_{in2}}$$

$$H(j\omega) = \frac{\widehat{V}_{out2}}{\widehat{V}_{in1}} = \underbrace{\frac{\widehat{V}_{out2}}{\widehat{V}_{in2}}}_{H_2(j\omega)} \cdot \underbrace{\frac{\widehat{V}_{in2}}{\widehat{V}_{out1}}}_{H_{buf}(j\omega)} \cdot \underbrace{\frac{\widehat{V}_{out1}}{\widehat{V}_{in1}}}_{H_1(j\omega)}$$

$$H(j\omega) = H_2(j\omega) \cdot H_{buf}(j\omega) \cdot H_1(j\omega)$$

For Ex 1:


$$H_1(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_{01}}} ; H_{buf}(j\omega) = 1$$

$$H_2(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_{02}}} \quad \omega_{01} = \frac{1}{R_1 C_1}$$


$$\omega_{02} = \frac{1}{R_2 C_2}$$

$$H(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_{01}}} \cdot 1 \cdot \frac{1}{1 + j\frac{\omega}{\omega_{02}}}$$

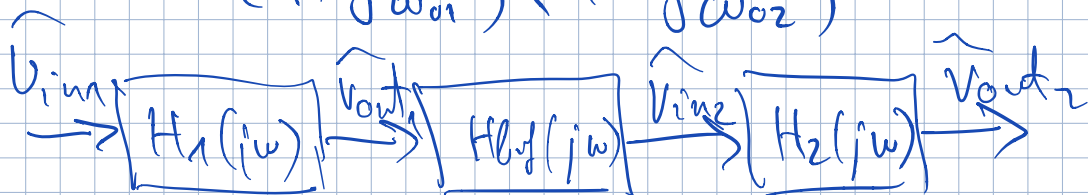
$$= \frac{1}{(1 + j\frac{\omega}{\omega_{01}})(1 + j\frac{\omega}{\omega_{02}})}$$



As operators $H(j\omega)$

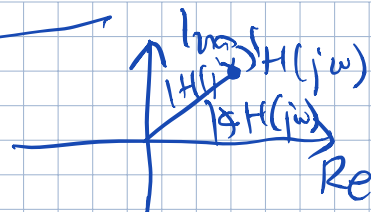

In general:

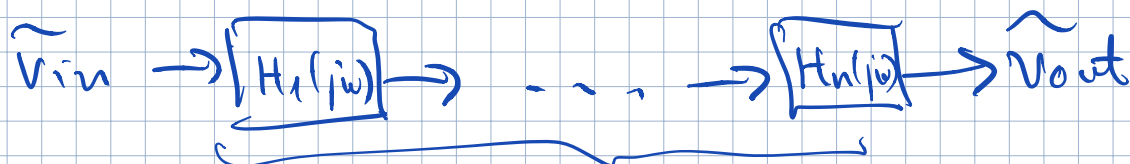

$$H(j\omega) \quad H_k(j\omega) = |H_k(j\omega)| \cdot e^{j\phi_k(j\omega)}$$

$$\frac{\tilde{v}_{out}}{\tilde{v}_{in}} = H(j\omega) = H_1(j\omega) \cdot \dots \cdot H_n(j\omega)$$

$$= \underbrace{|H_1(j\omega)| \cdot \dots \cdot |H_n(j\omega)|}_{|H(j\omega)|} \cdot e^{j(\phi_1(j\omega) + \dots + \phi_n(j\omega))}$$
$$\quad \quad \quad \phi H(j\omega)$$

Time-domain:

$$v_{out}(t) = |H(j\omega)| \cdot 2|\tilde{v}_{in}| \cos(\omega t + \phi_{\tilde{v}_{in}} + \phi H(j\omega))$$

for $v_{in}(t) = v_{in} \cos(\omega t + \phi)$

$$v_{out}(t) = |H(j\omega)| \cdot v_{in} \cos(\omega t + \phi + \phi H(j\omega))$$


Trick:

$$v_{in}(t) = v_{in} \cos(\omega t + \phi) =$$
$$= v_{in} \left(\frac{e^{j(\omega t + \phi)}}{2} + \frac{e^{-j(\omega t + \phi)}}{2} \right) =$$

$$= \underbrace{\frac{v_{in} e^{j\phi}}{2}}_{\hat{v}_{in}} \cdot e^{j\omega t} + \underbrace{\frac{v_{in} e^{-j\phi}}{2}}_{\hat{v}_{in}} \cdot e^{-j\omega t}$$

$$= \hat{v}_{in} e^{j\omega t} + \hat{v}_{in} e^{-j\omega t}$$

Design example:

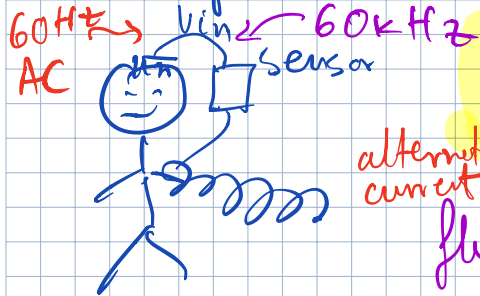

signal: 600 Hz 1 mV

alternating current AC: 60 Hz 10 mV

fluorescent light: 60 kHz 20 mV


Want to attenuate AC and fluorescent by 100x.

$$v_{in}(t) = V_{AC} \cos(\omega_{AC} t + \phi_{AC}) + V_S \cos(\omega_S t + \phi_S) + V_F \cos(\omega_F t + \phi_F)$$

$$\omega_{AC} = 2\pi \cdot 60 \text{ Hz}$$

$$\omega_S = 2\pi \cdot 600 \text{ Hz}$$

$$\omega_F = 2\pi \cdot 60 \text{ kHz}$$

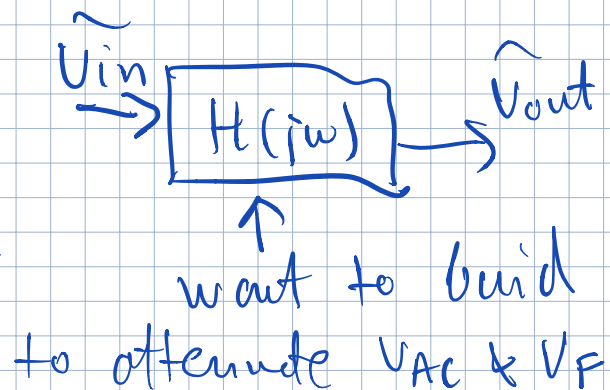

$$V_{out}(t) = |H(j\omega_{AC})| \cdot V_{AC} \cos(\omega_{AC} t + \phi_{AC} + \angle H(j\omega_{AC}))$$


$$+ |H(j\omega_S)| \cdot V_S \cos(\omega_S t + \phi_S + \angle H(j\omega_S))$$

$$+ |H(j\omega_F)| \cdot V_F \cos(\omega_F t + \phi_F + \angle H(j\omega_F))$$


Goal was to attenuate AC & Flurs
by 100x :

$$\Rightarrow |H(j\omega_{AC})| = \frac{1}{100}$$

$$|H(j\omega_F)| = \frac{1}{100}$$

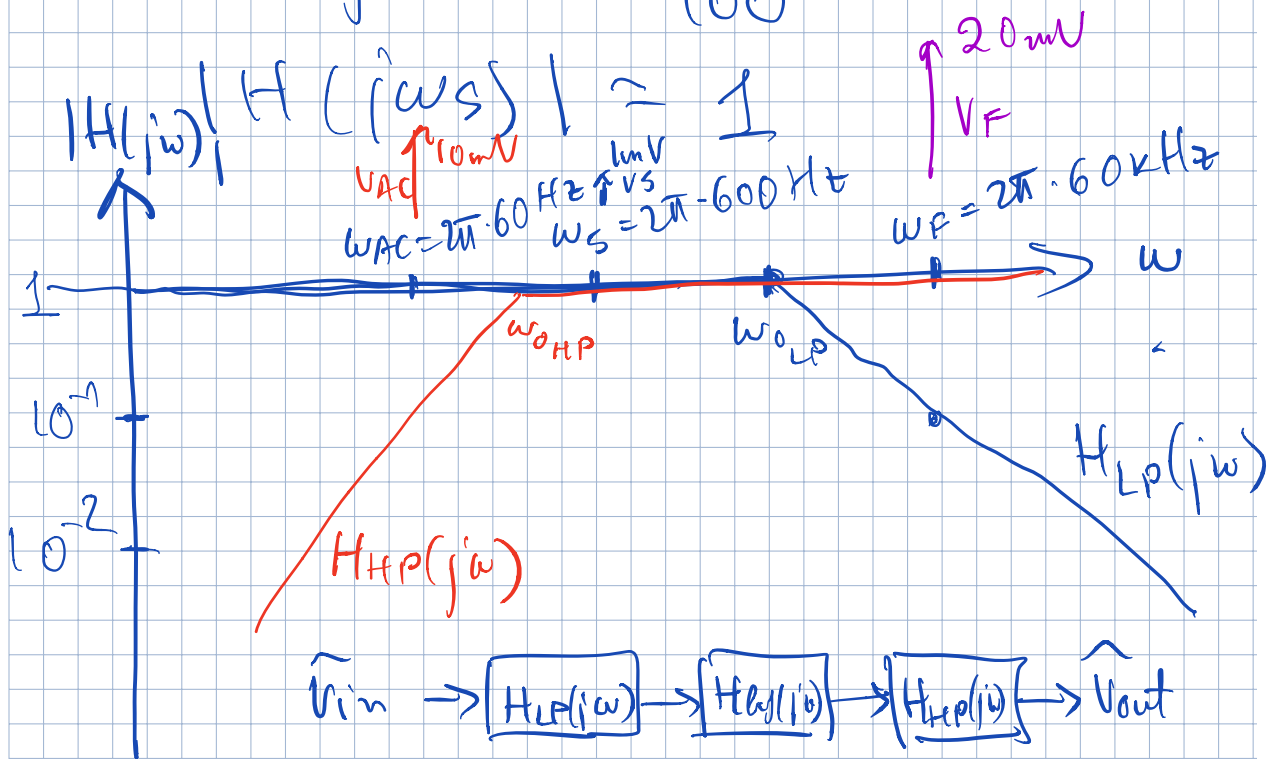


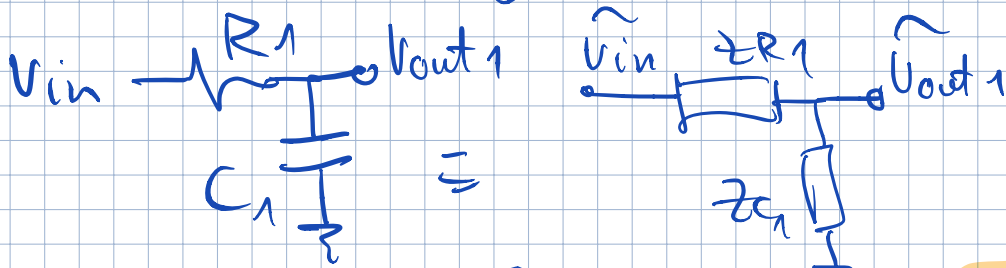$H_{LP}(j\omega)$ a low-pass filter already know how to build:



$$\hat{=} H_{LP}(j\omega) = \frac{\hat{V}_{out1}}{\hat{V}_{in}} = \frac{1}{1 + j\frac{\omega}{\omega_{OLP}}} \quad \left. \begin{array}{l} \omega_{OLP} = \frac{1}{RC_1} \end{array} \right\}$$

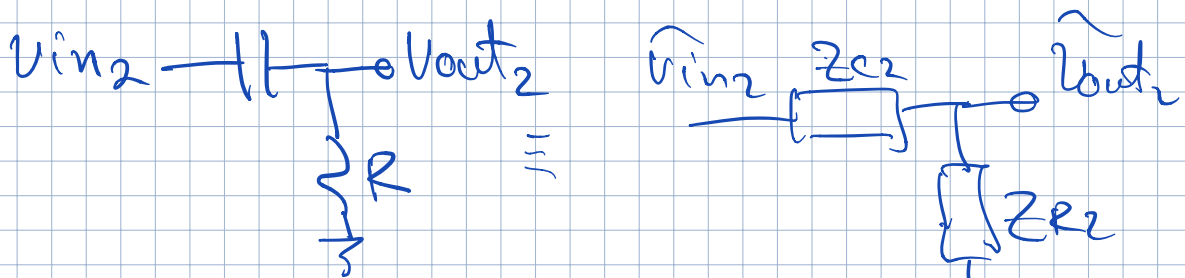$H_{HP}(j\omega)$ - a "high-pass" filter:



$$H_{HP}(j\omega) = \frac{\hat{V}_{out2}}{\hat{V}_{in2}} = \frac{Z_{R2}}{Z_{R2} + Z_{C2}} = \frac{R_2}{R_2 + \frac{1}{j\omega C_2}}$$

$$= \frac{j\omega R_2 C_2}{1 + j\omega R_2 C_2} = \frac{j\frac{\omega}{\omega_{OHP}}}{1 + j\frac{\omega}{\omega_{OHP}}} \quad \left. \begin{array}{l} \omega_{OHP} = \frac{1}{R_2 C_2} \end{array} \right\}$$

$$= \frac{1}{1 - j\frac{\omega_{OHP}}{\omega}} \quad \begin{array}{l} \omega \rightarrow 0 \quad \omega \rightarrow \infty \\ |H_{HP}(j\omega)| \rightarrow 0 \quad |H_{HP}(j\omega)| \rightarrow 1 \end{array}$$

$$H(j\omega) = H_{LP}(j\omega) \cdot H_{\log}(j\omega) \cdot H_{HP}(j\omega)$$

$$= \frac{1}{1 + j \frac{\omega}{\omega_{OLP}}} \cdot \frac{1}{1 - j \frac{\omega_{OHP}}{\omega}}$$

$$\omega_{OHP} = \sqrt{\omega_{AC} \cdot \omega_S}$$

$$\omega_{OLP} = \sqrt{\omega_S \cdot \omega_F}$$

$$\Gamma \log \omega_{OHP} = \frac{1}{2} \log \omega_{AC} + \frac{1}{2} \log \omega_S$$

$$\omega_{OHP} = \frac{1}{R_2 C_2} \quad ; \quad \omega_{OLP} = \frac{1}{R_1 C_1}$$

$$\omega_{OHP} = \sqrt{2\pi \cdot 60\text{Hz} \cdot 2\pi \cdot 600\text{Hz}} = 2\pi \cdot 190\text{Hz}$$

$$\omega_{OLP} = \sqrt{2\pi \cdot 600\text{Hz} \cdot 2\pi \cdot 60\text{kHz}} = 2\pi \cdot 6000\text{Hz}$$

$$\text{For } C_1 = 1\text{nF} \Rightarrow R_1 = \frac{1}{\omega_{OLP} C_1} = 26\text{k}\Omega$$

$$\text{For } C_2 = 1\mu\text{F} \Rightarrow R_2 = \frac{1}{\omega_{OHP} C_2} = 840\Omega$$

