

Lecture 11

EECS 16B

* Filter design

Design example:



AC: $V_{AC} \cos(\omega_{AC} t + \phi_{AC})$
10mV
 ω_{AC}

Sig: $V_S \cos(2\pi \cdot 600\text{Hz} t + \phi_S)$
10mV

fluoresc. glüher:
 $V_F \cos(2\pi \cdot 60\text{kHz} t + \phi_F)$
20mV

$\omega_{AC} = 2\pi \cdot 60\text{Hz}$
 $= 377 \frac{\text{rad}}{\text{s}}$


$\omega_S = 2\pi \cdot 600\text{Hz}$

$\omega_F = 2\pi \cdot 60\text{kHz}$

Want to attenuate

V_{AC} & V_F by 100x!

Designed a filter:

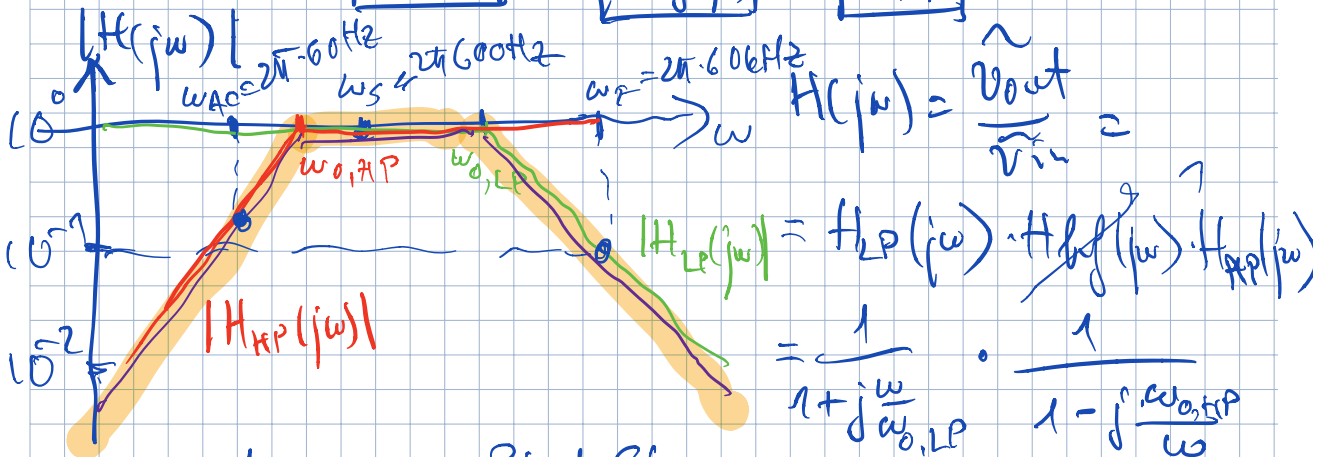

determine R's & C's


$\omega_{0,LP} = \frac{1}{R_{LP} \cdot C_{LP}}$

$\omega_{0,HP} = \frac{1}{R_{HP} \cdot C_{HP}}$

$\omega_{0,LP} = \sqrt{\omega_S \cdot \omega_F}$

$\omega_{0,HP} = \sqrt{\omega_{AC} \cdot \omega_S}$

Circuit representation:

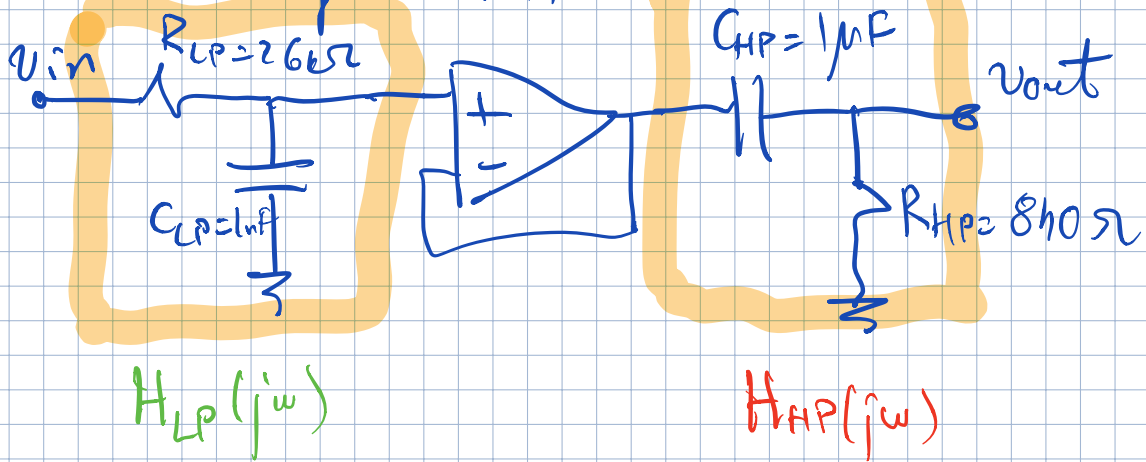

$$H(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_{0,LP}}} \cdot \frac{1}{1 - j\frac{\omega_{0,HP}}{\omega}}$$

ω	$ H_{LP}(j\omega) $	$ H_{HP}(j\omega) $	$ H(j\omega) $	$V_{in} \cdot H(j\omega) $
$2\pi \cdot 60\text{Hz}$	$\frac{1}{\sqrt{1 + \left(\frac{2\pi \cdot 60\text{Hz}}{2\pi \cdot 6\text{kHz}}\right)^2}} \approx 1$	$\frac{1}{\sqrt{1 + \left(\frac{2\pi \cdot 190}{2\pi \cdot 60}\right)^2}} \approx 0.3$	$1 \cdot 0.3 = 0.3$	$10\text{mV} \cdot 0.3 = 3\text{mV}$
$2\pi \cdot 600\text{Hz}$	$\frac{1}{\sqrt{1 + \left(\frac{2\pi \cdot 600\text{Hz}}{2\pi \cdot 6\text{kHz}}\right)^2}} \approx 1$	$\frac{1}{\sqrt{1 + \left(\frac{190}{600}\right)^2}} \approx 0.95$	$1 \cdot 0.95 = 0.95$	$1\text{mV} \cdot 0.95 = 0.95\text{mV}$
$2\pi \cdot 60\text{kHz}$	$\frac{1}{\sqrt{1 + \left(\frac{2\pi \cdot 60\text{kHz}}{2\pi \cdot 6\text{kHz}}\right)^2}} \approx 0.1$	$\frac{1}{\sqrt{1 + \left(\frac{190}{60\text{k}}\right)^2}} \approx 1$	$0.1 \cdot 1 = 0.1$	$20\text{mV} \cdot 0.1 = 2\text{mV}$

$$\begin{aligned}
 V_{out}(t) = & |H(j\omega_{AC})| \cdot V_{AC} \cdot \cos(\omega_{act} + \phi_{AC} + \angle H(j\omega_{AC})) \\
 & + |H(j\omega_S)| \cdot V_S \cdot \cos(\omega_{st} + \phi_S + \angle H(j\omega_S)) \\
 & + |H(j\omega_F)| \cdot V_F \cdot \cos(\omega_{ft} + \phi_F + \angle H(j\omega_F))
 \end{aligned}$$

Want $|H(j\omega_{AC})|$ & $|H(j\omega_F)| = \frac{1}{100}$
 & $|H(j\omega_S)| \approx 1$

Current design is not enough!
 Only get $|H(j\omega_{AC})| = 0.3$ 😞

$|H(j\omega_F)| = 0.1$ 😞

$|H(j\omega_S)| = 0.95$ 😞



$H^*(j\omega) = H_{LP}^n(j\omega) H_{HP}^m(j\omega)$

Want: $|H^*(j\omega_{AC})| = \frac{1}{100} = 0.3^m \Rightarrow m=4$


$|H^*(j\omega_F)| = \frac{1}{100} = 0.1^m \Rightarrow m=2$

$|H^*(j\omega_S)| = 0.95^4 = 0.8$ o.k. - not great

In general:


$$H(j\omega) = K \frac{(j\omega)^{N_{z0}} \cdot \overset{\text{origin zeros}}{(1 + j\frac{\omega}{\omega_{z1}})} \cdots (1 + j\frac{\omega}{\omega_{zn}})}{(j\omega)^{N_{p0}} \cdot \underset{\text{origin poles}}{(1 + j\frac{\omega}{\omega_{p1}})} \cdots (1 + j\frac{\omega}{\omega_{pm}})}$$

ω_{zn} - zero ω_{pm} - pole

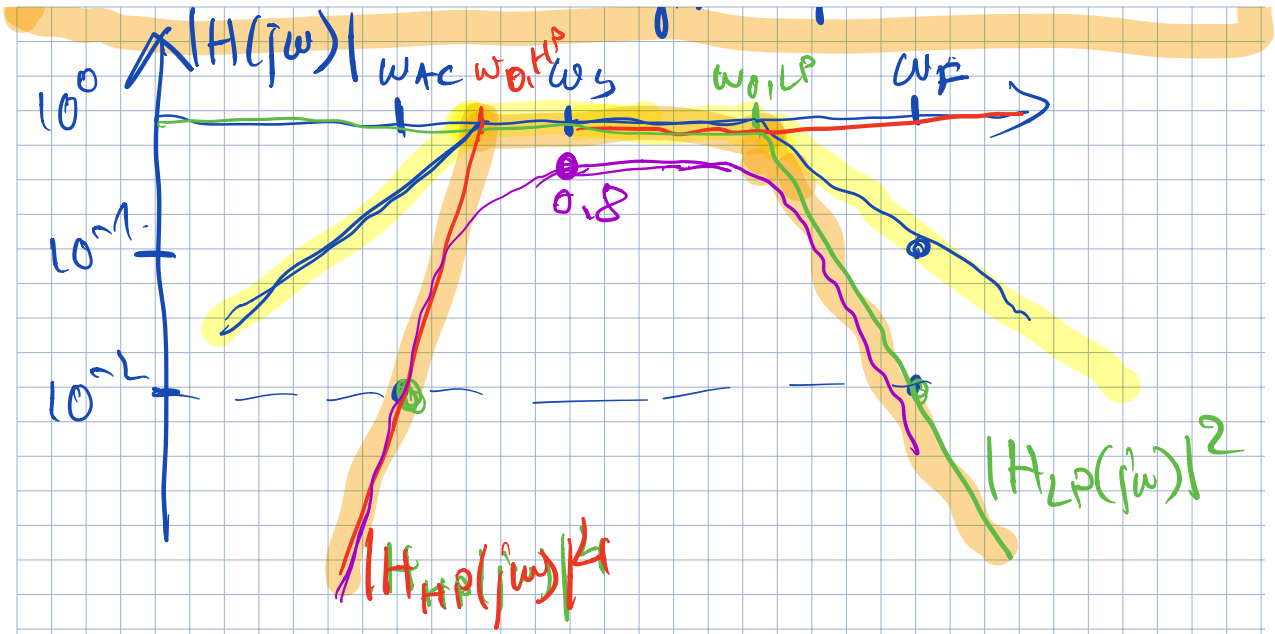

What if our desired signal is at 100Hz?
 Our parents design won't work.
 Too close to ω_{ac} .

Need a different filter!

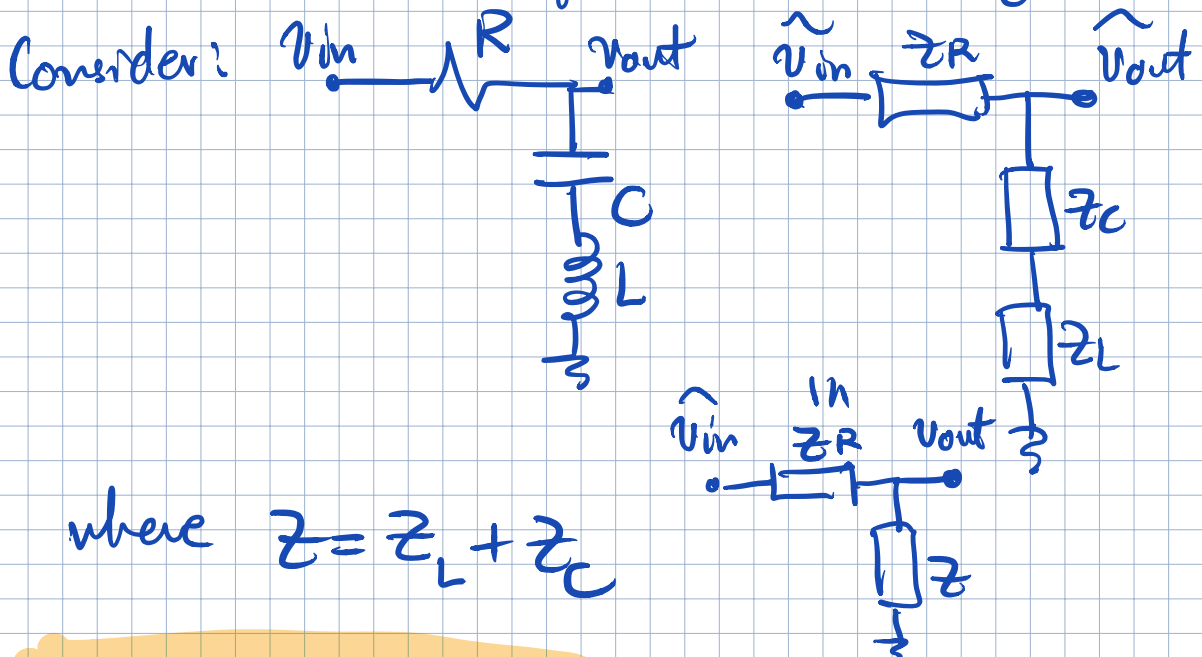

$$\tilde{v}_{out} = \frac{z}{z+z_R} \cdot \tilde{v}_{in}$$

$$z = j\omega L + \frac{1}{j\omega C}$$

Want $z(\omega_0) = 0$

$$= j\left(\omega L - \frac{1}{\omega C}\right)$$

$$\omega_0 L - \frac{1}{\omega_0 C} = 0$$


fantastic!

$$\omega_0^2 = \frac{1}{LC} \quad \text{choose } \omega_0 = \omega_{AC} = 2\pi 60 \text{ Hz}$$

Pick $C = 100 \mu\text{F} \Rightarrow L \approx 70 \text{ mH}$

$$z(\omega_0) = z(\omega_{AC}) = 0$$
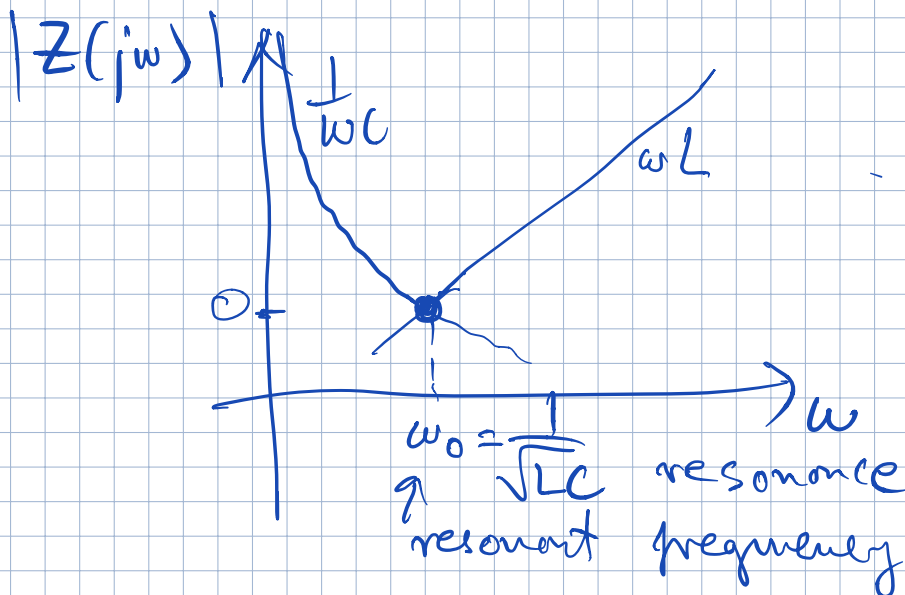
$$\tilde{v}_{out}(j\omega) = \frac{z}{z+z_R} \cdot \tilde{v}_{in}(j\omega) \Rightarrow v_{out}(j\omega_{AC}) = \frac{0}{0+z_R} \tilde{v}_{in}(j\omega_{AC}) = 0$$



$$H(j\omega) = \frac{\widehat{v}_{out}}{v_{in}} = \frac{z}{z+z_R} = \frac{j(\omega L - \frac{1}{\omega C})}{R + j(\omega L - \frac{1}{\omega C})}$$


$$H(j\omega_0) = 0$$

$$H(j2\pi \cdot 65\text{Hz}) = \frac{j \cdot 3.5\Omega}{R + j(3.5\Omega)}$$



Pick $R = 3\Omega$

$$H(j2\pi \cdot 55\text{Hz}) = \frac{j \cdot 4.7\Omega}{R + j(4.7\Omega)}$$

less than
50%
attenuation

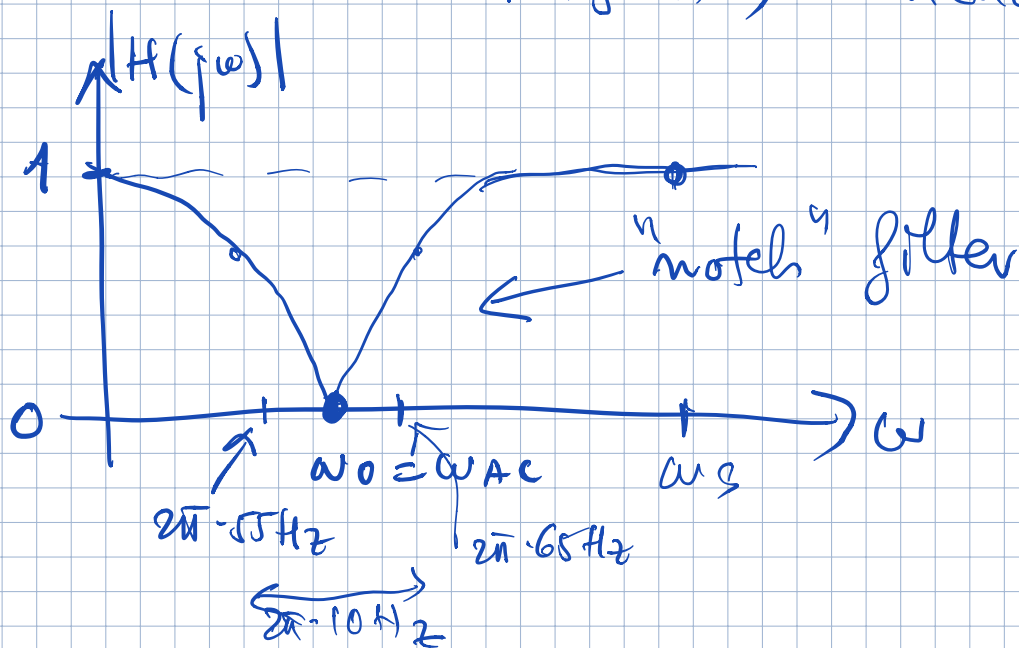

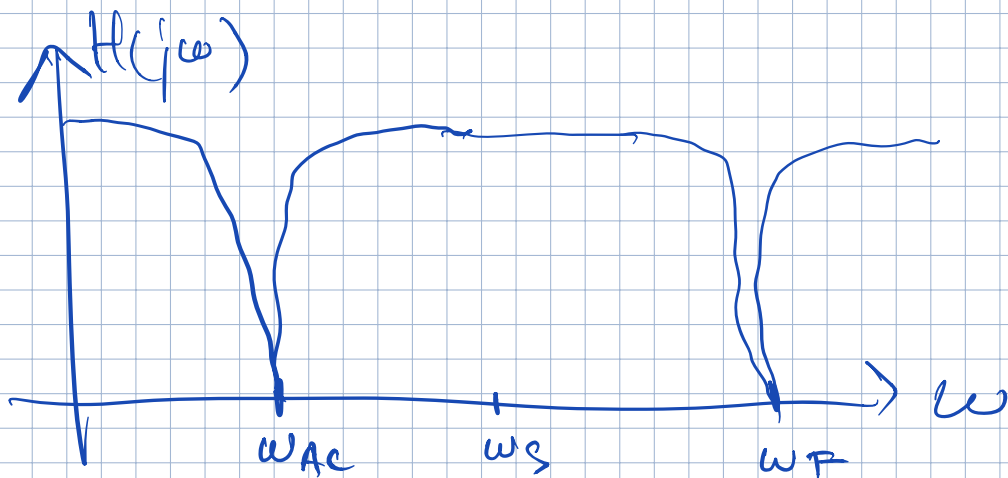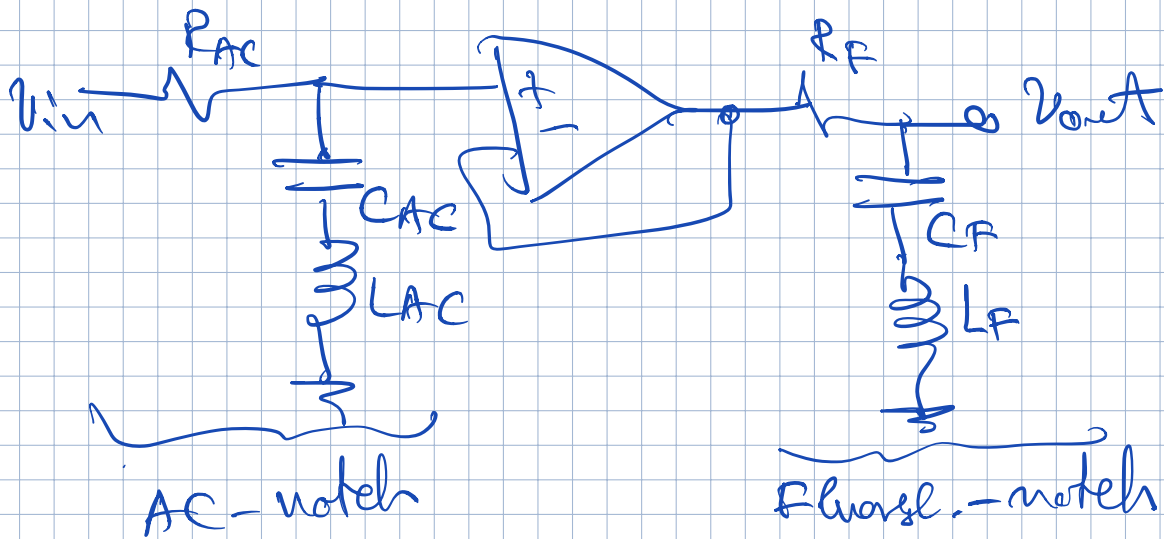can also set $\omega_{0,2} = \omega_F \Rightarrow L_F \& C_F$
such that $\frac{1}{\sqrt{L_F \cdot C_F}} = \omega_F$



Can also design a sharp band-pass:

