

**UNIVERSITY OF CALIFORNIA, BERKELEY**  
Department of Electrical Engineering and Computer Sciences  
EE251B Advanced Digital Circuits and Systems

Spring 2024, Prof. Borivoje Nikolic  
Homework 2

Issued: Friday, February 16th, 2024  
Due: Friday, March 8th 11:59pm

---

## 1 Transistor IV Models (50 %)

- (a) Use simulator of your choice (Spectre or HSpice) to simulate the VGS/IDS curve for the following device

Cell	nfet_01v8
Width	.64 $\mu$ m
Length	.15 $\mu$ m
Process Corner	tt

Ground the body of the device ( $V_{BS} = 0$ ). The device should be in saturation ( $V_{DS} > V_{GS} - V_{th}$ ).

Provide your simulated  $V_{GS}/I_{DS}$  curve. What is the device's  $V_{th}$ ?

*Hints:*

- Set the drain of the device to  $V_{DD}(1.8v)$  and the source to a 0ohm resistor, with the other terminal of the resistor ground. You can measure the current through the resistor as your device's  $I_{DS}$ .
- Here is some starter code for a testbench that may be useful:

```
.lib '/home/ff/eecs251b/sky130/sky130_cds/sky130_release_0.0.1/models/sky130.lib.spice'  
tt  
.include '/home/ff/eecs251b/sky130/sky130_conv.spice'  
xnfet drain gate source body nfet_01v8 w=0.64u l=0.15u
```

- (b) For the  $I_{DSat}$  model used in class ( $I_{DSat} = \frac{W}{L} \frac{\mu_{eff} E_C L}{2} \frac{(V_{GS} - V_{Th})^2}{V_{GS} - V_{Th} + E_C L}$ ), find the values of  $E_C L$  and  $\mu_{eff}$  that best fits your device's curve. Use the  $V_{th}$  value you found in part a).

Note that you may want to modify the  $I_{DSat}$  equation to account for finite output resistance.

*Hint:* The `lsqcurvefit` function in MATLAB<sup>1</sup> may be useful.

- (c) Fit the simulated IV curve to the alpha-power-law model  $I_D = K(V_{GS} - V_{Th})^\alpha$ . Report  $K$ ,  $V_{Th}$ , and  $\alpha$ ; Attach an image of the fitted curve superimposed on top of the simulated one.
- i. is your fitted  $V_{th}$  different from the device model's? Why might this occur?
  - ii. We fit this curve for a device in saturation. when might this model be useful when the  $I_{DSat}$  one is not?

*Hint:* the `lsqcurvefit` function in MATLAB may also be useful here.

---

<sup>1</sup>You can find an example for how to export Spectre data to MATLAB at [https://courses.grainger.illinois.edu/ece483/sp2024/data/cadence/ECE483\\_MATLAB\\_export.pdf](https://courses.grainger.illinois.edu/ece483/sp2024/data/cadence/ECE483_MATLAB_export.pdf)

## 2 Standard Cells (50%)

You have been tasked with providing useful delay modeling abstractions to a digital design team. Your responses should reference the following Sky130 LIB file: `sky130_fd_sc_hd__tt_025C_1v80.lib`. It can be found in `/home/ff/eecs251b/sky130/sky130A/libs.ref/sky130_fd_sc_hd/lib/`

- (a) Using the lib file for `sky130_fd_sc_hd__inv_1`, plot (for both rising and falling outputs) the fanout (load) versus delay of using the tool of your choice.

*Hint:* the device has two 2d "delay" arrays, one for rise time (`cell_rise`) and one for fall time (`cell_fall`). One of the dimensions is the fanout (load) that device is driving.

- (b) Simulate and plot the fanout (load) versus delay of `sky130_fd_sc_hd__inv_1` using SPICE simulations. Does it differ from the .lib defined behavior?

*Hint:* what is the second column of the .delay array? What must you change in your simulation setup to ensure you are matching the environment the .lib parameters were extracted from?

- (c) Draw the schematic you could simulate to characterize the FO4 delay of an inverter `inv_custom` with size  $\frac{W}{L}$ .

- (d) Given the inverter `sky130_fd_sc_hd__inv_1` as your reference device, what is the logical effort of `sky130_fd_sc_hd__and2_0`? You may reference the .lib values.