

UNIVERSITY OF CALIFORNIA, BERKELEY
Department of Electrical Engineering and Computer Sciences
EE251B Advanced Digital Circuits and Systems

Spring 2024, Prof. Borivoje Nikolic
Homework 4

Issued: Thursday, April 4, 2024
Due: Friday, April 12th, 11:59pm

1 SRAM assists (50 %)

Consider a conventional 6-T SRAM cell, sized to be stable at nominal operating conditions. The cell is a part of a conventional, precharged bitline array. We would like to operate it at a reduced supply voltage, so we are considering assist techniques. Let's analyze the effect of peripheral signals on the operation of the cell. One-sentence answers, please!

- (a) How does increased wordline voltage affect the read stability of the cell?
- (b) How does increased wordline voltage affect the read access time of the cell?
- (c) How does increased wordline voltage affect the writeability of the cell?
- (d) How does decreased cell supply voltage (without changing other signal levels) affect the writeability of the cell?

2 SRAM yield (50 %)

We will analyze a $4 \text{ MiB} = 2^{22} \text{ B}$ SRAM array, consisting of 256×256 bit subarrays. Two columns share one sense amplifier. Bitline capacitance is 2 pF and the supply is 1.8 V . For this problem, assume that all the SRAM cells in the array are identical (i.e. not affected by the random process variation) and $I_{on} = 400 \mu\text{A}$, $I_{off} = 100 \text{ nA}$. Assume that the target access time of 1 ns is dominated by the bitline discharge.

If the sense amplifier offset has normal distribution, with zero mean and standard deviation of 30 mV , would you expect this array to have a high yield? How many redundant columns would need to be added per subarray to have at least 99% yield for the whole 4 MiB SRAM array (note that you may not have to do the exact calculation of this)?