

# EECS251B : Advanced Digital Circuits and Systems

## Lecture 12 – Standard Cells

Borivoje Nikolić



### Aries v.3.0

The ARIES v3.0 is a fully indigenous and a “Made in India” product to get started with basic microprocessor programming and embedded systems. This board is built upon a RISC-V ISA compliant VEGA Processor with easy-to-use hardware and software. The VEGA SDK also provides full ecosystem with numerous examples and support documentation.



<https://vegaprocessors.in/devboards/ariesv3.php>


# Announcements

- Lab 5 waiting on PDK correction
- Start project phase 1
- Homework 2 due next week
- Quiz 1 today!




## Transistor Leakage

# Transistor Leakage

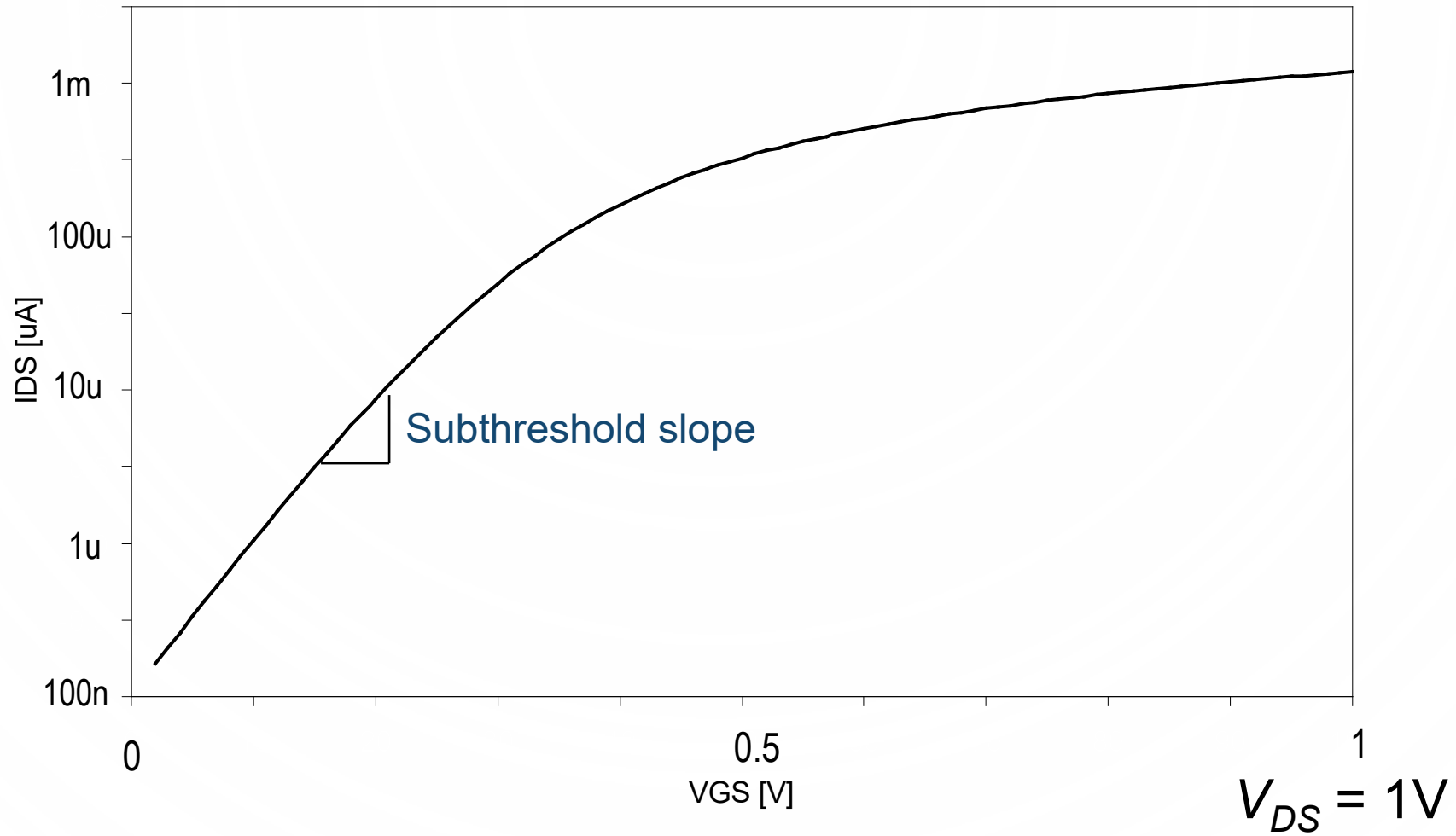

Leakage current is exponential with  $V_{G_S}$


# Transistor Leakage (130nm)

 

Two effects:

- diffusion current (like a bipolar transistor)
- exponential increase with  $V_{DS}$  (DIBL)

# Transistor Leakage (32nm LP PTM)

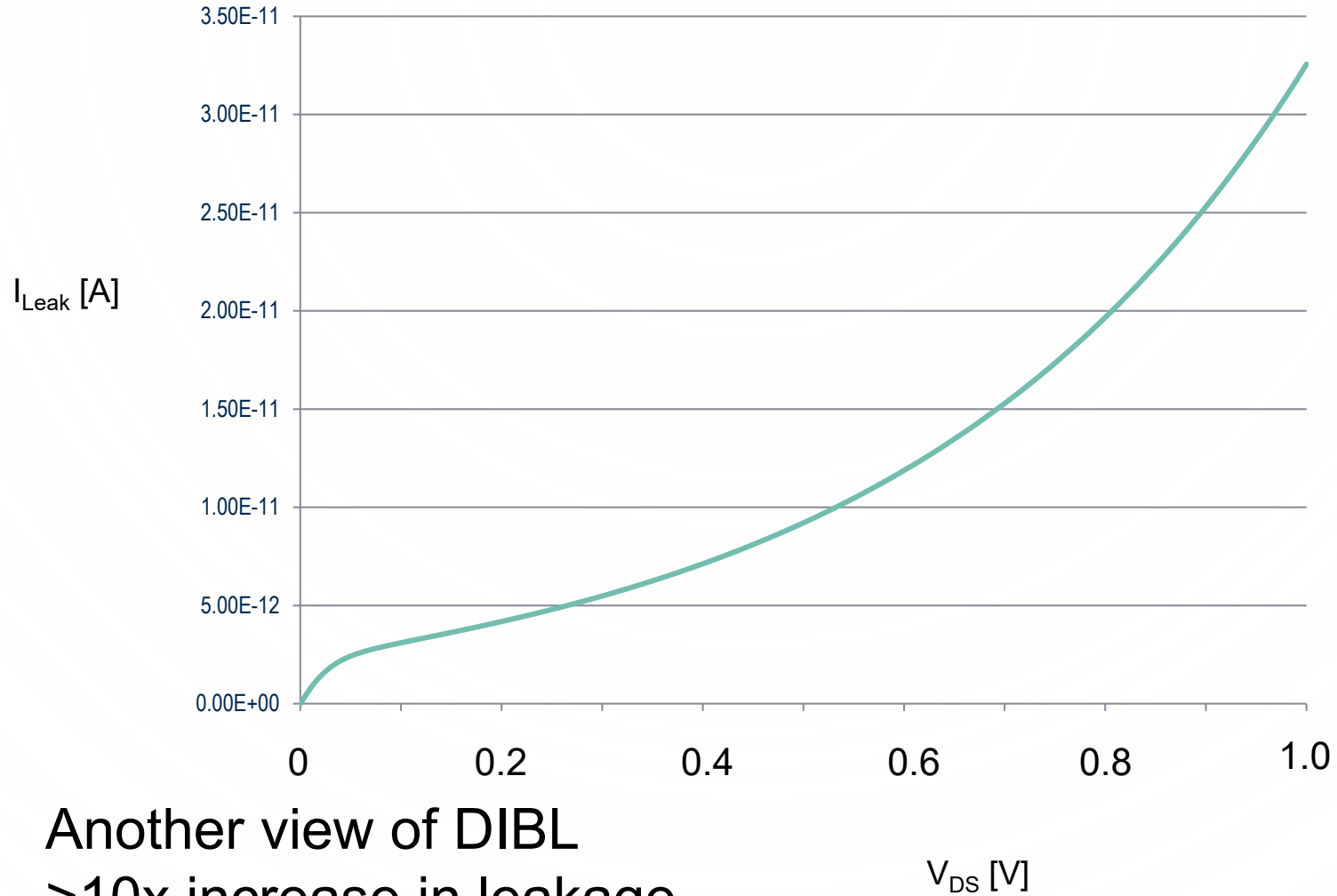

Another view of DIBL  
>10x increase in leakage

# Subthreshold Current

- Subthreshold behavior can be modeled physically

$$I_{ds,subth} = \mu_{eff} C_{ox} \frac{W}{L} (m-1) \left( \frac{kT}{q} \right)^2 e^{\frac{V_{GS}-V_{Th}}{m kT/q}} \left( 1 - e^{-\frac{V_{ds}}{kT/q}} \right)$$

$$m = 1 + \frac{C_{dm}}{C_{ox}} \quad (m \sim 1.1-1.4)$$

Or (approx):

$$I_{ds,subth} = I_0 \frac{W}{W_0} 10^{\frac{(V_{gs}-V_{Th})+\gamma V_{ds}}{S}}$$

$$S = 2.3m \frac{kT}{q}$$

Taur, Ning, Modern VLSI Devices



# Added Leakage Components

- Drain-induced barrier lowering (DIBL)
  - Voltage at the drain lowers the source potential barrier
  - Lowers  $V_{Th}$ , no change on  $S$
- Gate-induced drain leakage (GIDL)
  - High field between gate and drain increases injection of carriers into substrate -> leakage  
(band-to-band leakage)



# Leakage Components (250nm)

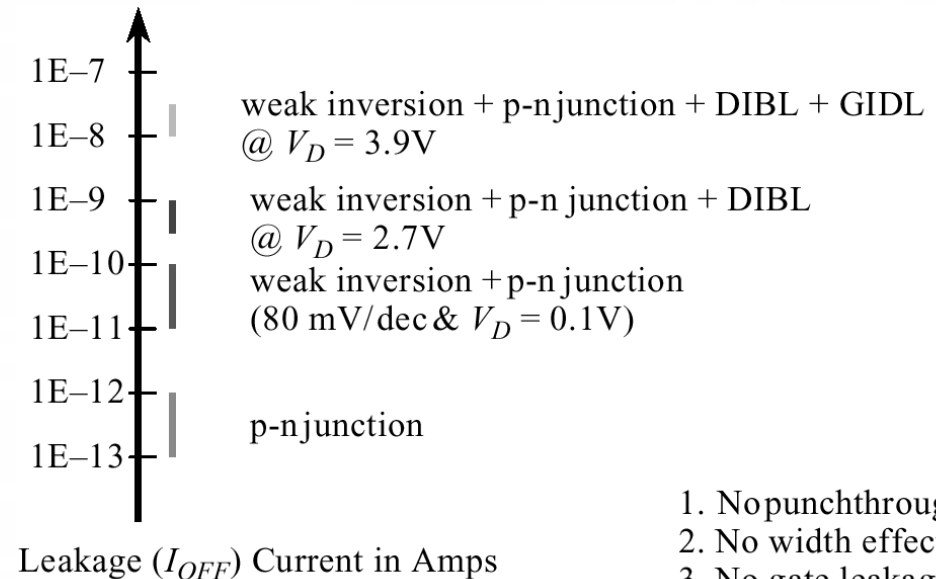 1. pn junction reverse bias current
2. Weak inversion
3. Drain-induced barrier lowering (DIBL)
4. Gate-induced drain leakage (GIDL)
5. Punchthrough
6. Narrow width effect
7. Gate oxide tunneling
8. Hot carrier injection




1. No punchthrough
2. No width effect
3. No gate leakage



## Transistor C-V

# MOS Transistor as a Switch

Discharging a capacitor

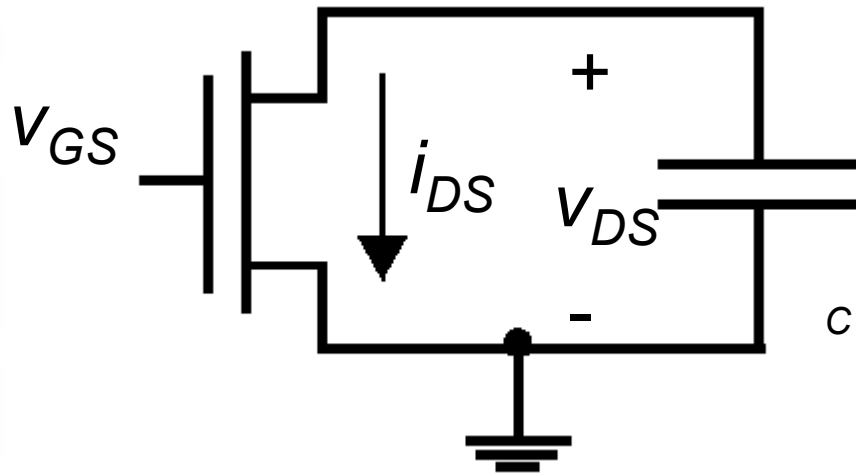

- Can solve:

$$i_{DS} = i_{DS}(V_{DS})$$

$$i_{DS} = C(V_{DS}) \frac{dv_{DS}}{dt}$$

- Prefer using equivalent resistances
- Find  $t_{pHL}$
- Find equivalent C, R

$$t_{pHL} = \int \frac{C(V_{DS}) dv_{DS}}{i_{DS}(V_{GS}, V_{DS})}$$

# MOS Capacitances

- Gate capacitance
  - Non-linear channel capacitance
  - Linear overlap, fringing capacitances
  - Miller effect on overlap, fringing capacitance
- Non-linear drain diffusion capacitance
  - PN junction
- Wiring capacitances
  - Linear

# Gate and Drain Capacitances

Gate capacitance

Drain capacitance


# Gate Capacitances

- Gate capacitance is non-linear
  - First order approximation with  $C_{ox}WL$  ( $C_{ox}L = 2\text{fF}/\mu\text{m}$ )
- Need to find the actual equivalent capacitance by simulating it
- Since this is a linear approximation of non-linear function, it is valid only over the certain range
  - Different capacitances for HL, LH transitions and power computation
- Drain capacitance non-linearity compensates
  - But this changes with fanout




## Delay Revisited

# MOS Transistor as a Switch (EECS251A)

 

Traversed path

 

$$R_{eq} = \text{average}_{t=t_1 \dots t_2} (R_{on}(t)) = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} R_{on}(t) dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} \frac{V_{DS}(t)}{I_D(t)} dt$$
$$\approx \frac{1}{2} (R_{on}(t_1) + R_{on}(t_2))$$



# MOS Transistor as a Switch (EECS251A)

Solving the integral:

$$R_{eq} = \frac{1}{-V_{DD}/2} \int_{V_{DD}}^{V_{DD}/2} \frac{V}{I_{DSAT}(1 + \lambda V)} dV \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left( 1 - \frac{7}{9} \lambda V_{DD} \right)$$


with appropriately calculated  $I_{dsat}$

Averaging resistances:


$$R_{eq} = \frac{1}{2} \left( \frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left( 1 - \frac{5}{6} \lambda V_{DD} \right)$$
 
# CMOS Performance

Propagation delay:  $t_{pHL} = (\ln 2)R_{eqn}C_L$      $t_{pLH} = (\ln 2)R_{eqp}C_L$



(a) schematic

 


(b) trajectory traversed on ID-VDS curve.

$\ln 2 = 0.7$
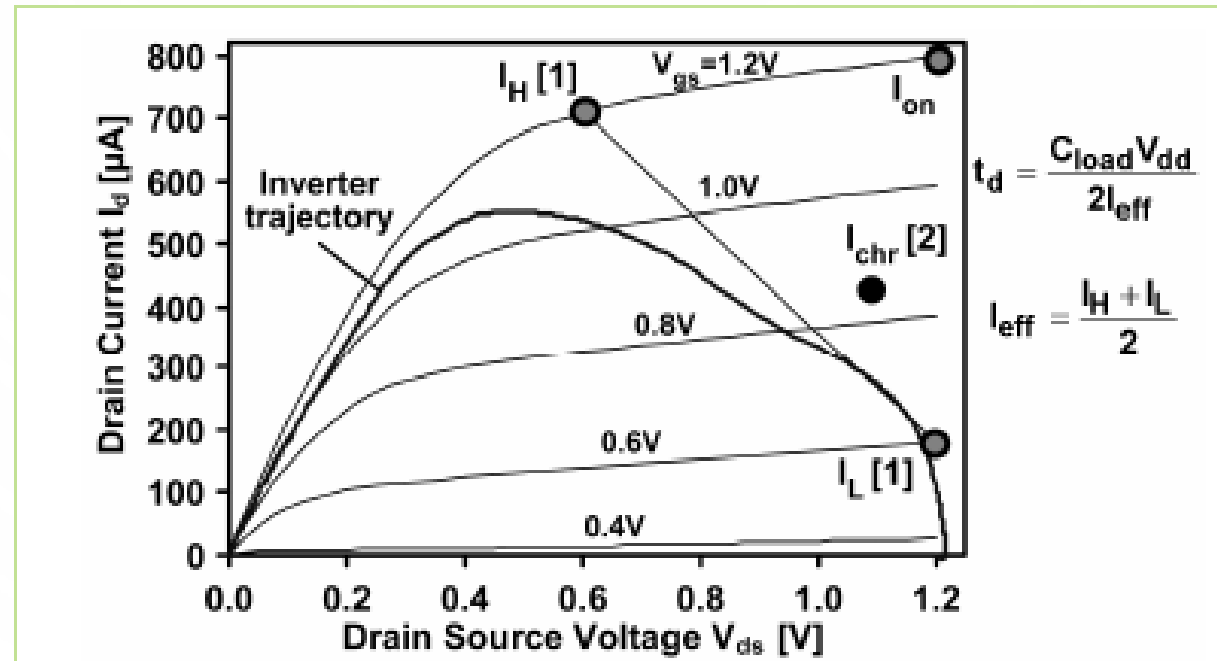
# Effective Current

- $I_{on}(V_{DD})$  is never reached
- Define  $I_{eff} = (I_H + I_L)/2$
- $I_L = I_{DS}(V_{GS}=V_{DD}/2, V_{DS}=V_{DD}); I_H = I_{DS}(V_{GS}=V_{DD}, V_{DS}=V_{DD}/2),$




Na, IEDM'2002  
Von Arnim, IEDM'2007

# DIBL Matters

- A. Loke, VLSI'16

## ▶ FinFET, FDSOI – less DIBL

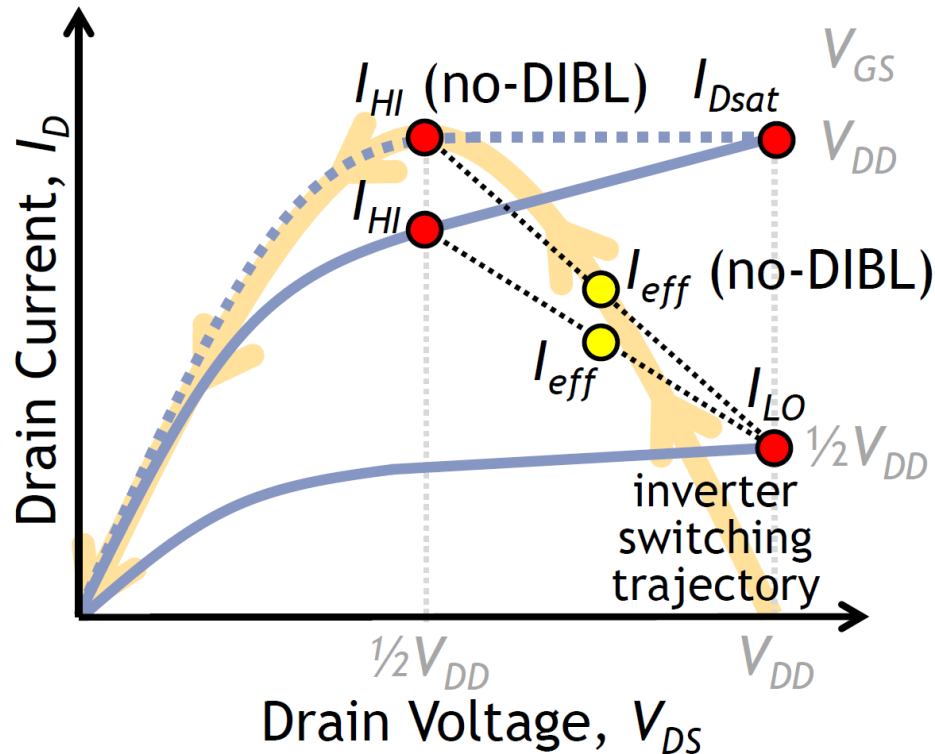

$$I_{eff} = \frac{I_{LO} + I_{HI}}{2}$$

$I_{LO}$  @  $V_{GS} = 1/2 V_{DD}$ ,  $V_{DS} = V_{DD}$


$I_{HI}$  @  $V_{GS} = V_{DD}$ ,  $V_{DS} = 1/2 V_{DD}$

$I_{eff}$  is better than  $I_{Dsat}$  for estimating inverter CV//I switching delay


Less DIBL  $\rightarrow$  higher  $I_{eff}$  &  $r_{out}$  for same  $I_{Dsat}$

# Effective Current in Stacks

- ▶ Add linear current,  $I_3$

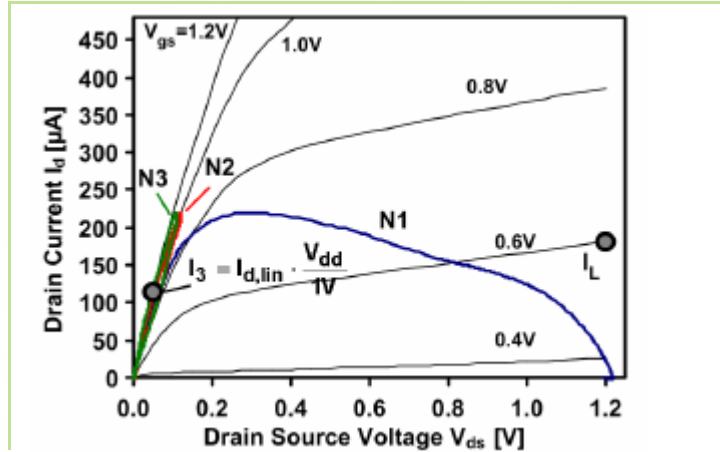



	$V_{gs}$	$V_{ds}$
$I_H$	$V_{dd}$	$V_{dd}/2$
$I_L$	$V_{dd}/2$	$V_{dd}$
$I_3$	$V_{dd}$	$0.05 \cdot V_{dd}$

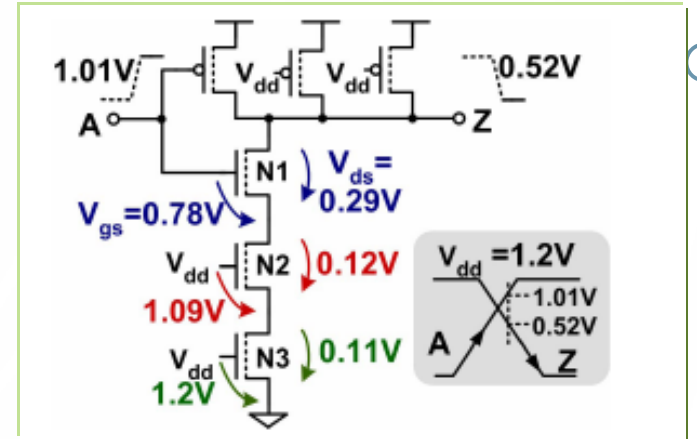

**Model:**  $I_{stack,i} = c_{H,i} I_H + c_{L,i} I_L + c_{3,i} I_3 \Rightarrow$   
**Inverter:**  $I_{stack1} = 0.45 \cdot I_H + 0.48 \cdot I_L + 0.07 \cdot I_3$   
**NAND2/NOR2:**  $I_{stack2} = 0.18 \cdot I_H + 0.38 \cdot I_L + 0.44 \cdot I_3$   
**NAND3/NOR3:**  $I_{stack3} = 0.08 \cdot I_H + 0.36 \cdot I_L + 0.56 \cdot I_3$

Von Arnim, IEDM'2007

 


 


## Standard Cells
 
# Standard Cell Inverter

- Schematic and layout  
(in a planar bulk process,  $\sim 250\text{nm}$ )



 
- Pitches are integer multiples of  $\lambda$




# Two Inverters

Share power and ground

Abut cells

 

► Delay is additive

 





# SkyWater 130nm Standard Cells

- Library options

Architecture Comparison	Low Speed	High Density	High Density Low Leakage	High Voltage
TAP BAR	NO	NO	NO	YES
X-GRID	0.480	0.460	0.460	0.480
Y-GRID	0.370	0.340	0.340	0.370
CELL HEIGHT	9 GRIDS	8 GRIDS	8 GRIDS	11 GRIDS
CELL HEIGHT	3.330	2.720	2.720	4.07
NAND2 WIDTH	3 GRIDS	3 GRIDS	4 GRIDS	5 GRIDS
NAND2 WIDTH	1.440	1.380	1.840	2.400
NAND2 AREA	4.7952	3.7536	5.0048	9.770
WPMAX	1.120	1.000	1.000	1.500
WNMAX	0.740	0.650	0.650	0.75



- Multiple gate sizes within a library

- Symbol

 
 


INVX3,  
INVX4,...

- Schematic

  



- Layout

  

# SkyWater 130nm Standard Cells
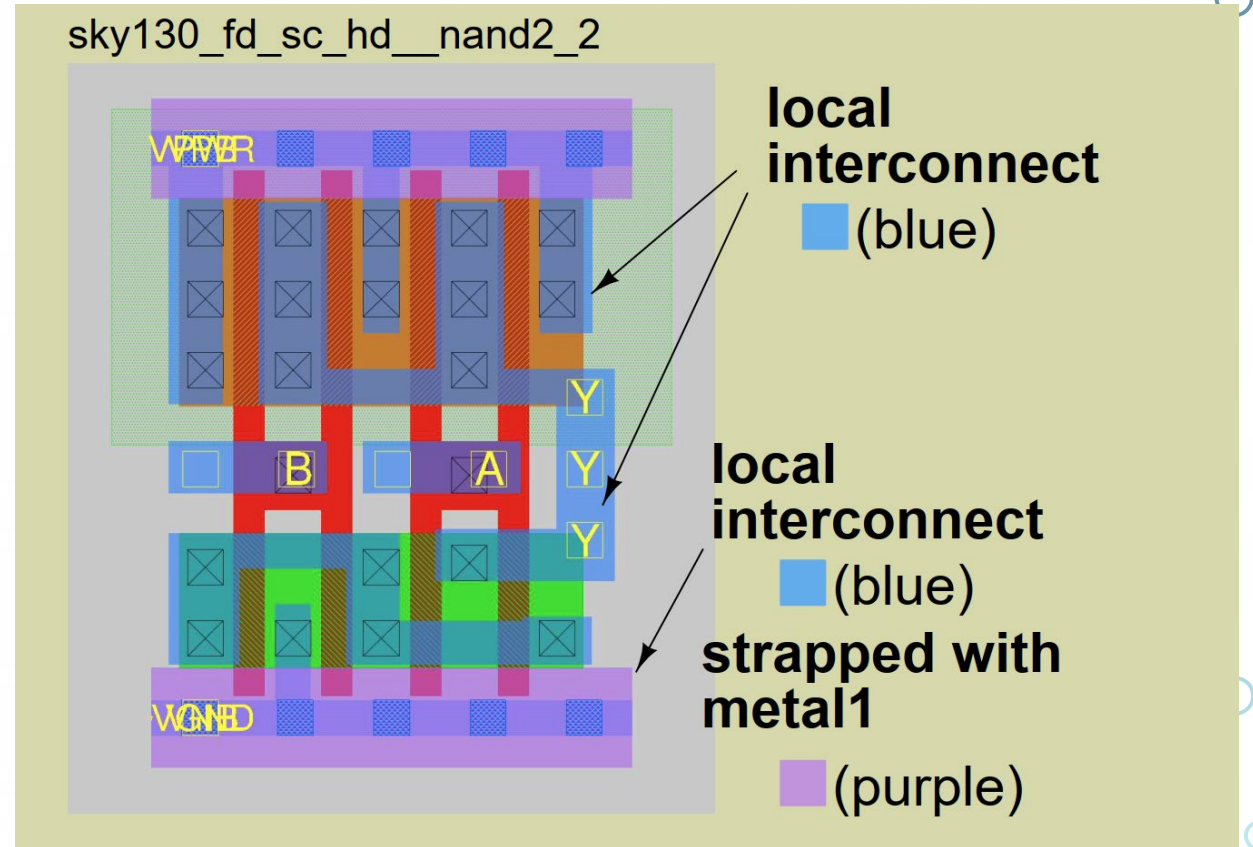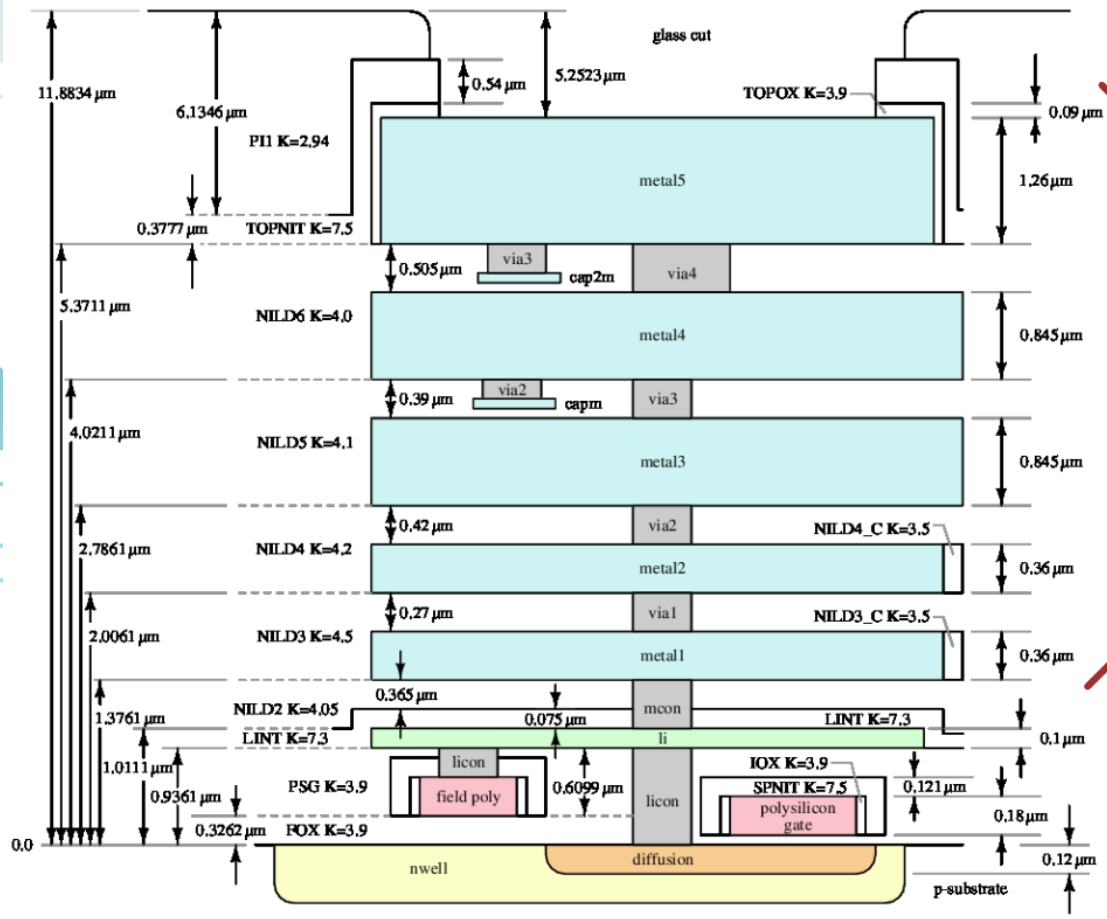
## Local interconnect

SkyWater Sky130A metal stack (not to scale!):



[https://isn.ucsd.edu/courses/beng207/lectures/Tim\\_Edwards\\_2021\\_slides.pdf](https://isn.ucsd.edu/courses/beng207/lectures/Tim_Edwards_2021_slides.pdf)

# FinFET Standard Cells

## ASAP7

- **Standard cell height selection is application specific**
  - Related to fins/gate, i.e. drive strength
- **Gear ratio: fin-to-metal pitch ratio**
  - Cell height needs to be integer # of fins and (mostly) an integer # of metals accessing the cell pins (e.g. M2)



ICCAD 2017 Embedded Tutorial ASAP7


16


V. Vashishtha, ICCAD'17

# ASAP7 Standard Cells

- **Cell architecture**
  - **7.5 M2 track height**
    - **Provides good gear ratio with fin, poly, and M2 pitch**




 Fin (pre-cut)

 Cell Boundary
 
# ASAP7 Standard Cells

- **Cell architecture**
  - **7.5 M2 track height**
    - Provides good gear ratio with fin, poly, and M2 pitch
  - **Adjacent NAND3 and inverter FEOL and MOL show the double diffusion break (DDB)**




□ Fin (pre-cut)

■ Active (drawn)

□ Cell Boundary
 
# ASAP7 Standard Cells

- **Cell architecture**
  - **7.5 M2 track height**
    - **Provides good gear ratio with fin, poly, and M2 pitch**
  - **Adjacent NAND3 and inverter FEOL and MOL show the double diffusion break (DDB)**
  - **Drawing is not WSYWIG—the fins extend to  $\frac{1}{2}$  the gate horizontally past drawn active**



□ Fin (pre-cut)


■ Active (drawn)

⊞ Active (actual fin block mask)

⊞ Cell Boundary
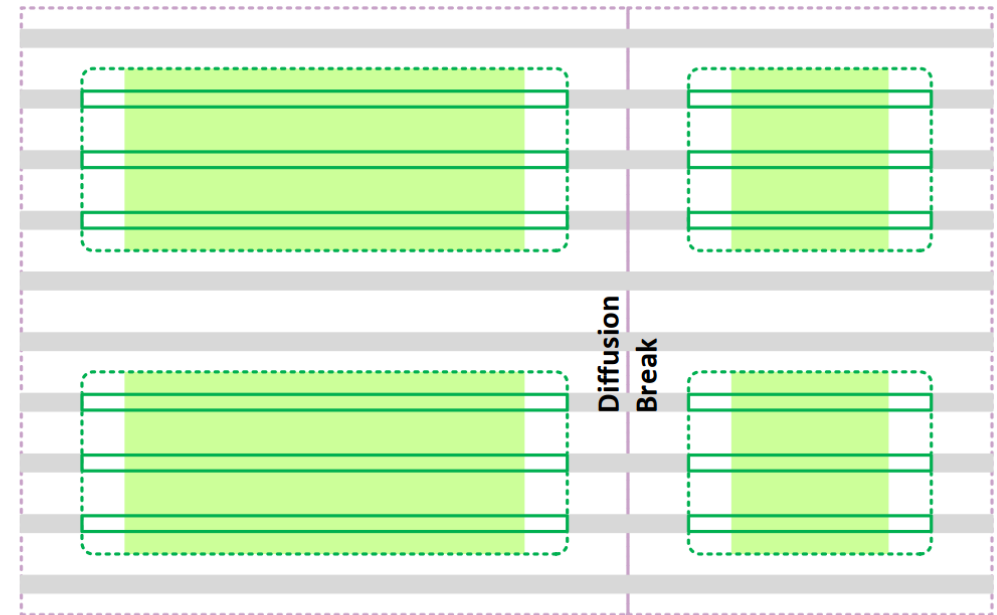
# ASAP7 Standard Cells

- **Cell architecture**
  - **7.5 M2 track height**
    - **Provides good gear ratio with fin, poly, and M2 pitch**
  - **Adjacent NAND3 and inverter FEOL and MOL show the double diffusion break (DDB)**
  - **Drawing is not WSYWIG—the fins extend to  $\frac{1}{2}$  the gate horizontally past drawn active**
- **DDB needed since the 32 nm node, depending on foundry**
  - **Design rules check for connectivity**




- Fin (post-cut)
- Fin (excised)
- Active (drawn)
- Active (actual fin block mask)

□ Cell Boundary
 
# ASAP7 Standard Cells

- **Cell architecture**
  - **7.5 M2 track height**
    - **Provides good gear ratio with fin, poly, and M2 pitch**
  - **Adjacent NAND3 and inverter FEOL and MOL show the double diffusion break (DDB)**
  - **Drawing is not WSYWIG—the fins extend to  $\frac{1}{2}$  the gate horizontally past drawn active**
- **DDB needed since the 32 nm node, depending on foundry**
  - **Design rules check for connectivity**





- Gate (pre-cut)
- Fin (post-cut)
- Fin (excised)
- Active (drawn)
- Active (actual fin block mask)

□ Cell Boundary



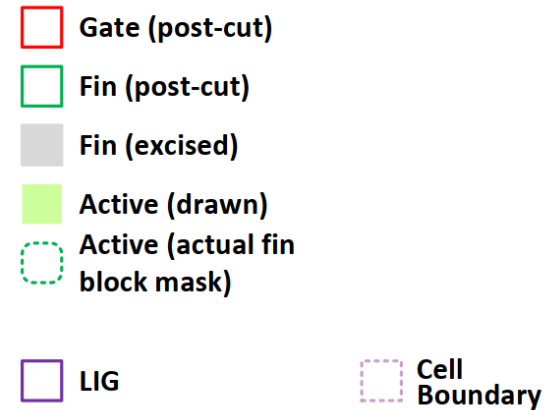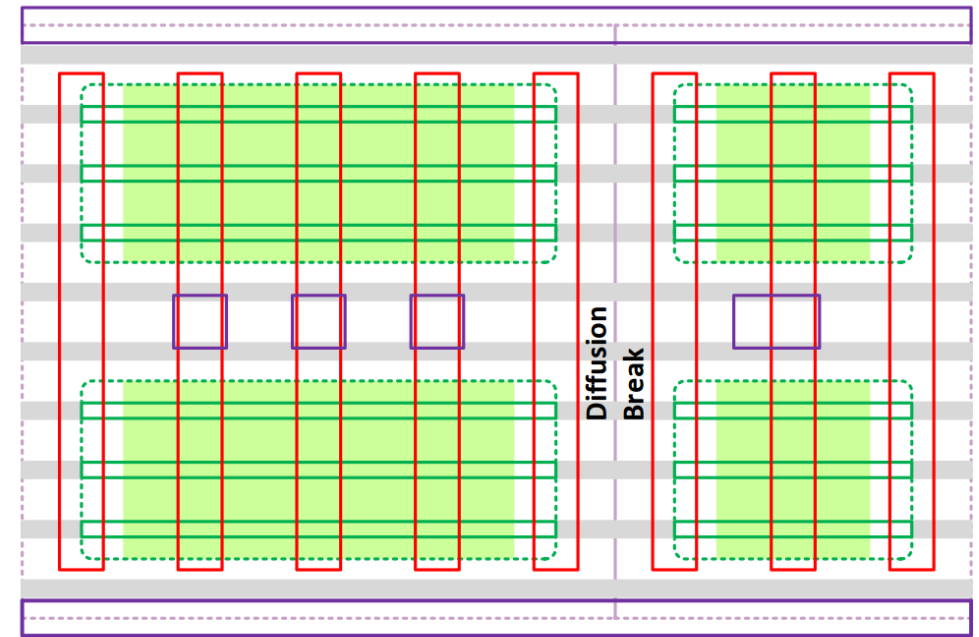
# ASAP7 Standard Cells

- **Cell architecture**
  - **7.5 M2 track height**
    - Provides good gear ratio with fin, poly, and M2 pitch
  - **Adjacent NAND3 and inverter FEOL and MOL show the double diffusion break (DDB)**
  - **Drawing is not WSYWIG—the fins extend to 1/2 the gate horizontally past drawn active**
- **DDB needed since the 32 nm node, depending on foundry**
  - **Design rules check for connectivity**



 
# ASAP7 Standard Cells

- **Cell architecture**
  - **7.5 M2 track height**
    - Provides good gear ratio with fin, poly, and M2 pitch
  - **Adjacent NAND3 and inverter FEOL and MOL show the double diffusion break (DDB)**
  - **Drawing is not WSYWIG—the fins extend to  $\frac{1}{2}$  the gate horizontally past drawn active**
- **DDB needed since the 32 nm node, depending on foundry**
  - **Design rules check for connectivity**



 
# ASAP7 Standard Cells

- **Cell architecture**
  - **7.5 M2 track height**
    - **Provides good gear ratio with fin, poly, and M2 pitch**
  - **Adjacent NAND3 and inverter FEOL and MOL show the double diffusion break (DDB)**
  - **Drawing is not WSYWIG—the fins extend to  $\frac{1}{2}$  the gate horizontally past drawn active**
- **DDB needed since the 32 nm node, depending on foundry**
  - **Design rules check for connectivity**



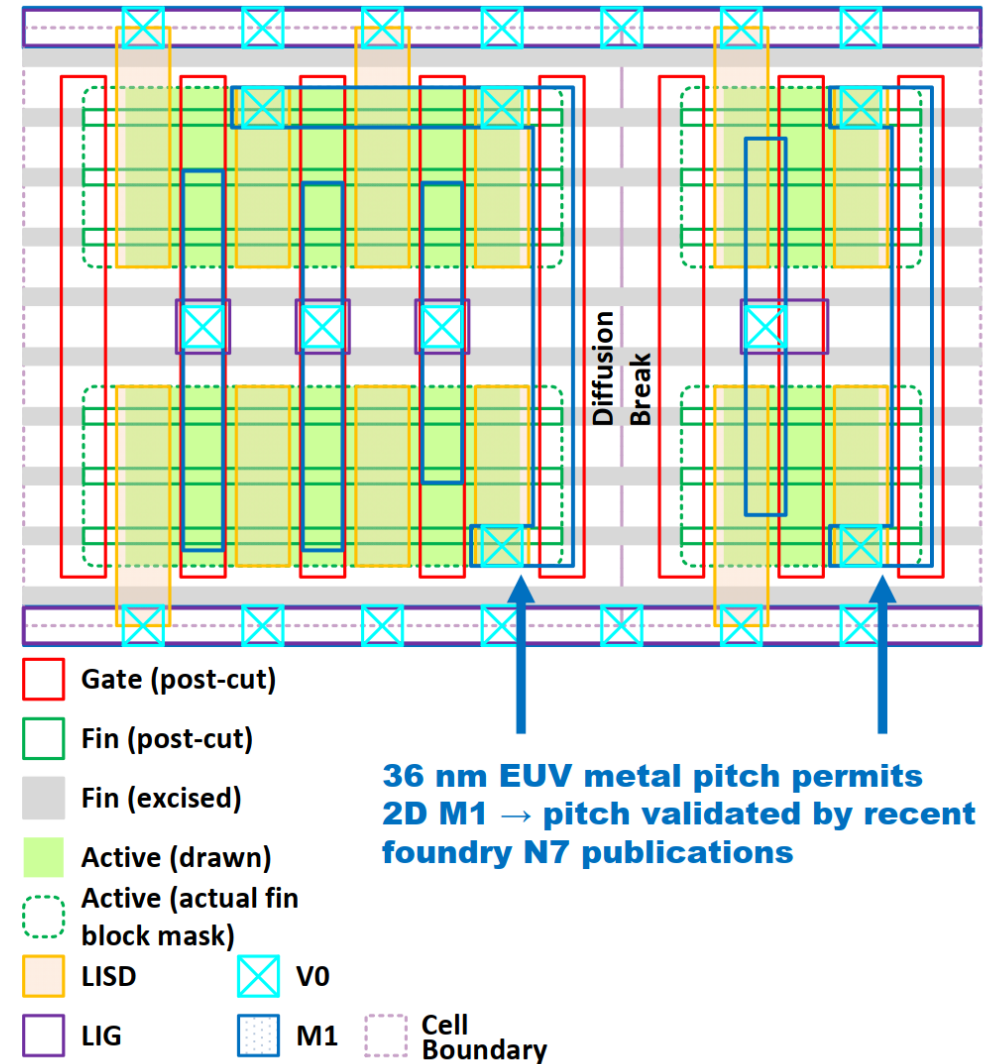
# ASAP7 Standard Cells

- **Cell architecture**
  - **7.5 M2 track height**
    - Provides good gear ratio with fin, poly, and M2 pitch
  - **Adjacent NAND3 and inverter FEOL and MOL show the double diffusion break (DDB)**
  - **Drawing is not WSYWIG—the fins extend to  $\frac{1}{2}$  the gate horizontally past drawn active**
- **DDB needed since the 32 nm node, depending on foundry**
  - **Design rules check for connectivity**



 
# ASAP7 Standard Cells

- **Cell architecture**
  - **7.5 M2 track height**
    - Provides good gear ratio with fin, poly, and M2 pitch
  - **Adjacent NAND3 and inverter FEOL and MOL show the double diffusion break (DDB)**
  - **Drawing is not WSYWIG—the fins extend to 1/2 the gate horizontally past drawn active**
- **DDB needed since the 32 nm node, depending on foundry**
  - **Design rules check for connectivity**



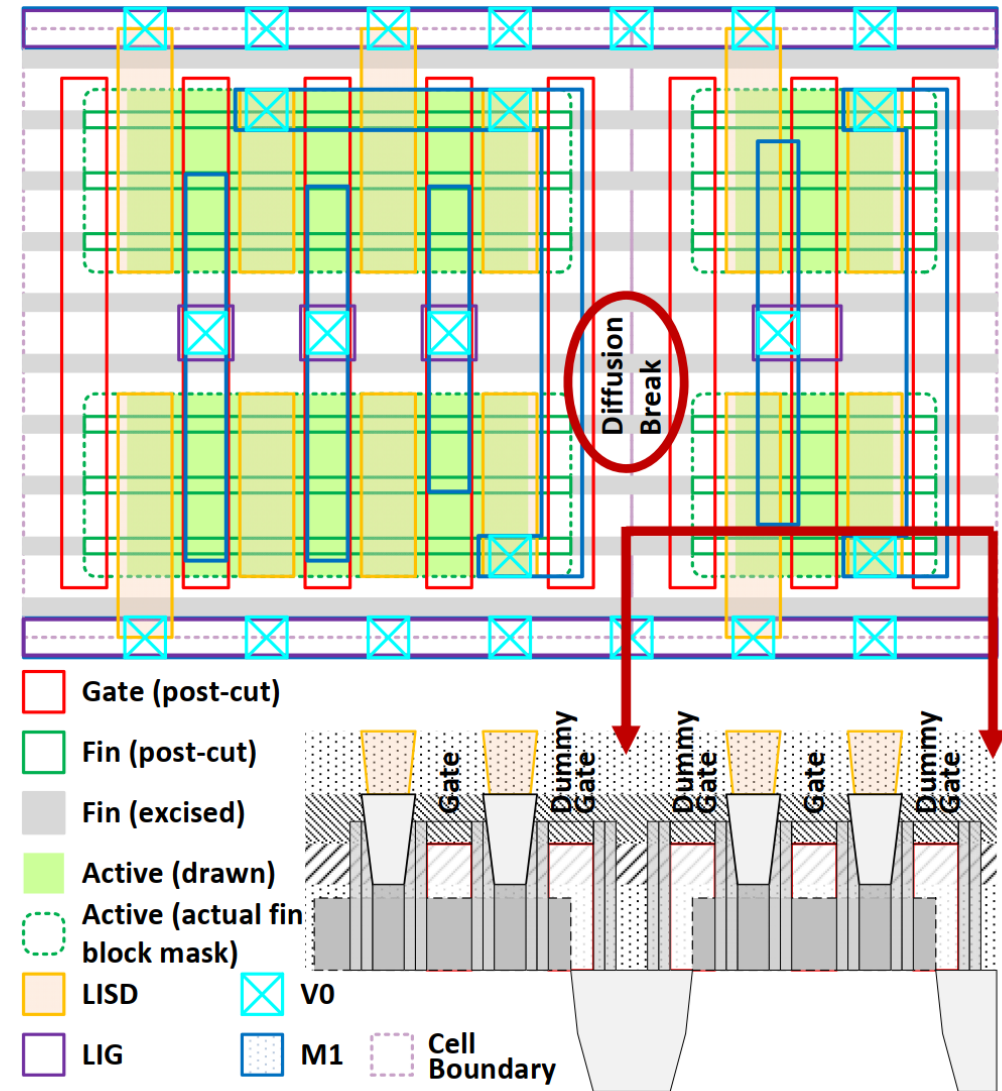
# ASAP7 Standard Cells

- **Cell architecture**
  - **7.5 M2 track height**
    - Provides good gear ratio with fin, poly, and M2 pitch
  - **Adjacent NAND3 and inverter FEOL and MOL show the double diffusion break (DDB)**
  - **Drawing is not WSYWIG—the fins extend to  $\frac{1}{2}$  the gate horizontally past drawn active**
- **DDB needed since the 32 nm node, depending on foundry**
  - **Design rules check for connectivity**





# ASAP7 Latch

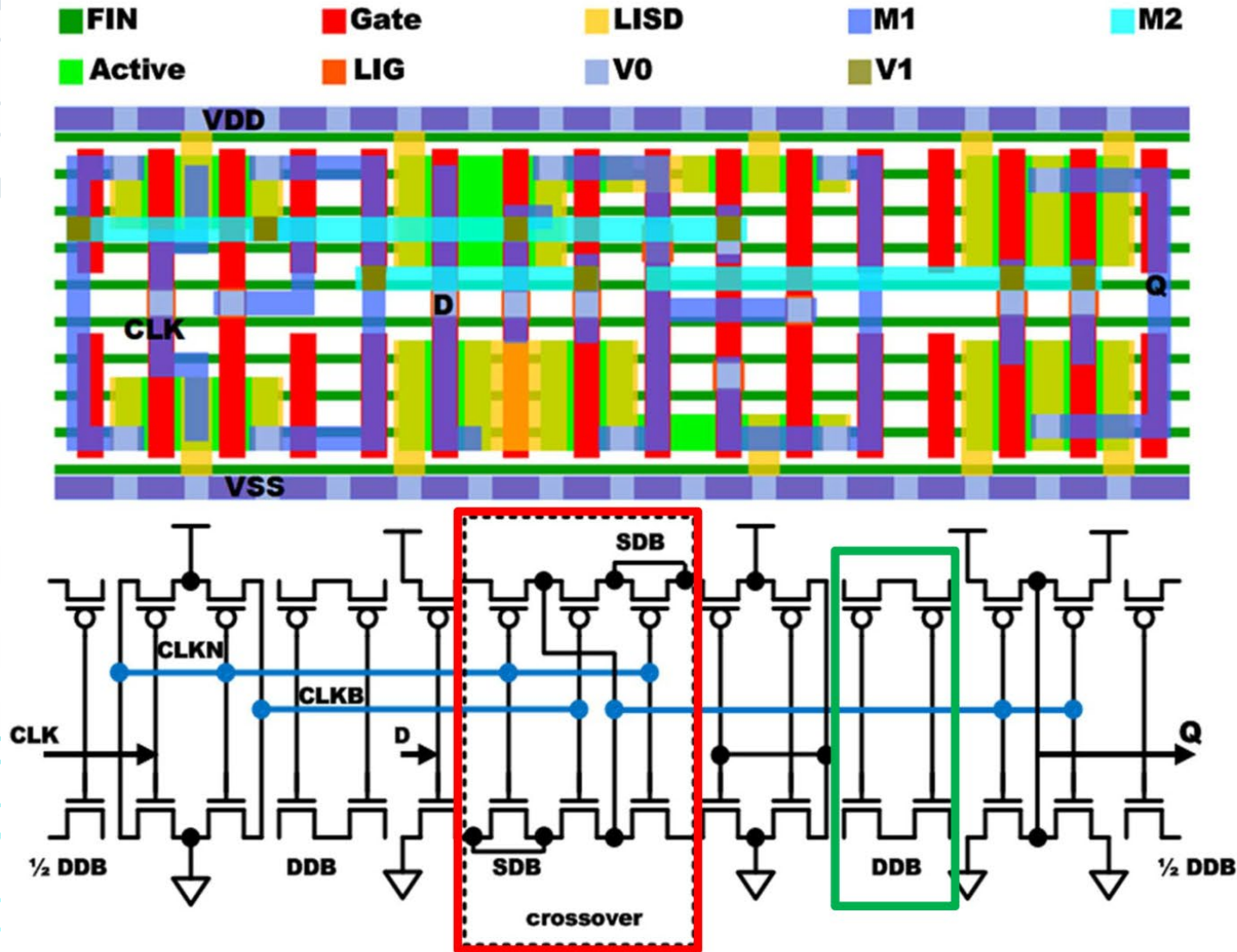


- **This demonstrates a crossover**
  - Note single diffusion breaks (SDBs)
  - Horizontal M2 can only support limited tracks
- **Intel, Samsung support SDBs (no DDBs) at N10/N7 [EETimes]**

# Standard Cell Scaling Beyond N3


- Fin depopulation

  

- Nanosheet cell

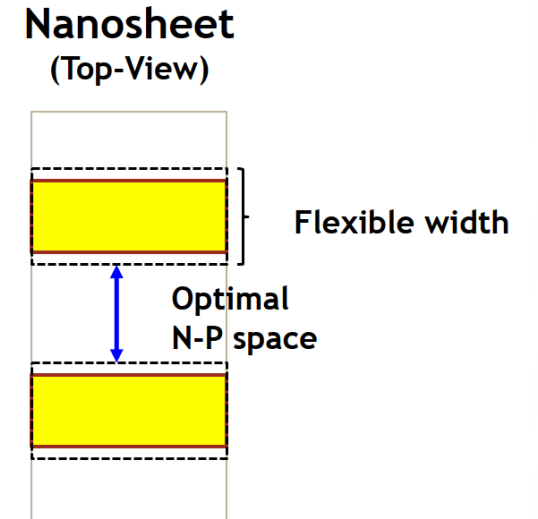

- Stacked CMOS with buried power rails

 



# Summary

- Leakage is hugely important
- Delay is modeled through equivalent R, C
  - We will see other models later
- Standard cells are an established abstraction layer today

# Next Lecture

- Gate models