

# EECS251B : Advanced Digital Circuits and Systems

## Lecture 14 – Timing

**Borivoje Nikolić**



### Data Centers Could Soon Break Lunar Ground

March 4, 2024, EETimes. When the world's first commercial lunar lander made its historic touchdown near the moon's south pole last week, the promise of another groundbreaking venture was also in the works. Stored within a software application loaded onto the craft's on-board computer were the makings of a lunar data center, along with the hopes of redefining deep-space computing.

One of six commercial payloads aboard the Intuitive Machines' Nova-C lander, the prototype belonged to a Florida-based company called Lonestar Data Holdings. Following a series of tests last week, the company said in prepared remarks that it had successfully tested the transmission, storage and receipt back of digital documents during lunar flight and again while on the surface of the moon.



Intuitive Machines' Nova-C lander touches down near the lunar south pole. Its on-board computer houses a software prototype for what could be the first lunar data center. (Source: Intuitive Machines)

# Announcements

- Lab 5 still waiting on PDK correction
  - The newest fix brings it very close
- Start project phase 1
  - Spec doc due this week
- Homework 2 due this week
  - Quiz 2 on March 12



# Standard Cell Library

# Standard Cell Library


- Contains for each cell:
  - Functional information:  $\text{cell} = a * b * c$
  - Timing information: function of
    - input slew
    - intrinsic delay
    - Input/output capacitance
- non-linear models used in tabular approach
- Physical footprint (area)
- Power characteristics
- Noise sensitivity
- Wire-load models - function of
  - Block size
  - Fan-out

Example: NAND2

```
"area": 3.7536,  
"cell_footprint": "sky130_fd_sc_hd__nand2",  
"cell_leakage_power": 0.00211796,  
"driver_waveform_fall": "ramp",  
"driver_waveform_rise": "ramp",  
"leakage_power": [  
  {  
    "value": 0.0002796,  
    "when": "!A&B"  
  },  
  {  
    "value": 3.005879e-05,  
    "when": "!A&!B"  
  },  
  {  
    "value": 0.0079423,  
    "when": "A&B"  
  },  
  {  
    "value": 0.0002199,  
    "when": "A&!B"  
  }  
],  
"pg_pin,VGND": {  
  "pg_type": "primary_ground",  
  "related_bias_pin": "VPB",  
  "voltage_name": "VGND"  
},  
"pg_pin,VNB": {  
  "pg_type": "nwell",  
  "physical_connection": "device_layer",  
  "voltage_name": "VNB"  
}
```
 
# Synopsys Delay Models

- Linear (CMOS2) delay model
  - Similar to what we have studied so far



# Example Cell Timing

- From Synopsys training materials

```
From pin: U28/A  
To pin: U28/Z
```

```
arc type :          cell  
arc sense :        unate  
Input net transition times:  Dt_rise = 0.1458, Dt_fall = 0.0653
```

```
Rise Delay computation:
```


```
rise_intrinsic      0.48 +  
rise_slope * Dt_rise 0 * 0.1458 +  
rise_resistance * (pin_cap + wire_cap) / driver_count  
0.1443 * (2 + 0) / 1  
rise_transition_delay : 0.2886  
-----  
Total                0.7686
```

# Cell Characterization (Linear Model)

```
cell(NAND2) {
  area : 1;
  pin(X) {
    function : "(A B)";
    direction : output;
    edge_rate_rise : 0.24;
    edge_rate_fall : 0.14;
    edge_rate_load_rise : 5.4;
    edge_rate_load_fall : 3.4;
    timing() {
      intrinsic_rise : 0.34;
      intrinsic_fall : 0.24;
      rise_resistance : 3.4;
      fall_resistance : 1.4;
      edge_rate_sensitivity_r0 : 0.24;
      edge_rate_sensitivity_f0 : 0.14;
      edge_rate_sensitivity_r1 : 0.14;
      edge_rate_sensitivity_f1 : 0.04;
      related_pin : "A";
    }
  }
}
```

```
timing() {
  intrinsic_rise : 0.34;
  intrinsic_fall : 0.24;
  rise_resistance : 3.4;
  fall_resistance : 1.4;
  edge_rate_sensitivity_r0 : 0.24;
  edge_rate_sensitivity_f0 : 0.14;
  edge_rate_sensitivity_r1 : 0.14;
  edge_rate_sensitivity_f1 : 0.04;
  related_pin : "B";
}
pin(A) {
  direction : input;
  capacitance : 0.10;
}
pin(B) {
  direction : input;
  capacitance : 0.10;
}
}
```
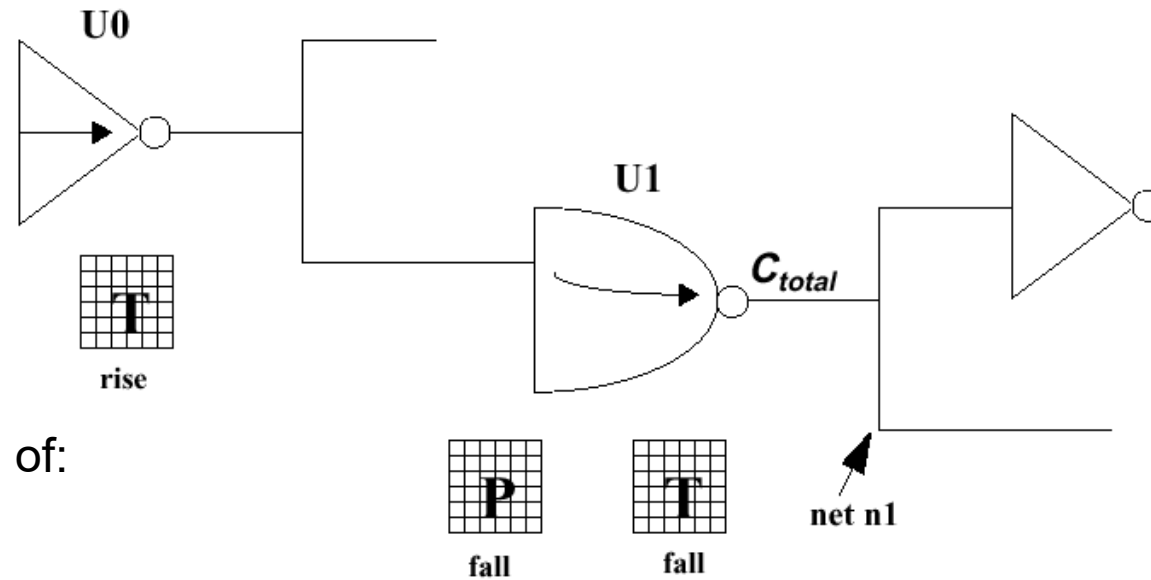
# (Synopsys) Nonlinear Delay Model (NLDM)



Delay is a function of:

- Rise propagation
- Cell rise
- Fall propagation
- Cell fall
- Rise transition
- Fall transition



# NAND2 (Sky130)

```
"timing": [  
  {  
    "cell_fall,del_1_7_7": {  
      "index_1": [  
        0.01,  
        0.0230506,  
        0.0531329,  
        0.122474,  
        0.282311,  
        0.650743,  
        1.5  
      ],  
      "index_2": [  
        0.0005,  
        0.00131655,  
        0.00346659,  
        0.00912787,  
        0.0240345,  
        0.0632852,  
        0.166636  
      ],  
      "values": [  
        0.0206305,  
        0.0250594,  
        0.0363371,  
        0.0651531,  
        0.1403625,  
        0.3379392,  
        0.8628026
```


```
"fall_transition,del_1_7_7": {  
  "index_1": [  
    0.01,  
    0.0230506,  
    0.0531329,  
    0.122474,  
    0.282311,  
    0.650743,  
    1.5  
  ],  
  "index_2": [  
    0.0005,  
    0.00131655,  
    0.00346659,  
    0.00912787,  
    0.0240345,  
    0.0632852,  
    0.166636  
  ],  
  "values": [  
    0.0143751,  
    0.0198544,  
    0.0342729,  
    0.0724393,  
    0.1726079,  
    0.4374054,  
    1.1358902  
  ],  
  [  
    0.0145368,  
    0.0198407,
```

Two-dimensional tables of pre-characterized delays/transition times as a function of input slope and output capacitance

Index1 – input transition  
Index2 – load capacitance
 
# Nonlinear Delay Model (NLDM)


- Interpolates between characterization points




# Composite Current Source (CCS) Model

- ▶ **Driver model**
  - ▶ Composite current source (time and voltage dependent)
- ▶ **Receiver model**
  - ▶ A set of capacitance models
  - ▶ Wire model
- ▶ **Interpolate**

Matches both delay and rise/fall times

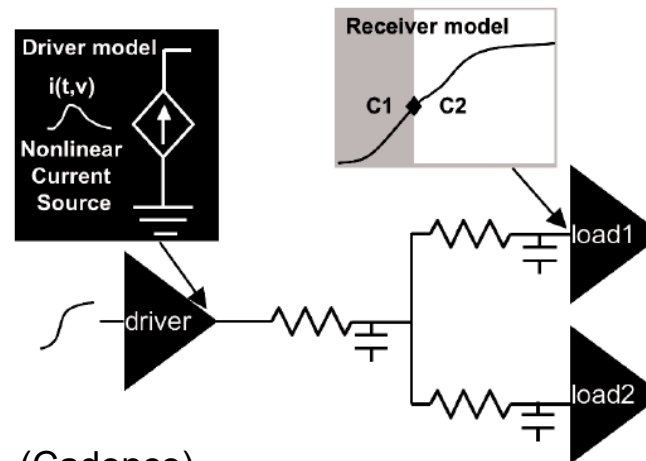

Synopsys

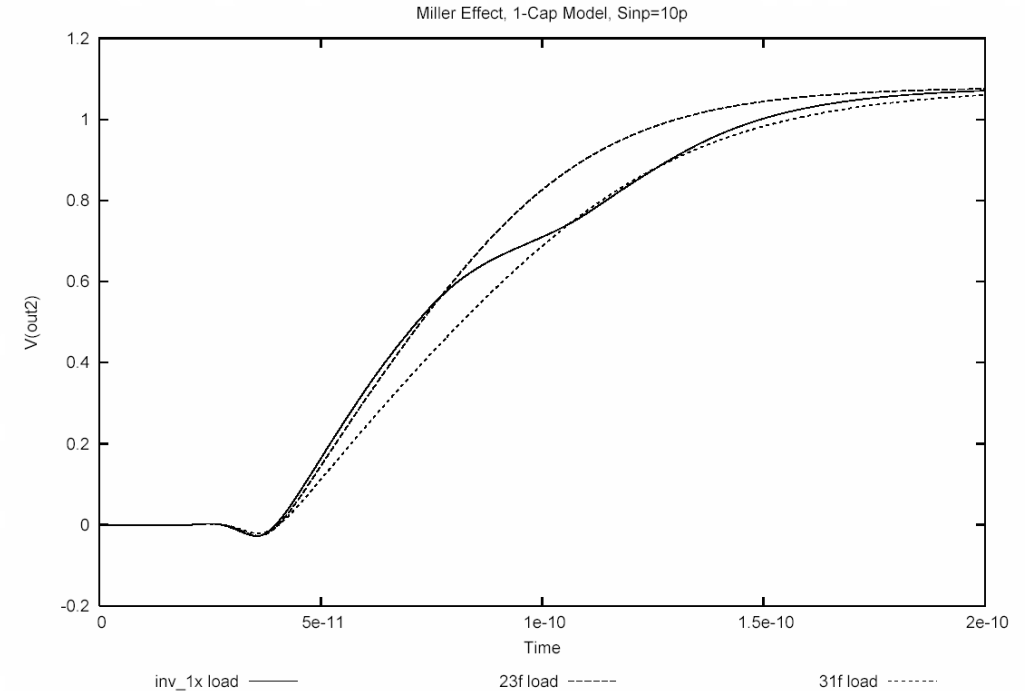




# Design for Performance

## Flip-Flop-Based Timing

# Example Clock System

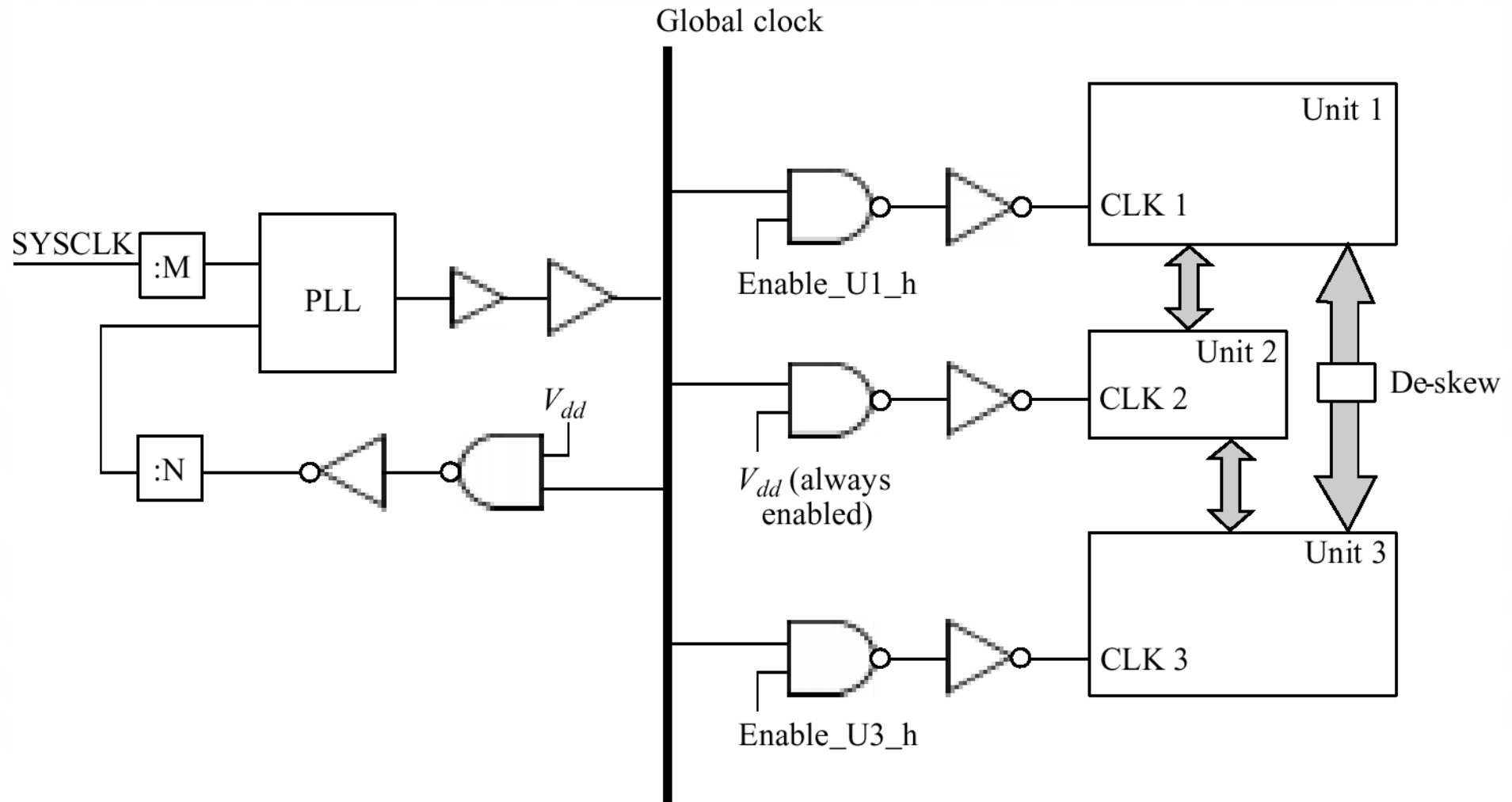


Courtesy of IEEE Press, New York. © 2000

# Clock Nonidealities


- **Clock skew**
  - Spatial variation in temporally equivalent clock edges; deterministic + random,  $t_{SK}$
- **Clock jitter**
  - Temporal variations in consecutive edges of the clock signal; modulation + random noise
  - Cycle-to-cycle (short-term) -  $t_{JS}$
  - Long-term -  $t_{JL}$
- **Variation of the pulse width**
  - for level-sensitive clocking

# Clock Skew and Jitter

 

- Both skew and jitter affect the effective cycle time
- Only skew affects the race margin, if jitter is from the source
  - Distribution-induced jitter affects both



# Clock Uncertainties

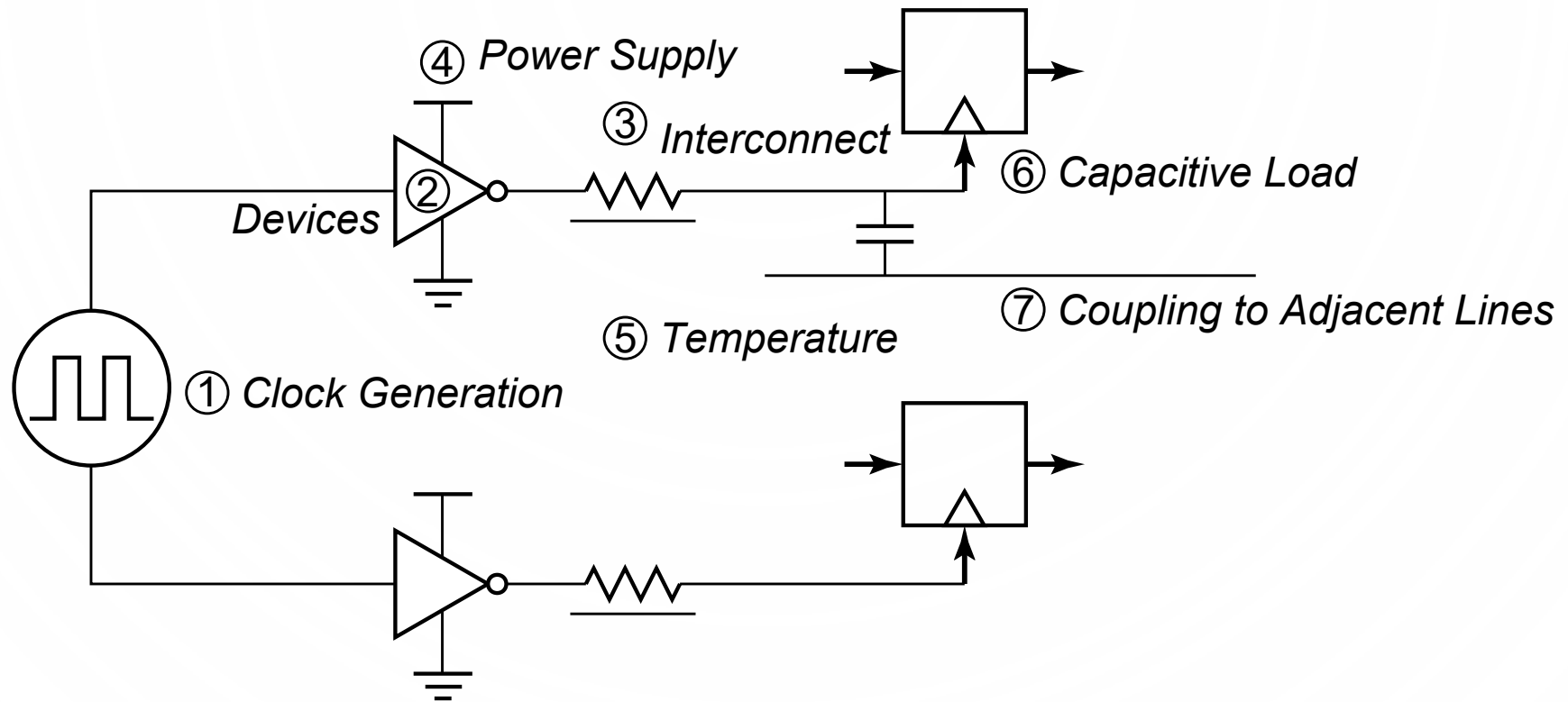

*Sources of clock uncertainty*




# Flip-Flop Parameters

  


*Delays can be different for rising and falling data transitions*

# Latch Parameters

 


Unger and Tan  
Trans. on Comp.  
10/86

 


*Delays can be different for rising and falling data transitions*
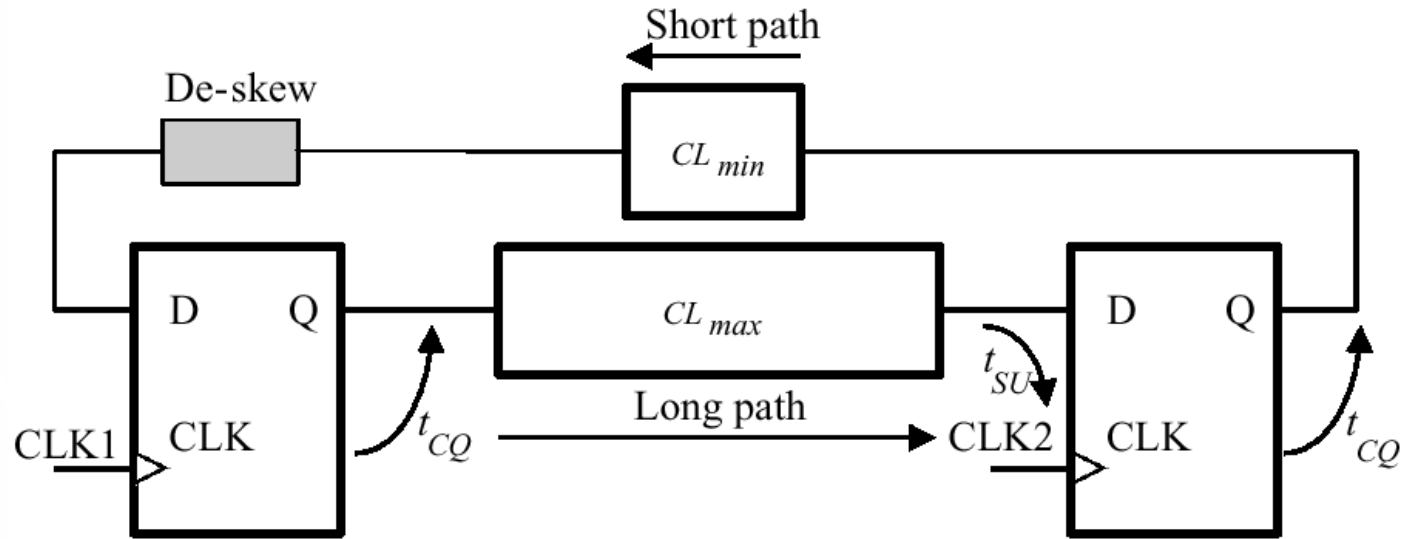
# Clock Constraints in Edge-Triggered Systems




$$t_{CL} \leq (t_{CY} - t_{SK} - t_{JS}) - (t_{SU} + t_{CQ})$$

$$t_{CL} \geq t_{SK} + (t_H - t_{CQ})$$

 

# Pictorial View of Setup and Hold Tests

 




## Latch Timing

## Key Point

- Latch-based sequencing can improve performance, but is more complicated
  - Timing analysis not limited to a consecutive pair of latches

# Latch Timing

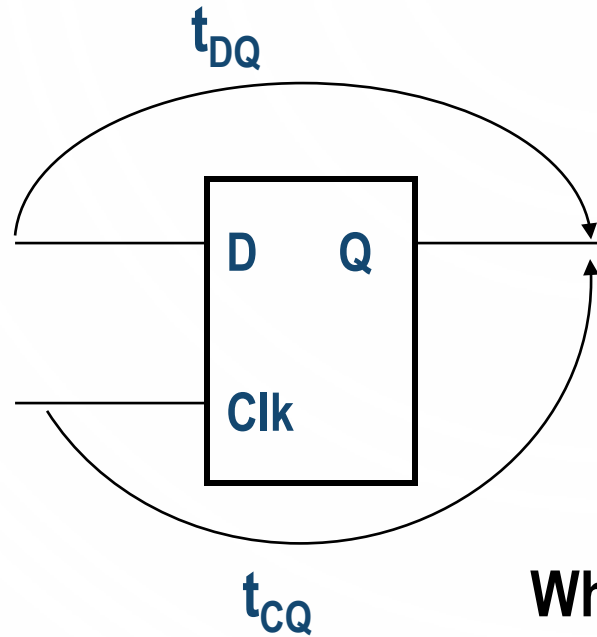



**When data arrives  
to transparent latch**

**Latch is a 'soft' barrier**

**When data arrives  
to non-transparent latch**

**Data has to be 're-launched'**



# Latch Sequencing

  




# Latch-Based Timing

- Single-phase, two-latch

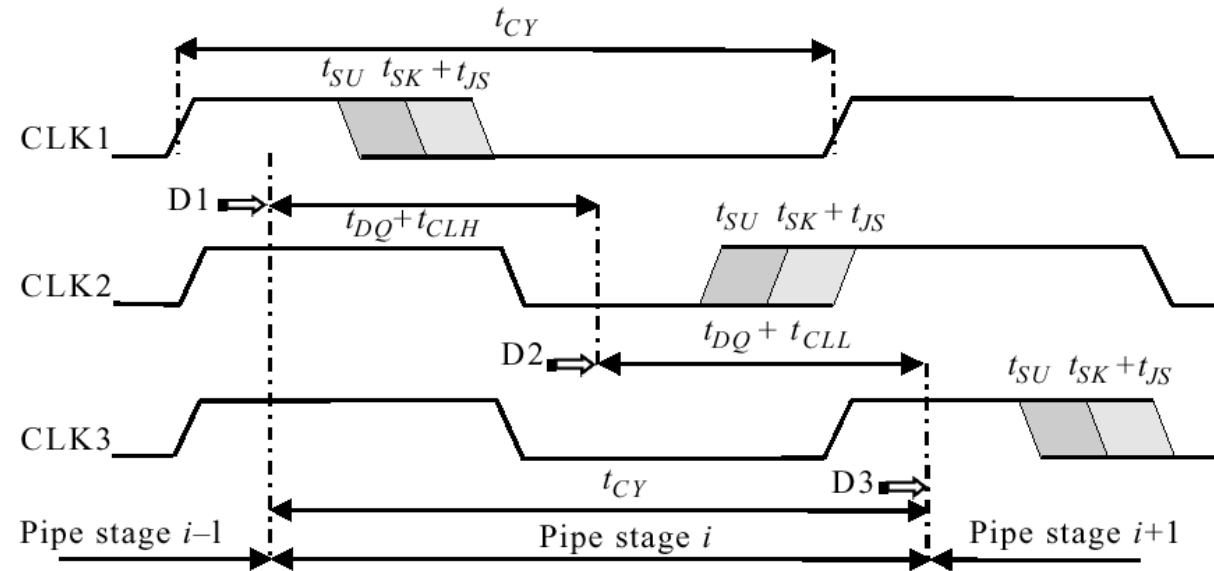 

As long as transitions are within the assertion period of the latch, no impact of position of clock edges

# Latch Design and Hold Times

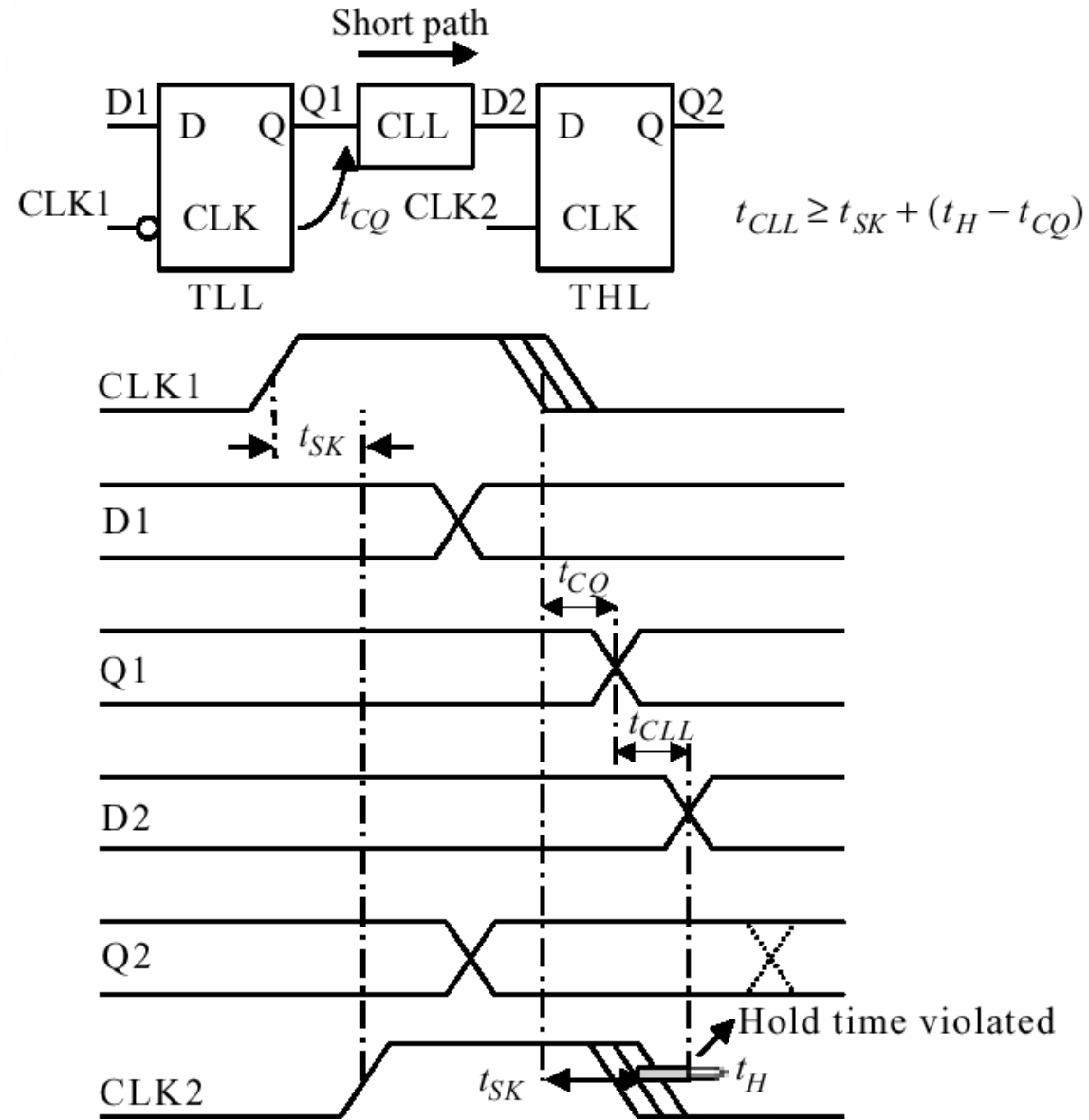


# Soft-Edge Properties of Latches

- **Slack passing** – logical partition uses left over time (slack) from the *previous* partition
- **Time borrowing** – logical partition utilizes a portion of time allotted to the *next* partition
- Makes most impact in unbalanced pipelines


Bernstein et al, Chapter 8, Chandrakasan, Chap 11 (by Partovi)

# Slack Passing and Time Borrowing

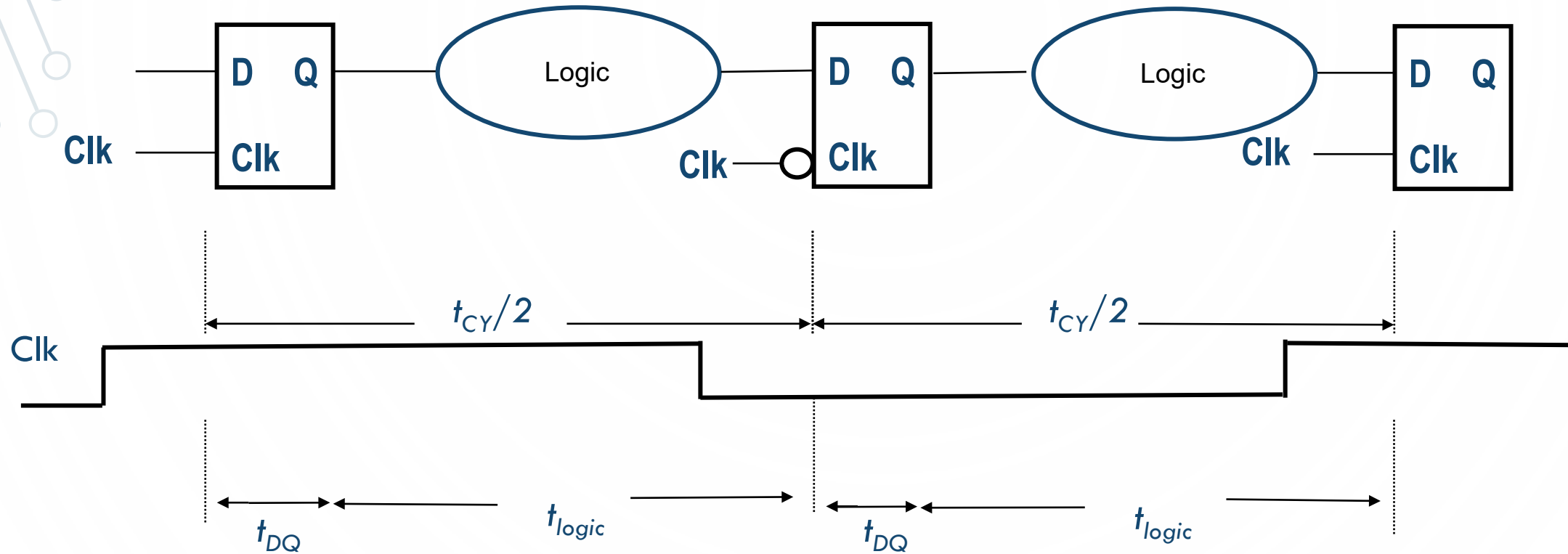




# Slack Passing and Time Borrowing

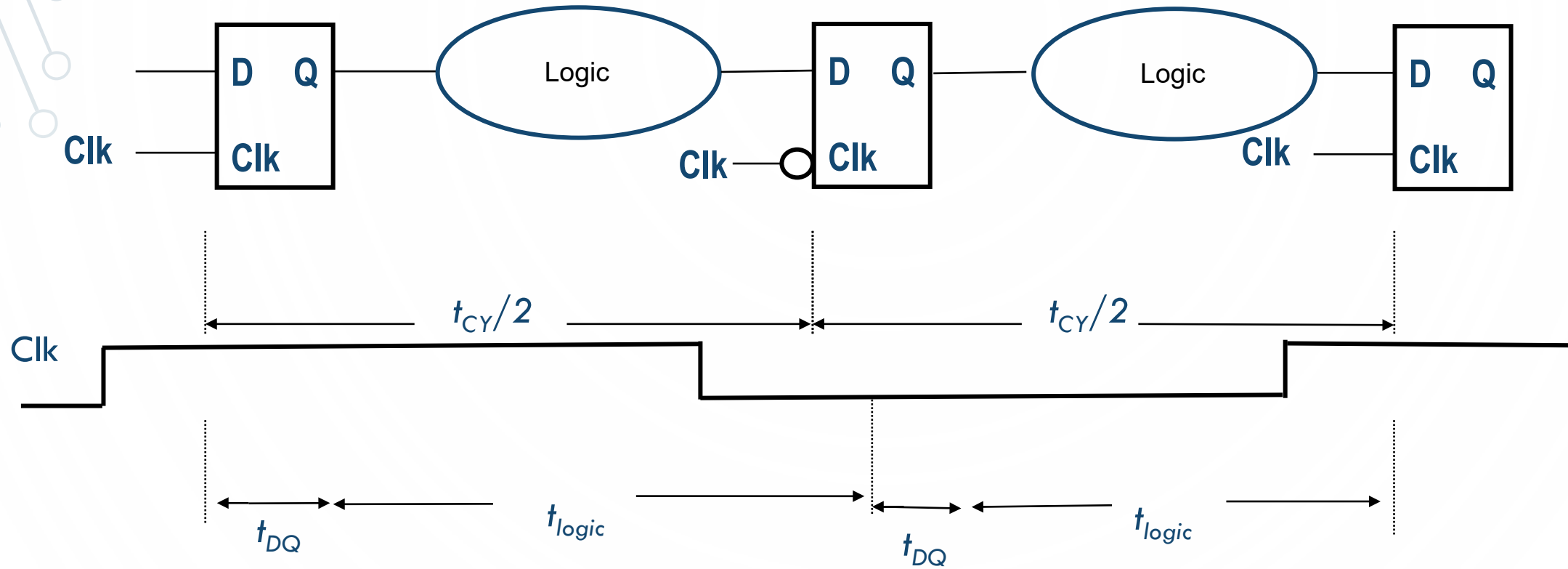

- Time borrowed

# Slack-Passing and Cycle Borrowing

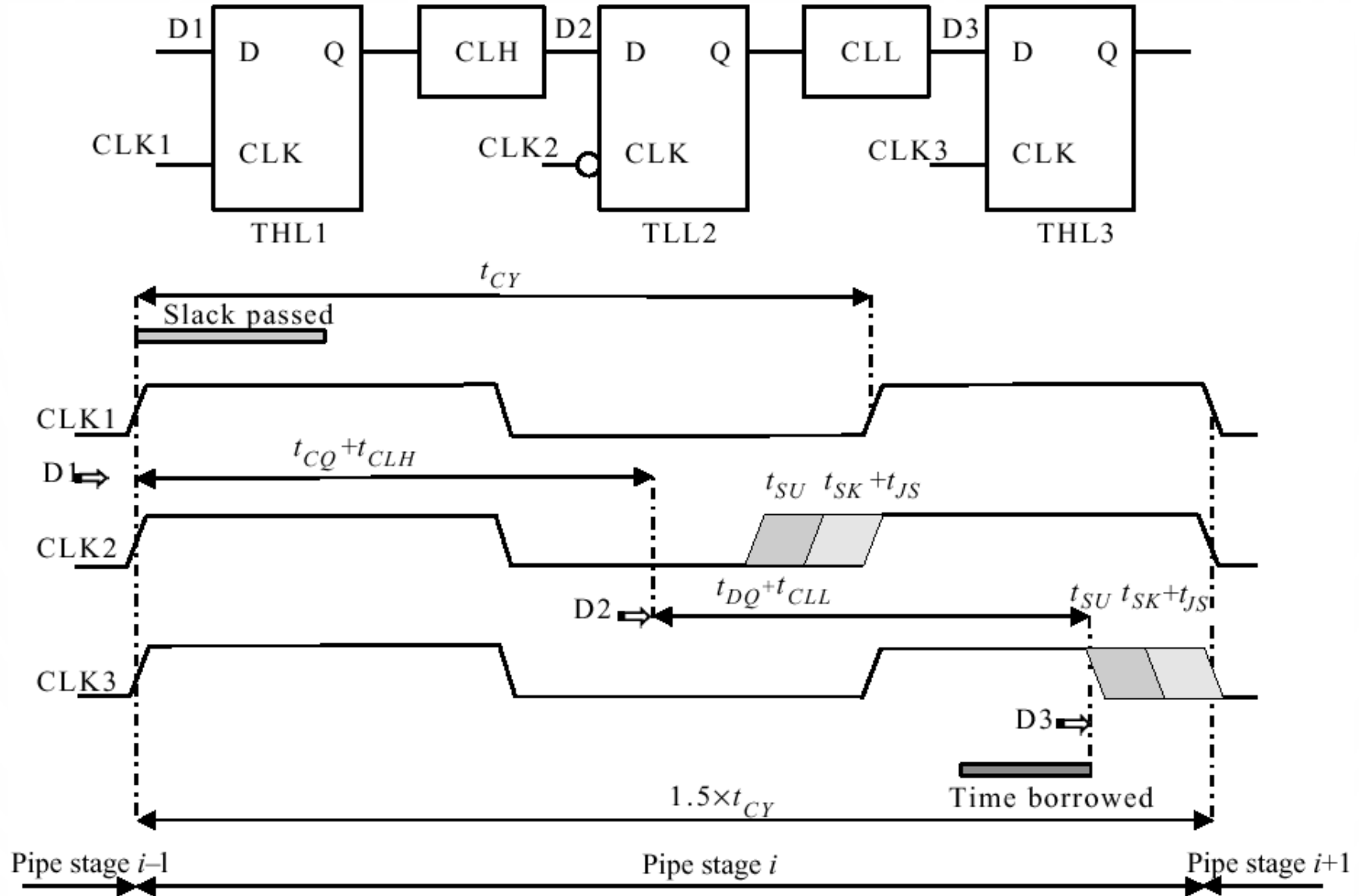

*For N stage pipeline, overall logic delay should be  $< N T_{cl}$*

# Summary

- **Standard cell libraries**
  - Linear model (not used anymore)
  - NLDM
  - CCS
  - Lots of options, details abstracted
- **Timing**
  - Flip-flop-based timing
  - Latch-based timing is more complex



## Next Lecture

- Latches and flip-flops